

EE 211 - Hwk5

Sept 16, 2019

Name _____

Find the node voltages v_1 , v_2 and v_3 for the circuit shown below. The independent current source supplies **6 A**.

