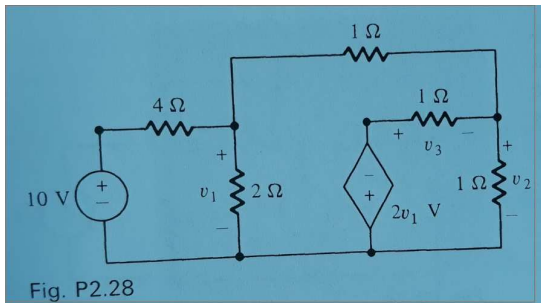


EE 211 - Hwk6

Sept 20, 2019

Name _____

1. Use mesh analysis to find v_1 , v_2 , and v_3 for the circuit shown below.



2. Find the resistance seen by the 1-A current source for the circuit shown below.

