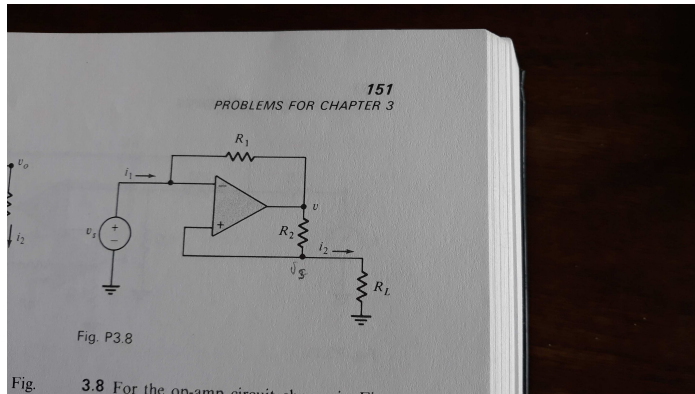


# EE 211 - Hwk6

Oct. 4, 2019

Name \_\_\_\_\_

1. P3.8.- For the op-amp circuit shown in Fig. P3.8, find a) the voltage  $v$ , b) the current gain  $i_2/i_1$ .



2. P3.20.- For the circuit shown in Fig. P3.20, use source transformations to determine  $v_1$  and  $v_2$ .

