

EE 311 Signals and Systems Hwk8

For the circuit below:

- Determine the expression for the Frequency Response $H(\omega)$.
- Determine the expressions for the Magnitude and Phase responses
- Derive the expressions for the Half-power frequencies (ω_{c1}) and (ω_{c2}).
- Use Matlab to plot the Magnitude and the Phase responses.

