


ES 332 Hwk 8

1.- For the circuit shown in the Figure below, find an expression for:

$$v_c(0) = \underline{\hspace{2cm}} \qquad i_c(0) = \underline{\hspace{2cm}}$$

$$v_c(t) = \underline{\hspace{2cm}} \text{ (for } t > 0) \qquad i_c(t) = \underline{\hspace{2cm}} \text{ (for } t > 0)$$
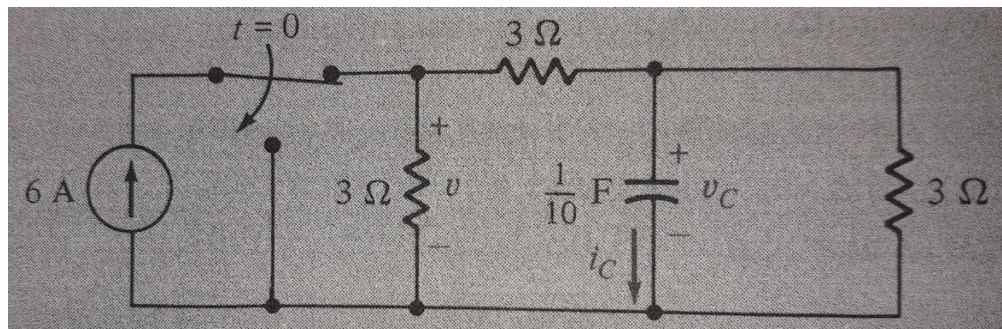
$$v(t) = \underline{\hspace{2cm}} \text{ (for } t > 0)$$



2.- For the circuit in the Figure below, suppose that $v_s(t) = -3 + 4u(t)$ V,

Find $v(t)$ for all t .

