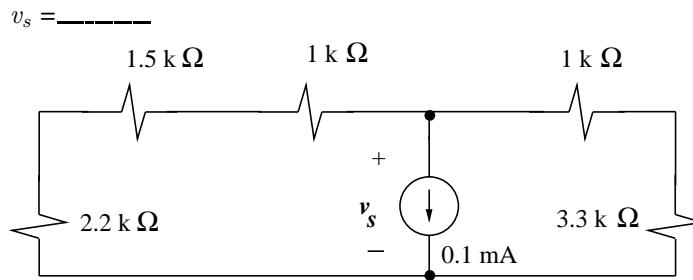


ES 332: Fall 2020, Hwk4


Name: _____

1. For the circuit shown in the figure below, find the voltage v_s across the current source.



2. For the circuit shown in the figure below,

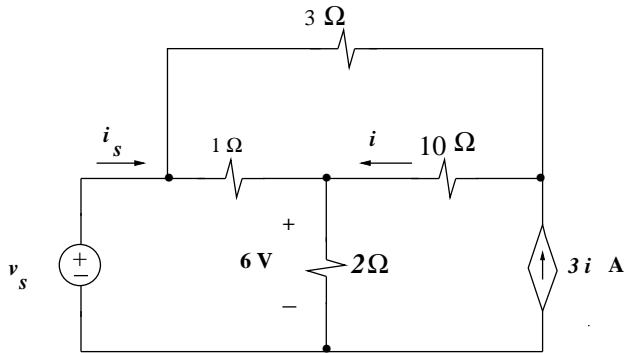- (a) Find the current across the 1Ω resistor: $i_{R_{1\Omega}} = \text{-----}$
- (b) Find the current across the 3Ω resistor: $i_{R_{3\Omega}} = \text{-----}$
- (c) Find i_s . $i_s = \text{-----}$
- (d) Find v_s . $v_s = \text{-----}$
- (e) Find the resistance $R_{eq} = v_s/i_s$ seen by the voltage source. $R_{eq} = \text{-----}$



3. For the circuit shown in the figure below,

- Write Mesh current equations (i_1 and i_2).
- Write Node voltage equations (V_1 , V_2 and V_3).

