

Homework # 2

ES 332 Electrical Engineering

Problems from Textbook

Drill Exercise: 1.12

Problem 1.38

Problem 1.41

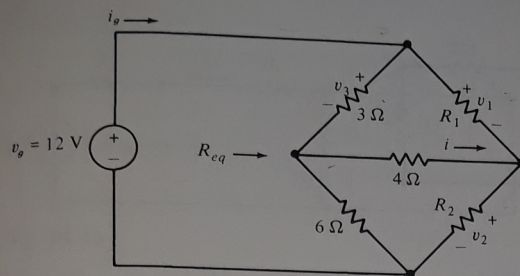


Fig. P1.38

1.38 Shown in Fig. P1.38 is a non-series-parallel connection known as a **bridge circuit**.

- Given that $R_1 = 6\ \Omega$, $R_2 = 3\ \Omega$, and $v_1 = 7\ \text{V}$, find v_2 , i , v_3 , and the resistance $R_{eq} = v_g/i_g$ seen by the voltage source.
 - Repeat part (a) for the case $R_1 = 3\ \Omega$, $R_2 = 6\ \Omega$, and $v_1 = 4\ \text{V}$.
 - When the current $i = 0$, we say that the bridge is **balanced**. Under what condition (find an expression relating R_1 and R_2) will this bridge be balanced?
- 1.39 Given the circuit shown in Fig. P1.39, find i_1 for (a) $K = 2$, (b) $K = 3$, and (c) $K = 4$.

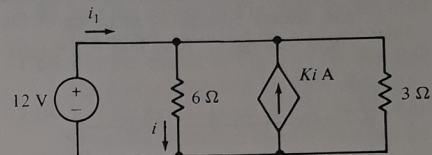


Fig. P1.39

- 1.40 The circuit given in Fig. P1.40 contains a **voltage-dependent voltage source** as well as a **current-dependent current source**. Repeat Problem 1.39 for this circuit.
- 1.41 Consider the circuit shown in Fig. P1.41. Find v for (a) $K = 2$ and (b) $K = 4$.

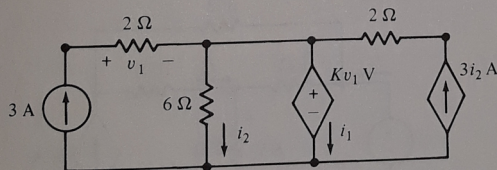


Fig. P1.40

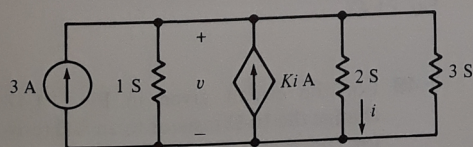


Fig. P1.41