

Name: \_\_\_\_\_

Calculate the current in the detector branch ( $R_5$ ) and the voltage across it.