

**Problems from Text:**

**4.68.- A half-wave rectifier...**

**4.87.- The clamped capacitor...**

**4.88.- For the circuits ...**