

Analog Electronics

Hwk 3a

For the circuit below,

- a) Find the transfer function:

$$T(s) = V_i(s)/V_s(s)$$

- b) Is this a high-pass or a low-pass network?
c) What is its transmission at very high frequencies?
d) What is the corner (-3 dB) frequency ω_o for

$$R_s = 20k\Omega, \quad R_i = 40k\Omega, \quad \text{and} \quad C_i = 2pF$$

- e) What is the value of

$$|T(j\omega_o)|$$

