

**\*2.44** Figure P2.44 shows a circuit for a digital-to-analog converter (DAC). The circuit accepts a 4-bit input binary word  $a_3a_2a_1a_0$ , where  $a_0, a_1, a_2,$  and  $a_3$  take the values of 0 or 1, and it provides an analog output voltage  $v_o$  proportional to the value of the digital input. Each of the bits of the input word controls the correspondingly numbered switch. For instance, if  $a_2$  is 0 then switch  $S_2$  connects the 20-k $\Omega$  resistor to ground, while if  $a_2$  is 1 then  $S_2$  connects the 20-k $\Omega$  resistor to the +5-V power supply. Show that  $v_o$  is given by

$$v_o = -\frac{R_f}{16} [2^0 a_0 + 2^1 a_1 + 2^2 a_2 + 2^3 a_3]$$

where  $R_f$  is in kilohms. Find the value of  $R_f$  so that  $v_o$  ranges from 0 to -5 volts.


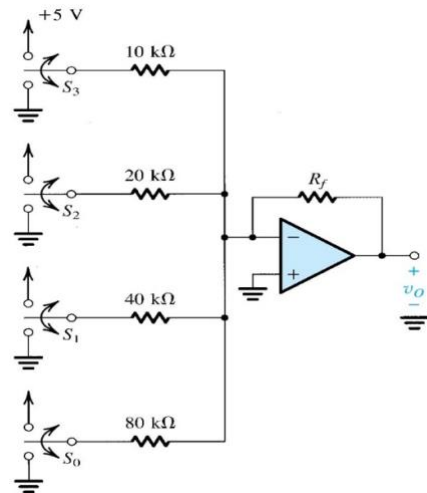


Figure P 2.44

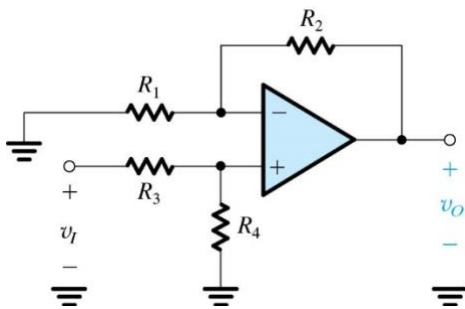P 2.50. Derive an expression for the voltage gain  $v_o/v_I$  for the circuit below.



P 2.51. For the circuit below, use superposition to find  $v_0$  in terms of the input voltages  $v_1$  and  $v_2$

$$v_1 = 10 \sin(2\pi \times 60t) - 0.1 \sin(2\pi \times 5000t), \text{ volts}$$

$$v_2 = 10 \sin(2\pi \times 60t) + 0.1 \sin(2\pi \times 5000t), \text{ volts}$$

