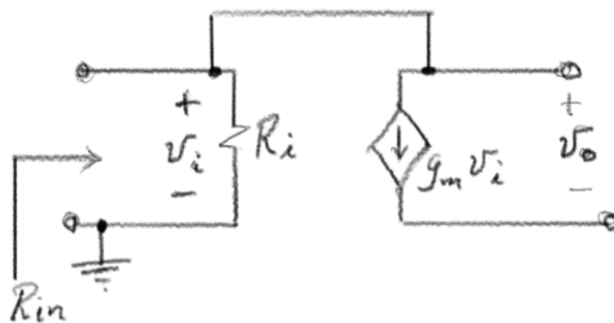


Name: \_\_\_\_\_

1.- Find the input resistance  $R_{in}$  of the network below. (Hint: Apply a test voltage between the two input terminals, and find the current drawn from the source).




2.- For the circuit below,


a) Find the transfer function:

$$T(s) = V_o(s)/V_i(s)$$

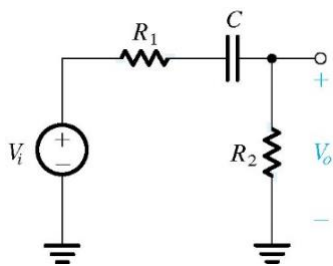b) Find the expression for the corner (-3 dB) frequency  $\omega_o$



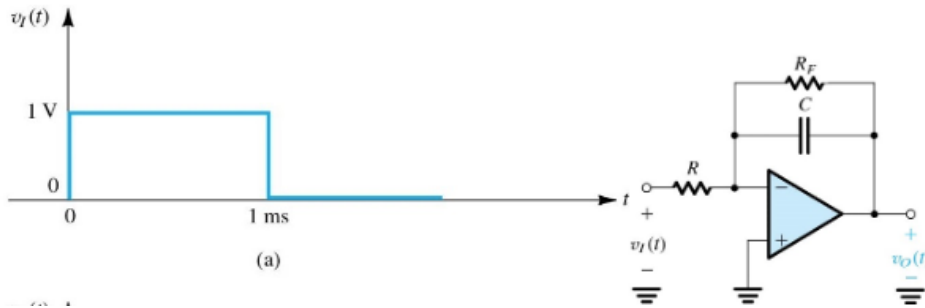3.- Find the output produced by the circuit below in response to the input pulse of 1 -V and 1-ms.  $R = 10k\Omega$ ,  $R_F = 1M\Omega$  The output saturates at  $\pm 13V$ .



4.- (Exa 2.8) The op amp below, is specified to have output saturation voltages of  $\pm 13V$  and output current limit of  $\pm 20mA$ .

a) For a sine-wave signal of peak voltage  $V_p = 1.5V$  and  $R_L = 1k\Omega$  specify the signal resulting at the output of the amplifier.

b) For a sine-wave signal of peak voltage  $V_p = 1V$ , what is the lowest value of  $R_L$  for which an undistorted sine-wave output is obtained?

