

**EE 212 - homework 10**

**Due April 5, 2019**

Problems from Textbook:

I 10.21

II 10.27

Notes:

- a) Problem 10.27 substitutes Problem 10.28 (assigned before).
- b) Assume the circuit is driven by a current source of  $1\angle 0^\circ$  A
- c) Answer:  $Q = 0.85$