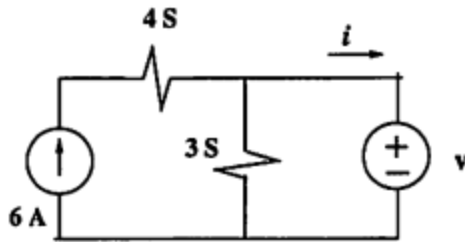


Name: Answers 1/2


Closed book. Show all work. Partial credit will be given. No credit will be given if an answer appears with no supporting work.

1. (a) For circuit (a) shown in the figure below, find  $i$  when the voltage source  $v = 2V$   
 (b) For circuit (b) shown in the figure below, find  $i_1$



(a)

$$\underline{i = 0 \text{ A}}$$

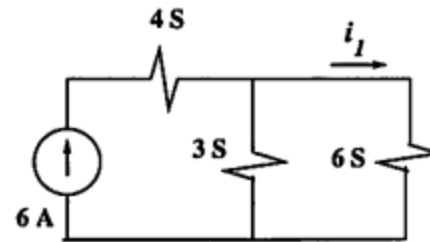


(b)

$$\underline{i_1 = 4 \text{ A}}$$

2. For the circuit shown in the figure below, use mesh analysis to find

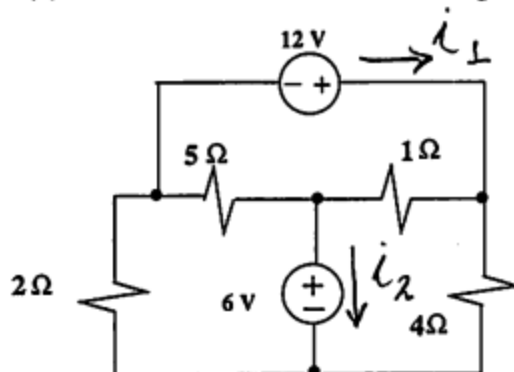
- (a) The current directed to the right, through the 12-V source  
 (b) The current, directed down, through the 6-V source



$$\frac{i_1 = 4 \text{ A}}{i_2 = 0 \text{ A}}$$

# Answers 2/2 Practice Exam

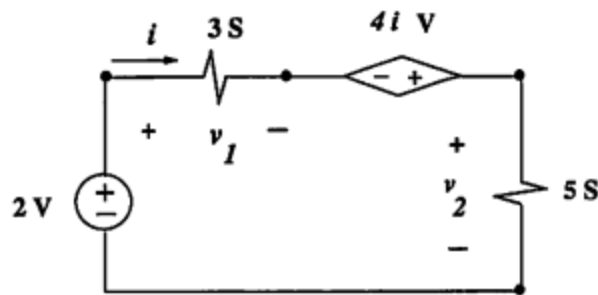3. For the circuit shown in the figure below, determine the values of  $v_1$  and  $v_2$




$$v_1 = -\frac{5}{26} \text{ V}$$

$$v_2 = -\frac{3}{26} \text{ V}$$

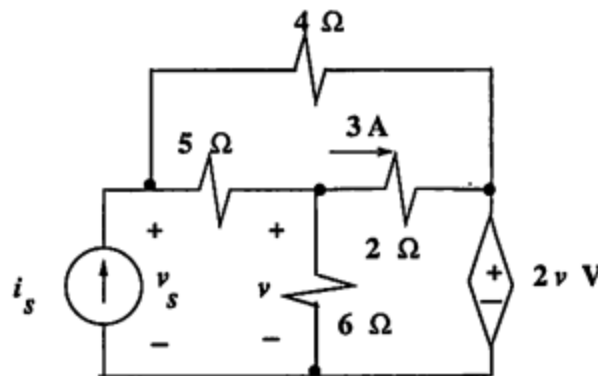4. For the circuit shown in the figure below,

- Find  $i_s$ ,
- Find the resistance  $R_{eq}$  seen by the current source.



$$a) i_s = 4 \text{ A}$$

$$b) R_{eq} = \frac{2}{3} \Omega$$