

ES 332 Hwk04, due Feb 10, 2020

Name _____

Note: This problem is the same as the quiz from Friday. So, it's optional.

For the circuit shown in the figure below, find the voltage across the current source and the current through the voltage source.

