

ES 332 Hwk04, due Feb 21, 2020

Name \_\_\_\_\_

P3.8.- For the op-amp circuit shown in Fig. P3.8, find a) the voltage  $v$ , b) the current gain  $i_2/i_1$ .

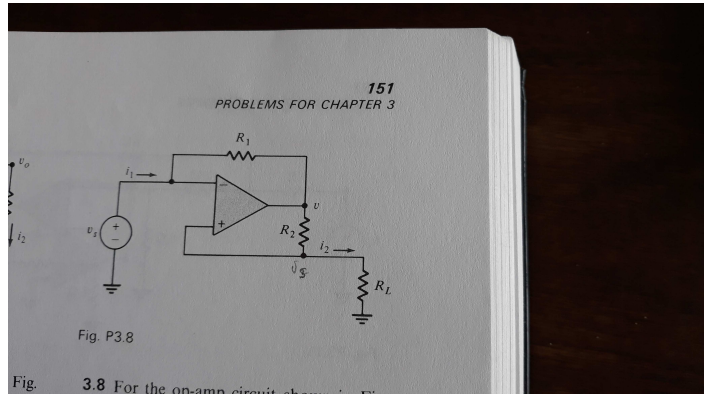


Fig. 3.8 For the op-amp circuit shown in Fig. P3.8