

ES 332 - hw09

April 6, 2020

Name _____

For the circuit shown in the figure below, determine the expression for $v_o(t)$ and sketch it.

Note: $v(t)$ is the voltage across the capacitor.

