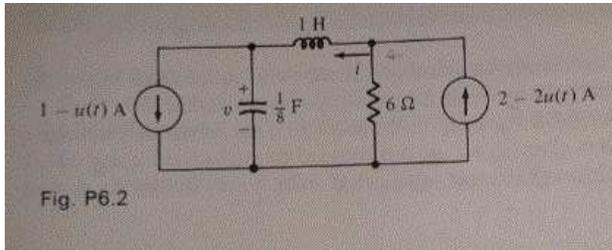


ES 332 - hw12
Due April 27 2020

Name _____

Problems from Text:

1. P 6.2 For the RLC circuit shown in Fig. P6.2, find $v(t)$ and $i(t)$ for all t



2. P 6.12 For the RLC circuit shown in Fig. P6.6, Suppose that $R = \frac{1}{2} \Omega$, $L = 1$ H, $C = 1$ F, and $V_s = 3$ V, find $i(t)$ and $v(t)$ for all t

