

Mixed Electronics II

Tentative Plan:

Install Vivado from Xilinx. (Spartan)

- 3 Projects
- No lectures
- Keep lab books
- 1-2 pages weekly reports on progress

Project 1: Weigh scale using strain gauges

Start with analysis of a bridge circuit

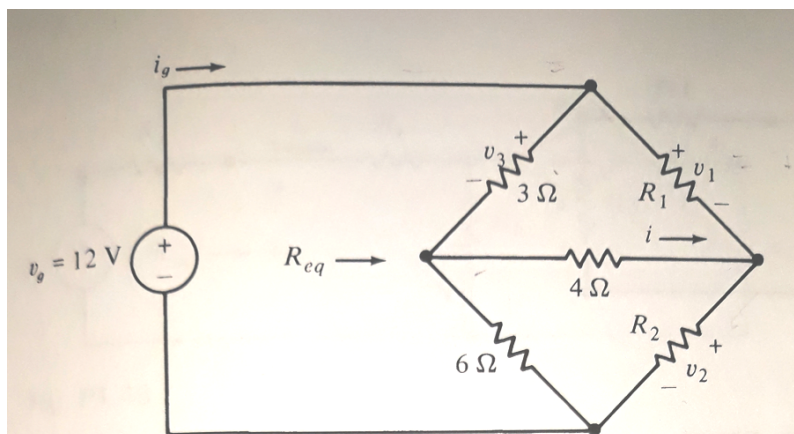


Fig. P1.38

1.38 Shown in Fig. P1.38 is a non-series-parallel connection known as a **bridge circuit**.

- Given that $R_1 = 6 \Omega$, $R_2 = 3 \Omega$, and $v_1 = 7 \text{ V}$, find v_2 , i , v_3 , and the resistance $R_{eq} = v_g/i_g$ seen by the voltage source.
- Repeat part (a) for the case $R_1 = 3 \Omega$, $R_2 = 6 \Omega$, and $v_1 = 4 \text{ V}$.
- When the current $i = 0$, we say that the bridge is **balanced**. Under what condition (find an expression relating R_1 and R_2) will this bridge be balanced?

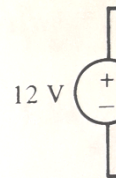


Fig. P1.3

1.40 The
a
we
so
cir

- a) Solve problem 1.38
- b) Test the circuit
- c) Use the circuit to measure a resistance
- d) How would you use strain gauge(s) in the circuit to Measure weights
- e) Use strain gauge(s) to build a scale
- f) If needed, use an amplifier (which type?) to get better measurements.
- g) Connect it to a computer and display the weight values.

How would you use strain gauge(s) to implement a scale

FPGAs. Install Vivado from Xilinx