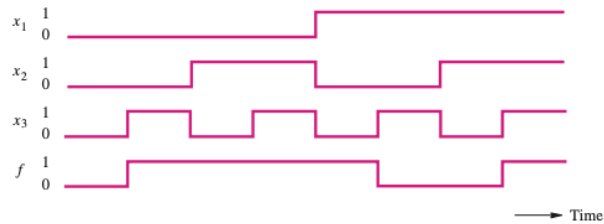


## Homework 4: EE 252 Digital Electronics

1. For the timing diagram in Figure P2.4, synthesize the function  $f(x_1, x_2, x_3)$  in the simplest product-of-sums form.



**Figure P2.4** A timing diagram representing a logic function.

2. Design a circuit with output  $f$  and inputs  $x_1, x_0, y_1$ , and  $y_0$ . Let  $X = x_1x_0$  and  $Y = y_1y_0$  represent two 2-digit binary numbers. The output  $f$  should be 1 if the numbers represented by  $X$  and  $Y$  are equal. Otherwise,  $f$  should be 0.

- (a) Show the truth table for  $f$ .
- (b) Synthesize the simplest possible product-of-sums expression for  $f$ .

3. Implement the function in Figure 2.31 using only NAND gates.

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

**Figure 2.31** Truth table for the three-way light control.

4. Implement the function in Figure 2.31 using only NOR gates.