

## EE 252 Digital Electronics:

Name: \_\_\_\_\_

1. Implement the sequential circuit described by the state table below, using T Flip Flops

	Present state $y_2y_1$	Next state		Output $z$
		$w = 0$	$w = 1$	
		$Y_2Y_1$	$Y_2Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	$dd$	$dd$	$d$

2. Implement the same sequential circuit, using JK Flip Flops.

- If a flip-flop in state 0 is to remain in state 0, then  $J = 0$  and  $K = d$  (where  $d$  means that  $K$  can be equal to either 0 or 1).
- If a flip-flop in state 0 is to change to state 1, then  $J = 1$  and  $K = d$ .
- If a flip-flop in state 1 is to remain in state 1, then  $J = d$  and  $K = 0$ .
- If a flip-flop in state 1 is to change to state 0, then  $J = d$  and  $K = 1$ .

3. - Design a counter that counts pulses on line  $w$  and displays the count in the sequence 0,2,1,5,0,2,.... Use JK flip-flops in your circuit.