

EE 252 Digital Electronics: Quiz 4. --→ Homework_8

Name: _____


1. Determine the signal frequencies coming out of the following pins:

a) c_2 _____

b) c_5 _____

c) c_7 _____

d) c_9 _____

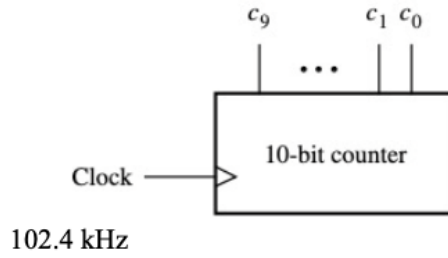

2. List 3 input signals and what values should they have for the LED to be ON? _____

3. List two events generated when the switch is closed. _____

4. The time **units** displayed at the end of the experiment are _____

