

Fig. P1.42

1.42 Repeat Problem 1.41 for the circuit given in Fig. P1.42.

1.43 For the circuit shown in Fig. P1.43, find the output voltage  $v_2$  in terms of the input voltage  $v_1$ . Also find  $R_{eq} = v_1/i_1$ .

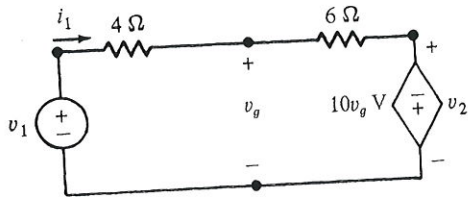


Fig. P1.43

- 1.44 Consider the circuit given in Fig. P1.44.
- Use voltage division to find  $v$  in terms of  $v_g$ .
  - Find the output voltage  $v_2$  in terms of the input voltage  $v_1$ .

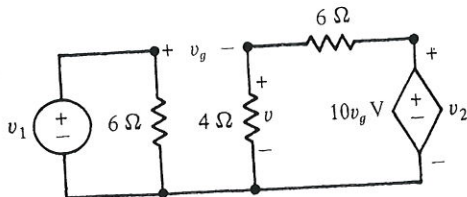


Fig. P1.44

- 1.45 Given the circuit shown in Fig. P1.45:
- Find  $i_s$ .
  - Find the resistance  $R_{eq} = v_s/i_s$  seen by the current source.

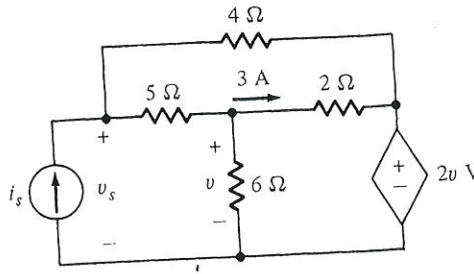


Fig. P1.45

1.46 For the circuit given in Fig. P1.45, change the 3-Ω resistor to a 5-Ω resistor and repeat Problem 1.45.

- 1.47 Given the circuit shown in Fig. P1.47:
- Find  $v_s$ .
  - Find the resistance  $R_{eq} = v_s/i_s$  seen by the voltage source.

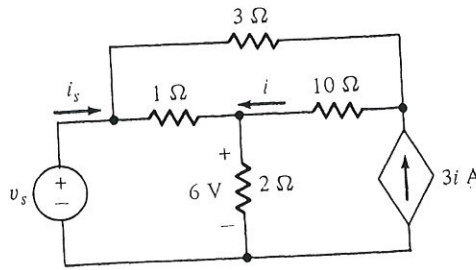


Fig. P1.47

1.48 For the circuit given in Fig. P1.47, change the 10-Ω resistor to an 8-Ω resistor and repeat Problem 1.47.

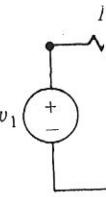


Fig. P1.49

- 1.49 The single circuit (a), (b), (c)

- 1.50 Co 1.4 (a), (b), (c)

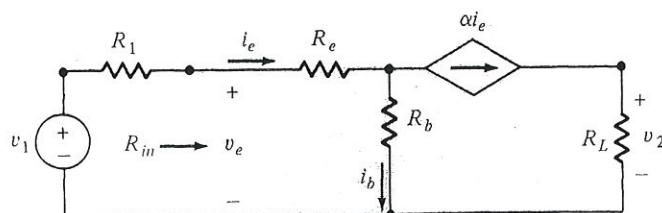


Fig. P1.49

- 1.49 The circuit in Fig. P1.49 is another single BJT amplifier. The portion of the circuit in the colored box is an alternative model of a BJT.
- Find  $i_e$  in terms of the various resistors,  $\alpha$ , and the input voltage  $v_1$ .
  - Find  $v_2$  in terms of the resistors,  $\alpha$ , and  $v_1$ .
  - Given that  $R_1 = 40 \Omega$ ,  $R_e = 27 \Omega$ ,  $R_b = 150 \Omega$ ,  $R_L = 1.5 \text{ k}\Omega$ , and  $\alpha = 0.98$ , find the voltage gain  $v_2/v_1$ .
- 1.50 Consider the circuit given in Problem 1.49 and the values given in part (c).
- Find the resistance  $R_{eq} = v_1/i_e$  seen by the voltage source.
  - Find the resistance  $R_{in} = v_e/i_e$  at the input of the amplifier.
  - Find the voltage gain  $v_2/v_e$ .
- 1.51 For the circuit in Fig. 1.45 (p. 28), find the power absorbed by each element.
- 1.52 For the circuit in Fig. 1.46 (p. 29), find the power absorbed by each element.
- 1.53 For the circuit in Fig. 1.47 (p. 30), find the power absorbed by each element.
- 1.54 For the circuit given in Fig. P1.41, find the power absorbed by each element for (a)  $K = 2$  and (b)  $K = 4$ .
- 1.55 For the circuit given in Fig. P1.42, find the power absorbed by each element for (a)  $K = 2$  and (b)  $K = 4$ .
- 1.56 For the single BJT amplifier given in Problem 1.49, find the power gain  $p_2/p_1$  from source to load, where  $p_1$  is the power supplied by the independent voltage source  $v_1$  and  $p_2$  is the power absorbed by the load  $R_L = 1.5 \text{ k}\Omega$ .

P1.45,  
sistor

P1.47:

s seen

i A

P1.47,  
2 resis-



In general, when an independent voltage source is connected between a nonreference node and the reference node, the voltage of the nonreference node is constrained by the voltage source and therefore is obtained by inspection.

To determine the remaining voltage variables  $v_2$  and  $v_3$ , we proceed as before. By KCL at node  $v_2$ ,

$$2(v_2 - v_1) + 2v_2 + 4(v_2 - v_3) = 0$$

Using the fact that  $v_1 = 3$  V, simplifying this expression results in

$$8v_2 - 4v_3 = 6 \quad (2.14)$$

At node  $v_3$ , by KCL,

$$4(v_3 - v_2) + \frac{1}{2}v_2 + 4v_3 = 0$$

from which

$$-7v_2 + 16v_3 = 0 \quad (2.15)$$

(Note the simplicity of dealing with the voltage-dependent current source.)

Solving Equations (2.14) and (2.15) results in

$$v_2 = 0.96 \text{ V} \quad \text{and} \quad v_3 = 0.42 \text{ V}$$

Since  $i_1 = 2(v_1 - v_2) = 2(3 - 0.96) = 4.08$  A, then the conductance seen by the voltage source is

$$G_{eq} = \frac{i_1}{v_1} = \frac{4.08}{3} = 1.36 \text{ S}$$

Furthermore, now we can use KCL at node  $v_1$  to determine  $i_2$ . Specifically,

$$i_2 = -i_1 = -4.08 \text{ A}$$


A dependent voltage source that is connected between the reference node and a nonreference node is treated similarly to that for an independent voltage source. Specifically, the value and polarity of the dependent source determines, by inspection, the equation for that nonreference node—KCL is not applied at that node. However, after the nodal analysis of the circuit is completed, KCL can be applied at that nonreference node in order to determine the current through the dependent voltage source.
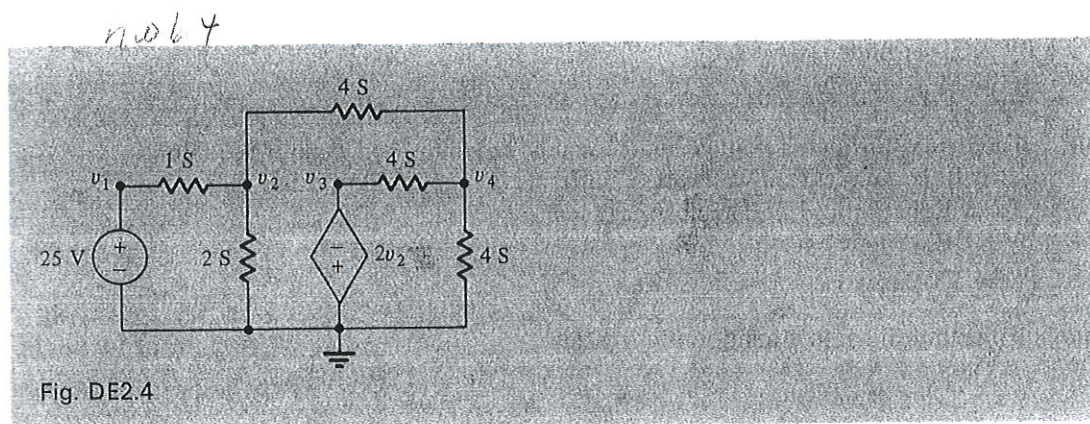
#### DRILL EXERCISE 2.4

For the circuit shown in Fig. DE2.4, find the node voltages  $v_1$ ,  $v_2$ ,  $v_3$ , and  $v_4$ . In addition, find the conductance seen by the independent voltage source and the current going down through the dependent voltage source.

Answer: 25 V; 3 V; -6 V; -1 V; 0.88 S; 20 A





Now let us consider the situation that a circuit contains a voltage source that is connected between two nonreference nodes.

#### EXAMPLE 2.5

The circuit shown in Fig. 2.10 has an independent voltage source connected between two nonreference nodes. Let us determine the node voltages  $v_1$ ,  $v_2$ , and  $v_3$  by using nodal analysis.

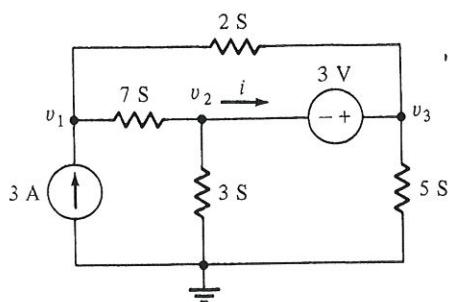


Fig. 2.10 Circuit with voltage source connected between nonreference nodes.

By KCL at node  $v_1$  we get

$$7(v_1 - v_2) + 2(v_1 - v_3) - 3 = 0$$

from which

$$9v_1 - 7v_2 - 2v_3 = 3 \quad (2.16)$$

and this is the first of the three equations needed to solve for the three voltage variables  $v_1$ ,  $v_2$ , and  $v_3$ .