


Important Remarks

- Homework is due on January 30 at the beginning of class.

1. For the circuit below,

(a) Find the output voltage v_2 in terms of the input voltage v_1 .

(b) Find $R_{eq} = v_1/i_1$

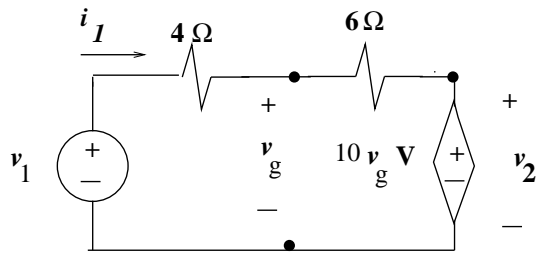

2. Problem 1.53

3. Problem 2.5

4. Problem 2.11

5. Problem 2.15