

**Important Remarks**

- Homework is due on March 9 at the beginning of class.
  1. Problem 3.12
  2. Problem 3.22
  3. Problem 3.32
  4. Problem 4.6
  5. Problem 5.1

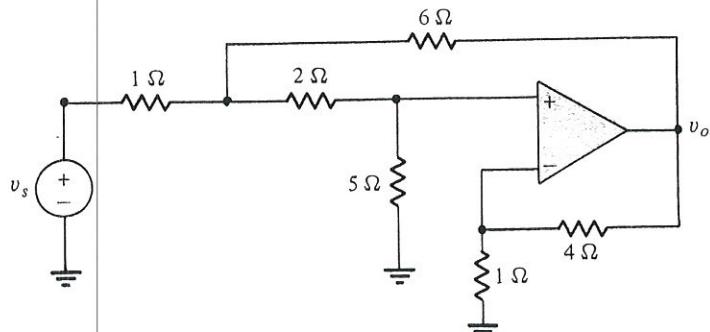


Fig. P3.11

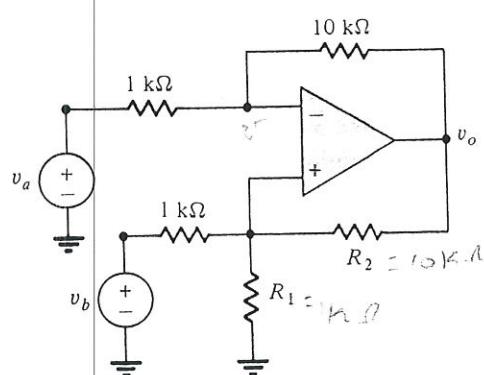


Fig. P3.12

**3.11** For the op-amp circuit given in Fig. P3.11, find the voltage gain  $v_o/v_s$ .

**3.12** For the op-amp circuit shown in Fig. P3.12, find  $v_o$  when  $R_1 = 1 \text{ k}\Omega$  and  $R_2 = 10 \text{ k}\Omega$ .

**3.13** Repeat Problem 3.12 for the case that  $R_1 = \infty$  and  $R_2 = 20 \text{ k}\Omega$ .

**3.14** For the op-amp circuit given in Fig. P3.14, find the voltage gain  $v_o/v_s$ .

**3.15** For the op-amp circuit given in Fig. P3.15, find the voltage gain  $v_o/v_s$  when  
(a)  $R_1 = 4 \Omega$ ,  $R_2 = 5 \Omega$  and (b)  $R_1 = 5 \Omega$ ,  $R_2 = 4 \Omega$ .

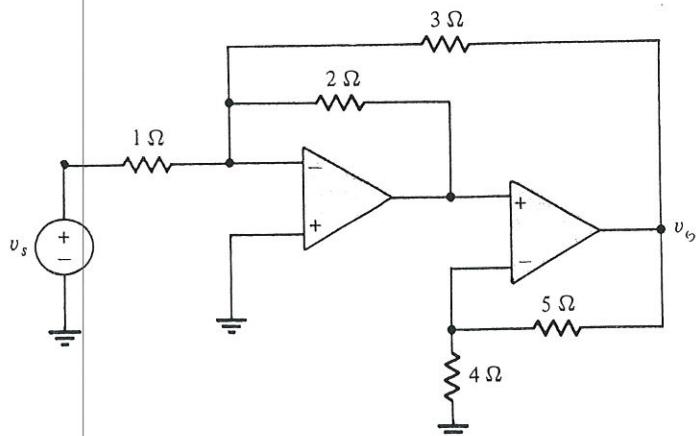


Fig. P3.14

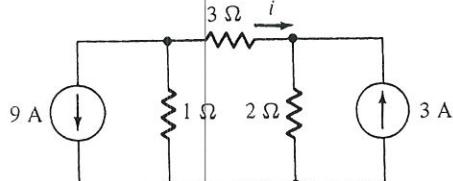


Fig. P3.19

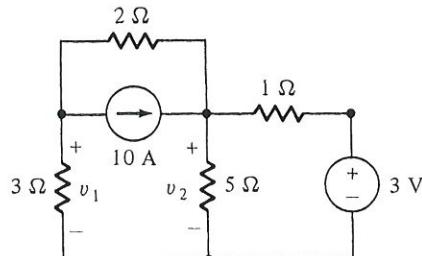


Fig. P3.20

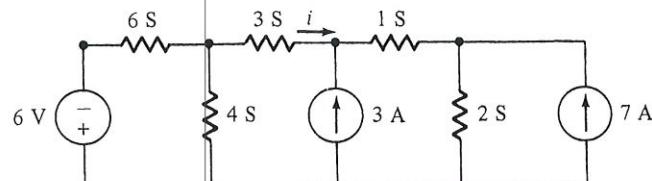


Fig. P3.21

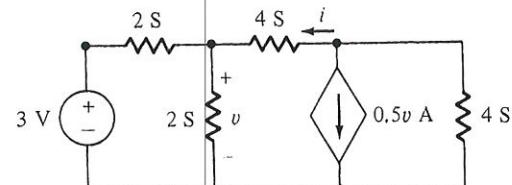


Fig. P3.22

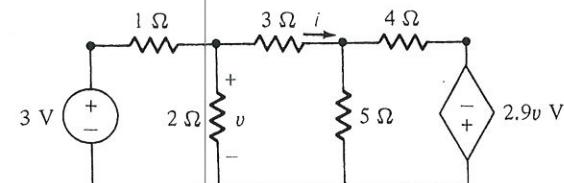


Fig. P3.23

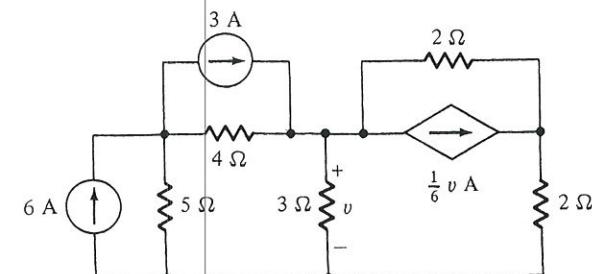


Fig. P3.24

**3.20** For the circuit shown in Fig. P3.20, use source transformations to determine  $v_1$  and  $v_2$ .

**3.21** Repeat Problem 3.18 for the circuit shown in Fig. P3.21.

**3.22** For the circuit shown in Fig. P3.22, use source transformations to determine  $i$  and  $v$ .

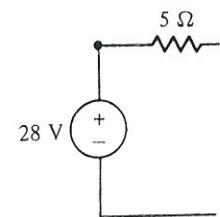


Fig. P3.25

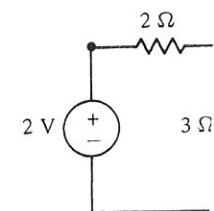


Fig. P3.26

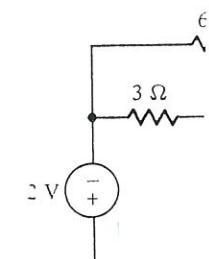


Fig. P3.27

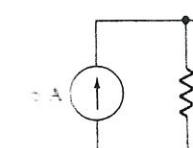


Fig. P3.28

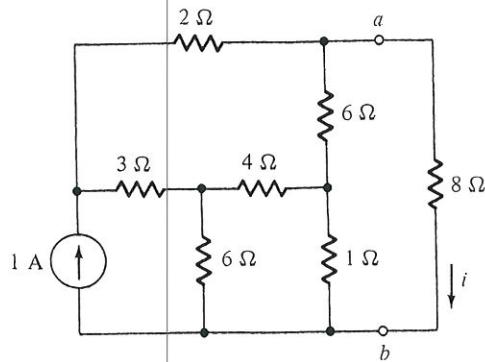


Fig. P3.29

**3.29** Repeat Problem 3.25 for the circuit shown in Fig. P3.29.

**3.30** Repeat Problem 3.25 for the circuit shown in Fig. P3.30.

**3.31** Find the Thévenin equivalent of the circuit shown in Fig. P3.31.

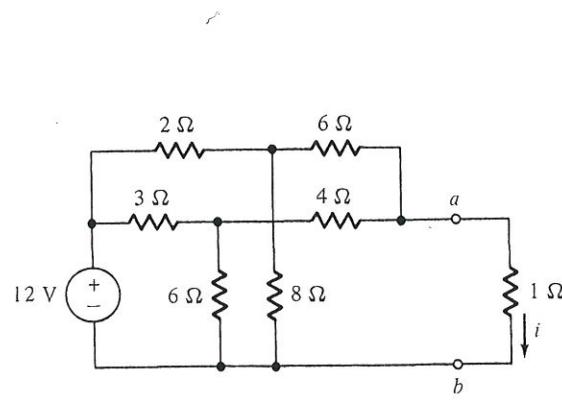


Fig. P3.30

**3.33** For the circuit given in Fig. 3.35 (p. 126), change the 2-Ω resistor to a 1-Ω resistor. Find the Thévenin equivalent of the resulting circuit.

**3.34** Find the Thévenin equivalent of the circuit shown in Fig. P3.34.

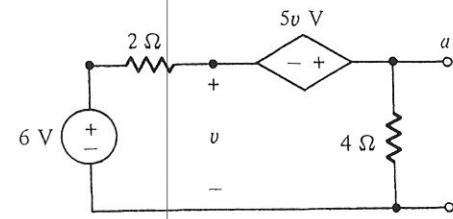


Fig. P3.31

**3.32** Find the Thévenin equivalent of the circuit shown in Fig. P3.32.

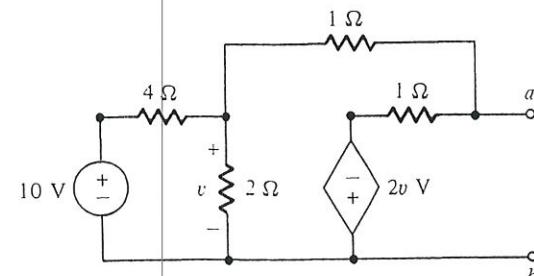


Fig. P3.32

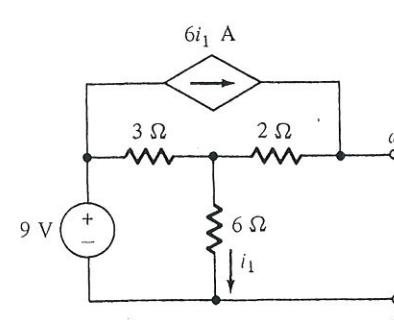


Fig. P3.34

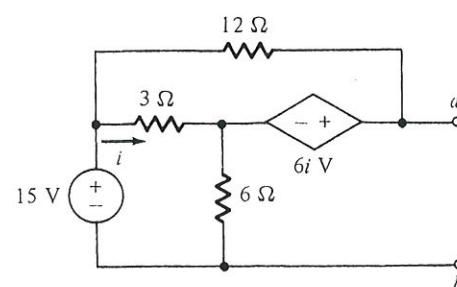


Fig. P3.35

✓ **3.35** Find  
circuit

✓ **3.36** Find  
circuit  
curr

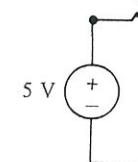


Fig. P3.36

✓ **3.37** Rep  
show

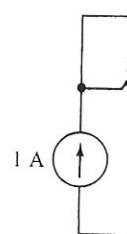


Fig. P3.37

**3.38** Find  
amp

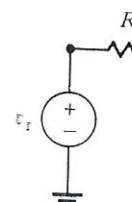


Fig. P3.38

**3.39** Find  
amp

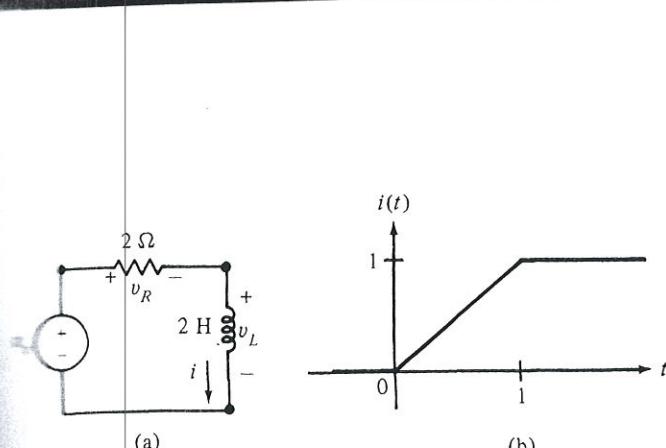


Fig. P4.6

**4.5** Repeat Problem 4.2 for the current described in Example 4.3 (p. 163). Sketch the functions.

**4.6** Given the circuit shown in Fig. P4.6(a), suppose that the current  $i(t)$  is given by the function in Fig. P4.6(b). Sketch  $v_L(t)$ ,  $w_L(t)$ ,  $p_R(t)$ ,  $v_R(t)$ , and  $v_s(t)$ .

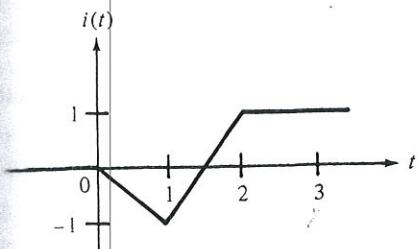


Fig. P4.7

**4.7** Repeat Problem 4.6 for the current given by the function in Fig. P4.7.

**4.8** Given the circuit shown in Fig. P4.2, suppose that the current  $i(t)$  is given by


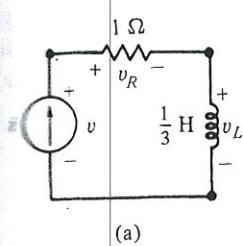


Fig. P4.10

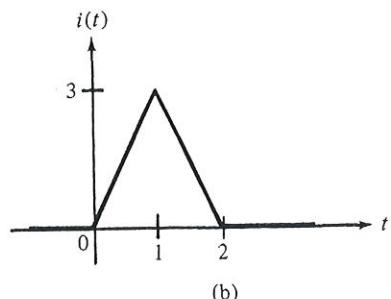

the function in Fig. P4.6(b). Sketch  $v_L(t)$ ,  $w_L(t)$ ,  $p_R(t)$ ,  $i_R(t)$ , and  $i_s(t)$ .

**4.9** Repeat Problem 4.8 for the current given in Fig. P4.7.

**4.10** For the circuit and current shown in Fig. P4.10(a) and P4.10(b), respectively, sketch  $v_R(t)$ ,  $v_L(t)$ , and  $v(t)$ .

**4.11** For the circuit shown in Fig. DE4.5 (p. 169), suppose that the voltage across the capacitor is

$$v(t) = \begin{cases} 0 & \text{for } -\infty < t < 0 \\ 1 - e^{-t/2} & \text{for } 0 \leq t < 1 \text{ s} \\ (e^{1/2} - 1)e^{-t/2} & \text{for } 1 \leq t < \infty \end{cases}$$

Find (a)  $i_C(t)$ ; (b)  $v_R(t)$ ; and (c)  $v_s(t)$ .

**4.12** For the circuit shown in Fig. P4.12, suppose that the voltage across the capacitor is

$$v(t) = \begin{cases} 0 & \text{for } -\infty < t < 0 \\ 1 - e^{-t/2} & \text{for } 0 \leq t < \infty \end{cases}$$

Find (a)  $i_C(t)$ ; (b)  $i_R(t)$ ; and (c)  $i_s(t)$ .

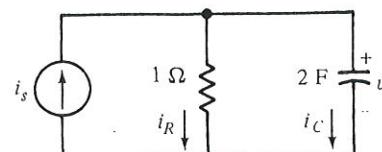
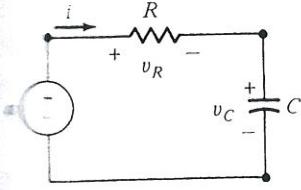
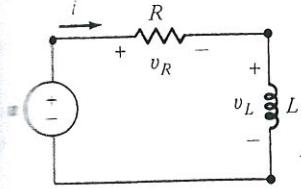
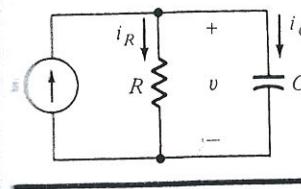
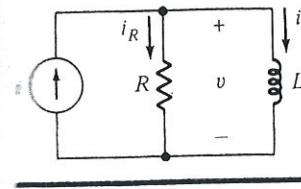


Fig. P4.12

8. In a linear circuit if the input is differentiated, then the zero-state output is differentiated; if the input is integrated, so is the output.
9. Zero-state step responses for  $RL$  and  $RC$  series and parallel circuits are summarized in Table 5.1.

**Table 5.1 SUMMARY OF SERIES AND PARALLEL  
 $RC$  AND  $RL$  CIRCUIT STEP RESPONSES**

	$v(t) = u(t)$ $i(t) = \frac{1}{R} e^{-t/RC} u(t)$ $v_R(t) = e^{-t/RC} u(t)$ $v_C(t) = (1 - e^{-t/RC}) u(t)$
	$v(t) = u(t)$ $i(t) = \frac{1}{R} (1 - e^{-Rt/L}) u(t)$ $v_R(t) = (1 - e^{-Rt/L}) u(t)$ $v_L(t) = e^{-Rt/L} u(t)$
	$i(t) = u(t)$ $v(t) = R(1 - e^{-t/RC}) u(t)$ $i_R(t) = (1 - e^{-t/RC}) u(t)$ $i_C(t) = e^{-t/RC} u(t)$
	$i(t) = u(t)$ $v(t) = Re^{-Rt/L} u(t)$ $i_R(t) = e^{-Rt/L} u(t)$ $i_L(t) = (1 - e^{-Rt/L}) u(t)$

### ● PROBLEMS FOR CHAPTER 5

- 5.1 For the circuit shown in Fig. P5.1, the switch is opened when  $t = 0$ . Find  $v(t)$  and  $i(t)$  for all  $t$ . Sketch these functions.
- 5.2 For the circuit shown in Fig. P5.1, replace the capacitor with a 5-H inductor and repeat Problem 5.1.

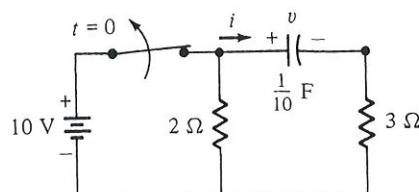


Fig. P5.1