

**Important Remarks**

- Homework is due on March 27 at the beginning of class.

1. Problem 4.16

2. Problem 4.20

3. Problem 5.3

4. Problem 5.27

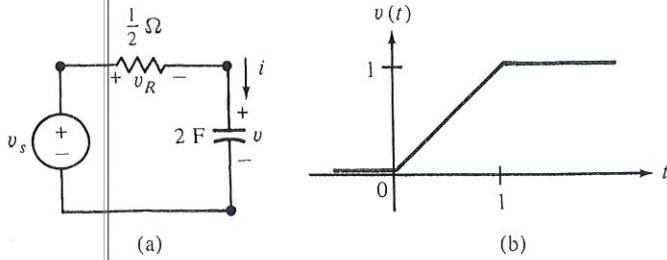


Fig. P4.14

- 4.13** Repeat Problem 4.12 for the voltage given in Problem 4.11.
- 4.14** Given the circuit and voltage shown in Fig. P4.14(a) and P4.14(b), respectively, sketch  $i(t)$ ,  $w_C(t)$ ,  $p_R(t)$ ,  $v_R(t)$ , and  $v_s(t)$ .
- 4.15** Given the circuit shown in Fig. P4.12, suppose that the voltage  $v(t)$  is described by the function given in Fig. P4.14(b). Find  $i_C(t)$ ,  $w_C(t)$ ,  $p_R(t)$ ,  $i_R(t)$ , and  $i_s(t)$ , and sketch these functions.
- 4.16** Given the op-amp circuit shown in Fig. P4.16, suppose that  $v(t)$  is described by the function given in Fig. P4.14(b). Sketch  $i(t)$ ,  $i_R(t)$ ,  $v_R(t)$ ,  $v_s(t)$ , and  $v_o(t)$ .

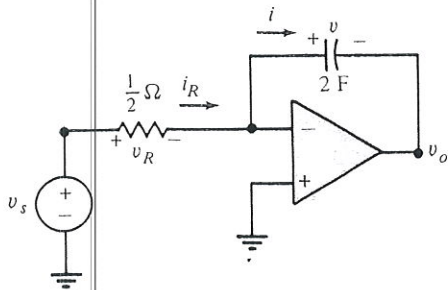


Fig. P4.16

- 4.17** Repeat Problem 4.16 for the case that there is an additional  $\frac{1}{2}\text{-}\Omega$  resistor in parallel with the capacitor.
- 4.18** Repeat Problem 4.16 for the op-amp circuit shown in Fig. P4.18.
- 4.19** For the op-amp circuit given in Fig. P4.18, place an additional  $\frac{1}{2}\text{-}\Omega$  resistor in parallel with the capacitor and repeat Problem 4.16.

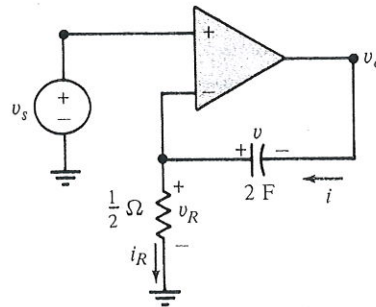


Fig. P4.18

- 4.20** Repeat Problem 4.16 for the op-amp circuit shown in Fig. P4.20.

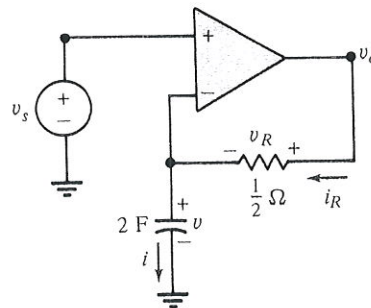


Fig. P4.20

- 4.21** For the op-amp circuit given in Fig. P4.20, place an additional  $\frac{1}{2}\text{-}\Omega$  resistor in parallel with the capacitor and repeat Problem 4.16.
- 4.22** Verify the following:
- $[u(t)]^2 = u(t)$
  - $[u(t-a)]^2 = u(t-a)$
  - $[r(t)]^2 = t^2 u(t)$
  - $[r(t-a)]^2 = (t-a)^2 u(t-a)$

- 5.3 For the circuit shown in Fig. P5.3, suppose that  $v_s(t) = 15 - 15u(t)$  V. Find  $v(t)$  and  $i(t)$  for all  $t$ . Sketch these functions.

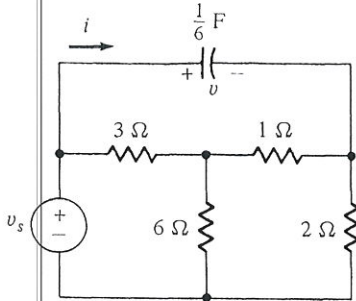


Fig. P5.3

- 5.4 For the circuit in Fig. P5.3, replace the capacitor with an 8-H inductor, change the 1- $\Omega$  resistor to 6  $\Omega$ , and suppose that  $v_s(t) = 8 - 8u(t)$  V; then repeat Problem 5.3.
- 5.5 For the circuit given in Fig. DE5.2 (p. 226), replace the capacitor with a 10-H inductor. Find the current through the inductor and the voltage across the inductor for all  $t$ .
- 5.6 For the circuit shown in Fig. P5.6, find  $v(t)$  and  $i(t)$  for all  $t$ .

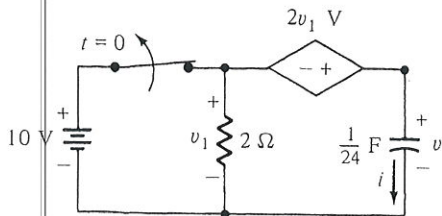


Fig. P5.6

- 5.7 For the circuit given in Fig. P5.6, connect a 6- $\Omega$  resistor in parallel with the capacitor, and repeat Problem 5.6.
- 5.8 For the circuit shown in Fig. P5.8, suppose that  $v_s(t) = 9 - 9u(t)$  V. Find  $i(t)$  and  $v(t)$  for all  $t$ .

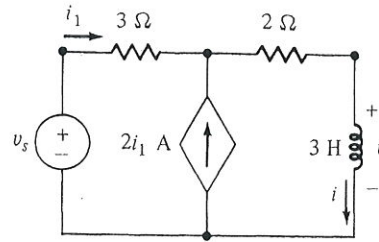


Fig. P5.8

- 5.9 For the circuit given in Fig. P5.8, replace the inductor with a 3-F capacitor, and repeat Problem 5.8.
- 5.10 For the op-amp circuit shown in Fig. P5.10, suppose that  $i_s(t) = 1 - u(t)$  A. Find  $v_C(t)$  and  $v_o(t)$  for all  $t$ .

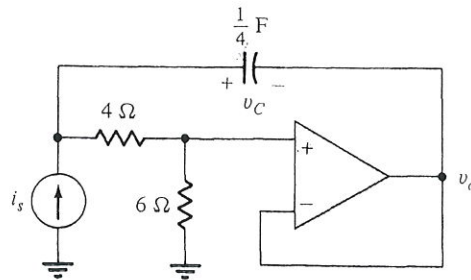


Fig. P5.10

- 5.11 For the op-amp circuit shown in Fig. P5.10, connect a 4- $\Omega$  resistor in parallel

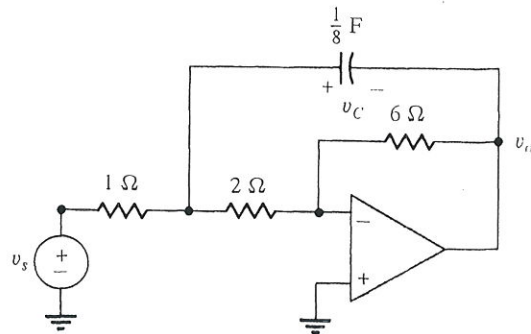


Fig. P5.12

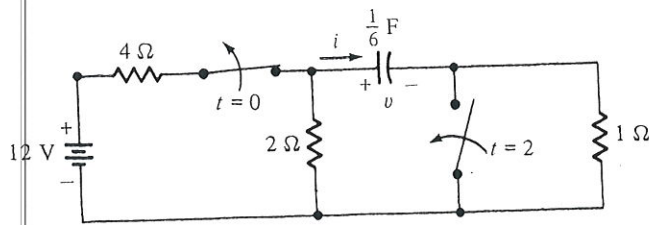


Fig. P5.20

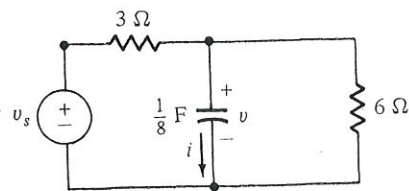


Fig. P5.22

- 5.21 For the circuit given in Fig. DE5.6 (p. 236), replace the 4-Ω resistor with a 3-H inductor, and repeat Drill Exercise 5.6.
- 5.22 For the circuit shown in Fig. P5.22, suppose that  $v_s(t) = u(t)$  V. Find the zero-state step responses  $v(t)$  and  $i(t)$ .
- 5.23 For the circuit shown in Fig. P5.22, replace the capacitor with a  $\frac{1}{8}$ -H inductor, and repeat Problem 5.22.
- 5.24 For the circuit given in Fig. P5.3, suppose that  $v_s(t) = u(t)$  V. Find the zero-state step responses  $v(t)$  and  $i(t)$ .
- 5.25 For the circuit given in Fig. P5.8, suppose that  $v_s(t) = u(t)$  V. Find the zero-state step responses  $i(t)$  and  $v(t)$ .
- 5.26 For the circuit given in Fig. P5.8, replace the inductor with a 3-F capacitor, and repeat Problem 5.25.
- 5.27 For the circuit shown in Fig. P5.27, suppose that  $v_s(t) = 7u(t)$  V. Find the zero-state response  $v(t)$ .
- 5.28 For the op-amp circuit given in Fig. P5.10, suppose that  $i_s(t) = u(t)$  A. Find the zero-state step responses  $v_C(t)$  and  $v_o(t)$ .
- 5.29 For the op-amp circuit given in Fig. P5.12, suppose that  $v_s(t) = u(t)$  V. Find the zero-state step responses  $v_C(t)$  and  $v_o(t)$ .
- 5.30 For the op-amp circuit shown in Fig. P5.10, connect a 4-Ω resistor in parallel with the capacitor. Suppose that  $i_s(t) = u(t)$  A. Find the zero-state step responses  $v_C(t)$  and  $v_o(t)$ .
- 5.31 For the op-amp circuit shown in Fig. P5.12, connect an 8-Ω resistor in parallel with the capacitor. Suppose that  $v_s(t) = u(t)$  V. Find the zero-state step responses  $v_C(t)$  and  $v_o(t)$ .
- 5.32 For the op-amp circuit in Fig. P5.32, suppose that  $R_1 = R_2 = R_3 = R$ . Find the zero-state step response  $v_o(t)$ .
- 5.33 For the circuit given in Fig. P5.32, interchange capacitor  $C$  and resistor  $R_3$  and repeat Problem 5.32.

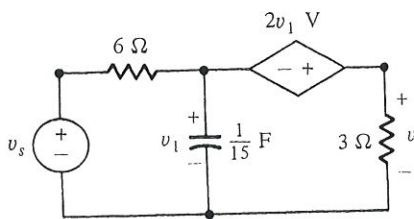


Fig. P5.27

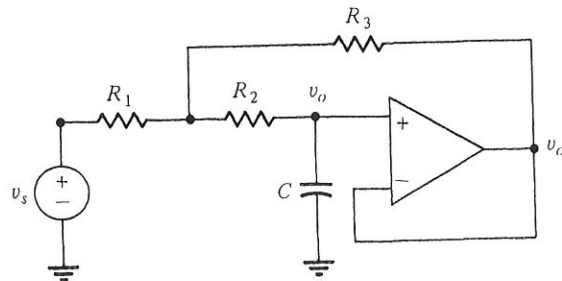


Fig. P5.32