

Important Remarks

- Homework is due on April 1st at the beginning of class.
1. Problem 8.1
 2. Problem 8.3
 3. Problem 8.14
 4. Problem 8.17

PROBLEMS FOR CHAPTER 8

- 8.1** For the circuit shown in Fig. P8.1, suppose that $v_s(t) = 12 \cos 2t + 5 \sin 2t$ V. Find $i(t)$ and $v_o(t)$ using time-domain analysis, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.

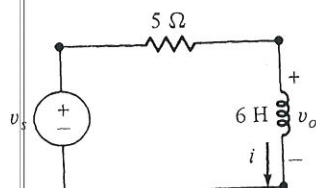


Fig. P8.1

- 8.2** For the circuit shown in Fig. P8.2, suppose that $i_s(t) = 8 \sin \sqrt{3}t$ A. Find $v_o(t)$ using time-domain analysis, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.

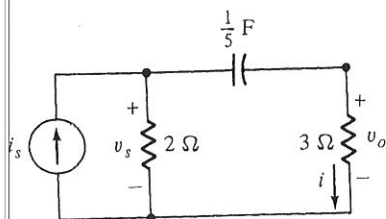


Fig. P8.2

- 8.3** For the circuit given in Fig. P8.1, place an additional $5\text{-}\Omega$ resistor in parallel with the inductor and repeat Problem 8.1.
- 8.4** For the simple series RC circuit given in Fig. 8.4(a) (p. 350), place an additional $1\text{-}\Omega$ resistor in parallel with the capacitor. Find $v_o(t)$ and $i(t)$ using time-domain analysis for the resulting circuit, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.
- 8.5** For the series RLC circuit given in Fig. 8.5 (p. 352) suppose that $R = \frac{5}{4}\text{ }\Omega$, $L = \frac{1}{4}\text{ H}$, $C = 1\text{ F}$, and $v_s(t) = 4 \cos 2t$ V. Find $v_C(t)$ using time-domain analysis,

and determine by how much $v_C(t)$ either leads or lags $v_s(t)$.

- 8.6** For the RLC circuit shown in Fig. P8.6, suppose that $v_s(t) = 3 \cos t$ V. Find $v_C(t)$ using time-domain analysis, and determine by how much $v_C(t)$ either leads or lags $v_s(t)$.

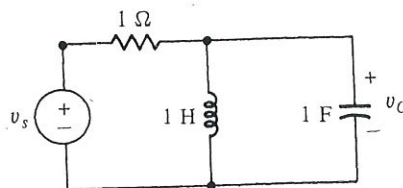


Fig. P8.6

- 8.7** For the RC circuit given in Fig. 8.4(a) (p. 350), find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 6 \sin 2t u(t)$ V. (Note: The zero-state response includes both the forced and the natural responses.)
- 8.8** For the series RLC circuit given in Fig. 8.5 (p. 352), suppose that $R = \frac{5}{4}\text{ }\Omega$, $L = \frac{1}{4}\text{ H}$, and $C = 1\text{ F}$. Find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 4 \cos 2t u(t)$ V.
- 8.9** For the circuit given in Fig. P8.6, find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 3 \cos t u(t)$ V.
- 8.10** Repeat Problem 8.9 for the case that the value of the resistor is changed to $0.5\text{ }\Omega$.
- 8.11** Find the exponential form of the following complex numbers given in rectangular form:
- | | |
|---------------|-----------|
| (a) $4 + j7$ | (e) 4 |
| (b) $3 - j5$ | (f) -5 |
| (c) $-2 + j3$ | (g) $j7$ |
| (d) $-1 - j6$ | (h) $-j2$ |
- 8.12** Find the rectangular form of the following complex numbers given in expo-

ponential form:

- (a) $3e^{j70^\circ}$ (e) $6e^{j90^\circ}$
 (b) $2e^{j120^\circ}$ (f) e^{-j90°
 (c) $5e^{-j60^\circ}$ (g) $2e^{j180^\circ}$
 (d) $4e^{-j150^\circ}$ (h) $2e^{-j180^\circ}$

8.13 Find the rectangular form of the sum $A_1 + A_2$ given that

- (a) $A_1 = 3e^{j30^\circ}$; $A_2 = 4e^{j60^\circ}$
 (b) $A_1 = 3e^{j30^\circ}$; $A_2 = 4e^{-j30^\circ}$
 (c) $A_1 = 5e^{-j60^\circ}$; $A_2 = 2e^{j120^\circ}$
 (d) $A_1 = 4e^{j45^\circ}$; $A_2 = 2e^{-j90^\circ}$

8.14 Express the following sums as a single sinusoid of the form $A \cos(\omega t + \theta)$:

- (a) $3 \cos(\omega t + 30^\circ) + 4 \cos(\omega t + 60^\circ)$
 (b) $3 \cos(\omega t + 30^\circ) + 4 \cos(\omega t - 60^\circ)$
 (c) $5 \cos(\omega t - 60^\circ) + 2 \cos(\omega t + 120^\circ)$
 (d) $4 \cos(\omega t + 45^\circ) + 2 \sin \omega t$

8.15 For the complex numbers given in Problem 8.13, find the rectangular form of the product $A_1 A_2$.

8.16 Verify the following identities:

- (a) $Me^{j90^\circ} = jM$
 (b) $Me^{-j90^\circ} = -jM$
 (c) $Me^{j180^\circ} = -M$
 (d) $Me^{-j180^\circ} = -M$
 (e) $Me^{j0^\circ} = M$
 (f) $-Me^{j\theta} = Me^{j(\theta \pm 180^\circ)}$

8.17 Express the following as a single complex number in exponential form:

- (a) $\frac{-j6}{1+j}$ (d) $\frac{85}{-1-j4}$
 (b) $\frac{-8}{2+j3}$ (e) $\frac{200(1-j)}{4+j3}$
 (c) $\frac{j3}{-2+j}$ (f) $\frac{20(1+j)}{4+j3} e^{-j30^\circ}$

(g) $37.1e^{j14^\circ} + 20.6e^{-j166^\circ}$

(h) $16.5e^{j14^\circ} + 4.12e^{-j76^\circ}$

8.18 Express each part of Problem 8.17 as a single complex number in rectangular form.

8.19 Express each of the following as a single complex number:

- (a) $2 + 2e^{j120^\circ} + 2e^{-j120^\circ}$
 (b) $2e^{j60^\circ} + 2e^{j180^\circ} + 2e^{-j60^\circ}$
 (c) $2e^{j45^\circ} + 2e^{j165^\circ} + 2e^{-j75^\circ}$

8.20 Repeat Problem 8.1 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.21 Repeat Problem 8.2 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.22 Repeat Problem 8.3 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.23 Repeat Problem 8.4 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.24 Repeat Problem 8.5 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.25 Repeat Problem 8.6 using frequency-domain analysis. Draw the corresponding phasor diagram.

8.26 For the series RLC circuit given in Fig. 8.5 (p. 352), suppose that $R = 4 \Omega$, $L = 2 \text{ H}$, and $v_s(t) = A \cos(3t + \theta) \text{ V}$. Determine by how much $v_C(t)$ either leads or lags $v_s(t)$ when C is (a) $\frac{1}{8} \text{ F}$, (b) $\frac{1}{18} \text{ F}$, and (c) $\frac{1}{32} \text{ F}$.

8.27 For the circuit shown in Fig. P8.27, (a) use mesh analysis to find $v_o(t)$, and

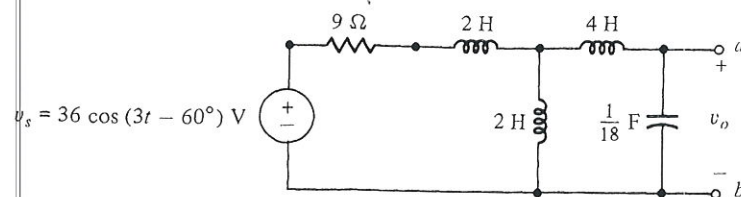


Fig. P8.27