

Important Remarks

- Homework is due on April 10 at the beginning of class.

1. Problem 8.24
2. Problem 8.28
3. Problem 8.36

- ponential form:
- (a) $3e^{j70^\circ}$ (e) $6e^{j90^\circ}$
 (b) $2e^{j120^\circ}$ (f) e^{-j90°
 (c) $5e^{-j60^\circ}$ (g) $2e^{j180^\circ}$
 (d) $4e^{-j150^\circ}$ (h) $2e^{-j180^\circ}$
- 8.13 Find the rectangular form of the sum $A_1 + A_2$ given that
 (a) $A_1 = 3e^{j30^\circ}$; $A_2 = 4e^{j60^\circ}$
 (b) $A_1 = 3e^{j30^\circ}$; $A_2 = 4e^{-j30^\circ}$
 (c) $A_1 = 5e^{-j60^\circ}$; $A_2 = 2e^{j120^\circ}$
 (d) $A_1 = 4e^{j45^\circ}$; $A_2 = 2e^{-j90^\circ}$
- 8.14 Express the following sums as a single sinusoid of the form $A \cos(\omega t + \theta)$:
 (a) $3 \cos(\omega t + 30^\circ) + 4 \cos(\omega t + 60^\circ)$
 (b) $3 \cos(\omega t + 30^\circ) + 4 \cos(\omega t - 60^\circ)$
 (c) $5 \cos(\omega t - 60^\circ) + 2 \cos(\omega t + 120^\circ)$
 (d) $4 \cos(\omega t + 45^\circ) + 2 \sin \omega t$
- 8.15 For the complex numbers given in Problem 8.13, find the rectangular form of the product $A_1 A_2$.
- 8.16 Verify the following identities:
 (a) $Me^{j90^\circ} = jM$
 (b) $Me^{-j90^\circ} = -jM$
 (c) $Me^{j180^\circ} = -M$
 (d) $Me^{-j180^\circ} = -M$
 (e) $Me^{j0^\circ} = M$
 (f) $-Me^{j\theta} = Me^{j(\theta \pm 180^\circ)}$
- 8.17 Express the following as a single complex number in exponential form:
 (a) $\frac{-j6}{1+j}$ (d) $\frac{85}{-1-j4}$
 (b) $\frac{-8}{2+j3}$ (e) $\frac{200(1-j)}{4+j3}$
 (c) $\frac{j3}{-2+j}$ (f) $\frac{20(1+j)}{4+j3} e^{-j30^\circ}$
- (g) $37.1e^{j14^\circ} + 20.6e^{-j166^\circ}$
 (h) $16.5e^{j14^\circ} + 4.12e^{-j76^\circ}$
- 8.18 Express each part of Problem 8.17 as a single complex number in rectangular form.
- 8.19 Express each of the following as a single complex number:
 (a) $2 + 2e^{j120^\circ} + 2e^{-j120^\circ}$
 (b) $2e^{j60^\circ} + 2e^{j180^\circ} + 2e^{-j60^\circ}$
 (c) $2e^{j45^\circ} + 2e^{j165^\circ} + 2e^{-j75^\circ}$
- 8.20 Repeat Problem 8.1 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.21 Repeat Problem 8.2 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.22 Repeat Problem 8.3 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.23 Repeat Problem 8.4 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.24 Repeat Problem 8.5 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.25 Repeat Problem 8.6 using frequency-domain analysis. Draw the corresponding phasor diagram.
- 8.26 For the series RLC circuit given in Fig. 8.5 (p. 352), suppose that $R = 4 \Omega$, $L = 2 \text{ H}$, and $v_s(t) = A \cos(3t + \theta) \text{ V}$. Determine by how much $v_c(t)$ either leads or lags $v_s(t)$ when C is (a) $\frac{1}{8} \text{ F}$, (b) $\frac{1}{18} \text{ F}$, and (c) $\frac{1}{32} \text{ F}$.
- 8.27 For the circuit shown in Fig. P8.27, (a) use mesh analysis to find $v_o(t)$, and

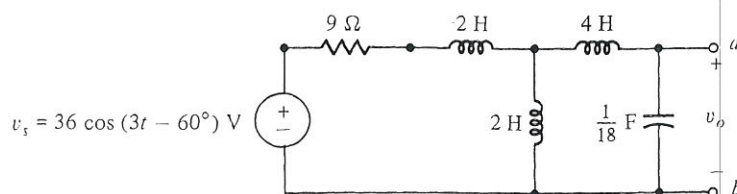


Fig. P8.27

● PROBLEMS FOR CHAPTER 8

- 8.1 For the circuit shown in Fig. P8.1, suppose that $v_s(t) = 12 \cos 2t + 5 \sin 2t$ V. Find $i(t)$ and $v_o(t)$ using time-domain analysis, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.

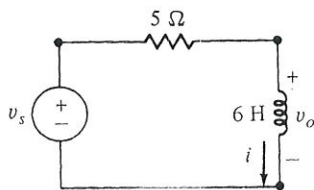


Fig. P8.1

- 8.2 For the circuit shown in Fig. P8.2, suppose that $i_s(t) = 8 \sin \sqrt{3}t$ A. Find $v_o(t)$ using time-domain analysis, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.

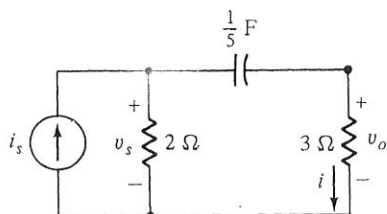


Fig. P8.2

- 8.3 For the circuit given in Fig. P8.1, place an additional 5- Ω resistor in parallel with the inductor and repeat Problem 8.1.
- 8.4 For the simple series RC circuit given in Fig. 8.4(a) (p. 350), place an additional 1- Ω resistor in parallel with the capacitor. Find $v_o(t)$ and $i(t)$ using time-domain analysis for the resulting circuit, and determine by how much $v_o(t)$ either leads or lags $v_s(t)$.
- 8.5 For the series RLC circuit given in Fig. 8.5 (p. 352) suppose that $R = \frac{5}{4} \Omega$, $L = \frac{1}{4}$ H, $C = 1$ F, and $v_s(t) = 4 \cos 2t$ V. Find $v_C(t)$ using time-domain analysis,

and determine by how much $v_C(t)$ either leads or lags $v_s(t)$.

- 8.6 For the RLC circuit shown in Fig. P8.6, suppose that $v_s(t) = 3 \cos t$ V. Find $v_C(t)$ using time-domain analysis, and determine by how much $v_C(t)$ either leads or lags $v_s(t)$.

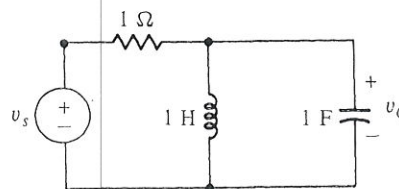


Fig. P8.6

- 8.7 For the RC circuit given in Fig. 8.4(a) (p. 350), find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 6 \sin 2t u(t)$ V. (Note: The zero-state response includes both the forced and the natural responses.)
- 8.8 For the series RLC circuit given in Fig. 8.5 (p. 352), suppose that $R = \frac{5}{4} \Omega$, $L = \frac{1}{4}$ H, and $C = 1$ F. Find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 4 \cos 2t u(t)$ V.
- 8.9 For the circuit given in Fig. P8.6, find the zero-state response $v_C(t)$ for the case that the input voltage is $v_s(t) = 3 \cos t u(t)$ V.
- 8.10 Repeat Problem 8.9 for the case that the value of the resistor is changed to 0.5 Ω .
- 8.11 Find the exponential form of the following complex numbers given in rectangular form:
- | | |
|---------------|-----------|
| (a) $4 + j7$ | (e) 4 |
| (b) $3 - j5$ | (f) -5 |
| (c) $-2 + j3$ | (g) $j7$ |
| (d) $-1 - j6$ | (h) $-j2$ |
- 8.12 Find the rectangular form of the following complex numbers given in expo-

8 13

8 14

8 15

8 16

8 17

DRILL EXERCISE 8.1

Find $i(t)$ and $v(t)$ for the circuit shown in Fig. DE8.1.
Answer: $2 \cos 2t$ A; $-8 \sin 2t$ V

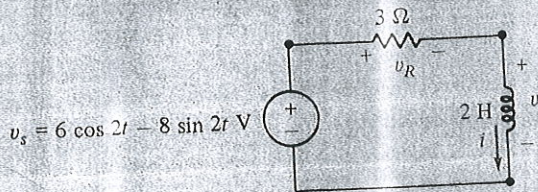


Fig. DE8.1

Having analyzed a first-order sinusoidal circuit, let us now look at an example of a second-order sinusoidal circuit.

EXAMPLE 8.2

For the series RLC shown in Fig. 8.5, we have already seen [Equation (6.26) on p. 295] that

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{1}{LC} v_C = \frac{v_s}{LC}$$

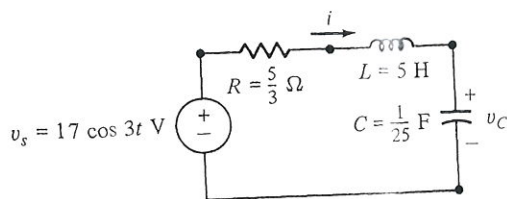


Fig. 8.5 Series RLC sinusoidal circuit.

Thus,

$$\frac{d^2 v_C}{dt^2} + \frac{1}{3} \frac{dv_C}{dt} + 5v_C = 85 \cos 3t$$

and the forced response has the form

$$v_C(t) = A_1 \cos 3t + A_2 \sin 3t$$

Substituting this into the differential equation and collecting terms, we get

$$(-4A_1 + A_2) \cos 3t + (-A_1 - 4A_2) \sin 3t = 85 \cos 3t$$

Equating coefficients yields the pair of simultaneous equations

$$-4A_1 + A_2 = 85 \quad \text{and} \quad -A_1 - 4A_2 = 0$$

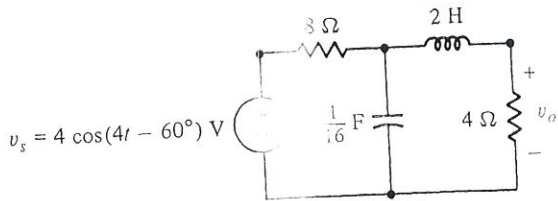


Fig. P8.28

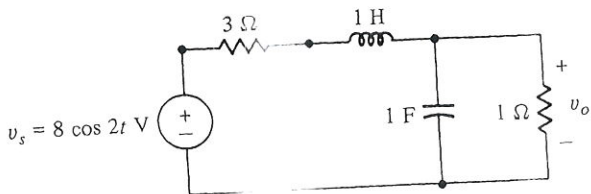


Fig. P8.29

(b) find the impedance seen by the voltage source.

8.28 For the circuit shown in Fig. P8.28, (a) use nodal analysis to find $v_o(t)$, and (b) find the impedance seen by the voltage source.

8.29 For the circuit shown in Fig. P8.29, (a) use nodal analysis to find $v_o(t)$, and (b) find the impedance seen by the voltage source.

8.30 For the circuit given in Fig. P8.29, change the value of the inductor to $\frac{1}{5}$ H, and repeat Problem 8.29.

8.31 For the RLC connection shown in Fig. P8.31, find the impedance Z when (a) $\omega = 1$ rad/s, (b) $\omega = 4$ rad/s, and (c) $\omega = 8$ rad/s.

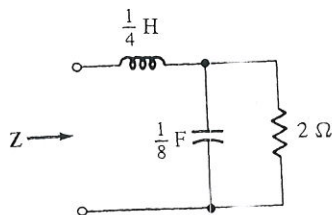


Fig. P8.31

8.32 For the RLC connection shown in Fig. P8.32, find the admittance Y when

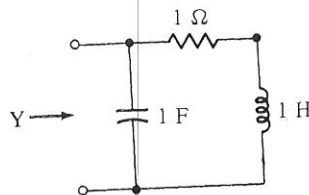


Fig. P8.32

(a) $\omega = 1$ rad/s, (b) $\omega = \frac{1}{2}$ rad/s, and (c) $\omega = \frac{1}{4}$ rad/s.

8.33 Consider the circuit given in Fig. P8.33. (a) Find $v_o(t)$ by using voltage division. (b) Place an additional 5-ohm resistor in parallel with the inductor, and find $v_o(t)$ for the resulting circuit by using voltage division.

8.34 For the circuit given in Fig. P8.27, find $i(t)$ by using current division.

8.35 For the circuit given in Fig. P8.27, find the Thévenin-equivalent circuit with respect to terminals a and b .

8.36 For the circuit given in Fig. P8.28, find $v_o(t)$ by first replacing the portion of the circuit to the left of the 4-ohm resistor with its Thévenin equivalent.

8.37 For the circuit given in Fig. P8.29, find $v_o(t)$ by first replacing the portion of the circuit to the left of the 1-ohm resistor with its Norton equivalent.

$150\sqrt{2} \angle$

$150\sqrt{2} \angle$

Fig. P8.30

8.38 For the circuit shown in Fig. P8.38, find the output voltage $v_o(t)$ when the input voltage is $v_s = 9 \cos t$ V.

8.39 For the circuit shown in Fig. P8.39, find the output voltage $v_o(t)$ when the input voltage is $v_s = 9 \cos t$ V.

8.40 For the circuit shown in Fig. P8.40, find the output voltage $v_o(t)$ when the input voltage is $v_s = 9 \cos t$ V.

8.41 For the circuit shown in Fig. P8.41, find the output voltage $v_o(t)$ when the input voltage is $v_s = 9 \cos t$ V.



Fig. P8.4

$v_s = 9 \cos t$

Fig. P8.4