
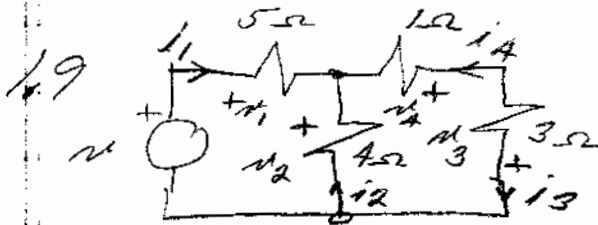


$$i(t) = \frac{dq}{dt}$$

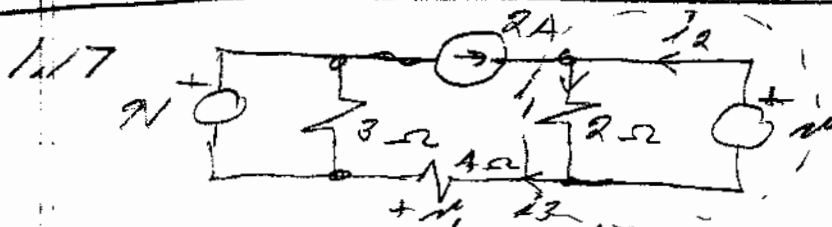

- a)  $i_1 = 4$ ;  $v_1 = 20V$
- b)  $i_2 = -2$ ;  $v_2 = 8V$
- c)  $i_3 = 2$ ;  $v_3 = -6V$
- d)  $i_4 = -2$ ;  $v_4 = -2V$



a)  $v = 2V$

$$i_1 = \frac{v}{2} = 1 \quad ; \quad 2 + i_2 - i_1 = 0 \quad \therefore i_2 = -1$$

$$i_3 = i_1 - i_2 = 1 - (-1) = 2A \quad \therefore v_1 = -2 \times 4 = -8V$$

b)  $v = 4V$

$$i_1 = \frac{4}{2} = 2 \quad ; \quad i_2 = i_1 - 2 = 0$$


$$i_3 = i_1 - i_2 = 2 \quad \therefore v_1 = 2 \times 4 = 8V$$

c)  $v = 6V$

$$i_1 = \frac{6}{2} = 3 \quad ; \quad i_2 = i_1 - 2 = 1$$

$$i_3 = i_1 - i_2 = 2 \quad \therefore v_1 = -2 \times 4 = -8V$$

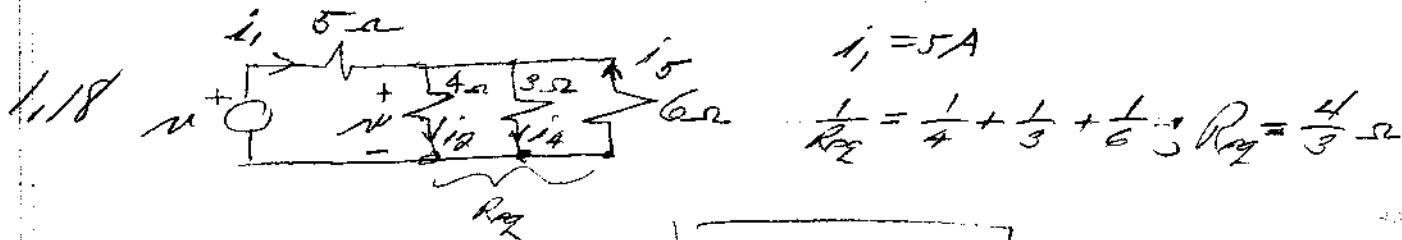Could work problem by realizing that current into dotted region = 2A  $\therefore$  current out of region  $i_3 = 2A$  independent of value of  $v$ !



$$i_1 = \frac{v}{5 + \frac{4}{3}} = \frac{5}{19/3} = \frac{15}{19} = 0.789A$$


$$v = i_1 \times R_{eq} = 5 \times \frac{4}{3} = \frac{20}{3} = 6.67V$$

$$i_2 = \frac{v}{4} = \frac{5}{3} \quad ; \quad i_4 = \frac{v}{3} = \frac{20}{9}A$$

$$i_5 = -\frac{v}{6} = -\frac{20}{3 \times 6} = -\frac{10}{9}A \quad ; \quad i_3 = i_4 - i_5 = \frac{30}{9}$$

1.26 a)  $i = -0.6A$

b)  $i = \text{anything}$

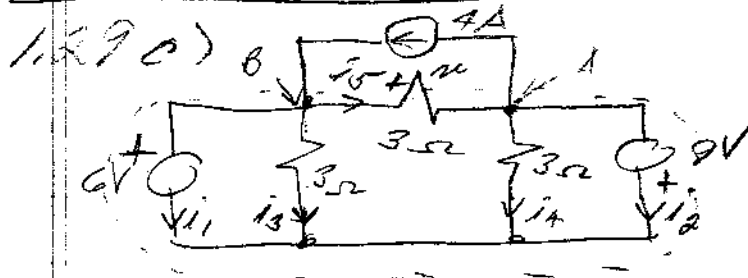

$$i_3 = \frac{6}{3} = 2A$$

$$i_4 = \frac{9}{3} = -3A$$

using KCL @ node A gives:

$$4 - i_5 + i_4 + i_2 = 0 \quad (1)$$

KVL around dotted loop gives:  $-6 + v - 9 = 0 \Rightarrow v = 15V$   
and  $i_5 = \frac{v}{3} = 5A$

from (1) above  $i_2 = i_5 - i_4 - 4 = 5 + 3 - 4 = 4A$  ←


KCL @ node B gives:  $i_1 + i_3 + i_5 - 4 = 0$

$$\therefore i_1 = 4 - i_3 - i_5 = 4 - 2 - 5 = -3A$$
 ←

EE 211

Homework 3

1.38c

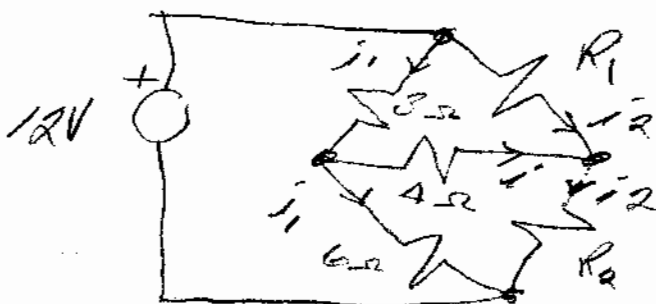


$$i = 0$$

$$\therefore i_{4\Omega} = 0$$

For balance  $3i_1 = i_2 R_1$  and  $6i_1 = i_2 R_2$

Dividing these two equations gives:  $\boxed{\frac{R_2}{R_1} = 2}$  ←

1.41a)

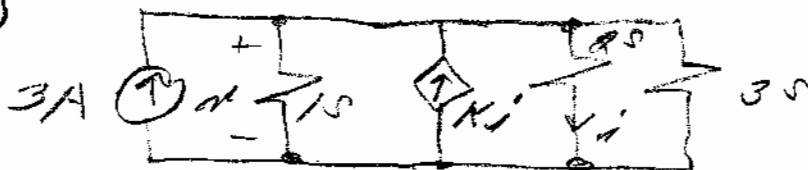


$$K = 2$$

$$i = 2v$$

KCL gives:  $-3 + i - 2i + 2v + 3v = 0$

$$\therefore v - 4v + 2v + 3v = 3$$

$$\boxed{v = \frac{3}{2}} \text{ V} \leftarrow$$

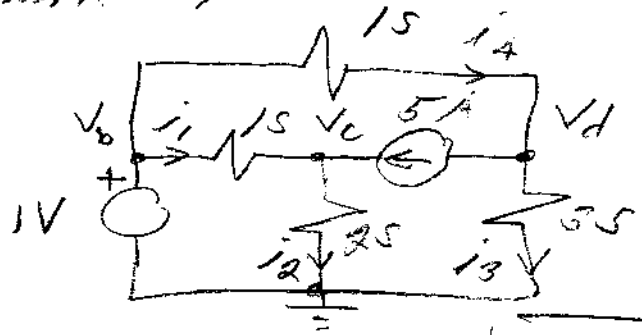Q.1 modified

$$V_b = 1V$$

$$(V_c - 1) + 2V_c = 5$$

$$(V_d - 1) + 3V_d = -5$$

$$3V_c = 6 \text{ S}$$

$$4V_d = -4 \text{ S}$$

$$V_c = 2V$$

$$V_d = -1V$$

$$i_1 = (V_b - V_c) \times 1 = -1A$$

$$i_2 = 2V_c = 4A$$

$$i_3 = 3V_d = -3A$$

$$i_4 = (V_b - V_d) \times 1 = 2A$$

power balance

$$P_{1V} = -(i_1 + i_4) \times 1 = -1W$$

$$P_{top\ 1\Omega} = i_4^2 \times 1 = 4W$$


$$P_{middle\ 1\Omega} = i_1^2 \times 1 = 1W$$

$$P_{2\Omega} = i_2^2 \left(\frac{1}{2}\right) = 8W$$

$$P_{3\Omega} = i_3^2 \left(\frac{1}{3}\right) = 3W$$

$$P_{5A} = 5 \times (V_d - V_c) = 5 \times (-3) = -15W$$

$$\sum P's = 0 \quad ?$$

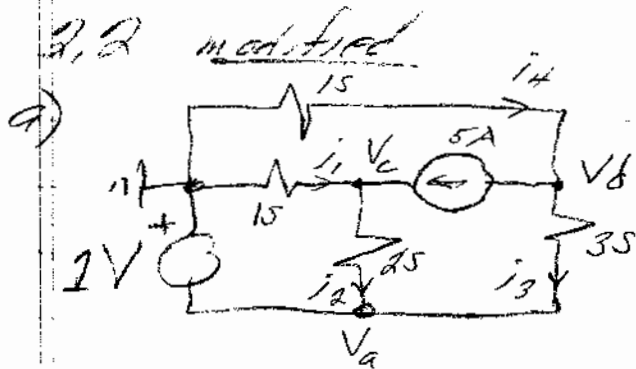

$$V_a = -1V$$

@ node c  $V_c + (V_c + 1)2 = 5$  (1)

@ node d  $V_d + (V_d + 1)3 = 5$  (2)

From (1)  $3V_c = 3$  ;

$$V_c = 1$$

From (2)  $4V_d = -8$

$$V_d = -2$$


b)  $i_1 = -V_c = -1A$

$i_2 = (V_c - V_a)2 = 4A$

$i_3 = (V_d - V_a)3 = -3A$

$i_4 = -V_d = 2A$

2.6

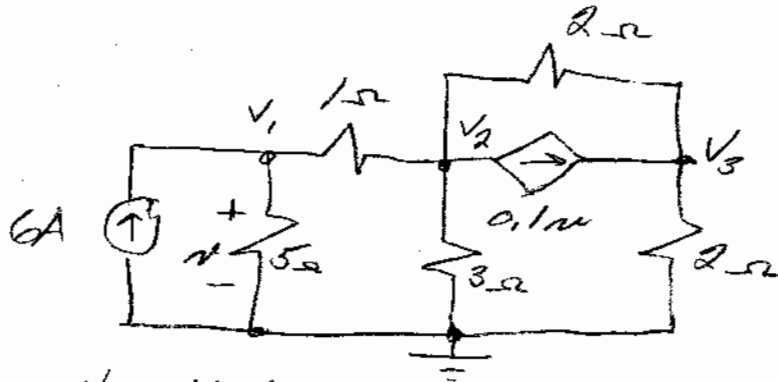

$$-6 + \frac{V_1}{5} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_2 - V_3}{2} + 0.1 \text{mA} = 0$$

$$\frac{V_3 - V_2}{2} + \frac{V_3}{2} - 0.1 \text{mA} = 0$$

$$\frac{6}{5}V_1 - V_2 = 6$$

$$\left(\frac{1}{10} - 1\right)V_1 + V_2\left(1 + \frac{1}{3} + \frac{1}{2}\right) - \frac{1}{2}V_3 = 0$$

$$-\frac{9}{10} - \frac{1}{2}V_2 + V_3 - \frac{1}{10}V_1 = 0$$

$$\text{or } 6V_1 - 5V_2 = 30$$

$$-54V_1 + 110V_2 - 30V_3 = 0$$

$$-2V_1 - 10V_2 + 20V_3 = 0$$

$$6V_1 - 5V_2 = 30$$

$$-27V_1 + 55V_2 - 15V_3 = 0$$

$$-V_1 - 5V_2 + 10V_3 = 0$$


$$V_1 = \frac{\begin{vmatrix} 30 & -5 & 0 \\ 0 & 55 & -15 \\ 0 & -5 & -10 \end{vmatrix}}{\begin{vmatrix} 6 & -5 & 0 \\ -27 & 55 & -15 \\ -1 & -5 & 10 \end{vmatrix}} = \frac{30(550 - 75)}{6(550 - 75) + 15(-270 - 15)} = \frac{14,250}{1,425} = 10$$

$$V_2 = \frac{\begin{vmatrix} 6 & 30 & 0 \\ -27 & 0 & -15 \\ -1 & 0 & 10 \end{vmatrix}}{1,425} = \frac{-30(-270 - 15)}{1,425} = \frac{8550}{1,425} = 6 \text{ V}$$

$$V_3 = \frac{\begin{vmatrix} 6 & -5 & 30 \\ -27 & 55 & 0 \\ -1 & -5 & 0 \end{vmatrix}}{1,425} = \frac{30(135 + 55)}{1,425} = 4 \text{ V}$$

EE 211

Homework 7

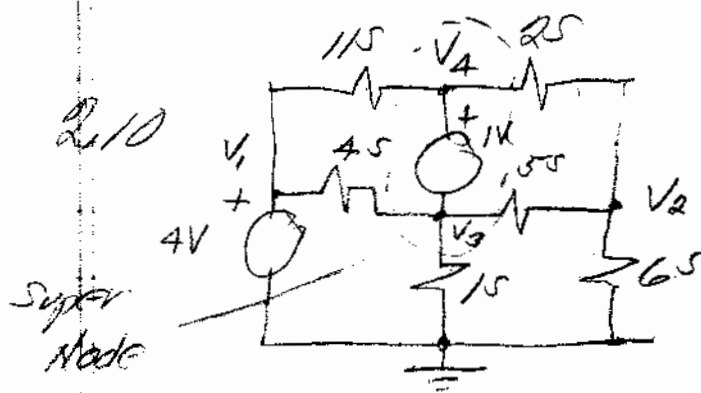

$$V_1 = 4V$$

$$V_4 - V_3 = 1 \quad \text{or } V_4 = 1 + V_3$$

$$(V_4 - V_1)11 + (V_3 - 4)4 + V_3 + (V_3 - V_2)5 + (V_4 - V_2)2 = 0$$

$$(V_2 - V_4)2 + (V_2 - V_3)5 + 6V_2 = 0$$

$$\text{or } (1 + V_3 - 4)11 + (V_3 - 4)4 + V_3 + (V_3 - V_2)5 + (1 + V_3 - V_2)2 = 0$$

$$(V_2 - 1 - V_3)2 + (V_2 - V_3)5 + 6V_2 = 0$$


$$\text{so } -7V_2 + 23V_3 = +47$$

$$13V_2 - 7V_3 = 2$$

$$V_2 = \frac{\begin{vmatrix} 447 & 23 \\ 2 & -7 \end{vmatrix}}{\begin{vmatrix} -7 & 23 \\ 13 & -7 \end{vmatrix}} = \frac{-375}{-250} = 1.5V$$

$$V_3 = \frac{\begin{vmatrix} -7 & 47 \\ 13 & 2 \end{vmatrix}}{-250} = \frac{-625}{-250} = 2.5V$$

Q2.3

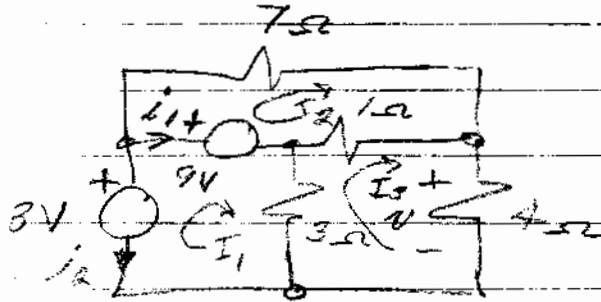

$$-3 + 9 + (I_1 - I_3)3 = 0$$

$$-9 + 7I_2 + (I_2 - I_3) = 0$$

$$(I_3 - I_1)3 + (I_3 - I_2)4 + 4I_3 = 0$$

$$\text{or } 3I_1 - 3I_3 = -6$$

$$8I_2 - I_3 = 9$$

$$-3I_1 - I_2 + 8I_3 = 0$$

$$I_1 = \frac{\begin{vmatrix} -6 & 0 & -3 \\ 9 & 8 & 1 \\ 0 & -1 & 8 \end{vmatrix}}{\begin{vmatrix} 3 & 0 & -3 \\ 0 & 8 & -1 \\ -3 & -1 & 8 \end{vmatrix}} = \frac{-6(64-1) - 3(-9)}{3(64-1) - 3(24)} = \frac{-351}{117} = -3A \leftarrow$$


$$I_2 = \frac{\begin{vmatrix} 3 & -6 & -3 \\ 0 & 9 & -1 \\ -3 & 0 & 8 \end{vmatrix}}{117} = \frac{3(72) - 3(6+27)}{117} = \frac{117}{117} = 1A \leftarrow$$

$$I_3 = \frac{\begin{vmatrix} 3 & 0 & -6 \\ 0 & 8 & 9 \\ -3 & -1 & 0 \end{vmatrix}}{-117} = \frac{3(9) - 6(24)}{117} = \frac{-117}{117} = -1A \leftarrow$$

$$a) i_2 = -I_1 = 3A \leftarrow$$

$$b) i_1 = (I_1 - I_2) = -4A \leftarrow$$

$$c) v = 4I_3 = -4V \leftarrow$$

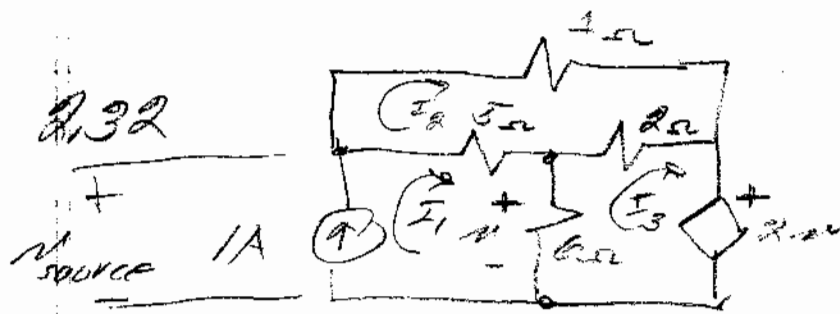

NASH

$$I_1 = 1$$

$$(I_2 - I_1)5 + 4I_2 + 2(I_2 - I_3) = 0$$

$$(I_3 - I_1)6 + (I_3 - I_2)2 + 2I_3 = 0$$

$$\text{but } I_1 = (I_1 - I_3)6$$

$$11I_2 - 2I_3 = 5$$

$$-2I_2 - 4I_3 = -6$$

$$I_2 = \frac{\begin{vmatrix} 5 & -2 \\ -6 & -4 \end{vmatrix}}{\begin{vmatrix} 11 & -2 \\ -2 & -4 \end{vmatrix}} = \frac{-20 - 12}{-44 - 4} = \frac{32}{48} = \frac{2}{3} \text{ A}$$


$$I_3 = \frac{\begin{vmatrix} 11 & 5 \\ -2 & -6 \end{vmatrix}}{-48} = \frac{-66 + 10}{-48} = \frac{56}{48} = \frac{7}{6} \text{ A}$$

$$N_{\text{source}} = (I_1 - I_2)5 + (I_1 - I_3)6 = \frac{5}{3} - \frac{6}{6} = \frac{2}{3} \text{ V}$$

$$\therefore R_{\text{in}} = \frac{N_{\text{source}}}{1} = \frac{2}{3} \Omega$$




EE 211 Homework 11

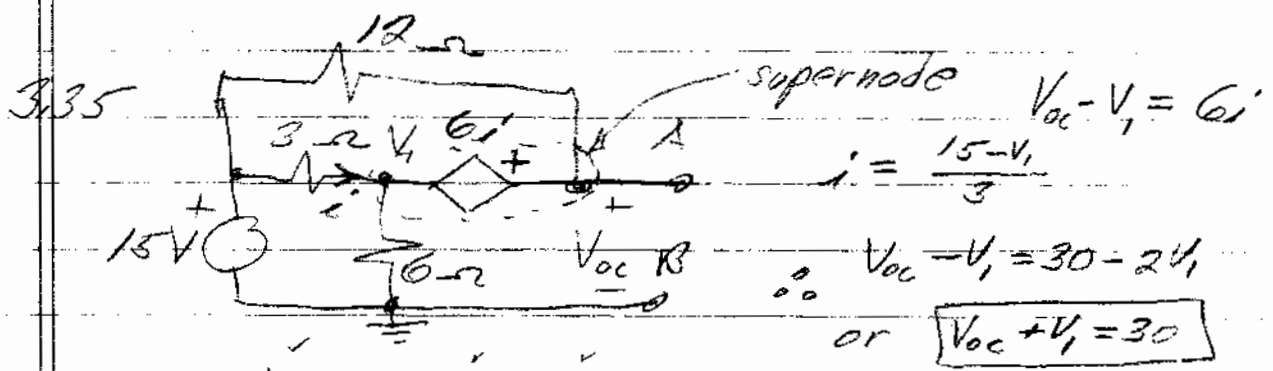

Node  $V_1$   $\frac{V_1 - 15}{3} + \frac{V_1}{6} + \frac{V_{oc} - 15}{12} = 0 \Rightarrow \frac{1}{12}V_{oc} + \frac{1}{6}V_1 = \frac{75}{12}$

$\begin{array}{c|c} 30 & 1 \\ \hline 75 & 6 \\ \hline 1 & 1 \\ \hline 1 & 6 \end{array} = \frac{180 - 75}{6 - 1} = \frac{105}{5} = 21V$

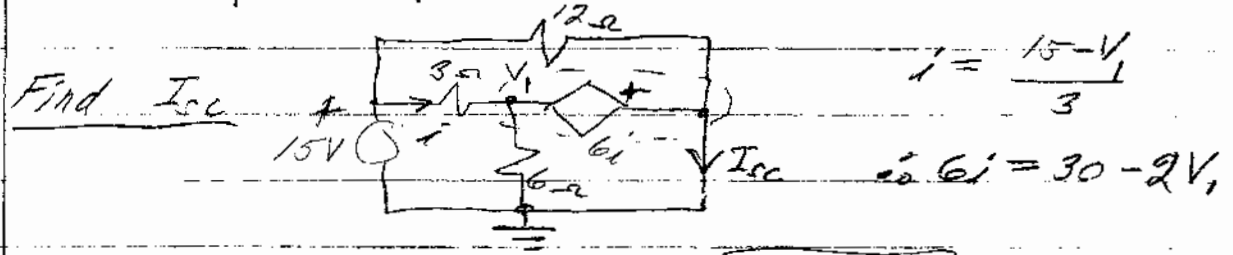


$V_1 = -6i = 2V_1 - 30$  so  $V_1 = 30$

KCL @ supernode gives:  $\frac{30 - 15}{3} + \frac{30}{6} - \frac{15}{12} + I_{sc} = 0$

$I_{sc} = -5 - 5 + \frac{3}{4} = -\frac{35}{4}$

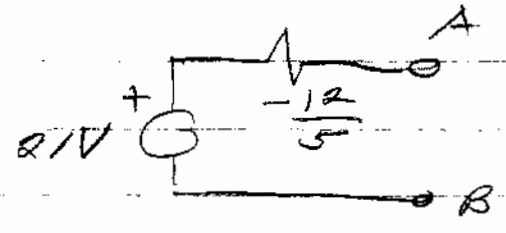and  $R_{th} = \frac{-21 \times 4}{35} = -\frac{12}{5}$




$-\frac{12}{5}$


EE 211

Homework 12

3.64

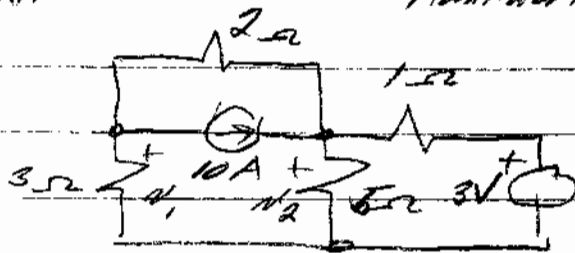

Current source = 0

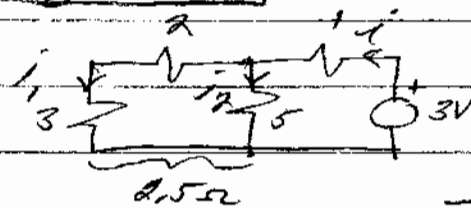


$$i = \frac{3}{7} = \frac{6}{7} \text{ A}$$

$$i_1 = i_2 = \frac{i}{2} = \frac{3}{7} \text{ A}$$

$$\therefore N_1 = \frac{9}{7} \text{ V}; N_2 = \frac{15}{7} \text{ V}$$

Voltage source = 0

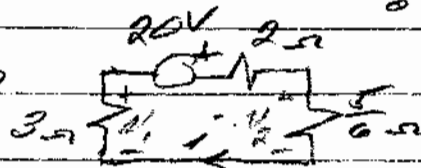



$$20 = \frac{35}{6} i \text{ or } i = \frac{24}{7} \text{ A}$$

$$\text{so } N_1 = -3i_1 = -\frac{3 \times 24}{7} \text{ V}; N_2 = \frac{5}{6} i = \frac{20}{7} \text{ V}$$

$$\therefore \text{total } N_1 = \frac{9}{7} - \frac{72}{7} = -9 \text{ V}$$

$$N_2 = \frac{20}{7} + \frac{15}{7} = \frac{35}{7} = 5 \text{ V}$$

EE 211 Homework 13

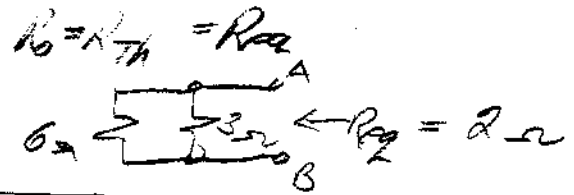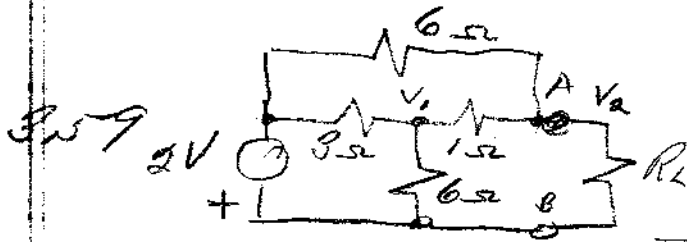


∴ for maximum power  $R_L = 2\Omega$

$$\frac{V_1 - 2}{3} + \frac{V_1}{6} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - 2}{6} + \frac{V_2 - V_1}{1} + \frac{V_2}{2} = 0$$

$$\left. \begin{aligned} V_1 \left( \frac{1}{3} + \frac{1}{6} + 1 \right) - V_2 &= \frac{2}{3} \\ -V_1 + V_2 \left( \frac{1}{6} + 1 + \frac{1}{2} \right) &= \frac{1}{3} \end{aligned} \right\} \begin{aligned} \frac{3}{2} V_1 - V_2 &= \frac{2}{3} \\ -V_1 + \frac{5}{3} V_2 &= \frac{1}{3} \end{aligned}$$
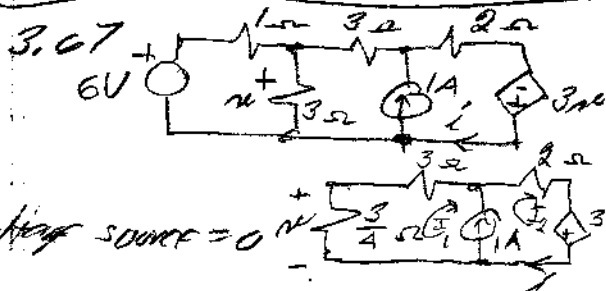
$$V_2 = \frac{\begin{vmatrix} \frac{3}{2} & -1 \\ \frac{3}{2} & -1 \end{vmatrix}}{\begin{vmatrix} \frac{3}{2} & -1 \\ -1 & \frac{5}{3} \end{vmatrix}} = \frac{\frac{3}{2} + \frac{2}{3}}{\frac{5}{2} - 1} = \frac{\frac{7}{6}}{\frac{3}{2}} = \frac{7}{9} \text{ V}; P_{L_{max}} = \frac{1}{2} \left( \frac{7}{9} \right)^2 \frac{49}{162} = \boxed{0.302 \text{ W}}$$




Supermesh Equation:

$$\frac{15}{4} I_1 + 2 I_2 - 3 \text{ A} = 0; \quad I_2 = -\frac{3}{4} I_1$$

$$I_2 - I_1 = 1; \quad \boxed{I_2 = 1 + I_1}$$

$$\frac{15}{4} I_1 + 2(1 + I_1) - 3(-\frac{3}{4} I_1) = 0$$
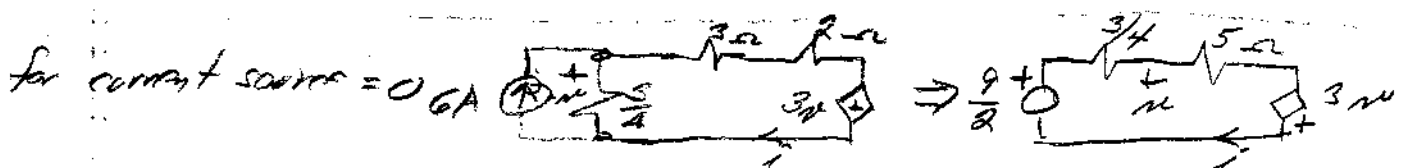
$$\text{so } I_1 \left( \frac{15}{4} + 2 + \frac{9}{4} \right) = -2; \quad \boxed{I_1 = -2 \left( \frac{4}{32} \right) = -\frac{1}{4} \text{ A}; \quad I_2 = \frac{3}{4} \text{ A}}$$




$$\frac{9}{2} = \frac{23}{4} i - 3 \left( \frac{9}{2} - \frac{3}{4} i \right) = i \left( \frac{23}{4} + \frac{9}{4} \right) - \frac{27}{2}$$

$$i = \frac{\frac{36}{2}}{\frac{32}{4}} = \frac{36 \times 4}{32 \times 2} = \frac{9 \times 4}{8 \times 2} = \frac{9}{4}$$

$$\text{so } i_{total} = \frac{9}{4} + \frac{3}{4} = \frac{12}{4} = \boxed{3 \text{ A}} \leftarrow$$
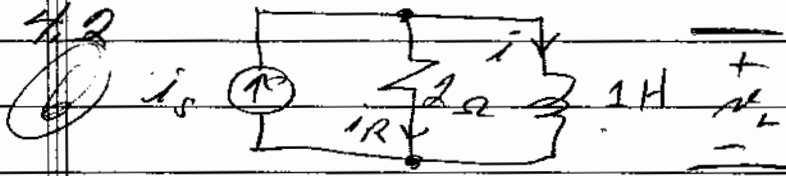
$$v_{total} = -\frac{3}{4} \left( -\frac{1}{4} \right) + \left( \frac{9}{2} - \frac{27}{16} \right) = \frac{3}{16} + \frac{45}{16} = \boxed{3 \text{ V}} \leftarrow$$










$i_L(t) = 0$  for  $t < 0$   
 $i_L(t) = 1 - e^{-2t}$  for  $t \geq 0$   
 $v_L = L \frac{di}{dt}$

a)  $v_L(t) = 0$  for  $t < 0$  ✓  
 $v_L(t) = 2e^{-2t}$  for  $t \geq 0$  ✓


b)  $i_R(t) = 0$  for  $t < 0$  ✓  
 $i_R(t) = \frac{v_L}{2} = e^{-2t}$  for  $t \geq 0$  ✓

c)  $i_s(t) = 0$  for  $t < 0$  ✓  
 $i_s(t) = i + i_R = 1 - e^{-2t} + e^{-2t} = 1A$  for  $t \geq 0$  ✓

(10)

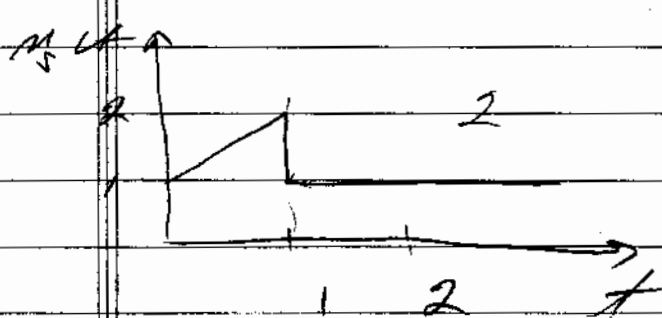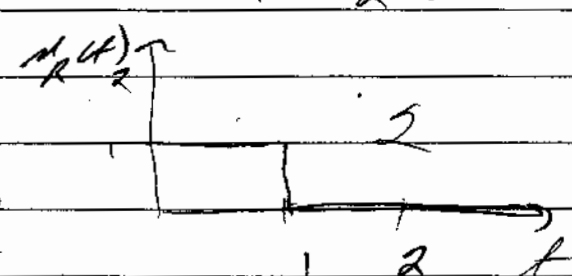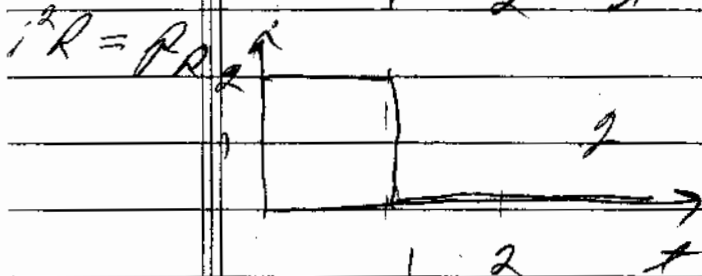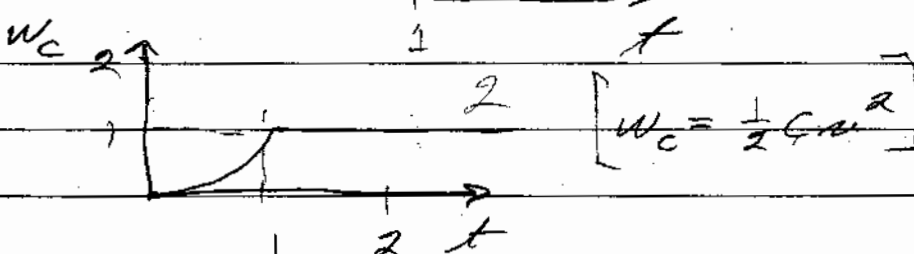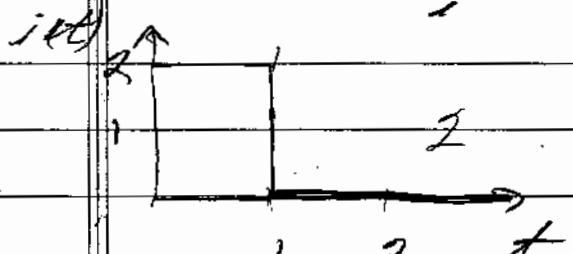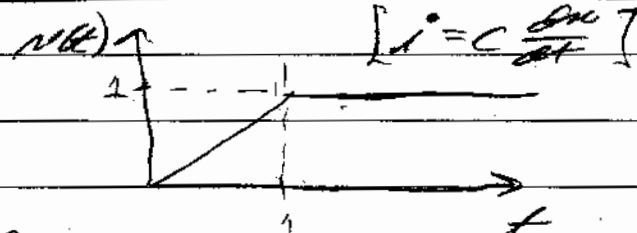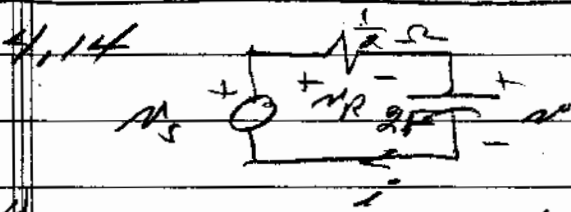



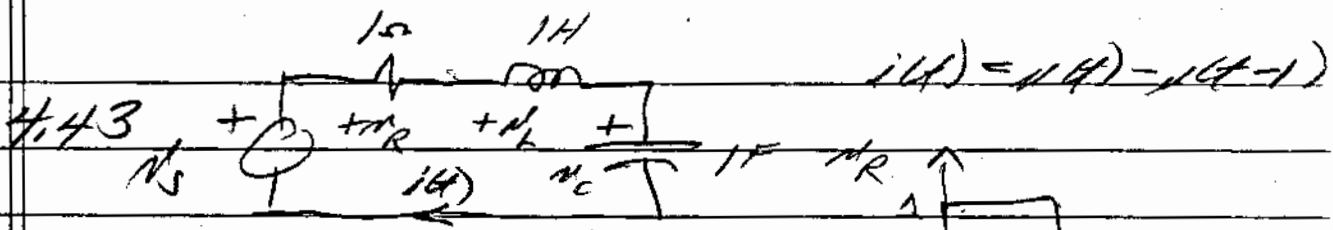
} 1 point for correct form  
 } 1 point for correct value





a)  $v_R(t) = iR = 10 \cos(2t) - 10 \cos(2t - 1)$

b)  $v_C(t) = \frac{1}{C} \int_0^t i(t) dt + v_C(0)$  [assume  $v_C(0) = 0$ ]

c)  $v_L(t) = L \frac{di}{dt}$

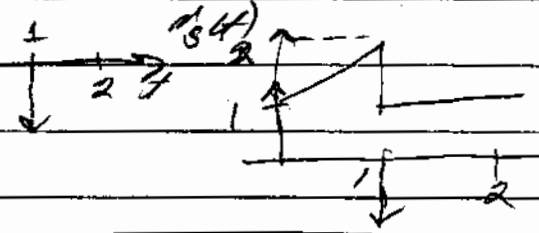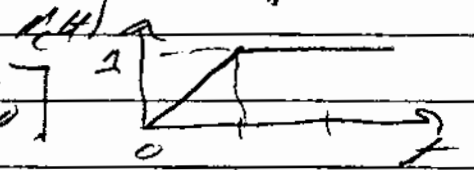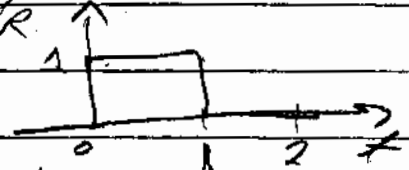


d)  $v_s(t) = v_R + v_L + v_C$

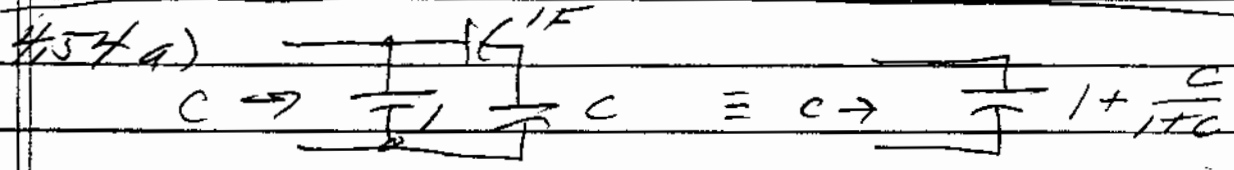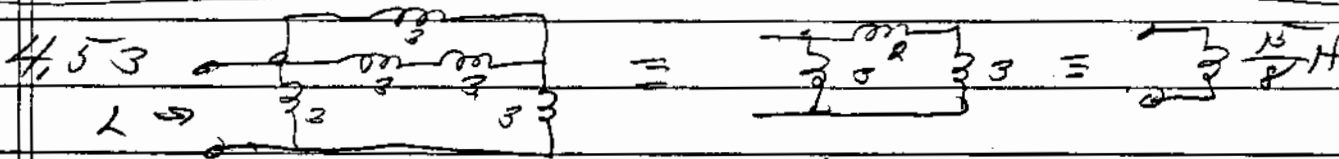

so  $C = 1 + \frac{C}{17C}$  or  $C + C^2 = 17C$   
 $C^2 - C - 1 = 0$

$C = \frac{1 \pm \sqrt{1+4}}{2} = \frac{1 \pm \sqrt{5}}{2} = \frac{1 + \sqrt{5}}{2} \approx 1.618 F$


4.55

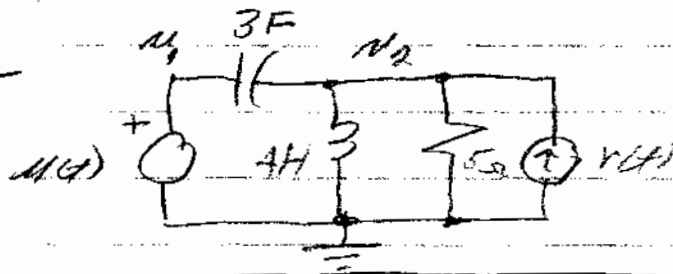

$$v_1 = v(t)$$

$$3 \frac{d}{dt} (v_2 - v_1) + \frac{1}{4} \int_{-\infty}^t i_2 dt + \frac{i_2}{5} = v(t)$$

5.1

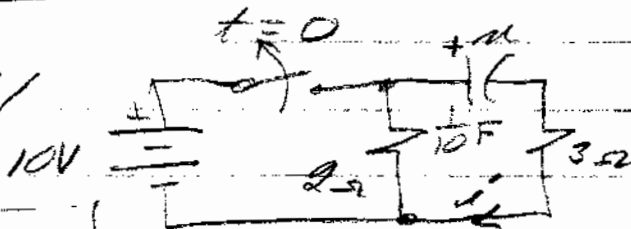

$$v(0^-) = v(0^+) = 10$$

for  $t > 0$


$$(1) \quad 5i + 10 \int_0^t i dt + 10 = 0 \Rightarrow 5 \frac{di}{dt} + 10i = 0$$

$$i = A e^{st} \text{ for } s = -2 \text{ so } i = A e^{-2t}$$

from (1)  $5i(0) = -10$  or  $i(0) = -2$

so  $i(t) = -2 e^{-2t}$  for  $t > 0$


$$v(t) = -5i = 10 e^{-2t}$$

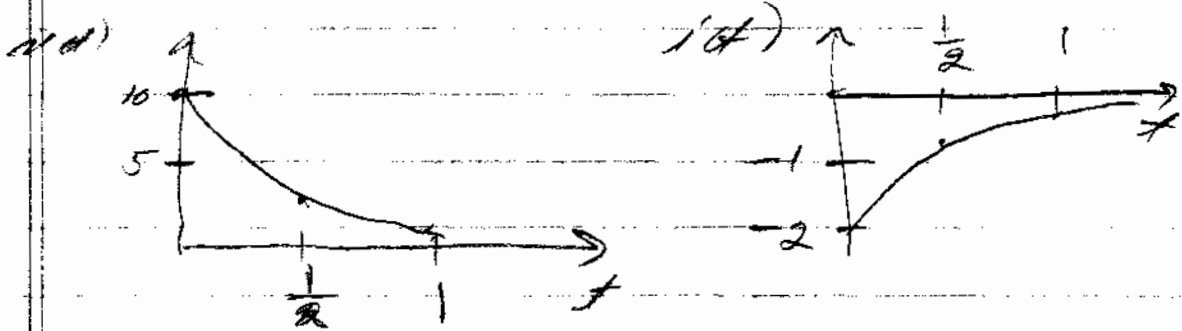

$$T = \frac{1}{2} \text{ sec}$$

EE 211


Homework 17

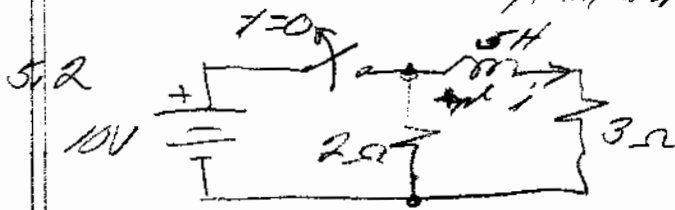

$i(0) = \frac{10}{3} \text{ A}$   
 for  $t > 0$   
 $5i + 5 \frac{di}{dt} = 0 ; i = A e^{st}$


$s = -1 \therefore i = A e^{-t} = \frac{10}{3} e^{-t}$  ←

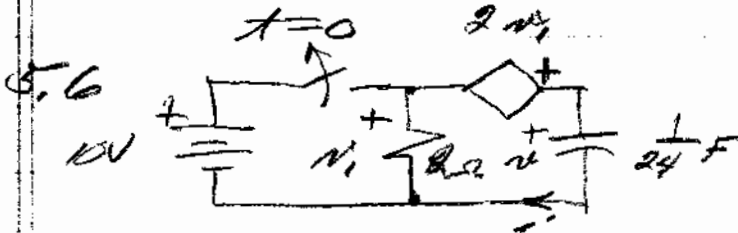$v(t) = 5 \frac{di}{dt} = -\frac{50}{3} e^{-t}$  ←



for  $t < 0$   $v_1 = 10$   
 $\therefore v = 3v_1 = 30 \text{ V}$   
 $i = 0$

for  $t > 0$  we have:

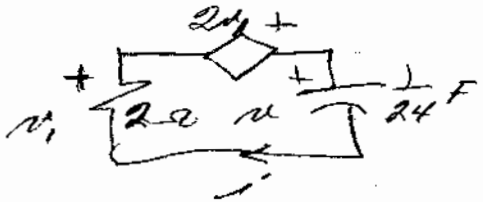



$2i - 2v_1 + 24 \int_0^t i dt + 30 = 0$   
 but  $v_1 = -2i$

(1)  $\therefore$  we have:  $2i + 4i + 24 \int_0^t i dt + 30 = 0$   
 or  $6 \frac{di}{dt} + 24i = 0$

$i = A e^{st} ; s = -\frac{24}{6} = -4$  so  $i = A e^{-4t}$


from (1)  $6i(0) = -30$  or  $i(0) = -5$

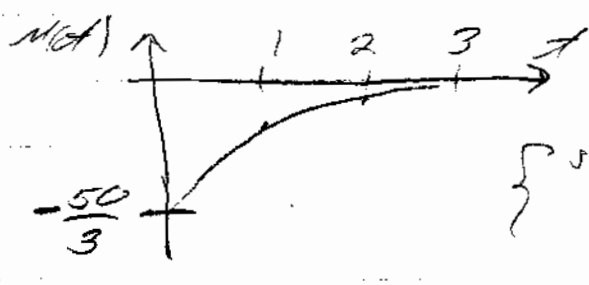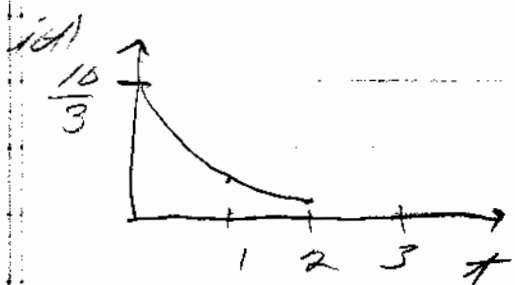$\therefore i = -5 e^{-4t}$  for  $t > 0$   
 $v = 3v_1 = -6i = 30 e^{-4t}$  ←



sketches for 5.2

5.7

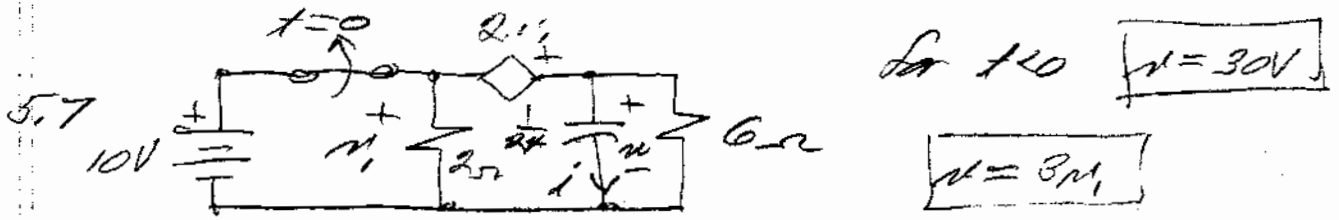

for  $t > 0$   $\frac{v_1}{2} + \frac{3v_1}{6} + \frac{1}{24} \frac{dv}{dt} (3m) = 0$


or  $\frac{v}{6} + \frac{v}{6} + \frac{1}{24} \frac{dv}{dt} = 0 \Rightarrow 8v + \frac{dv}{dt} = 0$

$v = A e^{st}$  ;  $s = -8$  so  $v(t) = A e^{-8t}$


but  $v(0) = 30 \therefore v(t) = 30 e^{-8t}$

$i(t) = \frac{1}{24} \frac{dv}{dt} = \frac{1}{24} (-8)(30) e^{-8t} = -10 e^{-8t}$

5.8

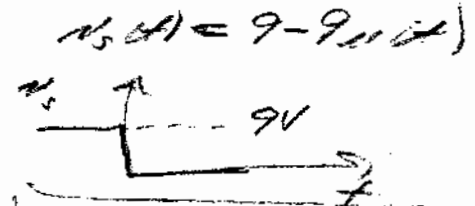

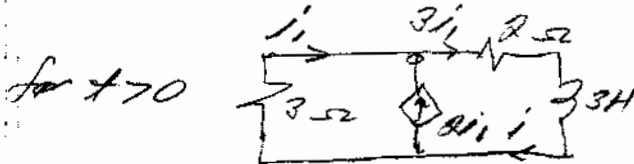$9 = 3i_1 + 6i_1 \Rightarrow i_1 = 1$   
 $i_L(0) = 3$




$i = 3i_1$   
 KVL  $\Rightarrow 3i_1 + 6i_1 + 3 \frac{di}{dt}$

or  $3i + 3 \frac{di}{dt} = 0$   $i = A e^{st}$   $s = -1$

so  $i = A e^{-t}$  but  $i(0) = 3$  so  $i = 3 e^{-t}$

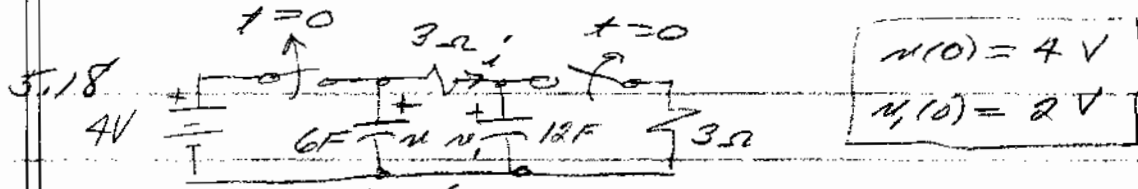$v(t) = 3 \frac{di}{dt} = 3(3)(-1) e^{-t} = -9 e^{-t}$






For  $t > 0$

$$\frac{1}{6} \int i dt - 4 + 3i + \frac{1}{12} \int i dt + 2 = 0$$

or  $(\frac{1}{6} + \frac{1}{12})i + 3 \frac{di}{dt} = 0 \Rightarrow \frac{1}{4}i + 3 \frac{di}{dt} = 0$   $i = A e^{st}, s = -\frac{1}{12}$

from (1)  $3i(0) = 2 \Rightarrow i(0) = \frac{2}{3} e^{-\frac{t}{12}}$

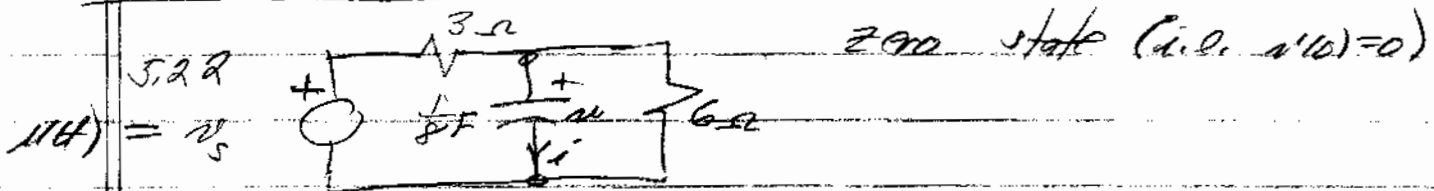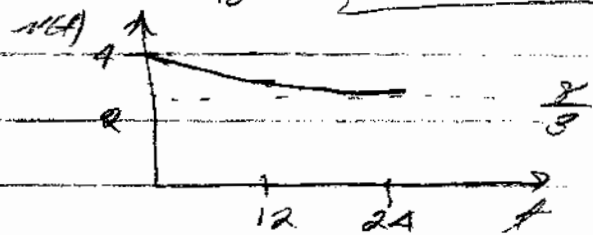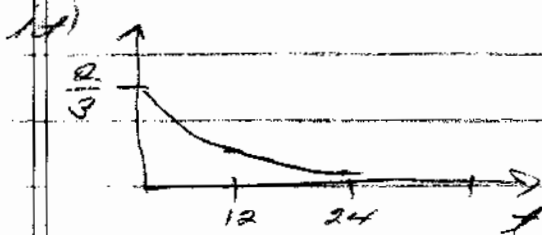$v(t) = \frac{1}{6} \int_0^t \frac{2}{3} e^{-\frac{\tau}{12}} d\tau + 4 = \frac{1}{9} (-12) e^{-\frac{t}{12}} + 4 = \frac{4}{3} e^{-\frac{t}{12}} + \frac{8}{3}$




for  $t > 0$   $\frac{v-1}{3} + \frac{v}{6} + \frac{1}{8} \frac{dv}{dt} = 0 \Rightarrow \frac{1}{8} \frac{dv}{dt} + \frac{1}{2}v = \frac{1}{3}$

so  $v_h = A e^{-4t}$   $v_p = K \therefore \frac{1}{2}K = \frac{1}{3}$  or  $K = \frac{2}{3}$

$v(t) = v_h + v_p = A e^{-4t} + \frac{2}{3}$  but  $v(0) = 0$

$\therefore v(t) = \frac{2}{3} (1 - e^{-4t})$

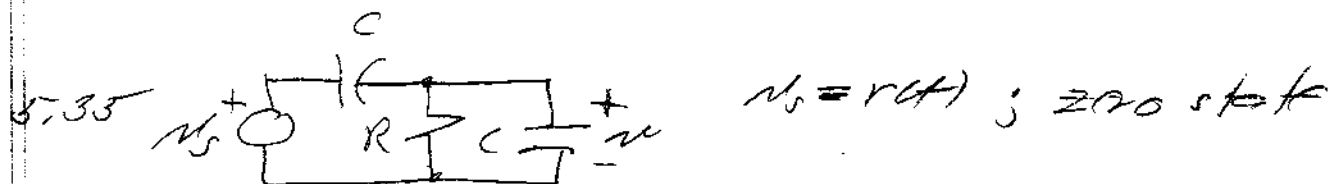$i(t) = \frac{1}{8} \frac{dv}{dt} = (-\frac{2}{3})(\frac{1}{8})(-4) e^{-4t} = \frac{1}{3} e^{-4t}$



KCL:  $C \frac{dv}{dt} [v - v(t)] + \frac{v}{R} + C \frac{dv}{dt} = 0$


or  $2C \frac{dv}{dt} - C v(t) + \frac{v}{R} = 0 \Rightarrow \left[ \frac{dv}{dt} + \frac{1}{2RC} v = \frac{1}{2} v(t) \right]$

$v_{homog} = A e^{st}$ ;  $s = -\frac{1}{2RC}$ ;  $v_p = K$ ;  $K = RC$


$\therefore v(t) = A e^{-\frac{t}{2RC}} + RC$

but  $v(0) = 0$   $\therefore v(t) = RC \left[ 1 - e^{-\frac{t}{2RC}} \right]$  for  $t > 0$


5.42

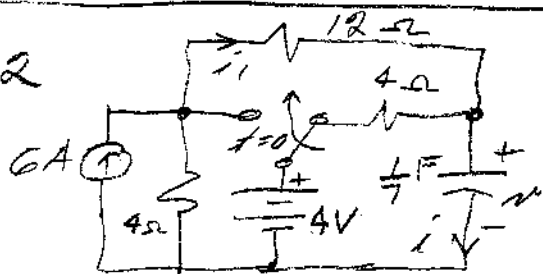

for  $t < 0$  circuit is:

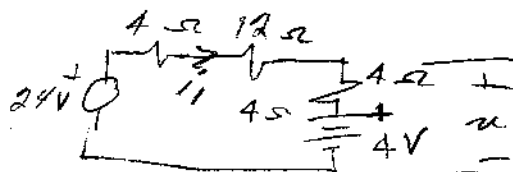

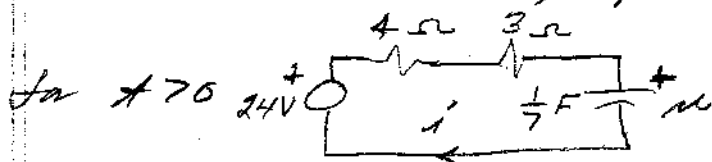for  $t < 0$   $i = 0$ ;  $i_1 = \frac{20}{20} = 1A$  so  $v(0) = 8V$



(1) so  $7 \int_0^t i dt + 8 + 7i = 24 \Rightarrow 7 \frac{di}{dt} + 7i = 0$


$i = A e^{-t}$

from (1)  $i(0) = \frac{16}{7}$

$\therefore i(t) = \frac{16}{7} e^{-t}$  for  $t > 0$

$v(t) = 24 - 7i = 24 - 16 e^{-t}$

# EE 211 Homework 2.1

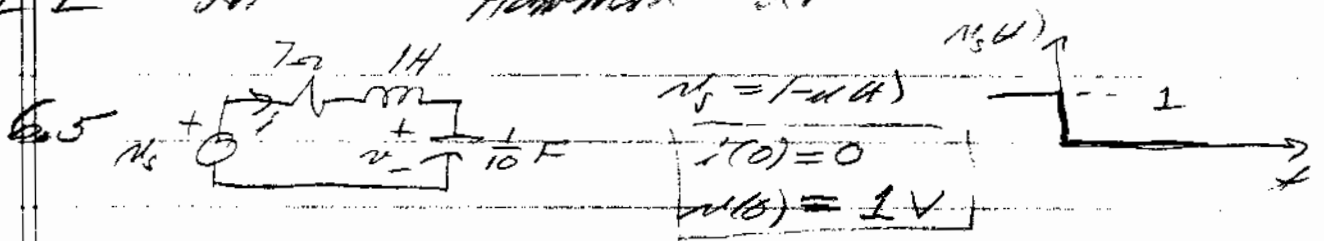

for  $t > 0$   $7i + \frac{di}{dt} + 10 \int i dt + 1 = 0$  (1)

$$\frac{d^2 i}{dt^2} + 7 \frac{di}{dt} + 10i = 0 ; i = A e^{st} \quad s^2 + 7s + 10 = 0$$

$$s_{1,2} = \frac{-7 \pm \sqrt{49 - 40}}{2} = -\frac{7}{2} \pm \frac{3}{2} = -5, -2$$

$$\text{so } i(t) = A_1 e^{-5t} + A_2 e^{-2t}$$

but  $i(0) = 0 \therefore A_2 = -A_1$

from (1)  $\left. \frac{di}{dt} \right|_{t=0} = -1 = -5A_1 + 2A_1 = -3A_1$

$$\text{so } A_1 = \frac{1}{3}$$

$$\text{and } i(t) = \frac{1}{3} e^{-5t} - \frac{1}{3} e^{-2t}$$

$$v(t) = -7i - \frac{di}{dt} = -\frac{7}{3} e^{-5t} + \frac{7}{3} e^{-2t} + \frac{5}{3} e^{-5t} - \frac{2}{3} e^{-2t}$$

$$\text{or } v(t) = -\frac{2}{3} e^{-5t} + \frac{5}{3} e^{-2t}$$



$$R = 1 \Omega, L = \frac{1}{2} \text{H}, C = \frac{1}{4} \text{F}$$

$$v_s(t) = 4 - 4 \cos(2t)$$

for  $t < 0$ ;  $v_s = 4$  so  $i(0) = 4 \text{A}$  and  $v_C(0) = 0$

for  $t \geq 0$   $v_s = 0$  so  $\left[ v + R \int_0^t v dt + 4 + \frac{1}{4} \frac{dv}{dt} = 0 \right] \quad (1)$

differentiating 9NPH  $\frac{dv}{dt} + 4 \frac{dv}{dt} + 8v = 0$

$v_{\text{hom}} = A e^{st}$  so  $s^2 + 4s + 8 = 0$ ;  $s_{1,2} = -2 \pm \sqrt{4-8}$

$$v = B_1 e^{-2t} \cos 2t + B_2 e^{-2t} \sin 2t$$

$v(0) = 0$  so  $B_1 = 0$

from (1) above  $v(t) + 4 + \frac{1}{4} \frac{dv}{dt} = 0$  so  $\left. \frac{dv}{dt} \right|_{t=0} = -16$

so  $-16 = B_2 \left. \left\{ 2e^{-2t} \cos 2t - 2e^{-2t} \sin 2t \right\} \right|_{t=0}$ ;  $B_2 = -8$

$v(t) = -8 e^{-2t} \sin 2t$  for  $t \geq 0$

$$i(t) = -\frac{dv}{R} - C \frac{dv}{dt} = +8 e^{-2t} \sin 2t + \frac{2}{4} \left\{ 2e^{-2t} \cos 2t - 2e^{-2t} \sin 2t \right\}$$

$i(t) = 4 e^{-2t} \sin 2t + 4 e^{-2t} \cos 2t$  for  $t \geq 0$

