

$$I_1 = \left(\frac{S_{AN}}{230} \right)^* = \frac{10,000 e^{-j40^\circ}}{230} = 43.478 e^{-j40^\circ}$$


$$I_2 = \left(\frac{S_{NB}}{230} \right)^* = \frac{9 \times 10^3 e^{-j10^\circ}}{230} = 34.782 e^{-j10^\circ}$$

$$I_3 = \left(\frac{S_{AB}}{230} \right)^* = \frac{1 \times 10^3 e^{-j90^\circ}}{460} = 8.696 e^{-j90^\circ}$$

$$I_A = I_1 + I_3 = 34.816 - j19.383 = 39.85 e^{-j29^\circ}$$

$$I_B = I_2 + I_3 = 35.76 + j2.52 = 35.85 e^{j4^\circ}$$
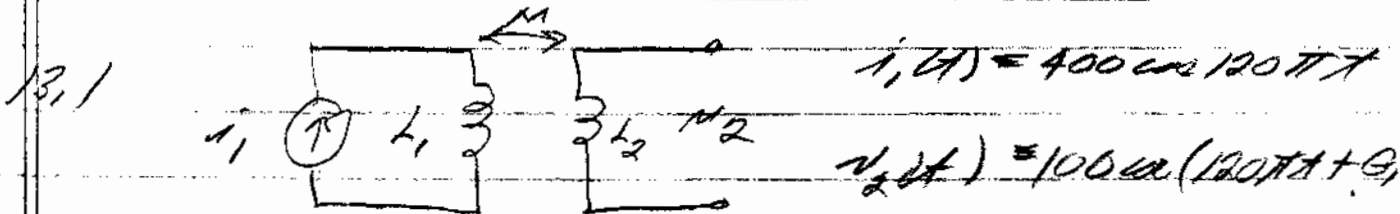
$$I_N = I_1 - I_2 = -0.946 - j21.91 = 21.98 e^{-j97.53^\circ}$$




but $v_2 = \pm M \frac{di_1}{dt} = \pm M 400 \times 120\pi (-\sin 120\pi t)$

$$\text{so } M = \frac{100}{400 \times 120\pi} = 0.663 \text{ mH}$$

12.8 a)

ck sign

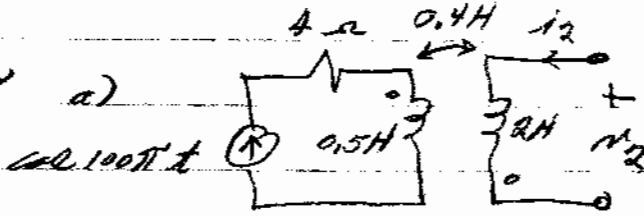


$$v_2 = 2 \frac{di_2}{dt} - 0.4 \frac{d}{dt} (u(100\pi t))$$

$$v_2 = 400 \sin 100\pi t$$

$$\text{or } v_2 = 400 \cos(100\pi t - 90^\circ)$$


b)

ck 100πt

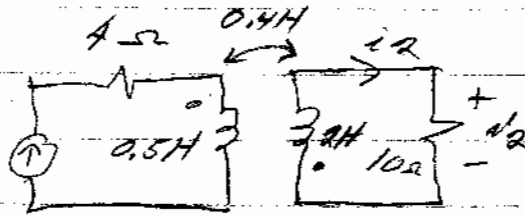

$$v_2 = +2 \frac{di_2}{dt} + 0.4 \frac{d}{dt} (u(100\pi t))$$

$$v_2 = +10 i_2$$

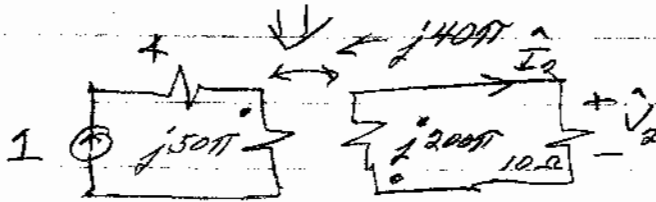


$$\hat{I}_2 j200 + j40 \hat{I}_2 + 10 \hat{I}_2 = 0; \hat{I}_2 = \frac{-j40}{10 + j200}$$

$$\hat{V}_2 = 10 \hat{I}_2 = \frac{-j400}{10 + j200} = \frac{-j2}{20 + j40} = \frac{2 \angle -90^\circ}{40 \angle 89.09^\circ} = 0.05 \angle -179.09^\circ$$

$$\text{or } v_2(t) = 0.05 \cos(100\pi t - 179.09^\circ)$$

c)

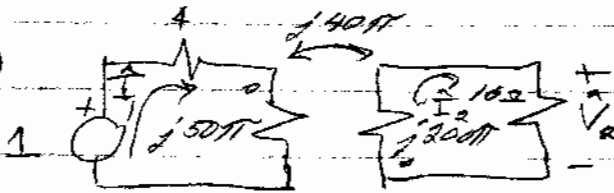

$$\hat{I}_1 + j50 \hat{I}_1 + j40 \hat{I}_2 = 1$$

$$j200 \hat{I}_2 + j40 \hat{I}_1 + 10 \hat{I}_2 = 0$$

$$\hat{I}_1 (4 + j50) + j40 \hat{I}_2 = 1 \quad (1)$$

$$\text{or } j40 \hat{I}_1 + (10 + j200) \hat{I}_2 = 0 \quad (2)$$

$$\hat{I}_2 = \frac{\begin{vmatrix} 4 + j50 & 1 \\ j40 & 0 \end{vmatrix}}{\begin{vmatrix} 4 + j50 & j40 \\ j40 & 10 + j200 \end{vmatrix}} = \frac{-j40}{40 - 10,000 + j(5000 + 2000) + 1600} = \frac{-j40}{-92,864.7 + j7000}$$

$$\text{or } \hat{V}_2 = 10 \hat{I}_2 = \frac{10 \times 40 \angle -90^\circ}{-92,864.7 + j7000} = \frac{400 \angle -90^\circ}{82,965 \angle 177.18^\circ} = 0.015 \angle -267.18^\circ$$



$$v_2(t) = 0.015 \cos(100\pi t + 92.82^\circ)$$

EE 212

Homework 3

13.15

100 $\angle 0^\circ$ V

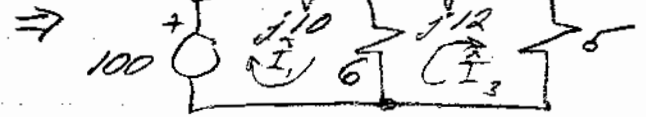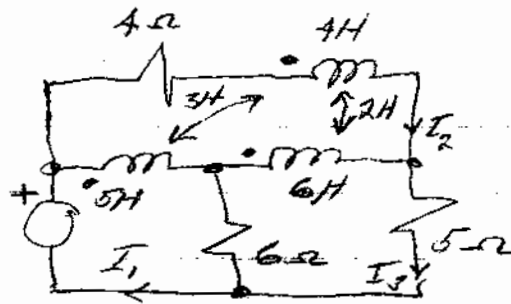

$$100 = (\hat{I}_1 - \hat{I}_2)j10 + j6\hat{I}_2 + (\hat{I}_1 - \hat{I}_3)6$$

$$0 = 4\hat{I}_2 + j8\hat{I}_2 + (\hat{I}_1 - \hat{I}_2)j6 + (\hat{I}_3 - \hat{I}_2)4 + (\hat{I}_2 - \hat{I}_3)j12$$


$$0 = (\hat{I}_3 - \hat{I}_1)6 + (\hat{I}_3 - \hat{I}_2)j12 + \hat{I}_2j4 + 5\hat{I}_3 = 0$$

or

$$\left[\begin{aligned} \hat{I}_1(6 + j10) + \hat{I}_2(-j4) - \hat{I}_3 6 &= 100 \\ \hat{I}_1(-j4) + \hat{I}_2(4 + j10) + \hat{I}_3(-j8) &= 0 \\ -6\hat{I}_1 + \hat{I}_2(-j8) + \hat{I}_3(11 + j12) &= 0 \end{aligned} \right]$$


from computer

$$\hat{I}_3 = 4.32 \angle -54.3^\circ$$

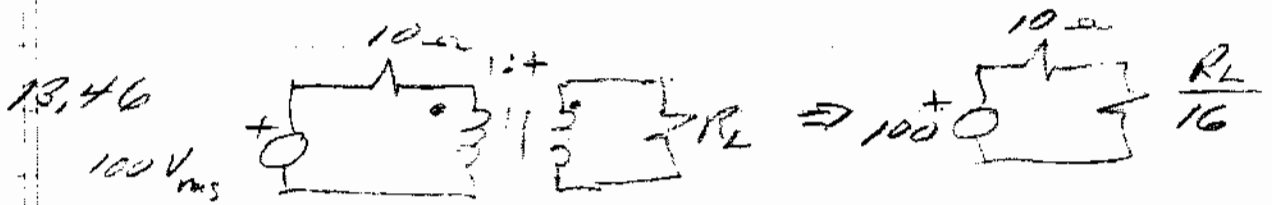


for maximum power $\frac{R_L}{16} = 10$ or $R_L = 160 \Omega$

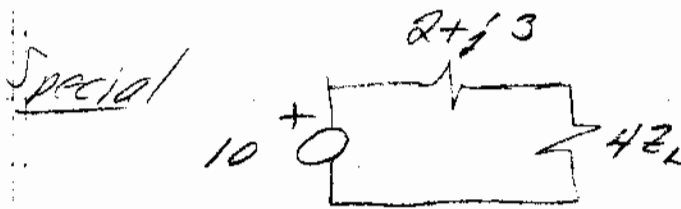$P_{max} = \frac{50^2}{10} = \frac{2500}{10} = 250 \text{ Watts}$



for maximum power transfer
 $4Z_L = 2-j3$

a) or $Z_L = \frac{2-j3}{4}$

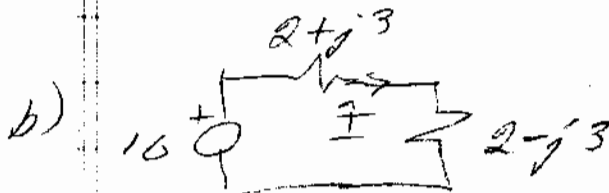

$I = \frac{10}{4}$

$P_{max} = |I|^2 \times 2 = \frac{100}{16} \times 2$

$P_{max} = \frac{25}{2} \text{ Watts}$

$$14.18 \text{ a) } \mathcal{L}\{3u(t)\} = \int_0^{\infty} 3e^{-st} dt = -\frac{3e^{-st}}{s} \Big|_0^{\infty} = \boxed{\frac{3}{s}} \leftarrow$$

$$\text{b) } \mathcal{L}\{3u(t-3)\} = \int_0^{\infty} 3u(t-3)e^{-st} dt = \int_3^{\infty} 3e^{-st} dt \\ = -\frac{3e^{-st}}{s} \Big|_3^{\infty} = \boxed{\frac{3}{s} e^{-3s}} \leftarrow$$

$$\text{c) } \mathcal{L}\{3u(t-3)-3\} = \frac{3}{s} e^{-3s} - \frac{3}{s} = \frac{3}{s} [e^{-3s} - 1] \leftarrow \\ \text{[using parts a) and b)]}$$

$$\text{d) } \mathcal{L}\{3u(3-t)\} = \int_0^{\infty} 3u(3-t)e^{-st} dt = \int_0^3 3e^{-st} dt \\ = -\frac{3e^{-st}}{s} \Big|_0^3 = \frac{3}{s} [1 - e^{-3s}] \leftarrow$$

14.19

$$\text{a) } \mathcal{L}\{2+3u(t)\} = \boxed{\frac{5}{s}} \text{ from a) above } \leftarrow$$

$$\text{b) } \mathcal{L}\{3e^{-8t}\} = \int_0^{\infty} 3e^{-8t} e^{-st} dt = 3 \left[\frac{-1}{s+8} \right] e^{-st} \Big|_0^{\infty} \\ = \boxed{\frac{3}{s+8}} \leftarrow$$

$$\text{c) } \mathcal{L}\{u(-t)\} = \int_0^{\infty} 0 \times e^{-st} dt = \boxed{0} \leftarrow$$

$$\text{d) } \mathcal{L}\{K\} = \int_0^{\infty} K e^{-st} dt = K \left(\frac{-1}{s} \right) e^{-st} \Big|_0^{\infty} = \boxed{\frac{K}{s}} \leftarrow$$

$$1425 \quad a) F(s) = \frac{1}{s+3} \quad \therefore f(t) = \frac{1}{3} e^{-3t} u(t)$$

$$b) F(s) = 1 \quad \therefore f(t) = \delta(t)$$

$$c) F(s) = \frac{1}{s^2} \quad \therefore f(t) = t u(t)$$

$$d) F(s) = 275 \quad \therefore f(t) = 275 \delta(t)$$

$$e) F(s) = \frac{s^2}{s^3} = \frac{1}{s} \quad \therefore f(t) = u(t)$$

$$14.32 \text{ a) } F(s) = 3 + \frac{1}{s} \Rightarrow f(t) = \boxed{3\delta(t) + u(t)}$$

$$\text{b) } F(s) = 3 + \frac{1}{s^2} \Rightarrow f(t) = 3\delta(t) + t u(t)$$

$$\text{c) } F(s) = \frac{1}{(s+3)(s+4)} = \frac{1}{s+3} + \frac{-1}{s+4} \Rightarrow f(t) = \{e^{-3t} - e^{-4t}\} u(t)$$

$$\text{d) } F(s) = \frac{1}{(s+3)(s+4)(s+5)} = \frac{\frac{1}{2}}{s+3} + \frac{-1}{s+4} + \frac{\frac{1}{2}}{s+5}$$

$$\therefore f(t) = \left\{ \frac{1}{2} e^{-3t} - e^{-4t} + \frac{1}{2} e^{-5t} \right\} u(t)$$

$$14.35 \quad V(s) = \frac{5}{s} \quad \text{so } v(t) = 5 u(t)$$

$$i_{2k\Omega} = \frac{v}{2 \times 10^3} = \frac{5}{2 \times 10^3} u(t)$$

$$\text{so } \boxed{i_{2k\Omega} = \frac{5}{2} \times 10^{-3} \text{ for all } t > 0} \quad \leftarrow$$

14.39 a) $F(s) = \frac{5}{s+1}$; $f(t) = 5e^{-t} u(t)$

b) $F(s) = \frac{5}{s+1} - \frac{2}{s+4}$; $f(t) = (5e^{-t} - 2e^{-4t}) u(t)$

c) $F(s) = \frac{18}{(s+1)(s+4)} = \frac{6}{s+1} + \frac{-6}{s+4}$; $f(t) = (6e^{-t} - 6e^{-4t}) u(t)$

d) $F(s) = \frac{18s}{(s+1)(s+4)} = \frac{-6}{s+1} + \frac{24}{s+4}$; $f(t) = (-6e^{-t} + 24e^{-4t}) u(t)$

e) $F(s) = \frac{18s^2}{(s+1)(s+4)} = \frac{18s^2}{s^2+5s+4} = 18 - \frac{90s+72}{(s+1)(s+4)}$

$$\left\{ \begin{array}{l} s^2+5s+4 \overline{) 18s^2} \\ \underline{18s^2+90s+72} \end{array} \right\}$$

$F(s) = 18 - \frac{-6}{s+1} - \frac{96}{s+4}$; $f(t) = 18\delta(t) + (6e^{-t} - 96e^{-4t}) u(t)$

14.43 a) $F(s) = \frac{(s+1)(s+2)}{s(s+3)} = \frac{s^2+3s+2}{s^2+3s} = 1 + \frac{2}{s(s+3)}$

$$\left\{ \begin{array}{l} s^2+3s \overline{) 1} \\ \underline{s^2+3s} \\ s+3 \end{array} \right\} \quad F(s) = 1 + \frac{2}{s} + \frac{-2}{s+3}$$

$f(t) = \delta(t) + \frac{2}{s} (1 - e^{-3t}) u(t)$

b) $F(s) = \frac{s+2}{s^2(s^2+4)} = \frac{As+B}{s^2} + \frac{Cs+D}{s^2+4}$

$B = \frac{1}{2}$; $s+2 = (As + \frac{1}{2})(s^2+4) + (Cs+D)s^2$

s^3 terms: $0 = A + C \Rightarrow C = -\frac{1}{4}$

s^2 terms: $0 = \frac{1}{2} + 0 \Rightarrow D = -\frac{1}{2}$


s terms: $1 = 4A \Rightarrow A = \frac{1}{4}$

constant terms: $2 = 2$ ✓

$F(s) = \frac{\frac{1}{4}s + \frac{1}{2}}{s^2} + \frac{-\frac{1}{4}s - \frac{1}{2}}{s^2+4}$

$f(t) = \frac{1}{4} u(t) + \frac{1}{2} t u(t) - \left(\frac{1}{4} \cos 2t + \frac{1}{4} \sin 2t \right) u(t)$

EE 212 Homework 9

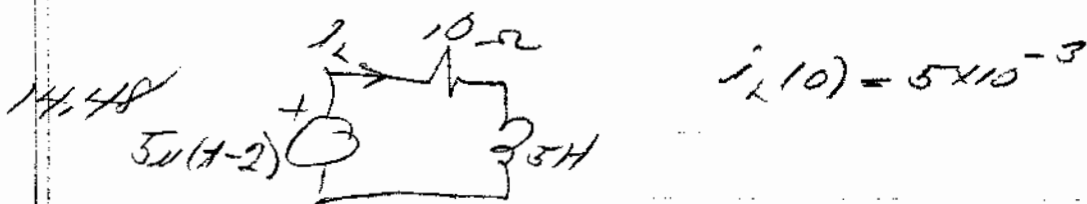

a) $5u(t-2) = 10i_L + 5 \frac{di_L}{dt}$

b) $\frac{5e^{-2s}}{s} = 10I(s) + 5\{sI(s) - 5 \times 10^{-3}\}$

$\therefore I(s) = \frac{5e^{-2s}}{s} + 25 \times 10^{-3} = \frac{5e^{-2s} + 25 \times 10^{-3}s}{s(s+2)}$

or $I(s) = \frac{e^{-2s} + 5 \times 10^{-3}s}{s(s+2)} = \frac{e^{-2s}}{s(s+2)} + \frac{5 \times 10^{-3}}{s+2}$

$I(s) = e^{-2s} \left[\frac{\frac{1}{2}}{s} + \frac{\frac{1}{2}}{s+2} \right] + \frac{5 \times 10^{-3}}{s+2}$

c) $i_L(t) = \frac{1}{2}u(t-2) - \frac{1}{2}e^{-2(t-2)}u(t-2) + 5 \times 10^{-3}e^{-2t}u(t)$

Special

$F(s) = \frac{-5s^2 - 30s + 15}{s^3 + 2s^2 + 5s} = \frac{-5s^2 - 30s + 15}{s(s^2 + 2s + 5)} = \frac{A}{s} + \frac{Bs + C}{s^2 + 2s + 5}$

$A = 3 \quad \left\{ -5s^2 - 30s + 15 = 3(s^2 + 2s + 5) + Bs^2 + Cs \right\}$

$-5 = 3 + B \Rightarrow B = -8$

$-30 = 6 + C \Rightarrow C = -36$



$15 = 15$

$F(s) = \frac{3}{s} - \frac{8s + 36}{(s+1)^2 + 4} = \frac{3}{s} - \frac{8(s+1) + 28(\frac{2}{2})}{(s+1)^2 + 4}$

$f(t) = 3u(t) - (8e^{-t} \cos 2t - 14e^{-t} \sin 2t)u(t)$

EE812

Homework 10

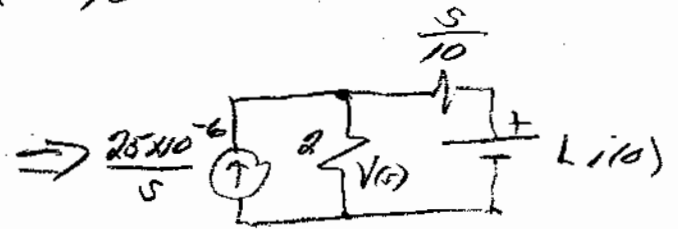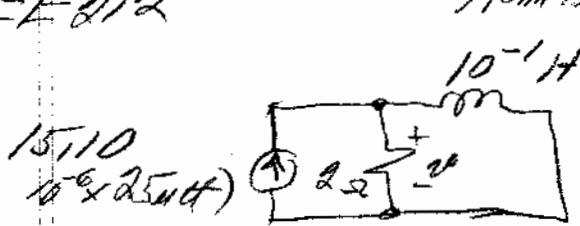with no source before $t=0$

$$i(0) = 0$$


$$V(s) = \frac{25 \times 10^{-6}}{5} \times \frac{2}{2 + \frac{5}{10}} = \frac{5 \times 10^{-6}}{2 + \frac{5}{10}} = \frac{5 \times 10^{-5}}{5 + 20}$$

$$\therefore N(s) = 5 \times 10^{-5} e^{-20t} \text{ (V)} \leftarrow$$


$$P_{\text{resistor}}(s) = \frac{V^2}{2} = 12.5 \times 10^{-10} e^{-40t} = 1.25 \times 10^{-9} e^{-40t} \text{ (W)} \leftarrow$$

EE 212

Homework 11

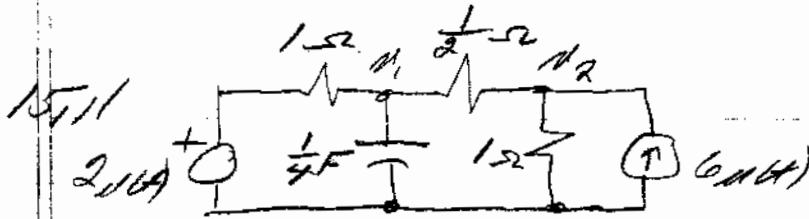

$$n_1(0^-) = -2$$

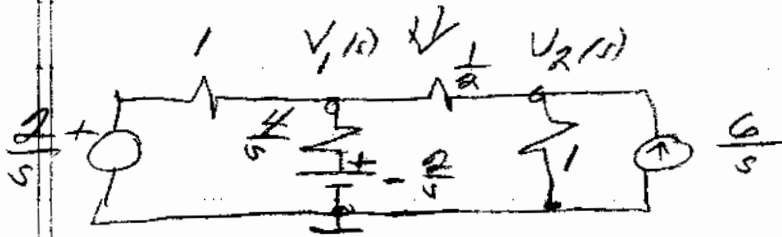

$$\frac{V_1 - \frac{20}{s}}{1} + \frac{V_1 + \frac{20}{s}}{4/s} + \frac{V_1 - V_2}{1/2} = 0$$

$$\frac{V_2 - V_1}{1/2} + \frac{V_2}{1} = \frac{6}{s}$$

$$\left. \begin{aligned} V_1(3 + \frac{5}{4}) - 2V_2 &= -\frac{1}{2} + \frac{10}{s} \\ -2V_1 + 3V_2 &= \frac{6}{s} \end{aligned} \right\}$$

or

$$V_1(12 + 5) - 8V_2 = -2 + \frac{40}{s}$$

$$V_1(-2s) + V_2(3s) = 6$$

$$V_1 = \frac{\begin{vmatrix} -2 + \frac{40}{s} & -8 \\ 6 & 3s \end{vmatrix}}{\begin{vmatrix} 12 + 5 & -8 \\ -2s & 3s \end{vmatrix}} = \frac{72 - 6s}{36s + 35s^2 - 16s} = \frac{72 - 6s}{35s^2 + 20s}$$

$$V_1 = \frac{24 - 2s}{s(5 + \frac{20}{3})} = \frac{18}{s} - \frac{28}{s + \frac{20}{3}}$$

$$V_2 = \frac{\begin{vmatrix} 12 + 5 & -2 + \frac{40}{s} \\ -2s & 6 \end{vmatrix}}{s(20 + 35)} = \frac{72 + 6s - 4s + 16}{s(20 + 35)} = \frac{88 + 2s}{35(s + \frac{20}{3})} = \frac{88}{3} + \frac{2}{3}s$$


$$V_2 = \frac{82}{s} - \frac{56}{s + \frac{20}{3}}$$

$$i_1(t) = \left\{ \frac{18}{s} - \frac{28}{s + \frac{20}{3}} \right\} (uA) = \left\{ 3.6 - 5.6e^{-6.67t} \right\} (uA)$$

$$i_2(t) = \left\{ \frac{82}{s} - \frac{56}{s + \frac{20}{3}} \right\} (uA) = \left\{ 44 - 3.73e^{-6.67t} \right\} (uA)$$

FE 212

Homework 12

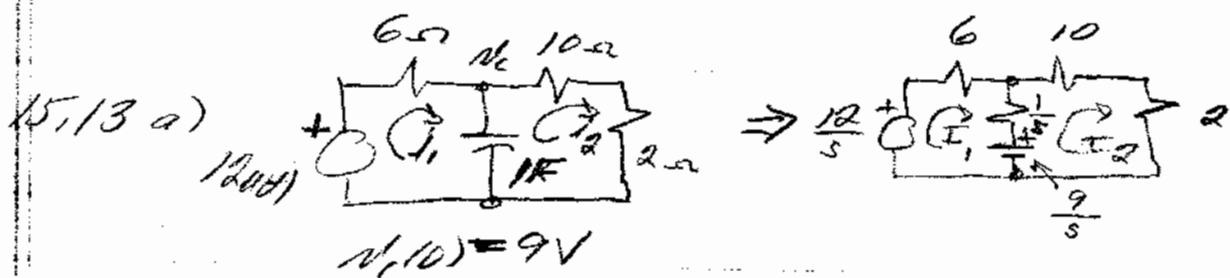

$$\begin{cases} \frac{12}{5} = 6I_1 + \frac{1}{5}(I_1 - I_2) + \frac{9}{5} & I_1(6 + \frac{1}{5}) - I_2 \frac{1}{5} = \frac{3}{5} \\ \frac{9}{5} = (I_2 - I_1) \frac{1}{5} + 12I_2 & -I_1 \frac{1}{5} + I_2(12 + \frac{1}{5}) = \frac{9}{5} \end{cases}$$

multiplying by 5 gives: $\begin{cases} I_1(6s+1) - I_2 = 3 \\ -I_1 + I_2(12s+1) = 9 \end{cases}$

$$I_1 = \frac{\begin{vmatrix} 3 & -1 \\ 9 & 12s+1 \end{vmatrix}}{\begin{vmatrix} 6s+1 & -1 \\ -1 & 12s+1 \end{vmatrix}} = \frac{36s+3+9}{72s^2+6s+12s+1} = \frac{36s+12}{5(72s+18)} = \frac{6s+2}{5(12s+3)}$$


$$I_1 = \frac{6s+2}{12s(s+\frac{1}{4})} = \frac{2}{3s} + \frac{1}{s+\frac{1}{4}} \quad \therefore i_1(t) = \left\{ \frac{2}{3} - \frac{1}{6} e^{-\frac{t}{4}} \right\} u(t)$$

$$I_2 = \frac{\begin{vmatrix} 6s+1 & 3 \\ -1 & 9 \end{vmatrix}}{5(72s+18)} = \frac{54s+9+3}{5(72s+18)} = \frac{9s+2}{12s(s+\frac{1}{4})} = \frac{2}{3s} + \frac{1}{s+\frac{1}{4}}$$

$$\text{so } i_2(t) = \left\{ \frac{2}{3} + \frac{1}{12} e^{-\frac{t}{4}} \right\} u(t) \leftarrow$$

Homework 13

Special

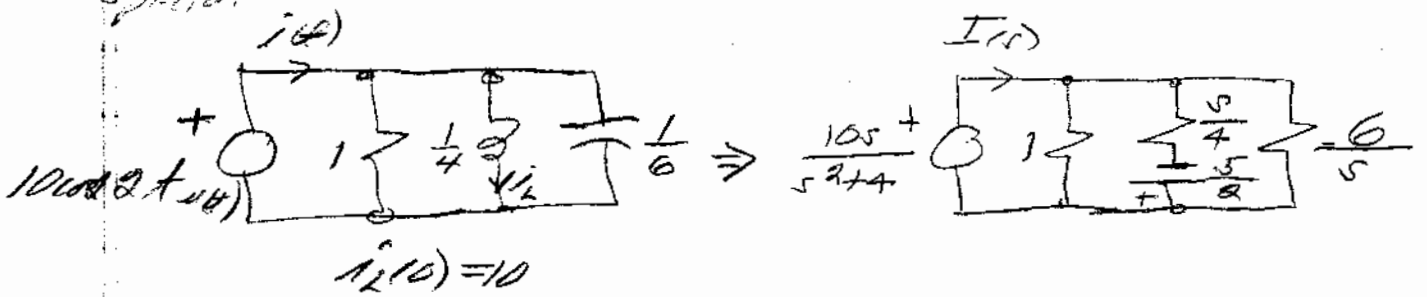

$$I(s) = \frac{10s}{s^2+4} + \frac{\frac{10s}{s^2+4} + \frac{5}{2}}{\frac{5}{4}} + \frac{\frac{10s}{s^2+4}}{\frac{6}{5}}$$

$$I(s) = \frac{10s}{s^2+4} + \frac{40}{s^2+4} + \frac{10}{5} + \frac{10s^2}{6(s^2+4)}$$

$$-\frac{20}{3} + \frac{120}{3}$$


$$I(s) = \frac{10s}{s^2+4} + \frac{40}{s^2+4} + \frac{10}{5} + \frac{5}{3} \left[1 - \frac{4}{s^2+4} \right]$$

$$I(s) = \frac{10s}{s^2+4} + \frac{50}{3} \cdot \frac{2}{s^2+4} + \frac{10}{5} + \frac{5}{3}$$

$$i(t) = \left\{ 10 \cos 2t + \frac{50}{3} \sin 2t + 10 \right\} \text{ A} + \frac{5}{3} \delta(t)$$


$$\text{or } i(t) = \left\{ \sqrt{10^2 + \left(\frac{50}{3}\right)^2} \cos\left(2t - \tan^{-1}\left(\frac{5}{3}\right)\right) + 10 \right\} \text{ A} + \frac{5}{3} \delta(t)$$

check of sinusoidal steady state

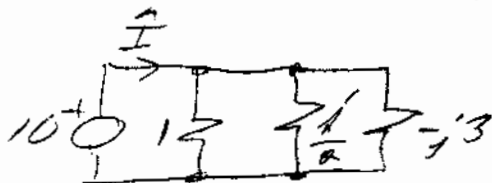

$$\hat{I} = 10 - j20 + j\frac{10}{3} = 10 - j\left(\frac{50}{3}\right) = \sqrt{10^2 + \left(\frac{50}{3}\right)^2} e^{-j \tan^{-1}\left(\frac{5}{3}\right)}$$
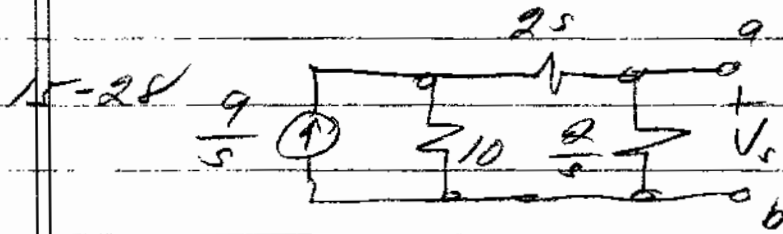
$$i(t) = \left\{ \sqrt{10^2 + \left(\frac{50}{3}\right)^2} \cos\left(2t - \tan^{-1}\left(\frac{5}{3}\right)\right) + 10 \right\} \text{ A}$$



$$V_{TH}(s) = \frac{9}{s} \cdot \frac{10}{10 + 2s + \frac{2}{s}} = \frac{9}{s} \cdot \frac{20}{2s^2 + 10s + 2}$$

$$V_{TH}(s) = \frac{90}{s(s^2 + 5s + 1)}$$

$$Z_{TH} = \frac{\frac{2}{s}(2s + 10)}{\frac{2}{s} + 2s + 10} = \frac{4s + 20}{2s^2 + 10s + 2} \left[\frac{2s + 10}{s^2 + 5s + 1} \right]$$

$$15.42 \quad f_1(t) = e^{-5t} u(t) ; \quad f_2(t) = (1 - e^{-2t}) u(t)$$

$$y(t) = \int_0^t e^{-5(t-z)} u(t-z) (1 - e^{-2z}) u(z) dz$$

$$= e^{-5t} \int_0^t e^{5z} (1 - e^{-2z}) dz = e^{-5t} \left\{ \frac{1}{5} e^{5z} - \frac{1}{3} e^{3z} \right\}_0^t u(t)$$

$$y(t) = e^{-5t} \left\{ \frac{1}{5} [e^{5t} - \frac{1}{5}] - \frac{1}{3} [e^{3t} - 1] \right\} u(t)$$

$$y(t) = \left\{ \frac{1}{5} [1 - e^{-5t}] - \frac{1}{3} [e^{-2t} - e^{-5t}] \right\} u(t)$$

$$\boxed{y(t) = \left\{ \frac{1}{5} + \frac{2}{15} e^{-5t} - \frac{1}{3} e^{-2t} \right\} u(t)} \quad \leftarrow$$

$$F_1(s) = \frac{1}{s+5} ; \quad F_2(s) = \frac{1}{s} - \frac{1}{s+2}$$

$$\therefore Y(s) = F_1(s)F_2(s) = \frac{1}{s} \cdot \frac{1}{s+5} - \frac{1}{(s+2)(s+5)}$$

$$Y(s) = \frac{\frac{1}{5}}{s} + \frac{-\frac{1}{5}}{s+5} - \frac{\frac{1}{3}}{s+2} - \frac{-\frac{1}{2}}{s+5} = \frac{1}{5} - \frac{1}{3} + \frac{\frac{2}{15}}{s+5}$$

$$\text{so } \boxed{y(t) = \left\{ \frac{1}{5} - \frac{1}{3} e^{-2t} + \frac{2}{15} e^{-5t} \right\} u(t)}$$

$$15.44 \quad h(t) = 2e^{-3t} u(t) ; \quad x(t) = u(t) - \delta(t)$$

$$a) \quad y(t) = \int_0^t 2e^{-3(t-z)} u(t-z) [u(z) - \delta(z)] dz$$

$$= 2e^{-3t} \left(\frac{1}{3} \right) e^{3z} \Big|_0^t - 2e^{-3t} \int_0^t e^{3z} \delta(z) dz$$

$$y(t) = \frac{2}{3} e^{-3t} [e^{3t} - 1] u(t) - 2e^{-3t} u(t)$$

$$y(t) = \left\{ \frac{2}{3} - \frac{8}{3} e^{-3t} \right\} u(t) \quad \leftarrow$$


$$b) \quad H(s) = \frac{2}{s+3} ; \quad X(s) = \frac{1}{s} - 1$$

$$Y(s) = H(s)X(s) = \frac{2}{s(s+3)} - \frac{2}{s+3} = \frac{2}{s} + \frac{2}{s+3} - \frac{2}{s+3}$$

$$Y(s) = \frac{2}{s} + \frac{-\frac{2}{3} - 2}{s+3} = \frac{2}{s} - \frac{8}{3} \frac{1}{s+3}$$

$$\text{so } y(t) = \left\{ \frac{2}{3} - \frac{8}{3} e^{-3t} \right\} u(t) \quad \leftarrow$$

Homework 17

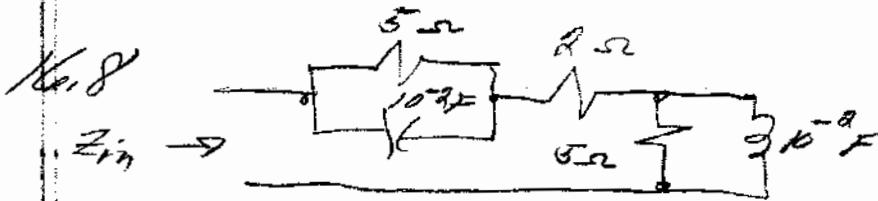

$$Z_{in} = 2 + \frac{5}{5 + \frac{1}{j\omega 10^{-2}}} + \frac{5 \cdot j\omega 10^{-2}}{5 + j\omega 10^{-2}} = 2 + \frac{5}{1 + j\omega 5 \times 10^{-2}} + \frac{j\omega 5 \times 10^{-2}}{5 + j\omega 10^{-2}}$$

$$Z_{in} = 2 + \frac{5(1 - j\omega 5 \times 10^{-2})}{1 + 25\omega^2 \times 10^{-4}} + \frac{j\omega 5 \times 10^{-2}(5 - j\omega 10^{-2})}{25 + \omega^2 \times 10^{-4}}$$

c) resonance $\frac{-25\omega \times 10^{-2}}{1 + 25\omega^2 \times 10^{-4}} + \frac{\omega 25 \times 10^{-2}}{25 + \omega^2 \times 10^{-4}} = 0$

or $25 + \omega^2 \times 10^{-4} = 1 + 25\omega^2 \times 10^{-4} \Rightarrow 24 = 24\omega^2 \times 10^{-4}$

$$\omega_0 = \sqrt{\frac{1}{10^{-4}}} = 10^2 \text{ or } f_0 = 15.9 \text{ Hz}$$

$$Z_{in}(\omega_0) = 2 + \frac{5}{1 + 25} + \frac{5 \times 10^4 \times 10^{-4}}{25 + 1} = \frac{52 + 10}{26} = \frac{62}{26} = \boxed{2.39 \Omega}$$

Ex. 25 $BW = 10^6 \text{ Hz}, f_1 = 5.5 \text{ kHz}$


a) $\omega_1 = 2\pi \times 5.5 \times 10^3$

$$f_2 = f_1 + BW = 5.5 \times 10^3 + 10^6 = \boxed{1.0055 \times 10^6 \text{ Hz}}$$

b) $f_0 = \sqrt{f_1 f_2} = \sqrt{5.5 \times 10^3 \times 1.0055 \times 10^6} = \boxed{74.37 \times 10^3 \text{ Hz}}$

c) $Q_0 = \frac{f_0}{BW} = \frac{74.37 \times 10^3}{10^6} = \boxed{0.074}$

16.57

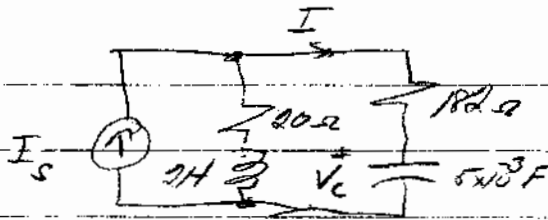

$$H(\omega) = \frac{\hat{V}_c}{\hat{I}_s}$$

$$H(s) = \frac{V_c(s)}{I_s(s)}$$


$$I(s) = I_s \frac{20 + 2s}{20 + 2s + \frac{1}{5 \times 10^{-3}}}$$

$$V_c(s) = I(s) \frac{1}{5 \times 10^{-3}} = \frac{(20 + 2s) I_s}{1.015 + 10^{-2} s^2 + 1} = \frac{(20 + 2s) I_s}{5 \times 10^{-5} s^2 + 1.015 + 1}$$

$$H(s) = \frac{10^2(20 + 2s)}{s^2 + 101s + 1} = \frac{2 \times 10^2 (s + 10)}{(s + 1)(s + 100)}$$

$$H(j\omega) = 20 \frac{(1 + j\frac{\omega}{10})}{(1 + j\frac{\omega}{1})(1 + j\frac{\omega}{100})}$$

$$20 / \log_{10} 20 = 26 \text{ dB}$$

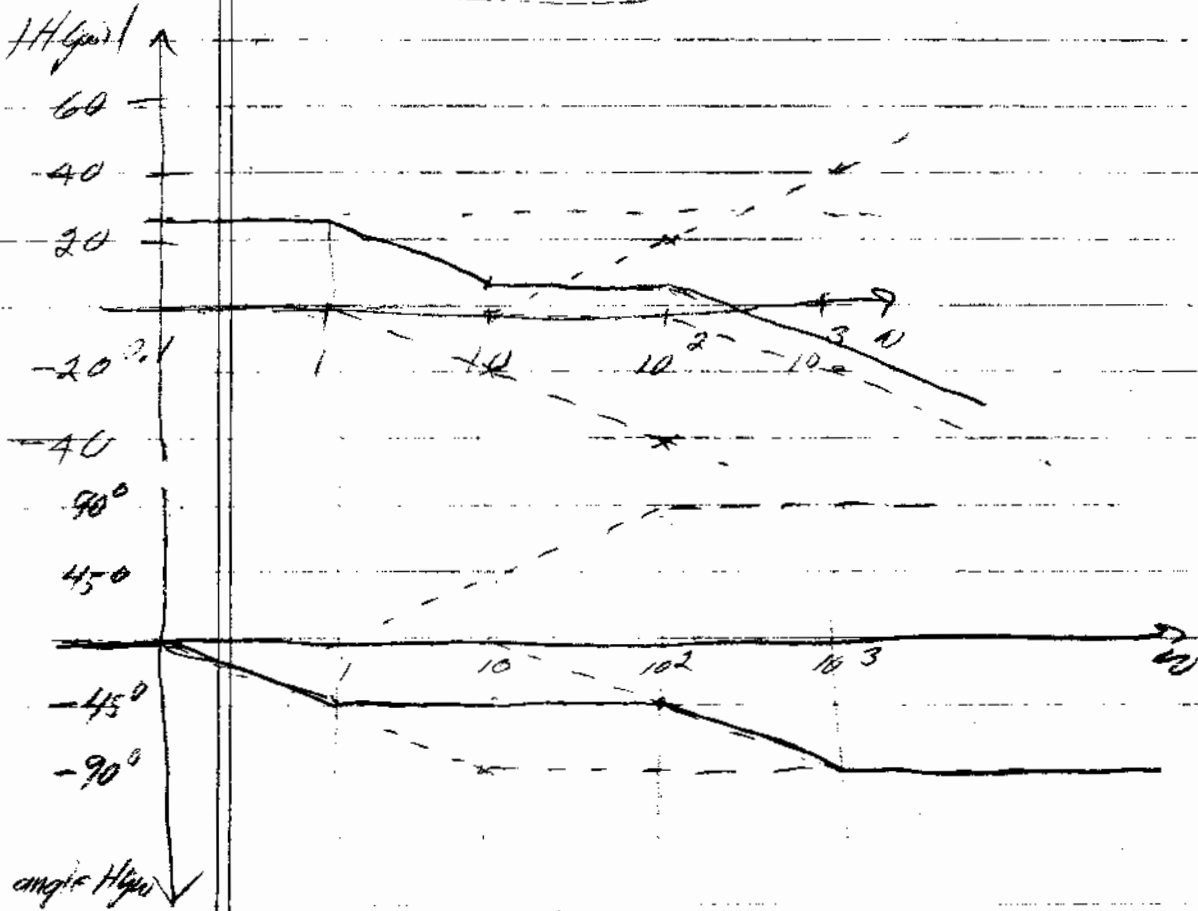


EE 212


Homework 19

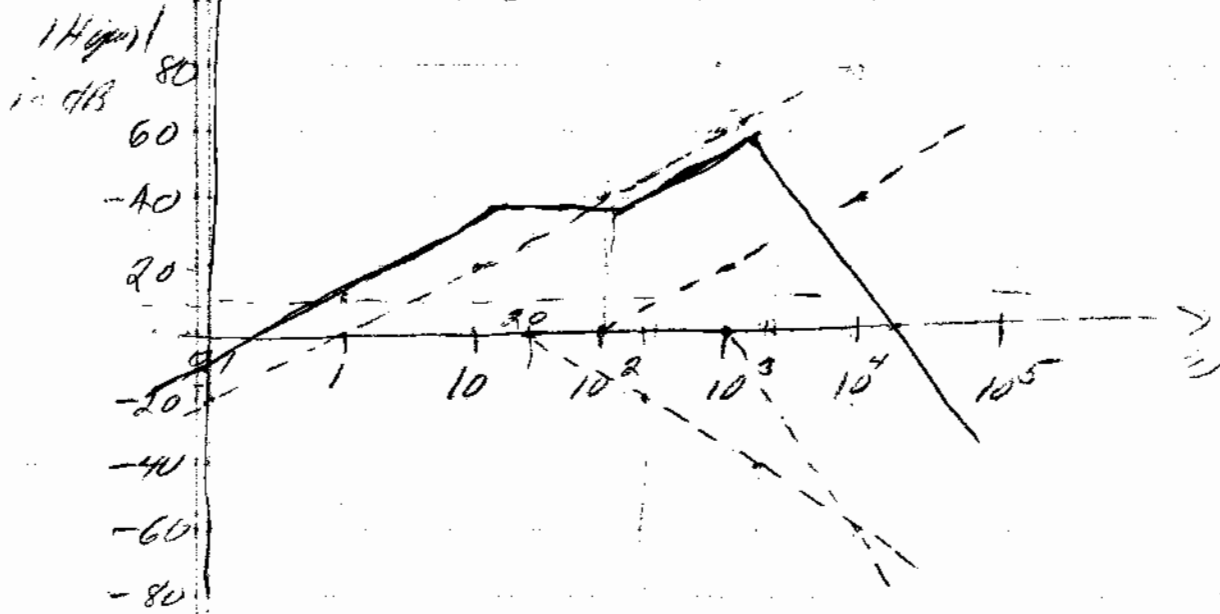16.58a) $H(s) = \frac{5 \times 10^8 (s+100)}{(s+20)(s+10^3)^3} = \frac{5 \times 10^8 \times 10^{-9} s (1 + \frac{s}{100})}{20 \times 10^9 (1 + \frac{s}{20})(1 + \frac{s}{10^3})^3}$


$H(j\omega) = \frac{5}{8} \frac{j\omega (1 + \frac{j\omega}{100})}{(1 + \frac{j\omega}{20}) (1 + \frac{j\omega}{10^3})^3}$; $20 \log_{10}(\frac{5}{8}) = 7.96$



16.59a)

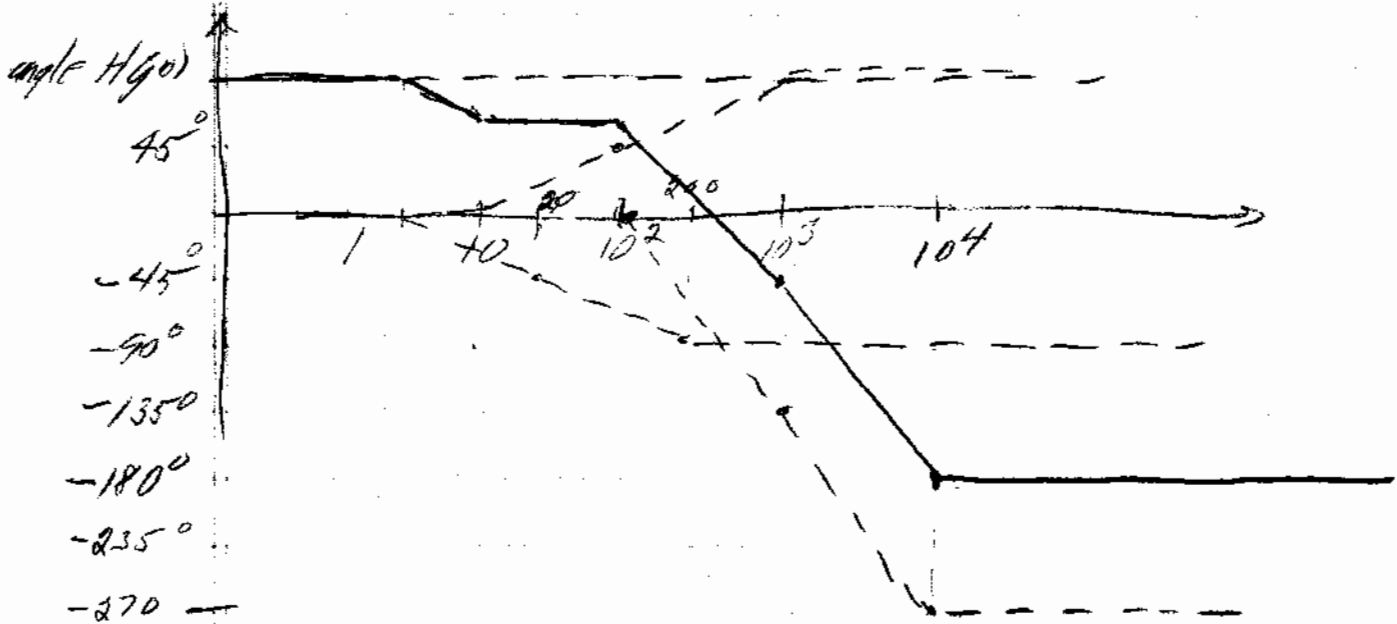

No. 61


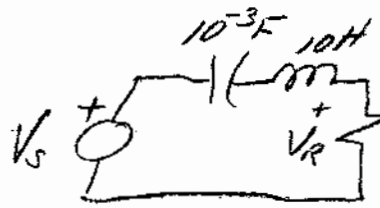


$$\frac{V_r(s)}{V_s(s)} = \frac{25}{25 + 10s + \frac{1}{10^{-3}s}} = H(s)$$

a) $H(s) = \frac{25s}{10s^2 + 25s + 10^3} = \frac{25}{10^3} \frac{s}{1 + 85 \times 10^{-3} s + \frac{s^2}{100}}$

$\omega_0 = 10$; $\frac{2\zeta}{\omega_0} = 25 \times 10^{-3}$; so $\zeta = \frac{25 \times 10^{-3} \times 10}{2}$


$\zeta = 0.125$

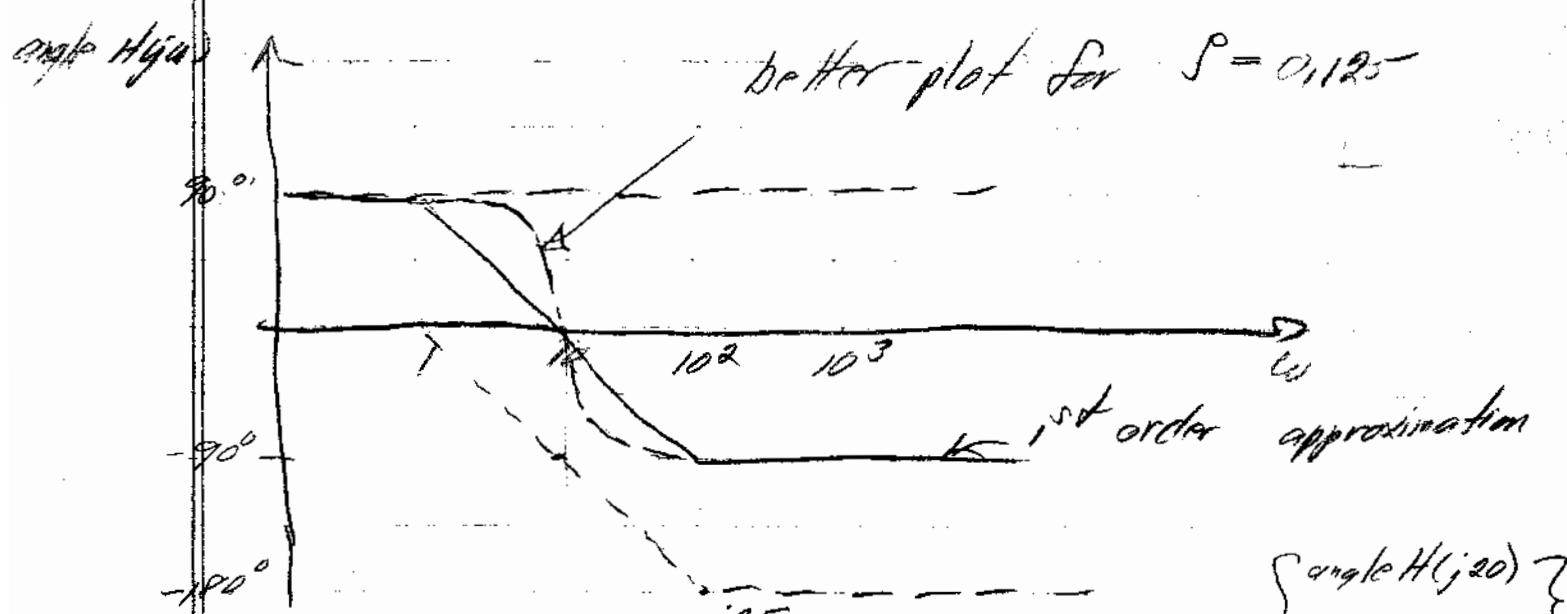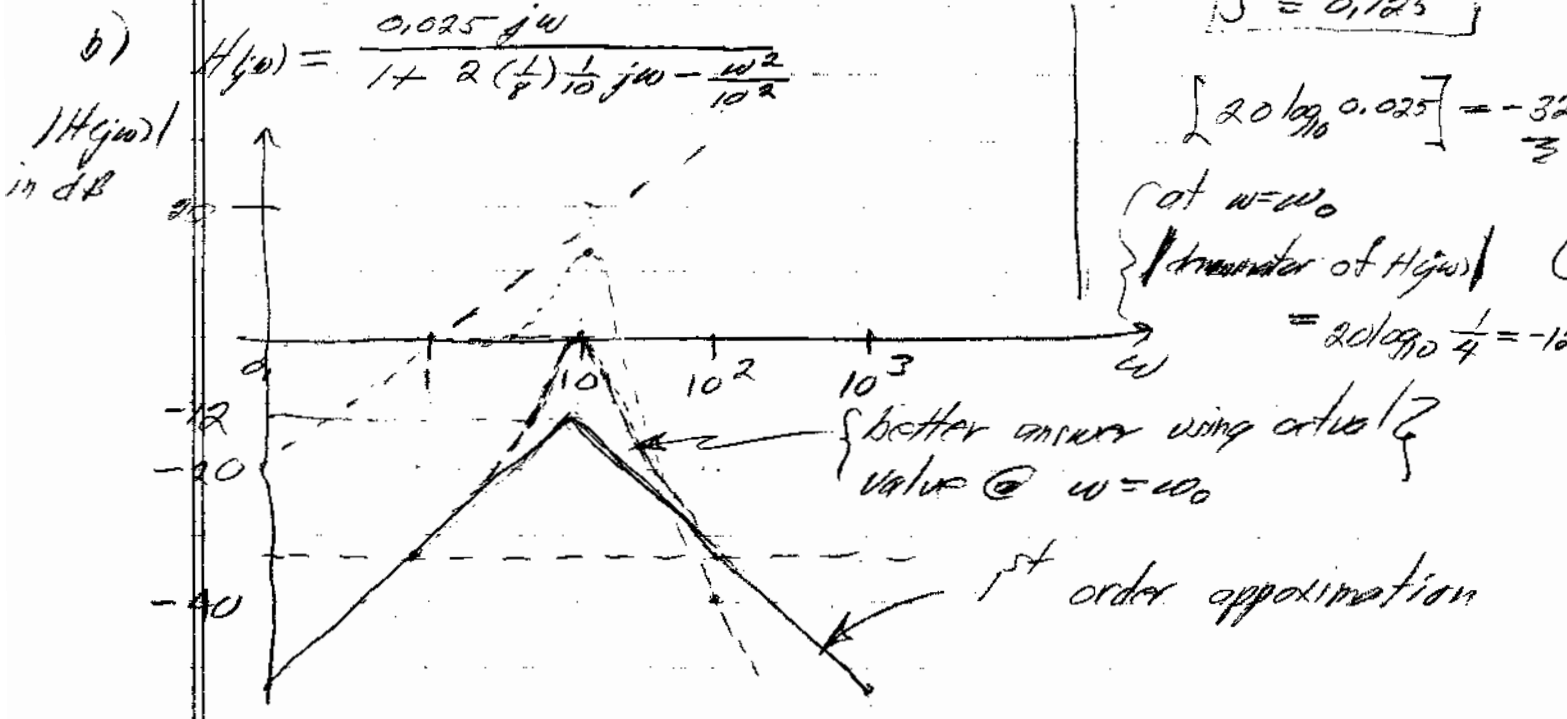

c) @ $\omega = 20$ $|H(j20)| = \left| \frac{j0.5}{1 - 4 + j0.5} \right| \Rightarrow |H(j20)|_{\text{in dB}} = -15.68$; $\left. \begin{matrix} \text{angle } H(j20) \\ = -80.54^\circ \end{matrix} \right\}$

16.162



16.50

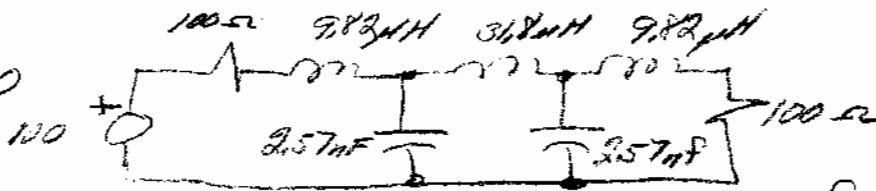

Magnitude scaling factor = $\frac{1}{2}$
 Frequency scaling factor = 2×10^3

$$\left\{ \begin{array}{l} R' = \frac{R}{2} \\ L' = \frac{L}{2} \\ C' = 2C \end{array} \right. \quad \left\{ \begin{array}{l} R' = R \\ L' = L / 2 \times 10^3 \\ C' = C / 2 \times 10^3 \end{array} \right.$$

New circuit:

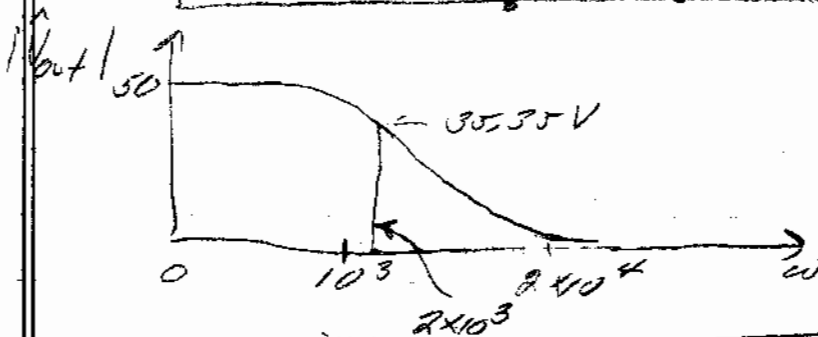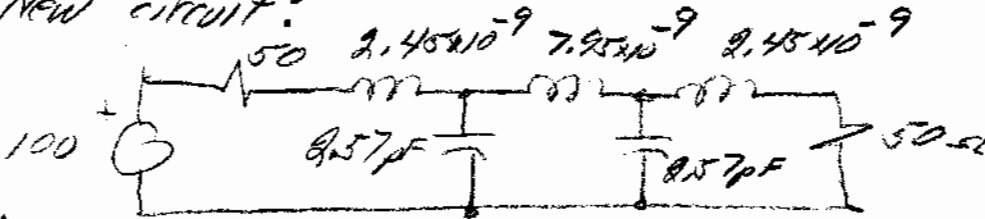


OK for original cutoff frequency = 1 (see next page for $f_c = 10^3$)

No. 62 1st stage $H_1(s) = -10$; 2nd stage $H_2(s) = -10$

$$3^{rd} \text{ stage } H_3(s) = - \frac{2 \times 10^5 \left(\frac{1}{5 \times 10^{-6}} \right)}{2 \times 10^5 + \frac{1}{5 \times 10^{-6}}} = - \frac{2 \times 10^5}{5 \times 10^4} \cdot \frac{1}{1 + 5 \times 10^{-1}}$$

$$\therefore \text{total } H(s) = H_1(s) H_2(s) H_3(s) = - \frac{2}{5} \times 10^3 \frac{1}{1 + 5 \times 10^{-1}} = -400 \frac{1}{1 + \frac{5}{5}}$$


$$20 \log_{10} 400 = 52 \text{ dB}$$

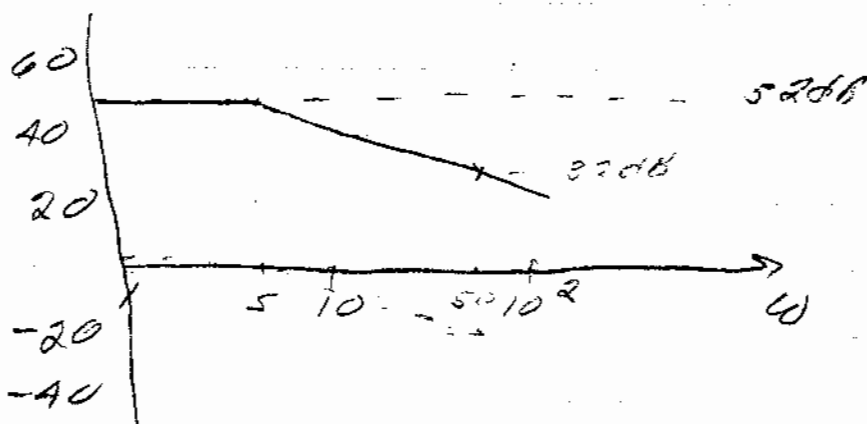

$K=50$ for original $f_{cutoff} = 10^6$ Hz

Magnitude scaling factor = $\frac{1}{2}$.

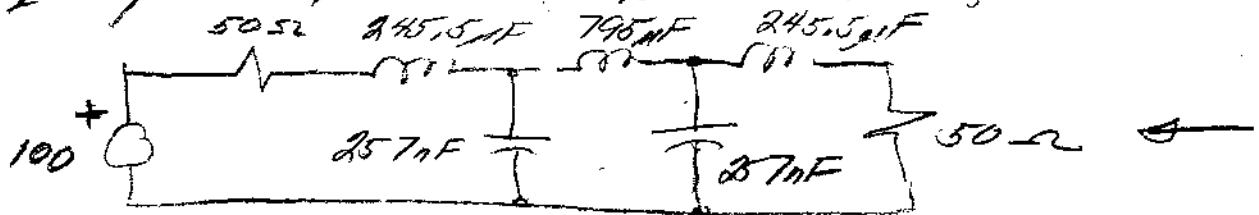Frequency scaling factor = $\frac{20 \times 10^3}{10^6} = 2 \times 10^{-2}$



plot the same as previous page!