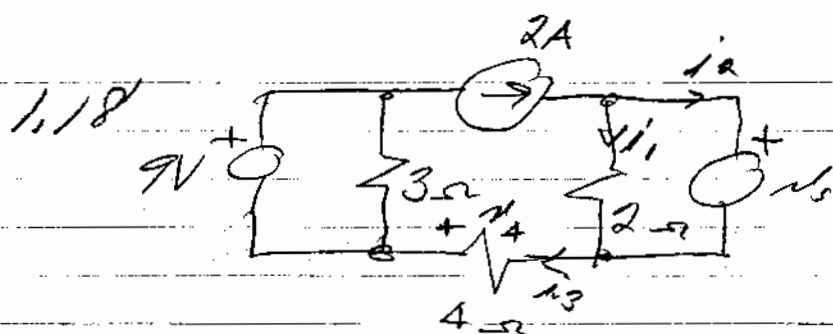





a)  $v_s = 2V$ ,  $i_1 = 1A$ ,  $i_2 = 2 - 1 = 1A$ ,  $i_3 = i_1 + i_2 = 2A$

$\therefore v_4 = -2 \times 4 = -8V$


b)  $v_s = 4V$ ,  $i_1 = \frac{4}{2} = 2A$  so  $i_3 = 2$  and  $v_4 = -8V$

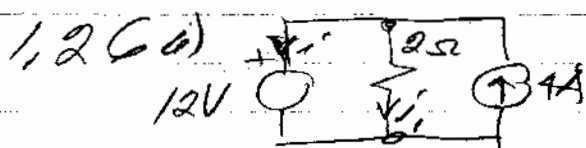c)  $v_s = 6V$ ,  $i_1 = \frac{6}{2} = 3A$  so  $i_3 = 2$  and  $v_4 = -8V$




$i_1 = \frac{12}{2} = 6A$

$i_2 = 4 - i_1 = -2A$

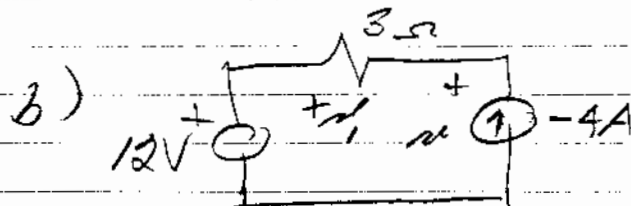

$v_1 = 3 \times 4 = 12V$

$v = 12 - 12 = 0$

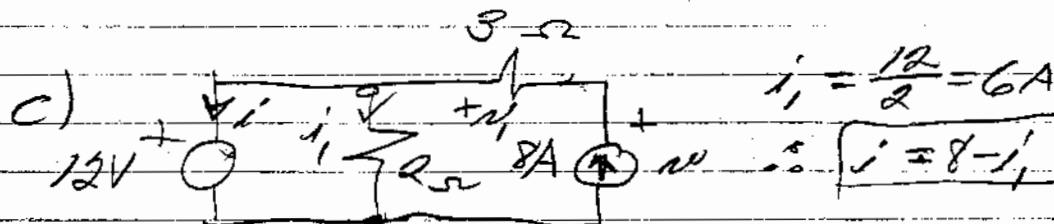


$i_1 = \frac{12}{2} = 6A$

$\therefore i_2 = 8 - i_1 = 2A$

$v_1 = -3 \times 8 = -24V$

$v = 12 - v_1 = 36V$

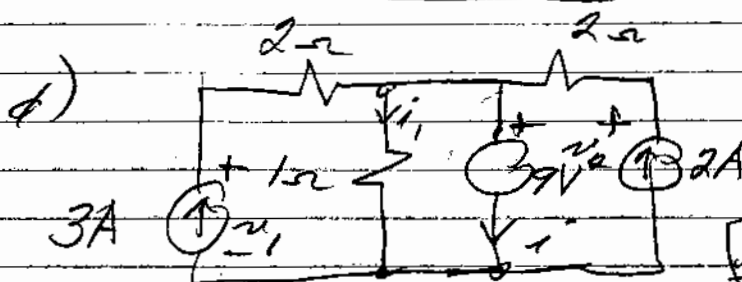


$v_2 = 9 + 2 \times 2 = 13V$

$i_1 = 9A$


so  $i = 2 - i_1 + 3 = -4A$

$v_1 = 3 \times 2 + 9 = 15V$

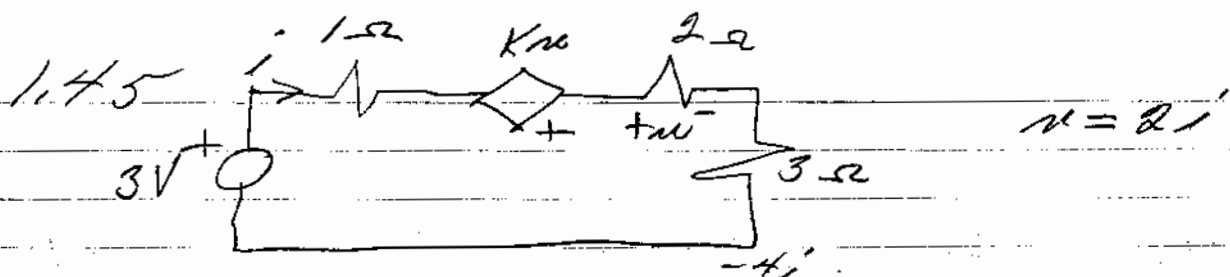

a)  $K=2$   $-3 + i' - 2u + 2i' + 3i' = 0$   
 $2i' = 3$   $i' = \frac{3}{2} \text{ A}$

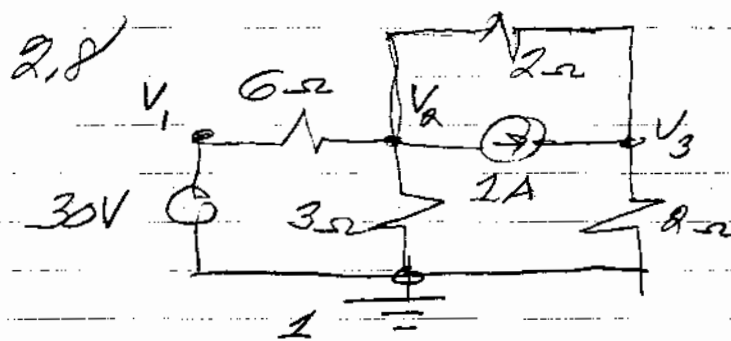b)  $K=4$   $-3 + i' - 8i' + 5i' = 0$ ;  $-2i' = 3$   
 $i' = -\frac{3}{2}$



$$\frac{V_2 - 30}{6} + \frac{V_2}{3} + \frac{V_2 - V_3}{2} = -1$$


$$\frac{V_3 - V_2}{2} + \frac{V_3}{2} = 1$$

or  $V_2(\frac{1}{6} + \frac{1}{3} + \frac{1}{2}) - \frac{1}{2}V_3 = 4$   $2V_2 - V_3 = 8$  (1)  
 $-\frac{1}{2}V_2 + V_3 = 1$   $-V_2 + 2V_3 = 2$  (2)

$$V_2 = \frac{\begin{vmatrix} 8 & -1 \\ 2 & 2 \end{vmatrix}}{\begin{vmatrix} 2 & -1 \\ -1 & 2 \end{vmatrix}} = \frac{16 + 2}{4 - 1} = \frac{18}{3} = 6 \text{ V}$$

from (2)  $V_3 = \frac{2 + V_2}{2} = 4 \text{ V}$

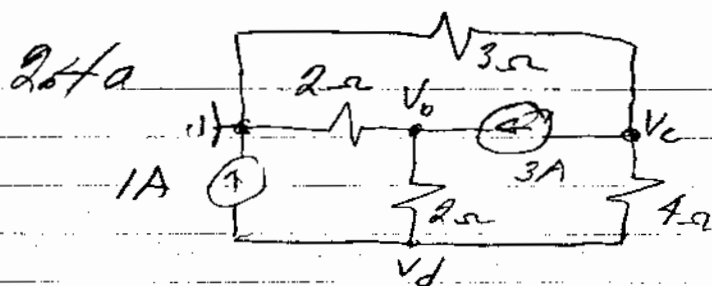or  $V_3 = \frac{\begin{vmatrix} 2 & 8 \\ -1 & 2 \end{vmatrix}}{\begin{vmatrix} 2 & -1 \\ -1 & 2 \end{vmatrix}} = \frac{-4 + 8}{4 - 1} = \frac{4}{3} = 4 \text{ V}$



$$\frac{V_b}{2} + \frac{V_b - V_d}{2} = 3$$

$$\frac{V_c}{3} + \frac{V_c - V_d}{4} = -3$$

$$\frac{V_d - V_b}{2} + \frac{V_d - V_c}{4} = -1$$


or

$$\begin{cases} V_b - \frac{1}{2}V_d = 3 \\ \frac{7}{12}V_c - \frac{1}{4}V_d = -3 \\ -\frac{1}{2}V_b - \frac{1}{4}V_c + \frac{3}{4}V_d = -1 \end{cases} \Rightarrow \begin{cases} 2V_b - V_d = 6 \\ 7V_c - 3V_d = -36 \\ -2V_b - V_c + 3V_d = -4 \end{cases}$$

$$V_b = \frac{\begin{vmatrix} 6 & 0 & -1 \\ -36 & 7 & -3 \\ -4 & -1 & 3 \end{vmatrix}}{\begin{vmatrix} 2 & 0 & -1 \\ 0 & 7 & -3 \\ -2 & -1 & 3 \end{vmatrix}} = \frac{108 - 64 = 44}{2(21-3) - 1(36+28)} = \frac{44}{22} = \boxed{2V}$$

$$V_c = \frac{\begin{vmatrix} 2 & 0 & -1 \\ 0 & 7 & -3 \\ -2 & -1 & 3 \end{vmatrix}}{\begin{vmatrix} 2 & 0 & -1 \\ 0 & 7 & -3 \\ -2 & -1 & 3 \end{vmatrix}} = \frac{-240 + 108 = -132}{22} = \boxed{-6V}$$
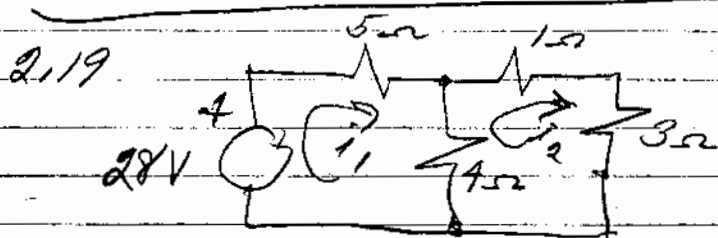
$$V_d = \frac{\begin{vmatrix} 2 & 0 & 6 \\ 0 & 7 & -36 \\ -2 & -1 & -4 \end{vmatrix}}{\begin{vmatrix} 2 & 0 & -1 \\ 0 & 7 & -3 \\ -2 & -1 & 3 \end{vmatrix}} = \frac{-124 + 84 = -40}{22} = \boxed{-2V}$$




$$28 = 5i_1 + 4(i_1 - i_2) = 9i_1 - 4i_2$$

$$0 = 4(i_2 - i_1) + 4i_2 = -4i_1 + 8i_2$$

$$i_1 = \frac{\begin{vmatrix} 28 & -4 \\ 0 & 8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -4 & 8 \end{vmatrix}} = \frac{8 \times 28}{72 - 16} = \frac{224}{56} = \boxed{4A}$$
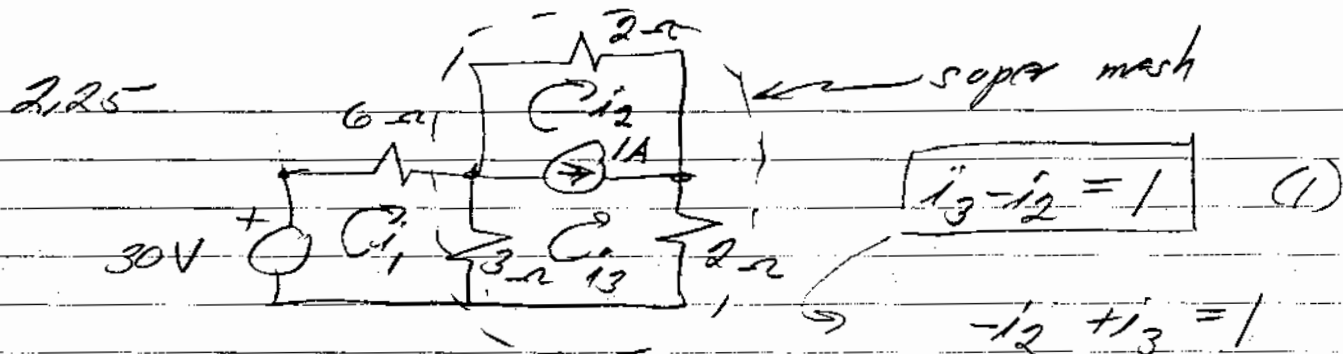
$$i_2 = \frac{\begin{vmatrix} 9 & 28 \\ -4 & 0 \end{vmatrix}}{56} = \frac{-4 \times 28}{56} = \boxed{-2A}$$




$$\begin{cases} 6i_1 + 3(i_1 - i_3) = 30 \\ 3(i_3 - i_1) + 2i_2 + 2i_3 = 0 \end{cases} \Rightarrow \begin{cases} 9i_1 - 3i_3 = 30 \\ -3i_1 + 2i_2 + 5i_3 = 0 \end{cases}$$

$$x_1 = \begin{bmatrix} 1 & -1 & 1 \\ 30 & 0 & -3 \\ 0 & 2 & 5 \end{bmatrix} \Rightarrow \frac{-2(-33) + 5(30)}{1(45 - 9) + 1(18)} = \frac{216}{54} = 4A$$

$$i_2 = \frac{\begin{bmatrix} 0 & 1 & -1 \\ 9 & 30 & -3 \\ -3 & 0 & 5 \end{bmatrix}}{54} = \frac{-1(45 - 9) + 1 \times 90}{54} = \frac{54}{54} = 1A$$

from (1)  $i_3 = 1 + i_2 = 2A$

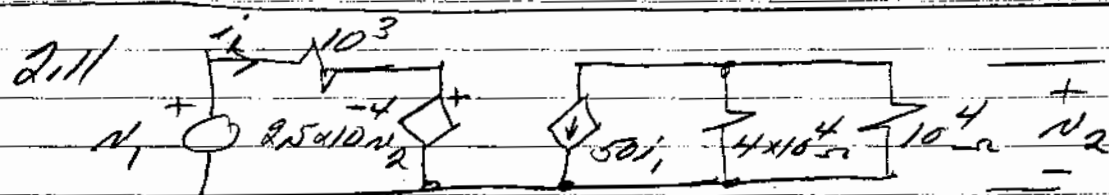

$$-N_1 + 10^3 i_1 + 2.5 \times 10^{-4} N_2 = 0 \quad \left( N_2 = -50i_1; \left(\frac{4}{5}\right) \times 10^4 = -40 \times 10^4 \right)$$

$$0 - N_1 + 10^3 \left( -\frac{N_2}{4 \times 10^5} \right) N_2 + 2.5 \times 10^{-4} N_2 = 0$$

$$\text{or } -N_1 = N_2 (0.25 \times 10^{-2} - 2.5 \times 10^{-4}) = 2.25 \times 10^{-3} N_2$$


a)

$$\frac{N_2}{N_1} = -\frac{1}{2.25 \times 10^{-3}} = -444.44$$

b)  $\frac{N_1}{i_1} = R_{in} = \frac{-N_1 \times 4 \times 10^3}{N_2} = \frac{4 \times 10^5}{444.44} = 900 \Omega$


ES 332

Homework 5

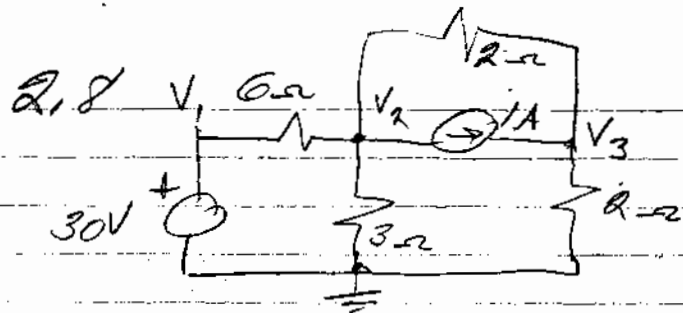

$$V_1 = 30V$$

Voltage source only

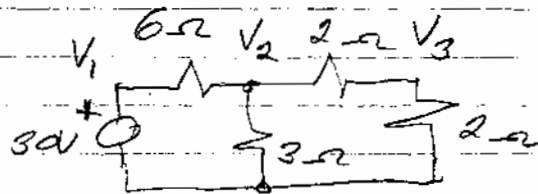


$$\frac{V_2 - 30}{6} + \frac{V_2}{3} + \frac{V_2}{4} = 0; \quad V_2 \left( \frac{1}{6} + \frac{1}{3} + \frac{1}{4} \right) = 5; \quad V_2 = \frac{20}{3}$$

using voltage division

$$V_3 = \frac{10}{3}$$

current source only

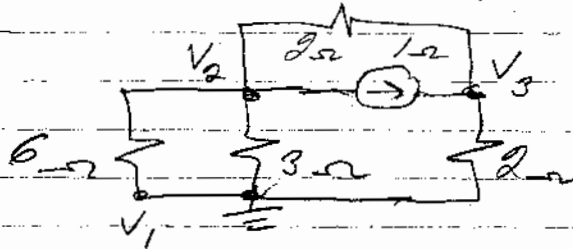

$$\frac{V_2}{2} + \frac{V_2 - V_3}{2} + 1 = 0$$

$$V_1 = 0$$

$$\frac{V_3 - V_2}{2} + \frac{V_3}{2} - 1 = 0$$

$$\text{or } V_2 - \frac{1}{2}V_3 = -1$$

$$-\frac{1}{2}V_2 + V_3 = 1$$


$$V_2 = \frac{\begin{vmatrix} -1 & -\frac{1}{2} \\ 1 & 1 \end{vmatrix}}{\begin{vmatrix} 1 & -\frac{1}{2} \\ -\frac{1}{2} & 1 \end{vmatrix}} = \frac{-1 + \frac{1}{2}}{1 - \frac{1}{4}} = \frac{-\frac{1}{2}}{\frac{3}{4}} = -\frac{2}{3}V$$

$$V_3 = \frac{\begin{vmatrix} 1 & -1 \\ -\frac{1}{2} & 1 \end{vmatrix}}{\frac{3}{4}} = \frac{1 - \frac{1}{2}}{\frac{3}{4}} = \frac{2}{3}V$$


$$V_1 = 30 + 0 = 30V$$

$$V_2 = \frac{20}{3} - \frac{2}{3} = 6V$$
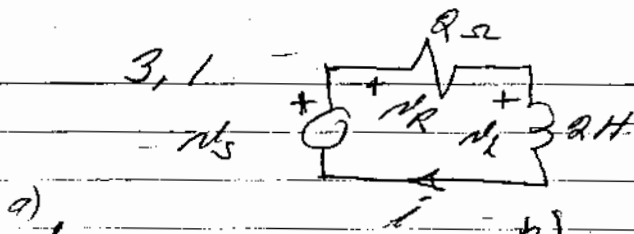
$$V_3 = \frac{10}{3} + \frac{2}{3} = 4V$$









$i(t)$

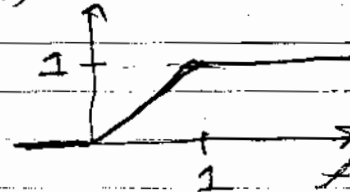


$$v_L = L \frac{di}{dt}$$

$$w_L = \frac{1}{2} L i^2$$

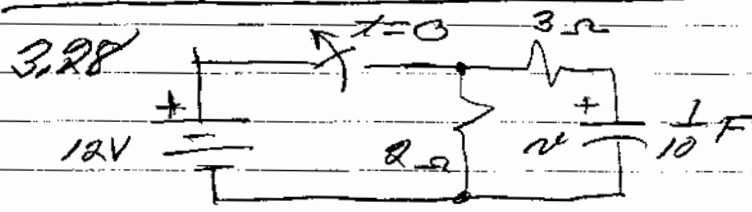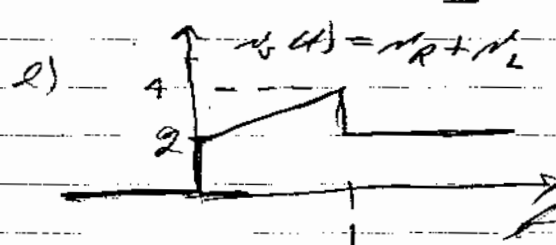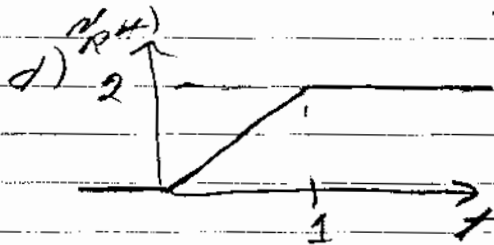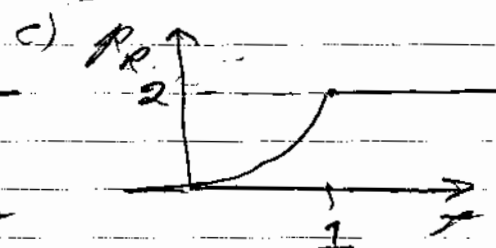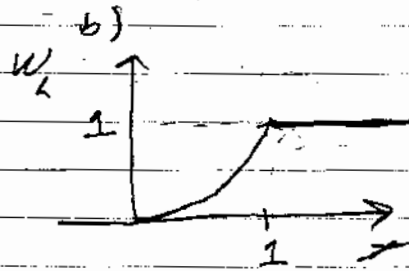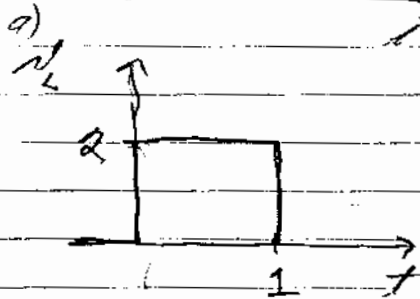

$$v(0) = 12V$$



s domain circuit for  $t > 0$

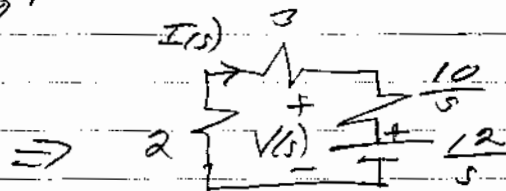

$$I(s) \left[ 2 + \frac{10}{s} \right] = - \frac{12}{s} ; I(s) = - \frac{12/s}{s + 2} = - \frac{12}{s(s + 2)}$$

$$\therefore i(t) = - \frac{12}{5} e^{-2t} u(t)$$


$$v(t) = -5 i(t) = 12 e^{-2t} u(t)$$

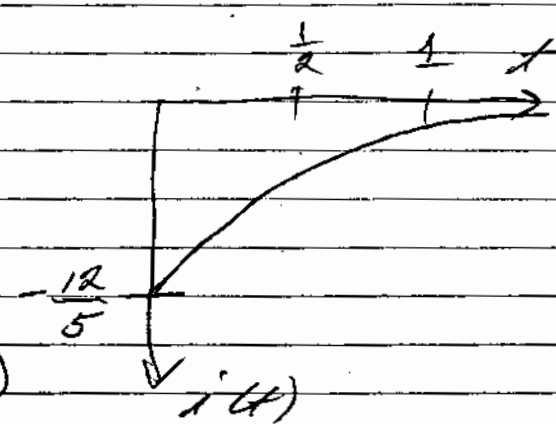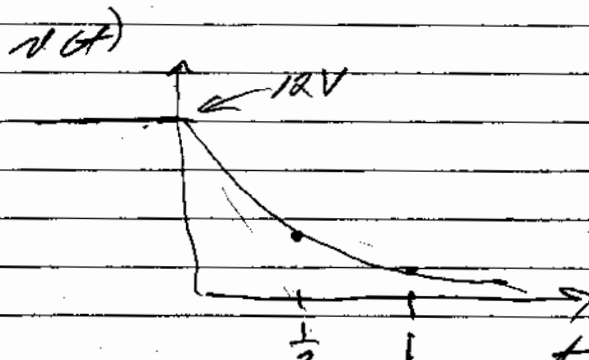

(in seconds)


ES 332

Homework 7

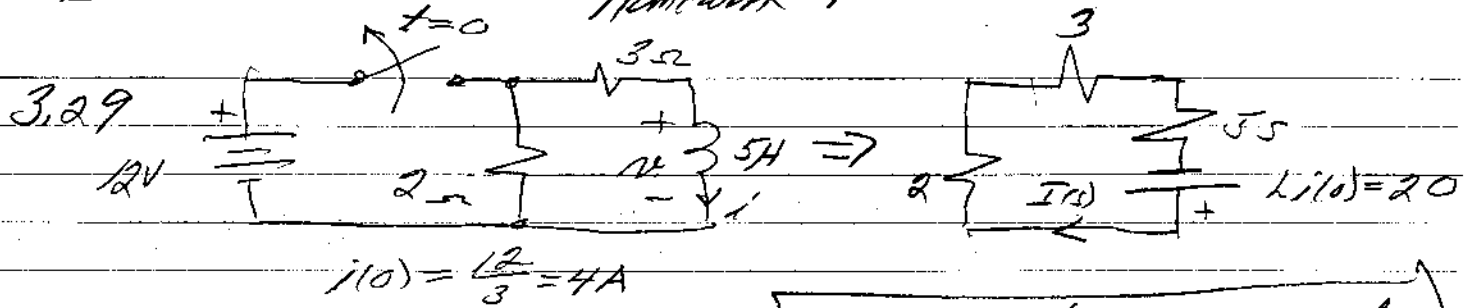

$$\therefore I(s)[5 + 5s] = 20 \quad \text{or} \quad \boxed{I(s) = \frac{4}{s+1}; i(t) = 4e^{-t} \mu A}$$
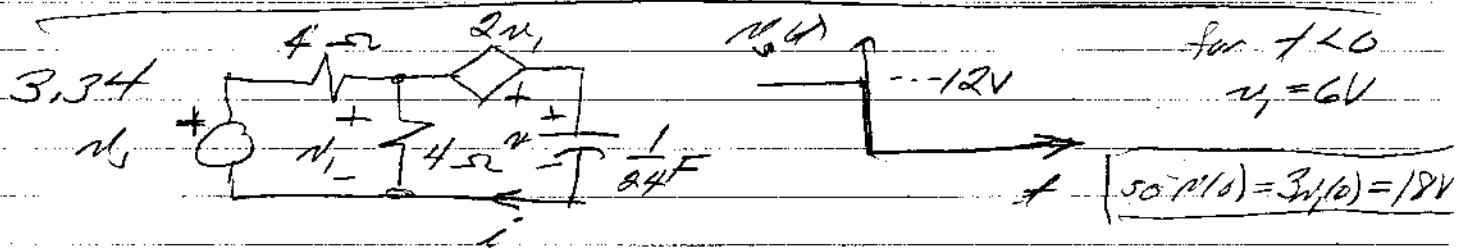
$$V(s) = I(s) \times 5s - 20 = \frac{20s}{s+1} - 20 = -\frac{20}{s+1}; \quad \boxed{v(t) = -20e^{-t} \mu A}$$



$$2I(s) - 2V_1 + \frac{24}{s} I + \frac{18}{s} = 0$$

$$I(s) \left\{ 2 + \frac{24}{s} \right\} = 2V_1 - \frac{18}{s}$$

but  $V_1 = -2I(s)$





$$\therefore I(s) \left\{ 2 + \frac{24}{s} + 4 \right\} = -\frac{18}{s}; \quad I(s) = \frac{-\frac{18}{s}}{6 + \frac{24}{s}} = \frac{-18}{6s + 24} = \frac{-3}{s+4}$$

$$\text{so } \boxed{i(t) = -3e^{-4t} \mu A}$$


$$V(s) = I(s) \times \frac{24}{s} + \frac{18}{s} = \frac{-72}{s(s+4)} + \frac{18}{s} = \frac{-18}{s} + \frac{18}{s+4} + \frac{18}{s}$$

$$v(t) = 18e^{-4t} \mu A$$

{ sketches on next page! }

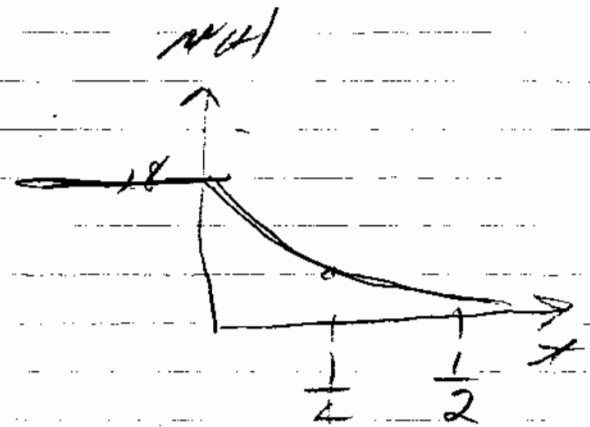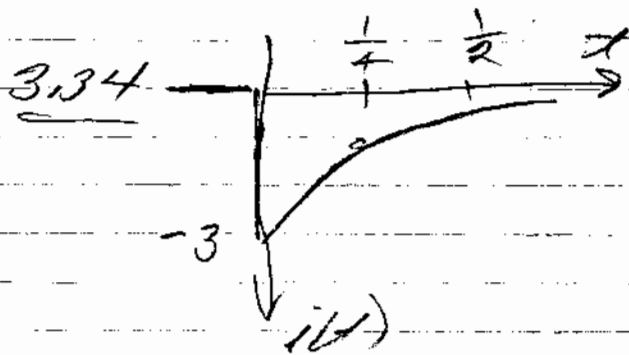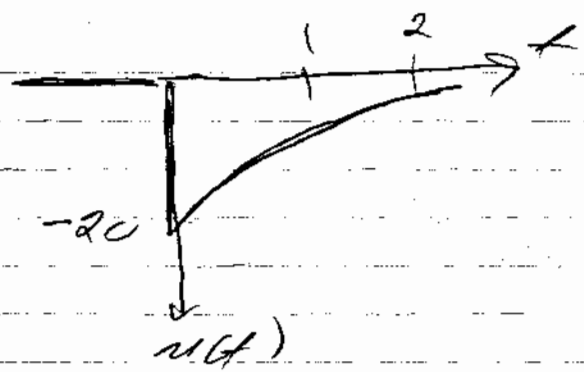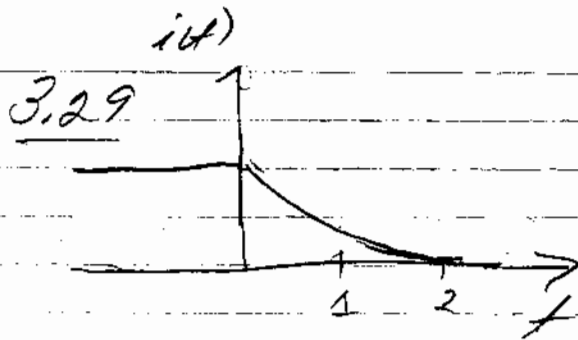



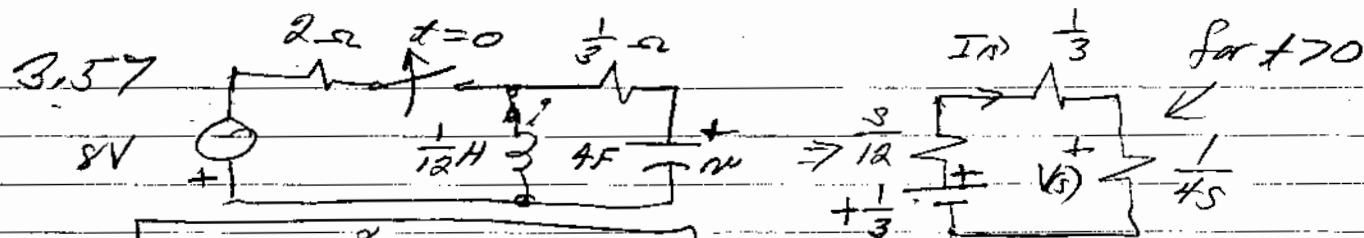


$$i(0) = +\frac{8}{2} = +4A; v(0) = 0$$

$$I(s) \left[ \frac{5}{12} + \frac{1}{3} + \frac{1}{45} \right] - \frac{1}{3} = 0; I(s) = \frac{45}{s^2 + 45 + 3} = \frac{45}{(s+1)(s+3)}$$

$$I(s) = \frac{-2}{s+1} + \frac{+6}{s+3}; i(t) = \left[ -2e^{-t} + 6e^{-3t} \right] u(t)$$
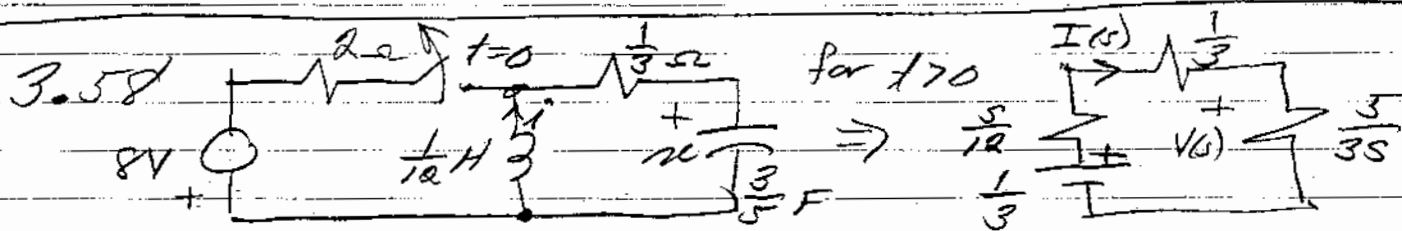
$$V(s) = I(s) \frac{1}{45} = \frac{1}{(s+1)(s+3)} = \frac{\frac{1}{2}}{s+1} + \frac{-\frac{1}{2}}{s+3}; v(t) = \frac{1}{2} \left[ e^{-t} - e^{-3t} \right] u(t)$$



$$i(0) = 4A; v(0) = 0$$

$$I(s) = \frac{\frac{1}{3}}{\frac{5}{12} + \frac{1}{3} + \frac{3}{35}} = \frac{45}{s^2 + 45 + 20} = \frac{4(s+2) - 8}{(s+2)^2 + 16}$$


$$\text{and } i(t) = \left[ 4e^{-2t} \cos 4t - 2e^{-2t} \sin 4t \right] u(t)$$

$$V(s) = I(s) \times \frac{3}{35} = \frac{20}{3} \cdot \frac{1}{s^2 + 45 + 20} = \frac{20}{3} \cdot \frac{1}{(s+2)^2 + 16}$$

$$v(t) = \left[ \frac{20}{3 \times 4} e^{-2t} \sin 4t \right] u(t)$$

$$v(t) = \left[ \frac{5}{3} e^{-2t} \sin 4t \right] u(t)$$

# Special problem

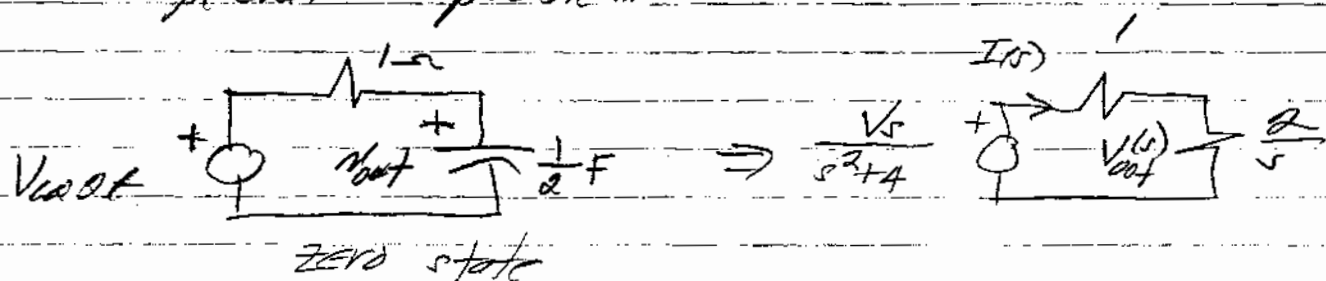

$$\frac{V_s}{s^2+4} = I(s) \left[ 1 + \frac{2}{s} \right] \quad \therefore I(s) = \frac{\frac{V_s}{s^2+4}}{\frac{s+2}{s}} = \frac{V_s s}{(s+2)(s^2+4)}$$

$$I(s) = \frac{K_1}{s+2} + \frac{K_2 s + K_3}{s^2+4} \quad ; K_1 = \frac{4V}{8} = \frac{V}{2}$$

$$\text{so } V_s s = \frac{V}{2} (s^2+4) + (K_2 s + K_3)(s+2)$$

$$s^2 \text{ terms} \quad V = \frac{V}{2} + K_2 \quad \text{or } K_2 = \frac{V}{2}$$

$$s \text{ terms} \quad 0 = 2K_2 + K_3 \quad \text{or } K_3 = -2K_2 = -V$$

$$I(s) = \frac{V/2}{s+2} + \frac{V/2 s - V}{s^2+4}$$

$$i(t) = \left[ \frac{V}{2} e^{-2t} + \frac{V}{2} \cos 2t - \frac{V}{2} \sin 2t \right] u(t) \quad \leftarrow$$

$$V_{out}(s) = I(s) \frac{2}{s} = \frac{2sV}{(s+2)(s^2+4)} = \frac{A}{s+2} + \frac{Bs+C}{s^2+4}$$

$$A = \frac{-4V}{8} = -\frac{V}{2}$$

$$2sV = -\frac{V}{2}(s^2+4) + (Bs+C)(s+2)$$

$$s^2 \text{ terms} \quad 0 = -\frac{V}{2} + B \quad \therefore B = \frac{V}{2}$$


$$s \text{ terms} \quad 2V = C + 2B = C + V \quad \therefore C = V$$

$$\text{and } V_{out}(s) = \frac{-V/2}{s+2} + \frac{V/2 s + V}{s^2+4}$$

$$v_{out}(t) = \left[ -\frac{V}{2} e^{-2t} + \frac{V}{2} \cos 2t + \frac{V}{2} \sin 2t \right] u(t) \quad \leftarrow$$
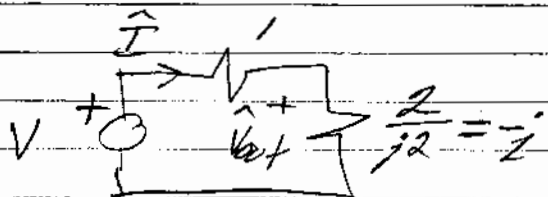
# Homework 9

Sinusoidal steady state solution to special prob.



$$\hat{I} = \frac{V}{1-j} = \frac{V}{\sqrt{2}} e^{j45^\circ}$$

$$i(t) = \text{Re}\{\hat{I} e^{j2t}\} = \frac{V}{\sqrt{2}} \cos(2t + 45^\circ)$$

$$\hat{V}_{out} = -j \hat{I} = e^{-j90^\circ} \frac{V}{\sqrt{2}} e^{j45^\circ}$$

$$\text{so } v_{out}(t) = \frac{V}{\sqrt{2}} \cos(2t - 45^\circ)$$