

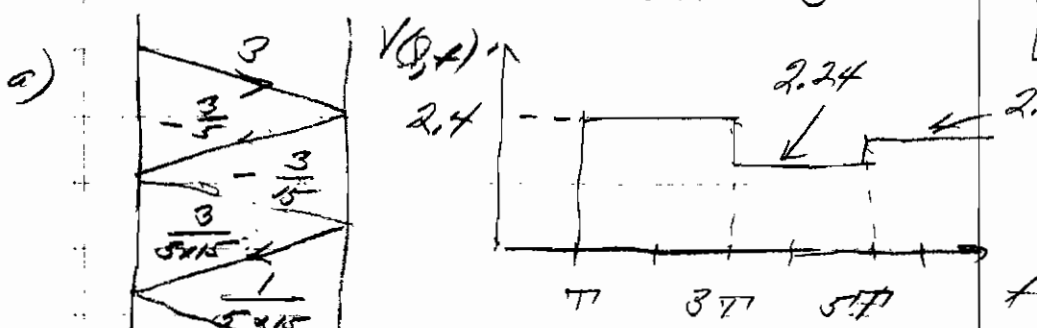
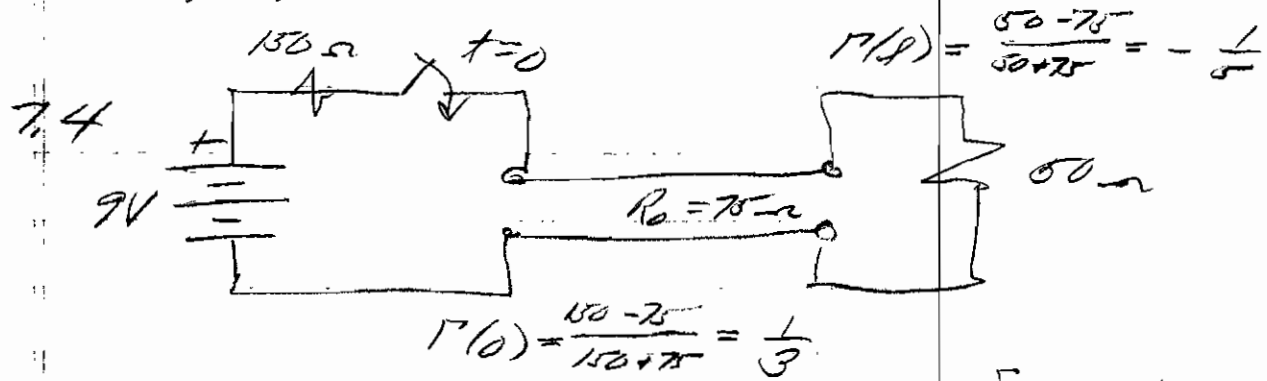


EE 434 Homework 1

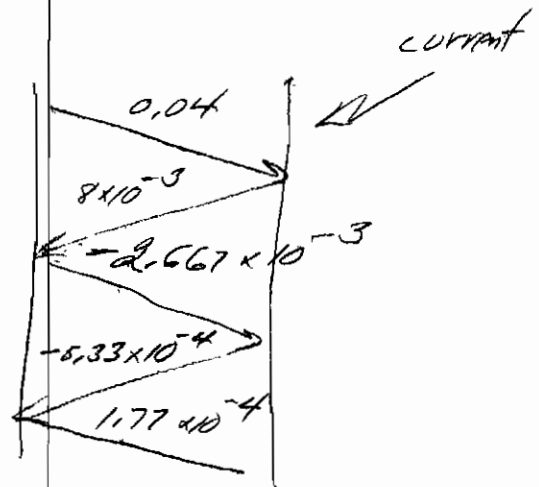

[τ = transit time $\frac{d}{u}$]

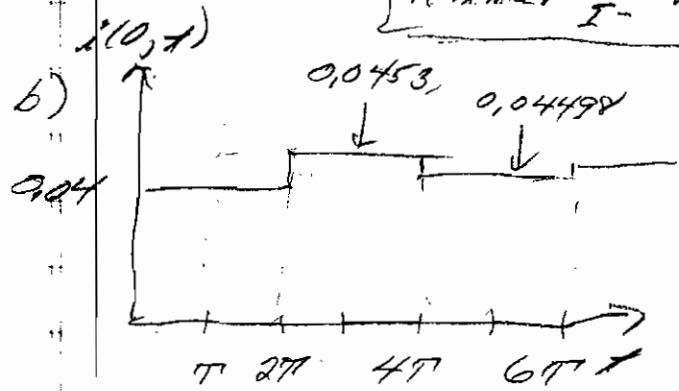
remember $\frac{V^+}{I^-} = R_0 = -\frac{V^-}{I^+}$



c) $N_{final} = 9 \frac{50}{200} = 2.25 \text{ VOLTS}$

$I_{final} = \frac{N_{final}}{50} = 0.045 \text{ Amperes}$

Q.54 from handout

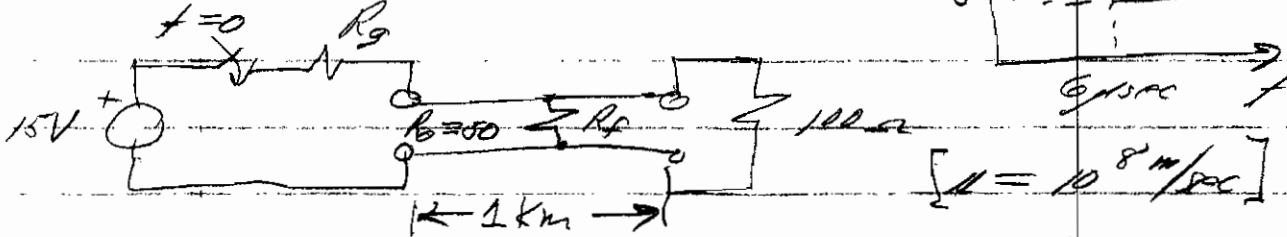

$$\text{Transit time} = \frac{1 \times 10^3}{10^8} = 10^{-5} = 10 \mu\text{sec}$$

Since the transit time is 10 μsec the reduction in $V(t)$ at 6 μsec is due to reflection from R_L not the 100 Ω load

a) $5 = 15 \frac{R_0}{R_0 + R_g}$ or $\frac{1}{3} = \frac{50}{50 + R_g}$; $R_g = 100 \Omega$


b) Reflection from load will not be seen for 20 μsec or 20 μsec .

c) At R_L the initial positive going wave sees a resistance of $\frac{R_L 50}{R_L + 50} = R_{eq}$

$$\Gamma(z=0) = \frac{100 - 50}{150} = \frac{1}{3}$$

To obtain waveform given

$$3 = 5(1 + \Gamma + \frac{\Gamma}{3})$$

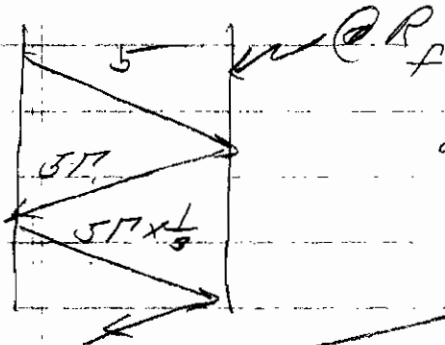


$$\therefore \Gamma = \frac{3 - 5}{5 + \frac{5}{3}} = \frac{3(-2)}{20} = -\frac{3}{10}$$

$$\text{but } \Gamma_{R_L} = \frac{R_{eq} - 50}{R_{eq} + 50}; R_{eq} = \frac{50 - 15}{1 + \frac{1}{3}} = \frac{350}{13} = 26.923 \Omega$$


from above, $R_L 50 = R_{eq} (R_L + 50)$

$$R_L = 58.33 \Omega$$

EE 434 Homework 2

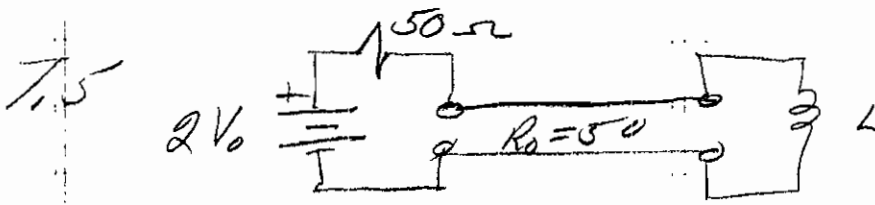
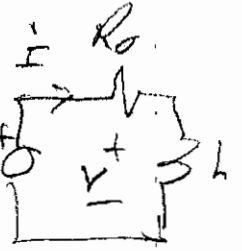
$$V_{load}^+ = V_0 \left(1 - \frac{t}{\tau}\right) \quad \therefore \text{load circuit is: } 2V_0 \left(1 - \frac{t}{\tau}\right)$$



$$\text{so } 2V_0 - IR_0 - L \frac{dI}{dt'} = 0 \quad \text{where } t' = t - \frac{L}{R_0}$$

$$I_{\text{homogeneous}} = K e^{bt} \quad \therefore R_0 K e^{bt} + L b K e^{bt} = 0 \Rightarrow b = -\frac{R_0}{L}$$




$$I_{\text{particular}} = K' \Rightarrow 2V_0 - K'R_0 = 0 \quad \text{or } K' = \frac{2V_0}{R_0}$$

$$I = I_h + I_p = \frac{2V_0}{R_0} + K_2 e^{-\frac{R_0 t'}{L}} \quad \text{but } I(0) = 0$$




$$\therefore I = \frac{2V_0}{R_0} \left(1 - e^{-\frac{R_0 t'}{L}}\right) \mu\text{A}$$

$$V = L \frac{dI}{dt'} = 2V_0 e^{-\frac{R_0 t'}{L}} \mu\text{A} = V_{load}^+ + V_{load}^-$$
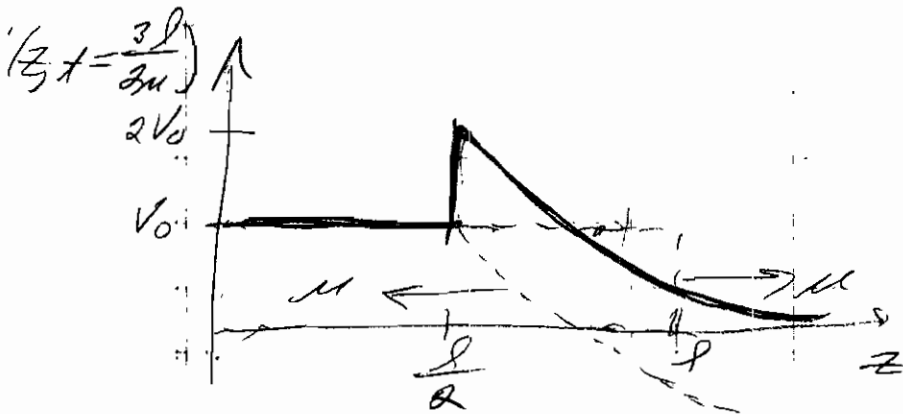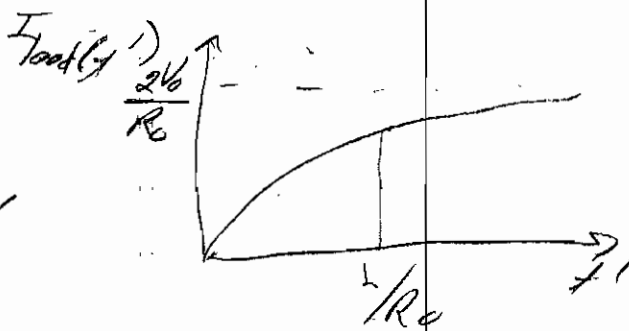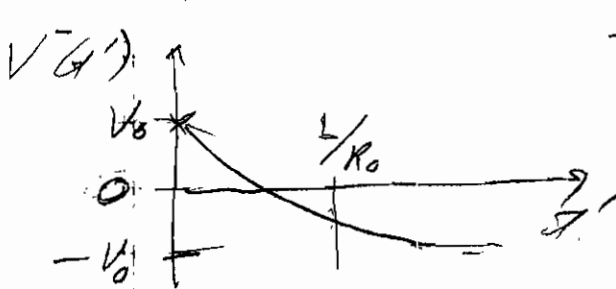
$$50V_{load}^- = \left[2V_0 e^{-\frac{R_0 t'}{L}} - V_0\right] \mu\text{A}$$



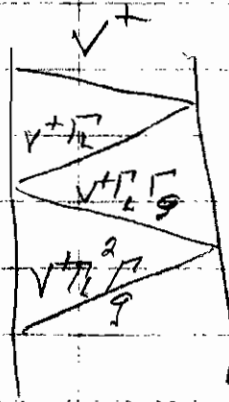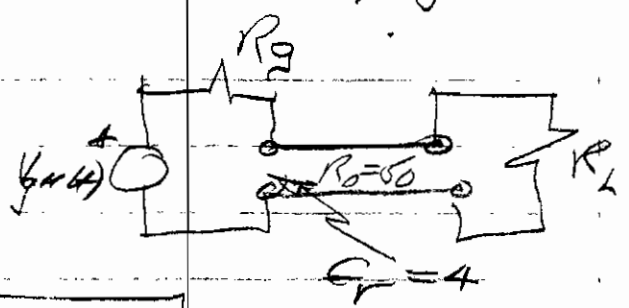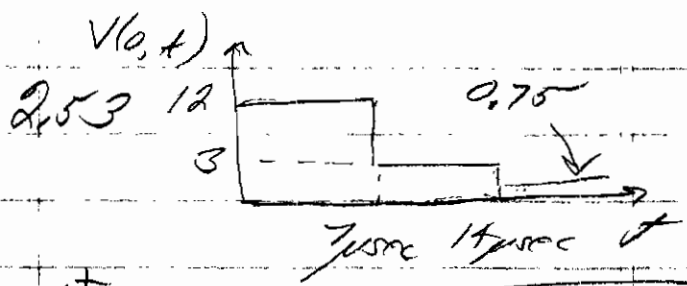Initially inductor looks like an open circuit $I = 0$
 After transients die out inductor looks like a short circuit



where $V^+ = V_g \frac{50}{50 + R_g} = 12$

From diagram we see that:

$$1) V^+ (\pi_L + \pi_L \pi_g) = -9$$

$$2) V^+ (\pi_L^2 \pi_g + \pi_L^2 \pi_g^2) = -\frac{9}{4}$$

$$\pi_L (1 + \pi_g) = -\frac{9}{12} = -\frac{3}{4}$$

$$\pi_L^2 \pi_g (1 + \pi_g) = -\frac{9}{16}$$

from 1) $\pi_L = -\frac{3}{4} \cdot \frac{1}{1 + \pi_g}$ substituting $\frac{9}{16} \frac{1}{(1 + \pi_g)^2} \pi_g$ into 2) $(\pi_g) = -\frac{3}{16}$


or $\frac{\pi_g}{1 + \pi_g} = -\frac{1}{3}$ giving $\pi_g = -\frac{1}{4}$

but $\pi_g = \frac{R_g - 50}{R_g + 50} \Rightarrow R_g = 50 \frac{1 + \pi_g}{1 - \pi_g} = 50 \frac{\frac{3}{4}}{\frac{5}{4}} = 30 \Omega$

so $V_g = 12 \frac{50 + 30}{50} = 19.2 \text{ Volts}$

Transit time = $\frac{7}{2} \mu\text{sec}$ and for $C_g = 4 \mu\text{F} = \frac{3 \times 10^{-8}}{2}$

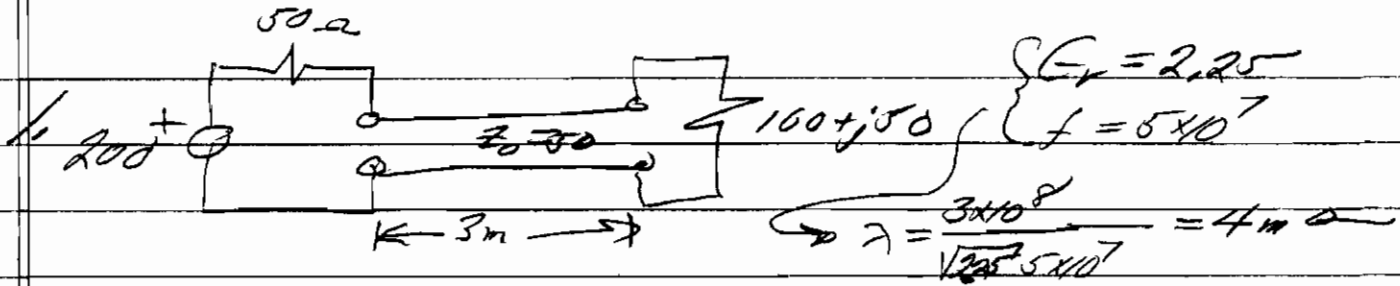so line length = $\frac{3 \times 10^8}{2} \times \frac{7}{2} \times 10^{-6} = 525 \text{ m}$



∴ line length is $\frac{3}{4} \lambda$

$$a) \Gamma_{load} = \frac{100 + j50 - 50}{100 + j50 + 50} = \frac{50(1 + j)}{50(3 + j)} = \frac{\sqrt{2} e^{j45^\circ}}{\sqrt{10} e^{j18.43^\circ}} = 0.447 e^{j26.56^\circ}$$

$$\Gamma_{input} = \Gamma_{load} e^{-j2 \times \frac{3\lambda}{4} \times \frac{32}{\lambda}} = 0.447 e^{j26.56^\circ} e^{-j153.4^\circ} = 0.447 e^{-j126.84^\circ}$$

$$b) Z_{in} = Z_0 \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} = 50 \frac{0.6 - j0.2}{1.4 + j0.2} = 50 \frac{0.78 e^{-j18.43^\circ}}{1.44 e^{j8.13^\circ}} = 29.37 e^{-j26.56^\circ}$$

$$I_{in} = \frac{200}{50 + 29.37 e^{-j26.56^\circ}} = 2.829 e^{j8.13^\circ}$$

$$and P_{avg} = \frac{1}{2} |I_{in}|^2 R_{in} = \frac{1}{2} |2.829|^2 \times 50 = 80 \text{ Watts}$$

$$\frac{I_{load}}{I_{in}} = e^{-j\frac{2\pi}{\lambda} \times 3} \frac{1 - \Gamma_{load}}{1 - \Gamma_{in}} = e^{-j9.42} \frac{1 - 0.447 e^{j26.56^\circ}}{1 - 0.447 e^{-j126.84^\circ}}$$

$$or I_{load} = 2.829 e^{j8.13^\circ} \times j \times \frac{0.6 - j0.2}{1.4 + j0.2} = 2.829 e^{j8.13^\circ} \times j \times \frac{0.6324 e^{-j18.43^\circ}}{1.44 e^{j8.13^\circ}}$$

$$I_{load} = 1.2648 e^{j71.57^\circ}$$

$$and P_{avg, load} = \frac{1}{2} |I_{load}|^2 \times 100 = 80 \text{ Watts}$$

$$2. a) \Gamma_{load} = \Gamma_{in} = 0$$

$$b) Z_{in} = Z_0 = 50 \Omega \quad \therefore \boxed{I_{in} = \frac{200}{100} = 2A} \quad \ominus$$

$$P_{avg_{in}} = \frac{1}{2} \times 2^2 \times 50 = 100 \text{ Watts} \quad \ominus$$

$$c) \hat{I}_{load} = \hat{I}_{in} e^{j90^\circ} \left\{ \frac{1 - \Gamma_{load}}{1 + \Gamma_{in}} \right\} = 2 e^{j90^\circ} \quad \ominus$$

$$\text{and } P_{avg_{load}} = \frac{1}{2} \times 2^2 \times 50 = 100 \text{ Watts} \quad \ominus$$

3. Distortionless Line $RC = LG$ or $\frac{R}{L} = \frac{G}{C}$


$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = \sqrt{LC} \sqrt{\left(\frac{R}{L} + j\omega\right)\left(\frac{G}{C} + j\omega\right)} = \sqrt{LC} \left(\frac{R}{L} + j\omega\right)$$

$$\text{so } \alpha = \frac{R}{L} \sqrt{LC} = R \sqrt{\frac{C}{L}} = R \sqrt{\frac{G}{R}} = \sqrt{RG} \quad \ominus$$

From above

$$\beta = \omega \sqrt{LC} \quad \ominus$$
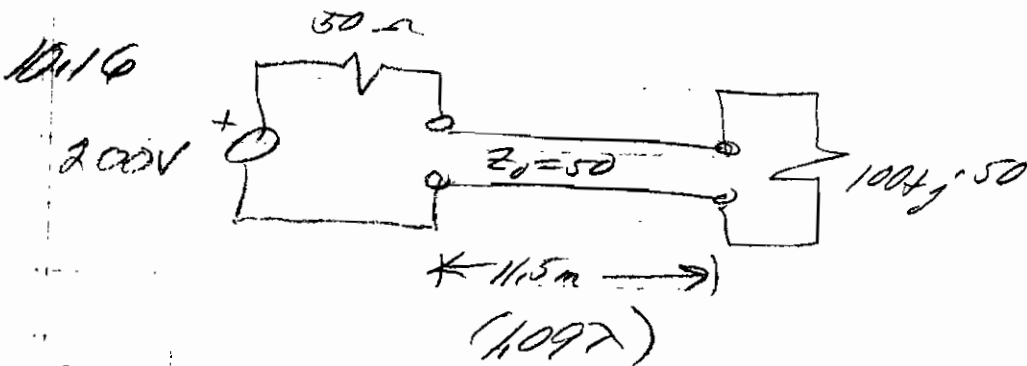
$$\boxed{Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L}{C}} \sqrt{\frac{R+j\omega L}{\frac{R}{L} + j\omega}} = \sqrt{\frac{L}{C}} \quad \ominus}$$



$$Z_{L, \text{norm}} = 2 + j$$

\Rightarrow From chart $\Gamma_{\text{load}} = 0.455 \angle 26.5^\circ$

rotating 1.092 toward generator $[0.2125 + 0.09 = 0.3025]$

gives $Z_{N, \text{norm}} = 1.16 - j1.13 \Rightarrow Z_{\text{in}} = 80 - j56.15 \Omega$

and $\Gamma_{\text{in}} = 0.455 \angle -139^\circ$

10.17 Same as 10.16 with $\alpha = 0.00197 \text{ Np/m}$

$$e^{-2\alpha l} = e^{-2 \times 1.9740 \times 11.5} = 0.956$$

\therefore @ input $|\Gamma| = 0.956 \times 0.455 = 0.435$

(rotation is not changed) so $Z_{\text{in, norm}} = 1.59 - j1.03 \Rightarrow Z_{\text{in}} = 79.5 - j61.5 \Omega$

10.21 $Z_{\text{norm, load}} = \frac{36 + j20}{50} = 0.72 + j0.4$

From chart $\Gamma_{L, \text{norm}} = 1.06 - j0.58$

$$\frac{1}{Z_{L, \text{norm}}} = \frac{1}{0.72 + j0.4} = \frac{1}{0.8237 \angle 89.105^\circ}$$

$$Z_{L, \text{norm}} = 1.06 - j0.59$$

IMPEDANCE OR ADMITTANCE COORDINATES

Problem 10.16
and 10.17
Load

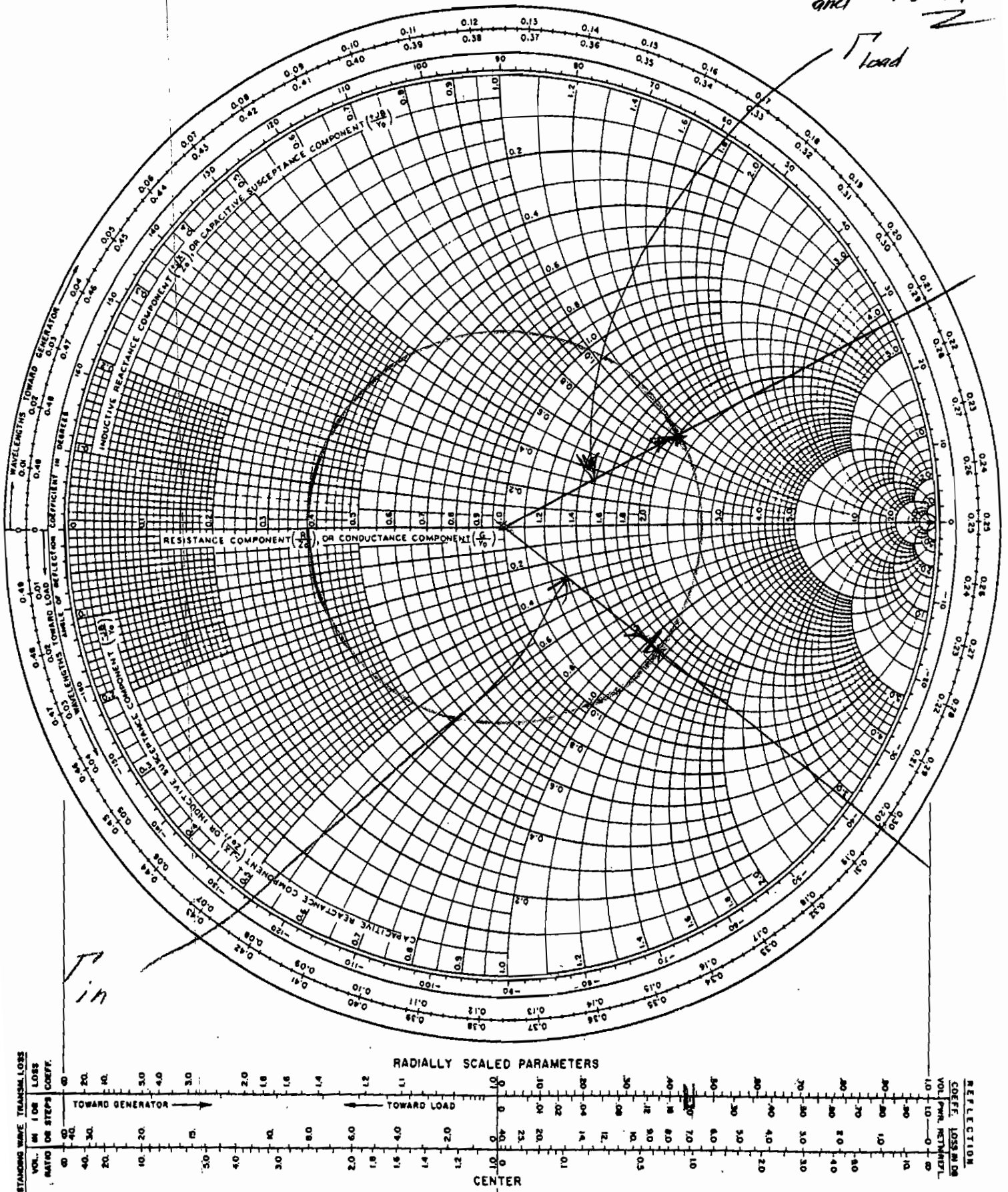


Fig. 9-3. A standard commercially available form of Smith chart graph paper. Copyrighted 1949 by Kay Electric Company, Pine Brook, N. J., and reprinted with their permission.

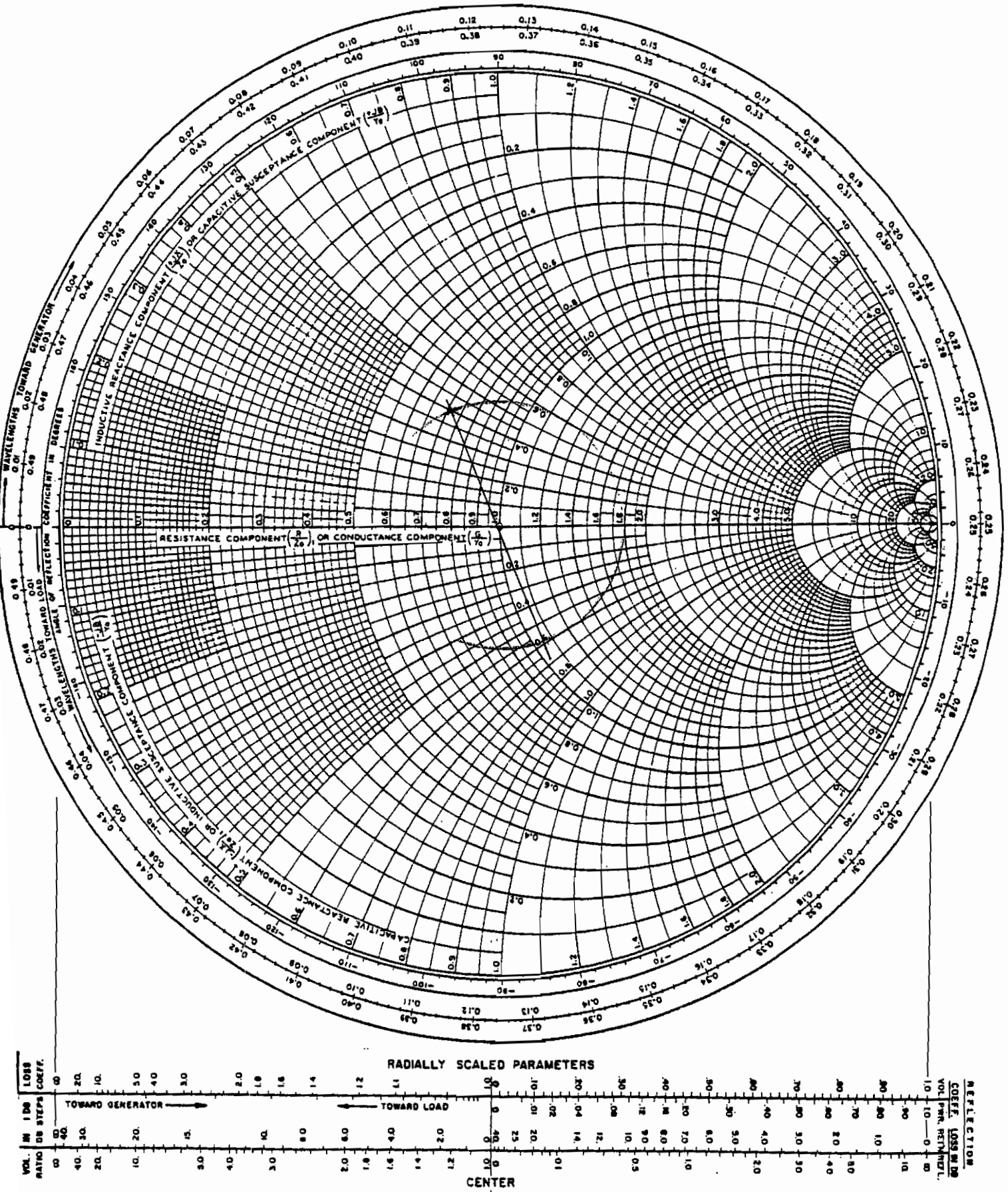


Fig. 9-3. A standard commercially available form of Smith chart graph paper. Copyrighted 1949 by Kay Electric Company, Pine Brook, N. J., and reprinted with their permission.

$$10.23 \quad Y_{A2} = G_2 + jB_2 ; Y_{in3} = G_3 + jB_3 ; I = \hat{V} Y$$

$$P_{avg} = \frac{1}{2} \operatorname{Re} \{ \hat{V} \hat{I}^* \} = \frac{1}{2} \operatorname{Re} \{ \hat{V} \hat{V}^* Y \} = \frac{1}{2} \operatorname{Re} \{ |\hat{V}|^2 (G + jB) \}$$

$$\text{or } P_{avg} = \frac{G |\hat{V}|^2}{2} ; |\hat{V}| \text{ the same for both lines}$$

$$\frac{P_{avg2}}{P_{avg3}} = \frac{G_2}{G_3} \quad \text{where } \begin{cases} G_2 = \frac{1.83}{50} = 0.0366 \\ G_3 = ? \end{cases}$$

$$Z_{in3} = \frac{36 + j20}{50} = 0.72 + j0.4$$

$$\text{from chart } Y_{in3} = 0.6 - j0.23 \text{ or } Y_{in3} = 0.012 - j0.0046$$

$$\text{so } G_3 \text{ for above is } 0.012$$

from
Example

$$Y_1(0) = \frac{0.39 + j0.47}{100} ; \text{ from Smith chart } Z_1(0) = 0.97 - j1.57$$

$$\therefore \hat{I}_{in} = \frac{100}{100 + j20(0.97 - j1.57)} = \frac{100}{167.9 - j109.9} = \frac{100}{200.67 \angle -38.2^\circ}$$

$$\text{so average power from source} = \frac{1}{2} |\hat{I}_{in}|^2 67.9 = 8.43 \text{ Watts}$$

$$\frac{1}{2} |\hat{V}_{in}|^2 (G_2 + G_3) = 8.43 = \frac{1}{2} |\hat{V}_{in}|^2 G_2 \left(1 + \frac{G_3}{G_2}\right) = P_{avg2} \left(1 + \frac{G_3}{G_2}\right)$$

$$\therefore P_{avg2} = \frac{8.43}{1 + \frac{G_3}{G_2}} = \frac{8.43}{1 + \frac{0.012}{0.0366}} = 6.34 \text{ Watts}$$


$$\text{and } P_{avg1} = 8.43 - 6.34 = 2.09 \text{ Watts}$$

IMPEDANCE OR ADMITTANCE COORDINATES

Problem 10.23

$Z_{L, norm}$

$Y_1(0)$
norm

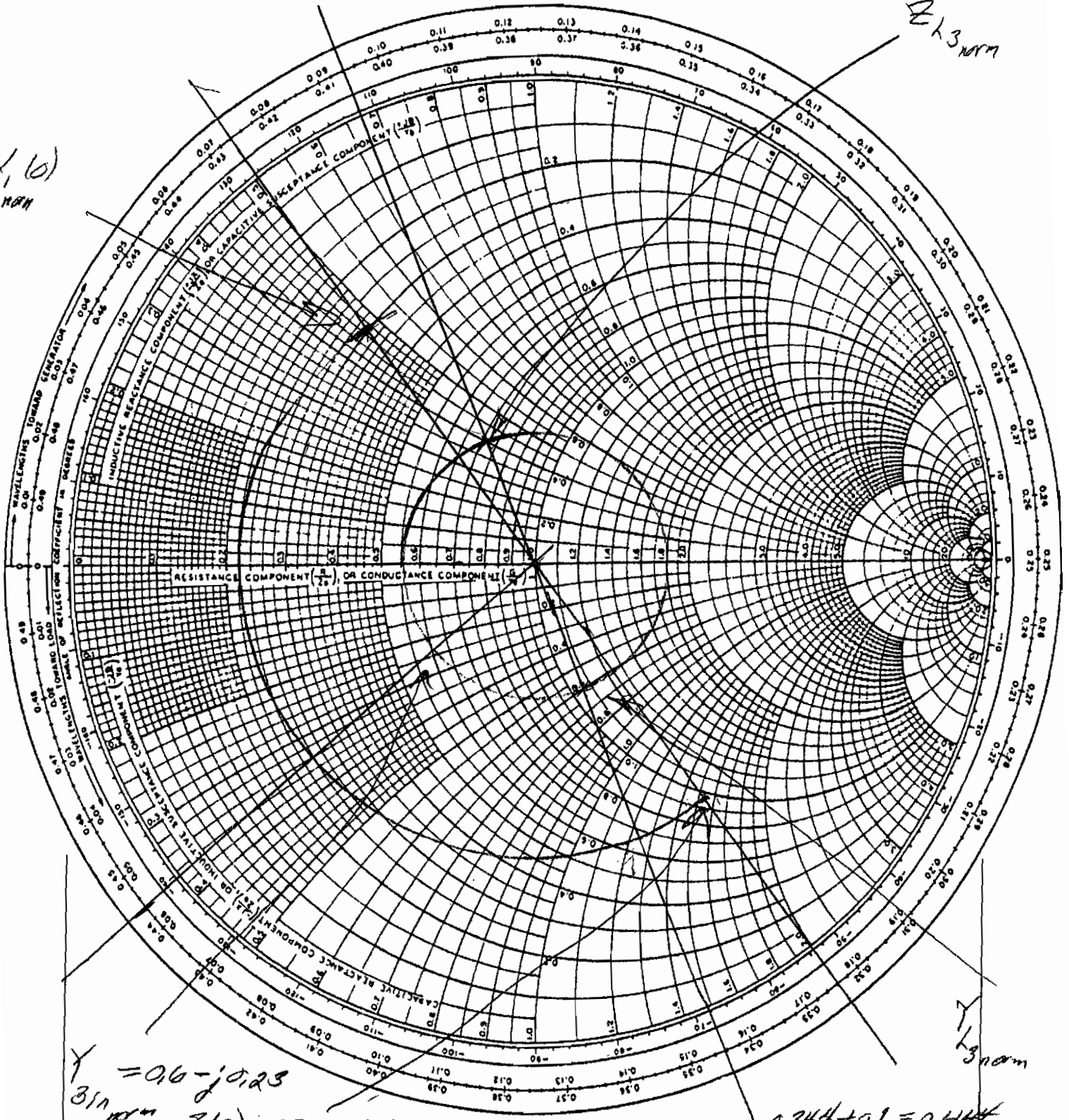

Y_2
norm

$Y = 0.6 - j0.25$
 $3/16$ norm
 $Z_1(0) = 0.97 - j1.57$

$0.344 + 0.1 = 0.444$

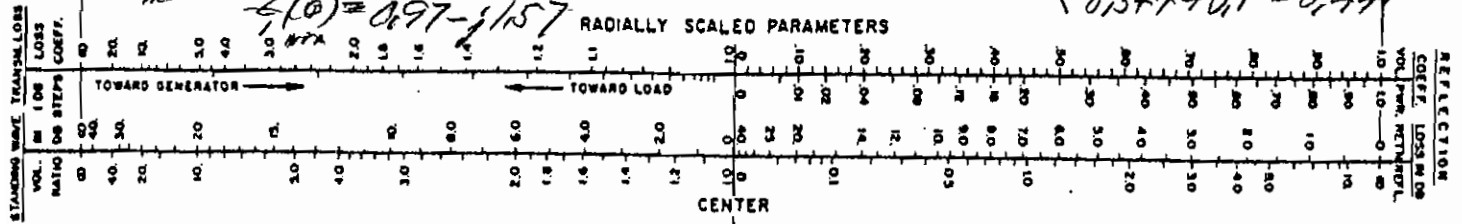


Fig. 9-3. A standard commercially available form of Smith chart graph paper. Copyrighted 1949 by Kay Electric Company, Pine Brook, N. J., and reprinted with their permission.

EE434



Homework 5

$$Z_{in} @ V_{min} = \frac{L}{VSWR} = 0.2857$$

$$VSWR = 3.5$$

$$f = 600 \text{ MHz}$$
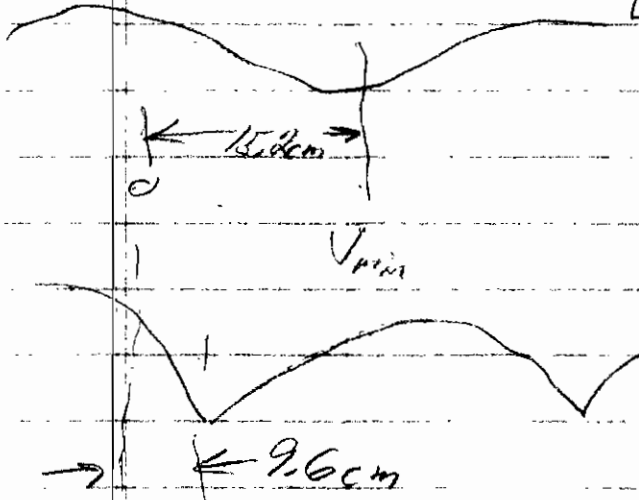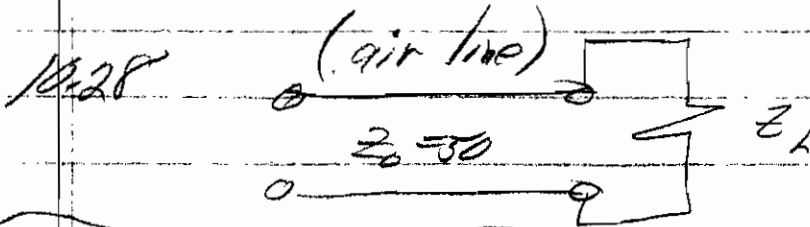
$$\lambda = \frac{3 \times 10^8}{6 \times 10^8} = 0.5 \text{ m} = 50 \text{ cm}$$




must move $(15.2 - 9.6) \text{ cm}$ from $Z_{norm} @ V_{min}$

to find $Z_{in} = 0.48 + j0.73$

5.6 cm = 0.112λ toward generator

$Z_{in} = 24 + j36.5$

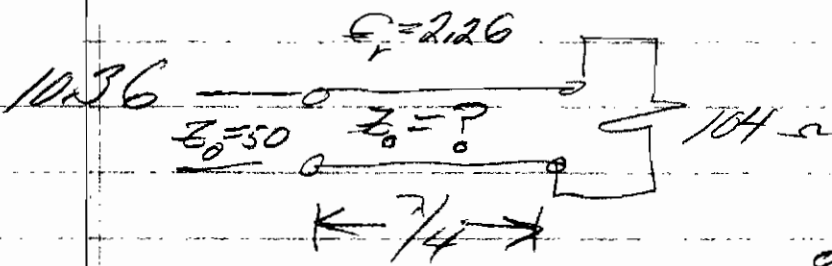

$f = 500 \text{ MHz}$

$$\lambda = \frac{3 \times 10^8}{\sqrt{2.26} \times 5 \times 10^8}$$

or $\lambda \approx 0.4 \text{ m}$


from above $\frac{7}{4} = 0.1 \text{ m}$

Z_0 of $\frac{7}{4}$ transformer = $\sqrt{50 \times 104} = 72.1 \Omega$

IMPEDANCE OR ADMITTANCE COORDINATES

$Z_{norm} = 0.484 + j0.73$

Problem 10.28

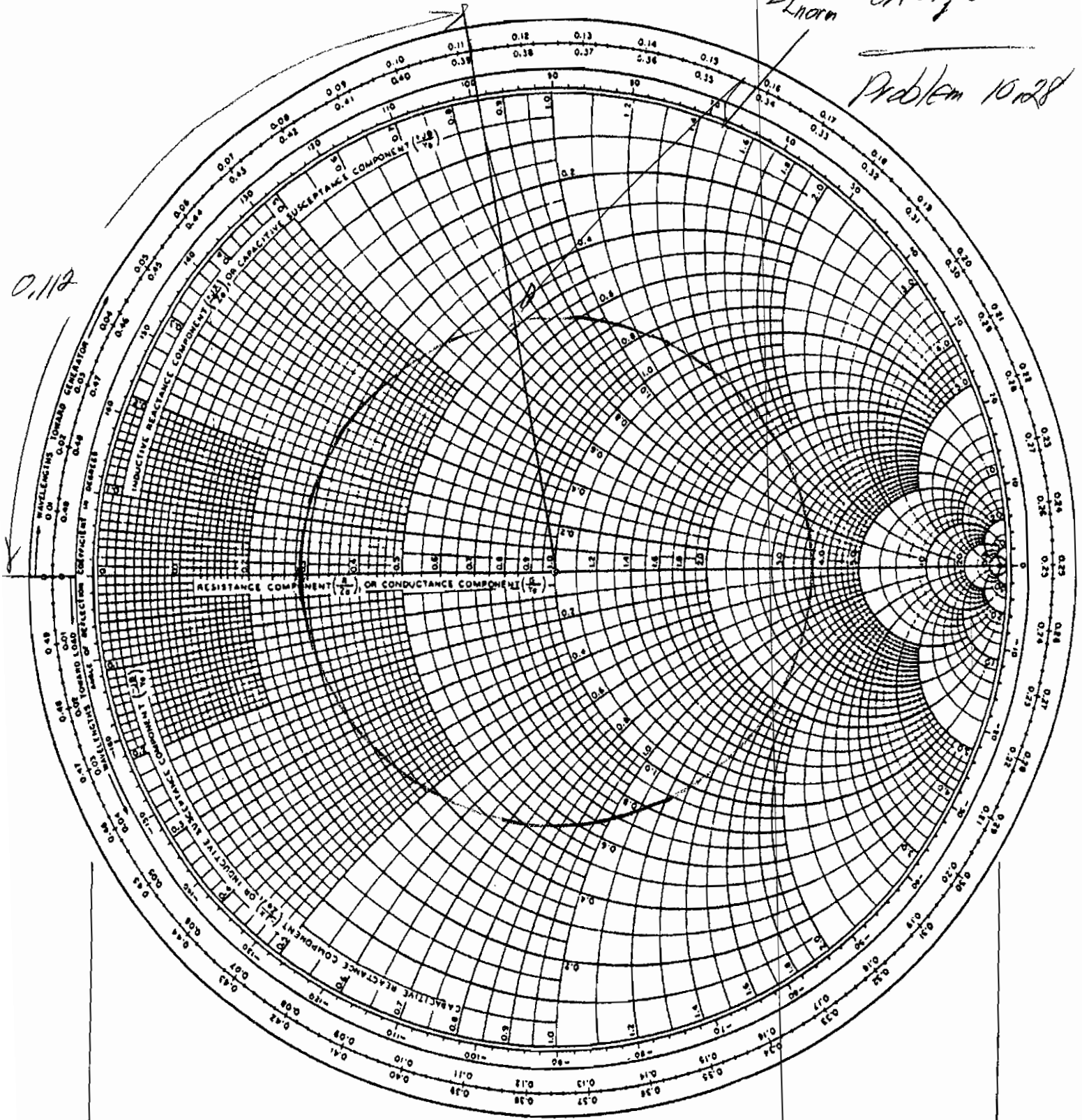

0.112

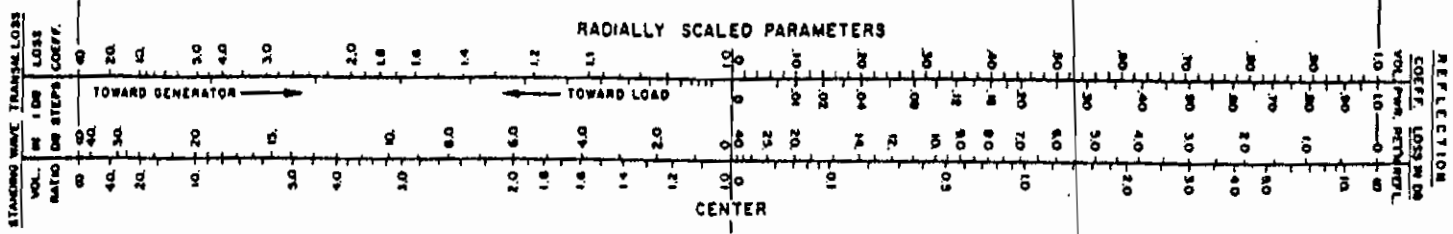


Fig. 9-3. A standard commercially available form of Smith chart graph paper. Copyrighted 1949 by Kay Electric Company, Pine Brook, N. J., and reprinted with their permission.

EE 434 Homework 6

1. a) rectangular tunnel 15m by 6m

$$\text{lowest } f_c = \frac{c}{2a} \sqrt{\left(\frac{\pi}{15}\right)^2} = \frac{3 \times 10^8}{30} = 10^7 \text{ Hertz}$$

b) Vertical polarization

c) AM 535 → 1605 KHz ∴ will not propagate

FM 88 → 108 MHz ∴ will propagate

8.11 TE₁₀ mode a = 2b

$$f_c = \frac{3 \times 10^8}{2a} \sqrt{\left(\frac{\pi}{a}\right)^2} = \frac{3 \times 10^8}{2a} \quad \text{next lowest cutoff frequency is twice this}$$

$$\text{Next } 1.5 f_c = 9 \times 10^7 = \frac{4.5 \times 10^8}{2a} \quad \text{or } a = \frac{4.5 \times 10^8}{18 \times 10^7} = 0.025 \text{ m}$$

$$\text{or } a = 2.5 \text{ cm}$$

8.18 $f = 1.3 f_c$ $E_{\text{max}} = 0.75 \times 2 \times 10^6 \text{ V/m}$

rectangular waveguide a = 2.3 cm, b = 1.2 cm

$$P_z = -\hat{E} \times \hat{H} = H_0^2 \frac{\omega \mu a^2 \beta_{10}}{\pi a} \sin^2\left(\frac{\pi x}{a}\right)$$

$$P_{\text{ave}} = \frac{1}{2} R_0 \int_0^b \int_0^a P_z \text{ only} = \frac{H_0^2 \omega \mu a^2 \beta_{10}}{4\pi a} \cdot b \cdot a$$


$$E_{\text{max}} = H_0 \frac{\omega \mu a}{\pi} \quad \therefore P_{\text{ave}} = \frac{E_{\text{max}}^2 \beta_{10} a b}{4 \omega \mu}$$

$$\text{or } P_{\text{ave}} = \frac{a b E_{\text{max}}^2}{4 \omega \mu} \omega \sqrt{\mu \epsilon} \sqrt{1 - \left(\frac{1}{1.3}\right)^2}$$

$$P_{\text{ave}} = E_{\text{max}}^2 \frac{a b \sqrt{1 - \left(\frac{1}{1.3}\right)^2}}{4 \eta_0} = E_{\text{max}}^2 1.169 \times 10^{-7}$$

$$\text{giving } P_{\text{ave max}} = 2.25 \times 10^{10} \times 1.169 \times 10^{-7} = 2.63 \times 10^6 \text{ Watts}$$


10.39

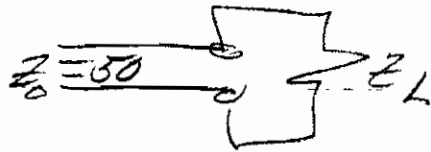

$$f = 560 \text{ MHz} ; \lambda = 60 \text{ cm}$$

$$\text{USWR} = 3.5$$

(see Smith chart)

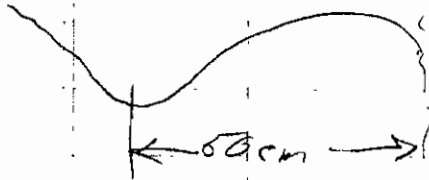

(place stub $(0.25 - 0.17)\lambda = 0.08\lambda = 4.8 \text{ cm}$
from V_{\min})

The stub can be placed 4.8 cm in either direction from V_{\min} because these positions are at $\Gamma_{\text{norm}} = 1 \pm j$.

a) For stub toward the load from V_{\min} $\Gamma_{\text{norm, stub}} = -j/3$
so stub length is $(0.355 - 0.25)\lambda = 0.105\lambda = 6.3 \text{ cm}$

b) USWR from generator to stub = 1 and from
stub to load USWR = 3.5
(USWR on stub = ∞)

c) For stub toward generator from V_{\min} $\Gamma_{\text{norm, stub}} = +j/3$
and stub length is 23.7 cm
{ $(0.25 + 0.145)\lambda = 0.395\lambda = 23.7 \text{ cm}$ }


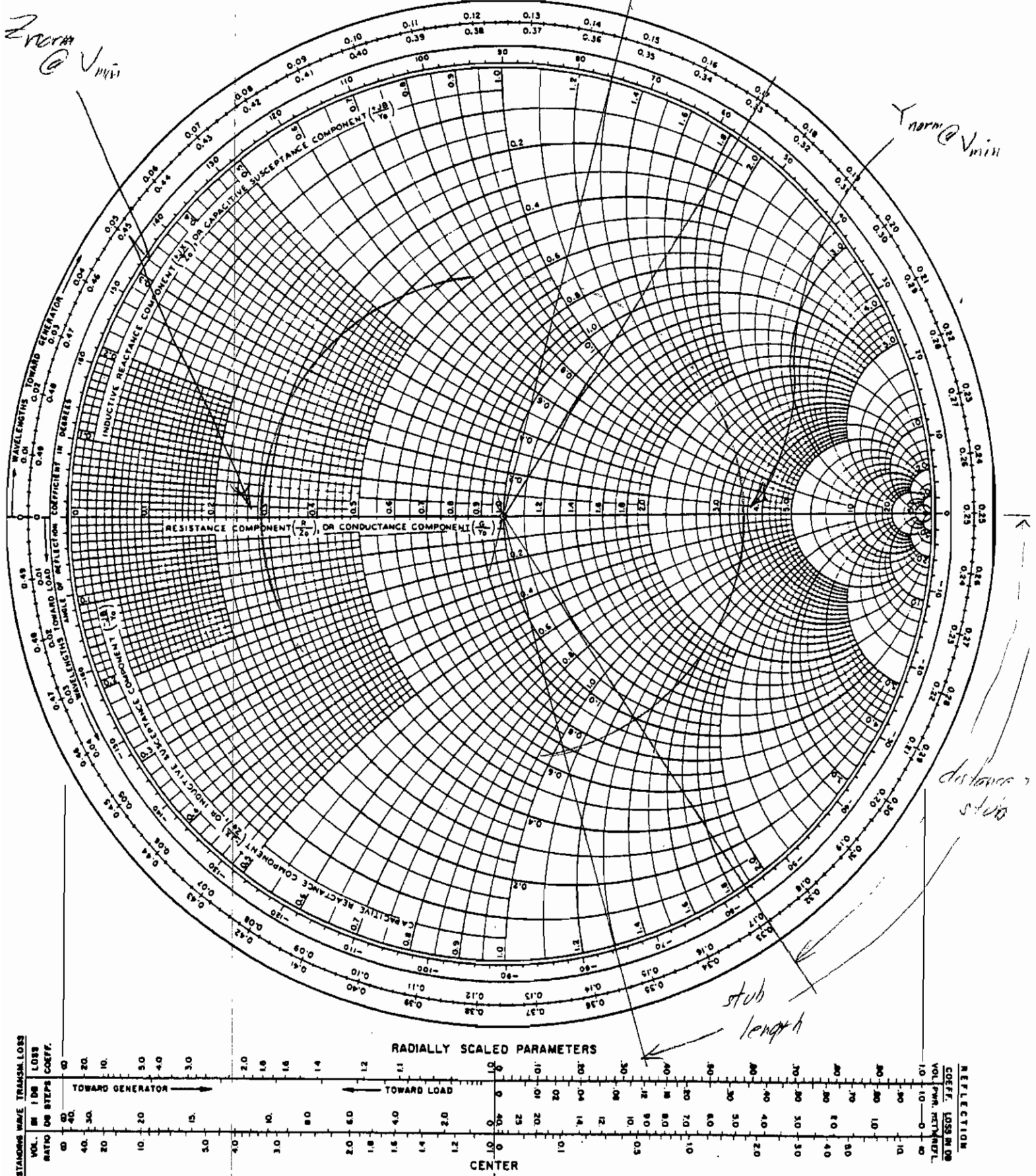


Fig. 9-3. A standard commercially available form of Smith chart graph paper. Copyrighted 1949 by Kay Electric Company, Pine Brook, N. J., and reprinted with their permission.

$$1. \beta = \sqrt{\omega^2 \mu \epsilon - \beta_z^2} = \omega \sqrt{\mu \epsilon} \sqrt{1 - \left(\frac{f_c}{f}\right)^2} \therefore \beta = \omega \sqrt{\mu \epsilon} \sqrt{1 - \left(\frac{f_c}{f}\right)^2}$$

$$v_{ph} = \frac{\omega}{\beta} = \frac{c}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}}; v_{group} = \frac{d\omega}{d\beta} = c \sqrt{1 - \left(\frac{f_c}{f}\right)^2}; f_c = 6.557 \text{ GHz}$$

f	v_{ph}	v_{group}
8.2 GHz	5×10^8	1.8×10^8
9 GHz	4.38×10^8	2.05×10^8
10 GHz	3.97×10^8	2.26×10^8
11 GHz	3.73×10^8	2.41×10^8
12.4 GHz	3.53×10^8	2.54×10^8

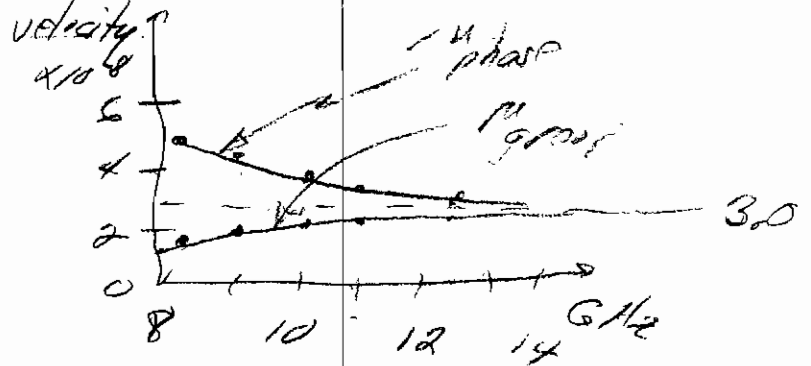

2. a) $\lambda = \frac{2\pi}{\beta} = \frac{2\pi \times 3 \times 10^8}{2\pi \times 10^8 \sqrt{1 - \left(\frac{6.557}{10}\right)^2}} = 3.97 \times 10^{-2} \text{ m}$

b) must use $v_{group} = 3 \times 10^8 \times 0.755 = 2.26 \times 10^8$
 ∴ transit time = $\frac{100}{2.26 \times 10^8} = 0.44 \text{ ns}$

c) change dielectric so that $f_c < 6 \text{ GHz}$

3. $f_c = \frac{3 \times 10^8}{2\pi} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$ $f_{c, TE_{10}} = 6.557$ (E field vertical)

for horizontal E field TE_{01} mode has the lowest cutoff frequency. Since $b < 2a$ cutoff frequency for TE_{01} mode is $> 2f_{c, TE_{10}}$ (i.e. $> 13 \text{ GHz}$)

Therefore horizontal portion of the circularly polarized wave will not propagate? Output would be linearly polarized

4. TE_{11} $f_c = \frac{3 \times 10^8}{2\pi} \left(\frac{\rho_{11}}{a}\right) = \frac{3 \times 10^8}{2\pi} \left(\frac{1.1841}{2.54 \times 10^{-2}}\right) = 3.46 \text{ GHz}$

TM_{01} $f_c = \frac{3 \times 10^8}{2\pi} \left(\frac{\rho_{01}}{a}\right) = \frac{3 \times 10^8}{2\pi} \left(\frac{2.405}{2.54 \times 10^{-2}}\right) = 4.52 \text{ GHz}$

TE_{01} $f_c = \frac{3 \times 10^8}{2\pi} \left(\frac{\rho_{01}}{a}\right) = \frac{3 \times 10^8}{2\pi} \left(\frac{3.832}{2.54 \times 10^{-2}}\right) = 7.2 \text{ GHz}$

9/ $d = 0.1m$, $I = 1$, $f = 10MHz$, $\therefore \lambda = \frac{3 \times 10^8}{10^7} = 30m$

a) $\theta = \frac{\pi}{2}$

$\theta_0 = \frac{\pi}{2}$ $\frac{\hat{E}}{e^{j\beta r}} = \frac{I \beta^2}{4\pi} \left\{ \frac{1 + 2j\beta r}{r^2} + j \left(\frac{\omega \mu}{r} - \frac{1}{\omega \epsilon r^3} \right) \right\} \frac{1}{\sin \theta} \hat{a}_\theta$; $\frac{\hat{H}}{e^{j\beta r}} = \frac{I \beta^2}{4\pi} \left(\frac{1}{r^2} + j \frac{\beta}{r} \right) \hat{a}_\phi$

i) $r = 1m$, $\frac{\hat{H}}{e^{j\beta r}} = \frac{I \beta^2}{4\pi} (1 + j\beta) \hat{a}_\phi$; $\beta = \frac{2\pi \times 10^7}{3 \times 10^8} = 2.094 \times 10^{-1}$
 or $\frac{\hat{H}}{e^{j\beta r}} = 7.958 \times 10^{-3} e^{j0.2094} (1.022 e^{j11.28^\circ}) \hat{a}_\phi$

$\frac{\hat{H}}{e^{j\beta r}} = 8.133 \times 10^{-3} e^{j0.1167^\circ} \hat{a}_\phi$ ← $0.058 e^{j16.4^\circ}$

ii) $r = 5m$, $\frac{\hat{H}}{e^{j\beta r}} = 7.958 \times 10^{-3} e^{-j0.5299} (0.04 + j0.042) \hat{a}_\phi$

$\frac{\hat{H}}{e^{j\beta r}} = 0.4616 \times 10^{-3} e^{-j13.59^\circ} \hat{a}_\phi$ ← $0.0232 e^{j64.47^\circ}$

iii) $r = 10m$, $\frac{\hat{H}}{e^{j\beta r}} = 7.958 \times 10^{-3} e^{-j1.0598} (0.01 + j0.02094) \hat{a}_\phi$

$\frac{\hat{H}}{e^{j\beta r}} = 0.11846 \times 10^{-3} e^{-j55.51^\circ} \hat{a}_\phi$ ←

b) our far zone criterion was $r \gg \frac{\lambda^2}{2\pi}$

$\frac{\lambda^2}{2\pi} = \frac{30}{2\pi} = 4.77m$

\therefore $r = 1m$ is in the near zone }
 $r = 5m$ is transitional } ←
 and $r = 10m$ is marginal for zone

c) see above 6

$$\begin{aligned}
 9.2 \overline{P}_{\text{ave}} &= \frac{1}{2} R_0 \left\{ \overline{E} \cdot \overline{H} \right\} = \frac{1}{2} R_0 \left\{ \overline{E}_0 / \hat{r}_r \parallel \hat{H}_\theta / \sin \theta \cos \left(-\frac{\beta}{r_a} + \frac{t}{r_b} \right) \right. \\
 &\quad \left. \times \left(-\frac{j\beta}{r} + \frac{1}{r_a} \right) + \overline{E}_0 \parallel \hat{H}_\theta / \sin^2 \theta \left(\frac{j\beta}{r} + \frac{\beta}{r_a} - \frac{1}{r_b} \right) \left(\frac{j\beta}{r} + \frac{1}{r_a} \right) \right\} \\
 &= \frac{1}{2} R_0 \left\{ \overline{E}_0 \parallel \hat{H}_\theta / \sin \theta \cos \left(\frac{j\beta}{r_b} - \frac{\beta}{r_a} + \frac{\beta}{r_b} + \frac{1}{r_b} \right) \right. \\
 &\quad \left. + \overline{E}_0 \parallel \hat{H}_\theta / \sin^2 \theta \left(\frac{\beta^3}{r_a} + \frac{j\beta^2}{r_b} - \frac{j\beta^2}{r_b} + \frac{\beta}{r_a} - \frac{\beta}{r_b} - \frac{1}{r_b} \right) \right\} \\
 &\quad \text{only real term!}
 \end{aligned}$$

$$\therefore \overline{P}_{\text{ave}} = \frac{1}{2} |E_0| |H_0| \sin^2 \theta \left(\frac{\beta^3}{r_a} \right) \overline{r}$$

from 9.14 and 9.15 $|E_0| = \frac{\eta I_0}{4\pi r}$, $|H_0| = \frac{I_0}{4\pi r}$

$$\therefore \overline{P}_{\text{ave}} = \frac{\eta}{2} \left(\frac{\beta I_0 \sin \theta}{4\pi r} \right)^2 \overline{r} \quad \text{which is equation 9.21}$$

9.5 (hard part) 2m linear antenna @ 1 MHz

$$\lambda = \frac{3 \times 10^8}{10^6} = 3 \times 10^2 \text{ m} \quad \therefore \text{short dipole}$$

for Cu $\sigma = 5.8 \times 10^7 \text{ gN/m}^2$ giving $\delta = \frac{1}{\sqrt{\pi \nu \mu_0 \sigma}} = 0.066 \times 10^{-3} \text{ m}$

because $\delta \ll$ radius of wire $R_{\text{loss}} = \frac{1}{2\pi a \sigma \delta} = 0.83 \times 10^{-1} \Omega$

$$P_{\text{rad}} = \frac{2\pi \eta}{3} \left(\frac{I}{r} \right)^2 = 0.0351 \text{ W}$$

$$\eta_{\text{eff}} = \frac{P_{\text{rad}}}{P_{\text{rad}} + R_{\text{loss}}} = \frac{0.0351}{0.0351 + 0.083} = 0.297; \quad \boxed{29.7\%}$$

b) $G = \eta_{\text{eff}} D = 1.5 \times 0.297 = \boxed{0.445 \text{ or } -3.5 \text{ dB}}$

c) $P_{\text{rad}} = \frac{1}{2} I^2 R_{\text{rad}} = 20 \text{ watts}; \quad \boxed{I = 33.76 \text{ A}}$


$$P_{\text{from transmitter}} = \frac{P_{\text{rad}}}{\eta_{\text{eff}}} = \frac{20}{0.297} = \boxed{67.34 \text{ Watts}}$$


9-14 (handout) $\lambda/2$ dipole; 100 MHz $\Rightarrow \lambda = \frac{3 \times 10^8}{10^8} = 3 \text{ m}$

$$A_{\text{eff}} = \frac{\lambda^2}{4\pi} \approx \frac{9 \times 1.64}{4\pi} = \boxed{1.17 \text{ m}^2}$$

$$\text{projected area} = 1.5 \times 10^{-2} = \boxed{0.015 \text{ m}^2}$$

9.3 $\vec{P} = K \frac{\sin\theta \cos\phi}{r^2} \hat{a}_r$ for $-\frac{\pi}{2} \leq \phi \leq \frac{\pi}{2}, 0 \leq \theta \leq \pi$

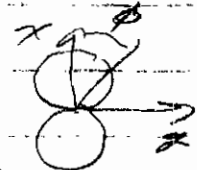a) azimuthal pattern = $K \cos\phi$  $\cos(\frac{\phi_{HP}}{2}) = \frac{1}{2}$
or $\phi_{HP} = 120^\circ$

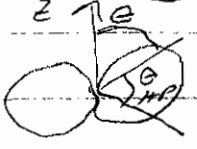equatorial pattern = $K \sin\theta$  $\frac{1}{2} \theta_{HP} = 90^\circ - \sin^{-1}(\frac{1}{2})$; $\theta_{HP} = 120^\circ$

b) ϕ_{BW} to first null = 180°
 θ_{BW} to first null = 180°

c) $P_{rad} = K \int_{\phi=-\frac{\pi}{2}}^{\frac{\pi}{2}} \int_{\theta=0}^{\pi} \frac{\sin\theta \cos\phi}{r^2} r^2 \sin\theta d\theta d\phi = K \int_{-\frac{\pi}{2}}^{\frac{\pi}{2}} \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^\pi d\phi$

$P_{rad} = 2K \frac{\pi}{2} = K\pi$; $\therefore D(\theta, \phi) = \frac{K \sin\theta \cos\phi \times 4\pi}{K\pi} = 4 \sin\theta \cos\phi$

and $D = D(\theta, \phi)_{max} = 4$

9.16 $\frac{1}{2}$ dipole, 50 MHz $\Rightarrow \lambda = \frac{3 \times 10^8}{5 \times 10^7} = 6m$

$G = 13dB = 19.95$ power ratio

so $P_r = P_t D_r D_t \left(\frac{\lambda}{4\pi r}\right)^2 = 10 \times 19.95 \times 1.64 \left(\frac{6}{4\pi \times 30 \times 10^3}\right)^2$

$P_r = 8.29 \times 10^{-6}$ Watts

9.18 $\left(\xleftarrow{2 \times 10^4} 20 \text{ km} \xrightarrow{\quad} \right)$

$$G_t = 20 \text{ dB} = 100$$

$$G_r = 23 \text{ dB} = 199.5$$

$$P_t = 10 \text{ W}, f = 6 \text{ GHz} \quad \lambda = \frac{3 \times 10^8}{6 \times 10^9} = 0.05 \text{ m}$$

a) $D_t = \frac{A_t}{\pi/4\pi r^2}$ or $D = \frac{P D_t}{4\pi r^2}$

$$\therefore P_t = \frac{10 \times 100}{4\pi \times 4 \times 10^8} = \frac{10^3}{16\pi \times 10^8} = 0.0199 \times 10^{-5} \text{ watts/m}$$

b) $P_r = P_t A_r = 1.99 \times 10^{-7} \times G_r \frac{\lambda^2}{4\pi} = 1.99 \times 10^{-7} \times 199.5 \times \frac{25 \times 10^{-4}}{4\pi}$


$$P_r = 789.59 \times 10^{-11} = 7.896 \times 10^{-9} \text{ Watts}$$

ck $P_r = P_t G_r G_t \left(\frac{\lambda}{4\pi r} \right)^2 = 10 \times 199.5 \times 100 \left(\frac{5 \times 10^{-2}}{4\pi \times 2 \times 10^4} \right)^2$

$$= 7.896 \times 10^{-9}$$

$$P_r = P_t A_r = P_t G_t \left(\frac{\lambda}{4\pi r} \right)^2 \left(\frac{\lambda^2}{4\pi} \right) G_r$$
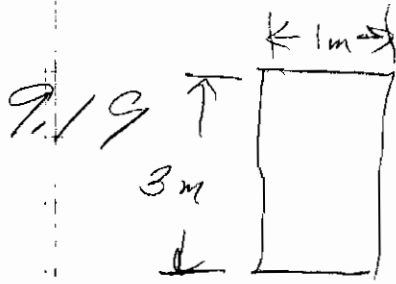
$$P_r = P_t G_t G_r \left(\frac{\lambda}{4\pi r} \right)^2$$



$f = 10 \text{ GHz}$ so $\lambda = \frac{3 \times 10^8}{10^{10}} = 3 \times 10^{-2} \text{ m}$

a) $\theta_{HP \text{ vertical}} \approx \frac{3 \times 10^{-2}}{3} = \sqrt{10^{-2}} = 0.57 \text{ radians} \approx 2^\circ$

$\theta_{HP \text{ horizontal}} = \frac{3 \times 10^{-2}}{1} = 3 \times 10^{-2} \text{ rad} = 1.72^\circ$

b) $D = \frac{4\pi}{\lambda^2} A_{eff} = \frac{4\pi \times 3}{9 \times 10^{-4}} = 4.19 \times 10^4 = 62.2 \text{ dB}$

9.20 $\theta_{HP} = 1.5^\circ$, $f = 20 \text{ GHz}$ so $\lambda = \frac{3 \times 10^8}{2 \times 10^{10}} = 1.5 \times 10^{-2} \text{ m}$

$\theta_{HP} = 0.026 \text{ radians}$

a) $D = \frac{4\pi}{\lambda^2} A_{eff}$ and $\theta_{HP} \approx \frac{\lambda}{\text{dia}}$ so $\text{dia} = \frac{\lambda}{\theta_{HP}} = 0.57 \text{ m}$

$A_{eff} = A_{actual} = \frac{\pi \text{dia}^2}{4} = 0.2578 \text{ m}^2$

and $D = \frac{4\pi \times 0.2578}{2.25 \times 10^{-4}} = 1.44 \times 10^4 = 41.58 \text{ dB}$

b) $D = K A_{eff}$ so $D_{new} \Rightarrow 2D_{old}$

$\theta_{HP} \approx \frac{\lambda}{\text{dia}}$ so $\theta_{HP \text{ new}} \Rightarrow \frac{\theta_{HP \text{ old}}}{\sqrt{2}}$

c) $f \Rightarrow 2f$ so $\lambda_{new} = \frac{\lambda_{old}}{2}$

so $\theta_{HP \text{ new}} = \frac{1}{2} \theta_{HP \text{ old}}$; $D_{new} = 4D_{old}$


9.21 94 GHz $\lambda = \frac{3 \times 10^8}{94 \times 10^9} = 0.0319 \times 10^{-1} \text{ m}$

a) $\theta_{HP \text{ azimuthal}} = \frac{\lambda}{1} = 3.19 \times 10^{-3} \text{ radians} = 0.18^\circ$

$\theta_{HP \text{ elevation}} = \frac{\lambda}{0.1} = 3.19 \times 10^{-2} \text{ radians} = 1.8^\circ$

b) 300 m $x = 300 \times 3.19 \times 10^{-3} = 0.957 \text{ m}$

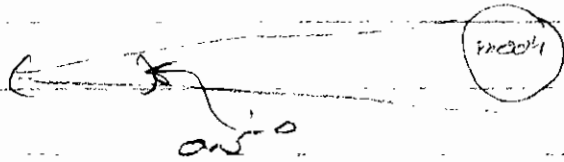9.22 100m parabolic dish, $f = 10.9 \text{ GHz}$



$$\theta_{\text{HP antenna}} \approx \frac{\lambda}{\text{dia}} = \frac{3 \times 10^8}{10^{10} \times 10^2} = 3 \times 10^{-4} \text{ radians}$$

distance to moon is $2.389 \times 10^5 \text{ miles} = 3.844 \times 10^5 \text{ km}$

$$\theta_{\text{HP antenna}} = 3 \times 10^{-4} \times \frac{180}{\pi} = 17.188 \times 10^{-4} \text{ degrees}$$

$$\frac{\text{diameter of area illuminated by antenna}}{\text{dia of moon}} = \frac{\theta_{\text{HP ant}} \times \text{distance}}{0.5 \times \frac{\pi}{180} \times \text{distance}}$$


$$= \frac{0.017188}{0.5} = 3.438 \times 10^{-2}$$

area goes as dia squared

so ratio of area illuminated to total area is:

$$(3.438 \times 10^{-2})^2 = 1.18 \times 10^{-3} = 0.118 \times 10^{-2}$$

(0.118% of moon is illuminated) ←

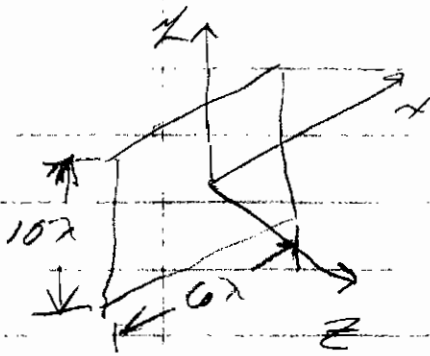

$\phi = 0$ pattern (i.e. xz plane)


$$E = \frac{j\beta E_m^+ ab(1 + \cos\theta) \sin^2 \frac{\beta a}{2} \sin(\frac{\beta a}{2} \sin\theta)}{4\pi r} \frac{1}{r^2}$$

i.e. $U = \frac{\beta a}{2} \sin\theta$

(aperture is 6λ wide in this plane)

so $\frac{\beta a}{2} = \frac{2\pi a}{\lambda} = \frac{2\pi \cdot 6\lambda}{\lambda} = 6\pi$ (which is the visible range) of U

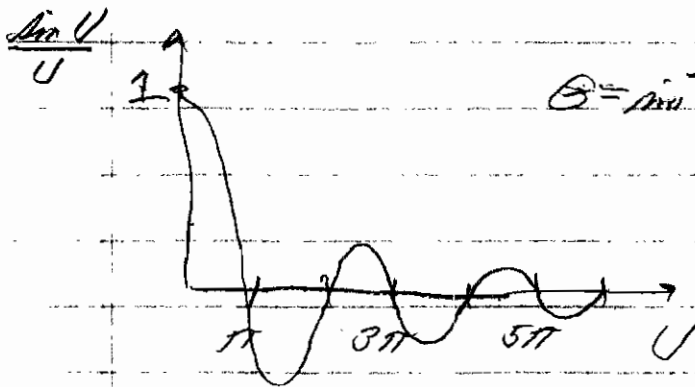
→ i.e. $0 < U < 6\pi$ for $0 < \theta < \frac{\pi}{2}$




$\theta = \sin^{-1}\left(\frac{U}{6\pi}\right)$ zeros of $\frac{\sin U}{U}$

U	θ
π	9.59°
2π	19.5°
3π	30.0°
4π	42.8°
5π	56.4°
6π	90°

Radiation pattern ($\phi = 0$)

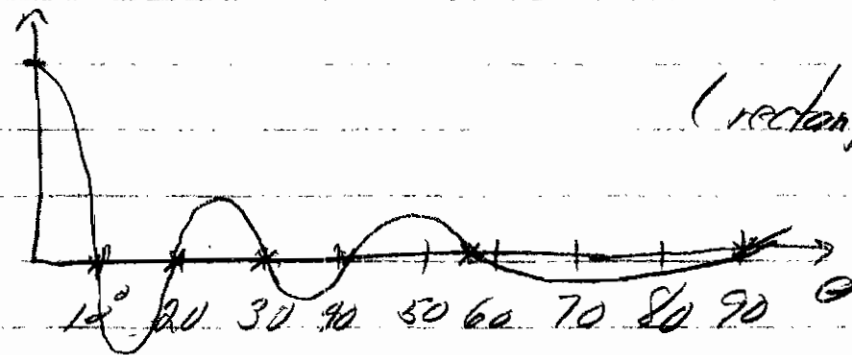


(rectangular plot)

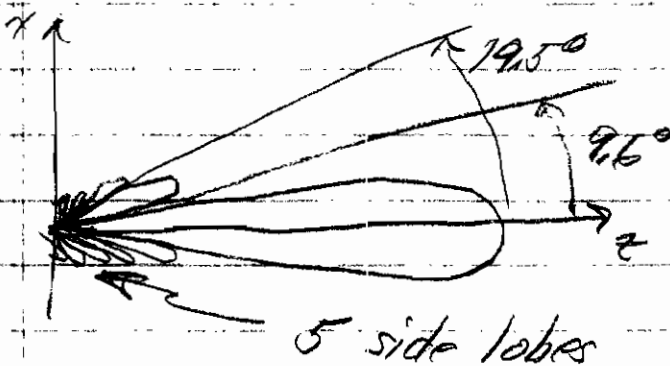

from table in hand out


$\theta_{HP} \approx \frac{50^\circ}{6} = 9.33^\circ$

first side lobe is down 13.2 dB

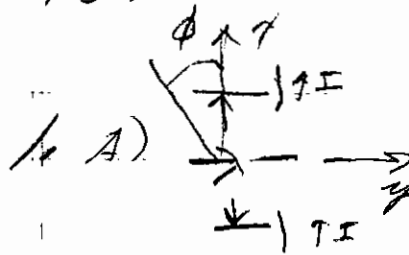

This is a 2 element array with $\psi=0, d=\lambda$

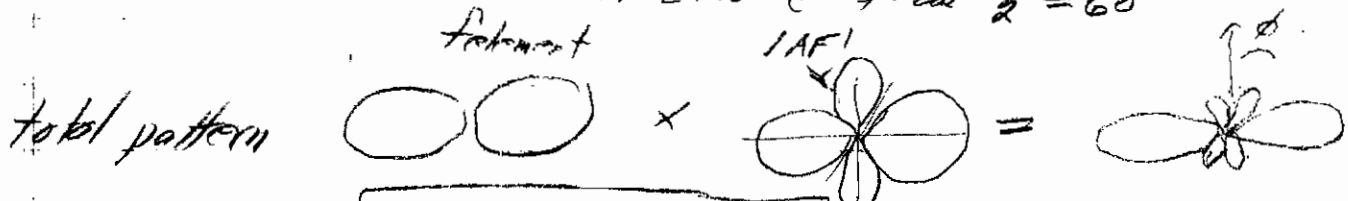So AF zeros @ $X = n\pi = 2\pi \cos\phi \Rightarrow \cos\phi = \frac{n}{2}$
 or zeros @ $\phi = \cos^{-1} \frac{n}{2} = 60^\circ$



zeros @ $\phi = \pm 60^\circ, 0^\circ, 180^\circ, \pm 120^\circ$

B) $\psi=0, d=4\lambda$ zeros @ $X = n\pi = \frac{2\pi \times 4\lambda \cos\phi}{\lambda}$
 or zeros @ $\cos\phi = \frac{n}{4}$


since $X_{zero} = n\pi$ only n odd produces zeros.
 i.e. $X=0, 2\pi, 4\pi \dots$ are maxima

or zeros @ $\phi = \pm 82.8^\circ, \pm 67.9^\circ, \pm 51.3^\circ, \pm 28.9^\circ$
 plus $\frac{1}{2}$ dipole zeros @ $\phi = 0^\circ$

There will also be zeros that are symmetrical to the above ... reflected about the $\frac{1}{2}$ plane

from text

9.9 1a

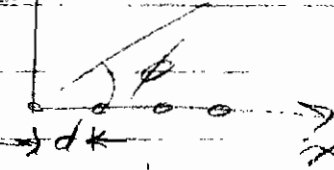a) $d = \frac{\lambda}{2}$, broadside so $\psi = 0$

$$\chi = \beta d \cos \phi$$

$$|AF| = \sum_{n=0}^3 e^{jn\beta d \cos \phi} = \sum_{n=0}^3 e^{jn \frac{2\pi d}{\lambda} \cos \phi}$$

[see attached plot]

b) $d = \frac{\lambda}{4}$, $\psi = \frac{\pi}{2}$


$$|AF| = \sum_{n=0}^3 e^{jn \left(\frac{2\pi d}{\lambda} \cos \phi - \frac{\pi}{2} \right)} = \sum_{n=0}^3 e^{jn \left(\frac{\pi}{2} \cos \phi - \frac{\pi}{2} \right)}$$

[see attached plot]

9.11 A desired uniform array, maximum @ $\phi = 45^\circ$
 (no part of 2nd main lobe present)

$$|AF| = \frac{\sin \frac{N\chi}{2}}{\sin \frac{\chi}{2}} \quad \chi = \frac{2\pi d}{\lambda} \cos \phi - \psi$$

maximum when $\chi = 0$ so $\psi = \frac{2\pi d}{\lambda} \cos 45^\circ = \frac{2\pi d}{\lambda} \frac{1}{\sqrt{2}} = \sqrt{2} \frac{\pi d}{\lambda}$

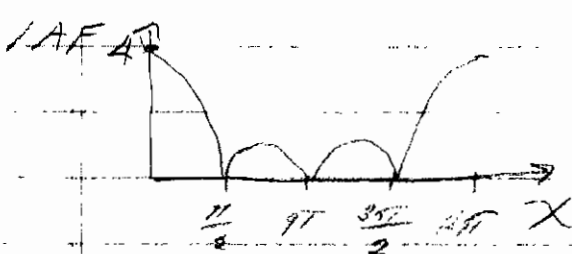for $N=4$; zeros of χ

$$\text{@ } \chi = \frac{n 2\pi}{4} = n \frac{\pi}{2}$$

for no part of 2nd main lobe in pattern

$$\beta d + \psi \leq \frac{3\pi}{2}, \quad \beta d \leq \frac{3\pi}{2} - \sqrt{2} \frac{\pi d}{\lambda}$$

$$\frac{2\pi d}{\lambda} + \sqrt{2} \frac{\pi d}{\lambda} \leq \frac{3\pi}{2} \quad \text{or} \quad \frac{d}{\lambda} \leq \frac{3/2}{2 + \sqrt{2}} = \frac{3}{4 + 2\sqrt{2}} = 0.439 <$$

$$\text{so } \psi = \sqrt{2} \frac{\pi d}{\lambda} = 1.9516 \leftarrow \text{[see attached plot]}$$


9.9a)

ANTENNA ARRAY RADIATION PATTERNS

The radiation pattern of a linear antenna array is given by the following:

$$N := 4 \quad d := \frac{1}{2} \quad \phi := 0 \quad ; \quad j := \sqrt{-1} \quad ; \quad \theta := 0, \frac{\pi}{100} .. 2 \cdot \pi \quad n := 0, 1 .. N - 1 \quad ; \quad F(\theta) := \left[\frac{1}{N} \cdot \sum_n e^{-j \cdot n \cdot (2 \cdot \pi \cdot d \cdot \cos(\theta) - \phi)} \right]^2$$

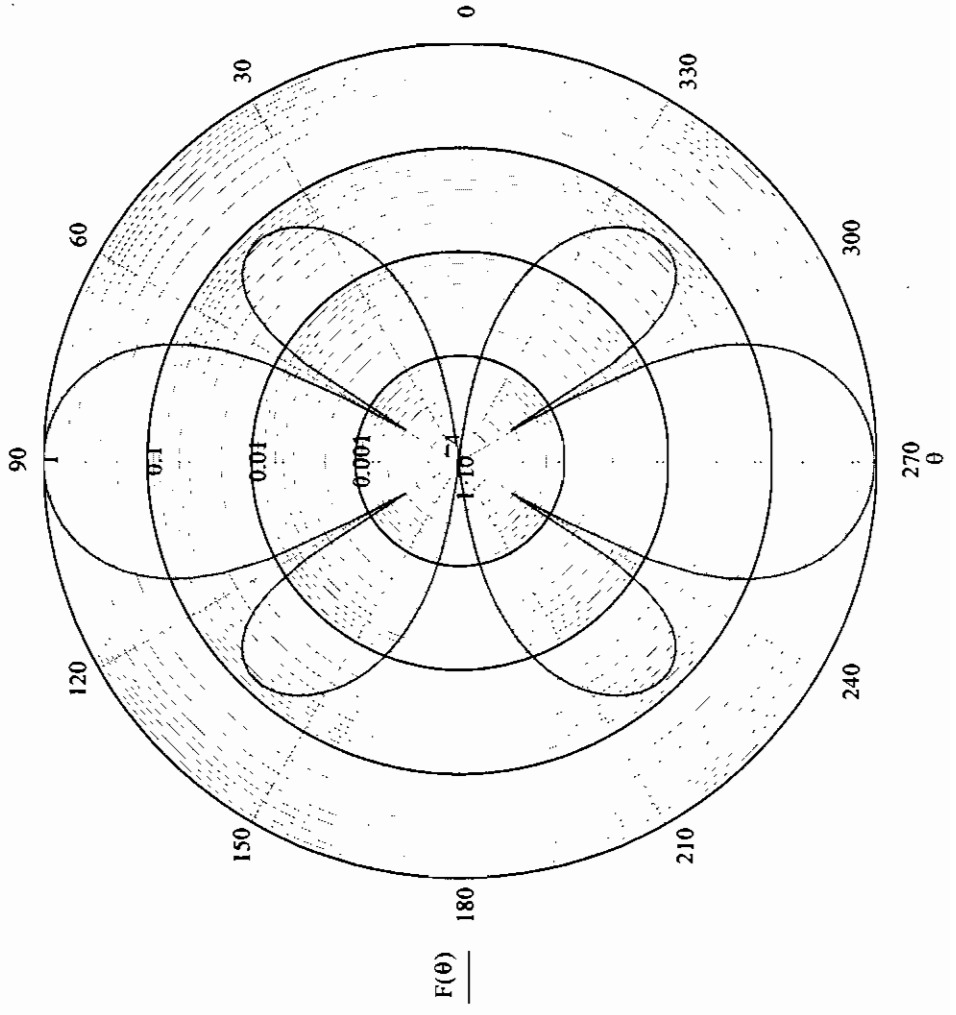Where "N" is the number of array elements, "φ" the progressive phase shift (element to element), and "d" the element spacing in wavelengths.




9.96)

ANTENNA ARRAY RADIATION PATTERNS

The radiation pattern of a linear antenna array is given by the following:

$$N := 4 \quad d := \frac{1}{4} \quad \phi := \frac{\pi}{2} \quad ; \quad j := \sqrt{-1} \quad ; \quad \theta := 0, \frac{\pi}{100} \dots 2 \cdot \pi \quad n := 0, 1 \dots N - 1 \quad ; \quad F(\theta) := \left[\frac{1}{N} \cdot \sum_n e^{-j \cdot n \cdot (2 \cdot \pi \cdot d \cdot \cos(\theta) - \phi)} \right]^2$$

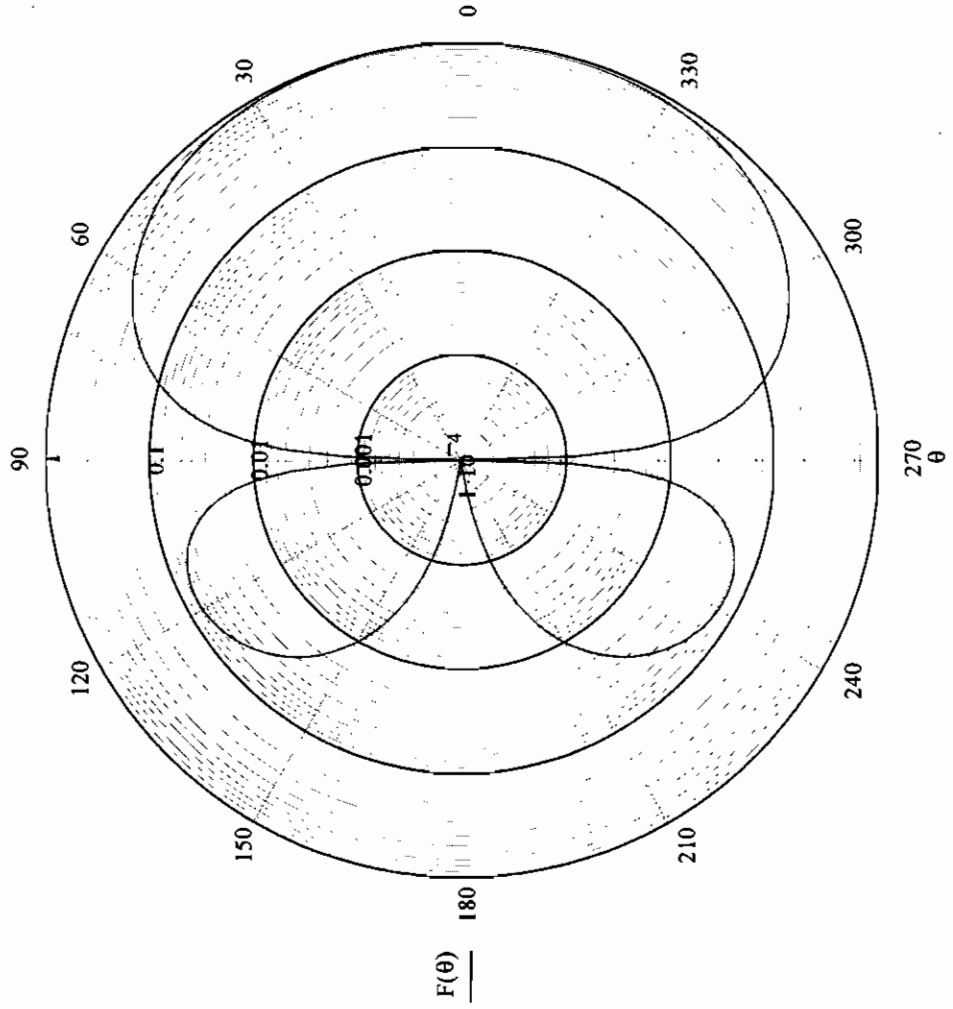Where "N" is the number of array elements, "φ" the progressive phase shift (element to element), and "d" the element spacing in wavelengths.



9.11

ANTENNA ARRAY RADIATION PATTERNS

The radiation pattern of a linear antenna array is given by the following:

$$N := 4 \quad d := 0.439 \quad \phi := 1.9516 \quad j := \sqrt{-1} \quad \theta := 0, \frac{\pi}{100} \dots 2 \cdot \pi \quad n := 0, 1 \dots N - 1; \quad F(\theta) := \left[\frac{1}{N} \cdot \sum_n e^{-j \cdot n \cdot (2 \cdot \pi \cdot d \cdot \cos(\theta) - \phi)} \right]^2$$

Where "N" is the number of array elements, "φ" the progressive phase shift (element to element), and "d" the element spacing in wavelengths.

