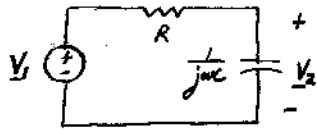


Problems 10.1, 10.4, 10.5, 10.7.

PRIO.1



$$V_2 = \frac{V_1 \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{V_1}{j\omega CR + 1} \Rightarrow H(j\omega) = \frac{V_2}{V_1} = \frac{1}{1 + j\omega CR}$$

\*amp. response:  $|H| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$

→ @  $\omega = 0$ :  $|H| = 1$  which is max

@  $\omega \rightarrow \infty$ :  $|H| \rightarrow 0$

@  $\omega = \omega_c$ :  $|H(j\omega_c)| = \frac{|H|_{max}}{\sqrt{2}} = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega_c^2 C^2 R^2}}$

$$\Rightarrow \frac{1}{2} = \frac{1}{1 + \omega_c^2 C^2 R^2}$$

$$\Rightarrow 1 + \omega_c^2 C^2 R^2 = 2$$

$$\Rightarrow \omega_c^2 = \frac{R^2}{C^2}$$

$$\Rightarrow \omega_c = \frac{1}{RC}$$



\*phase response:

$$\angle H = 0 - \tan^{-1}\left(\frac{\omega CR}{1}\right) = -\tan^{-1}(\omega CR)$$


→ @  $\omega = 0$ :  $\angle H = 0$

@  $\omega \rightarrow \infty$ :  $\angle H \rightarrow -90^\circ$

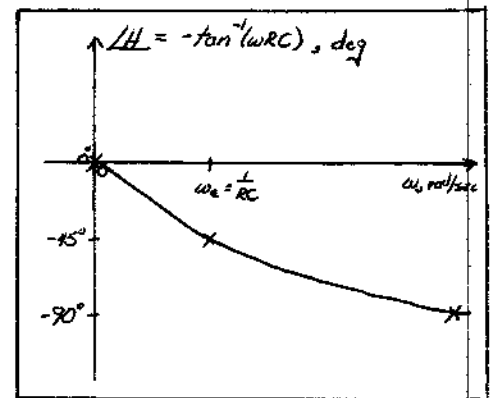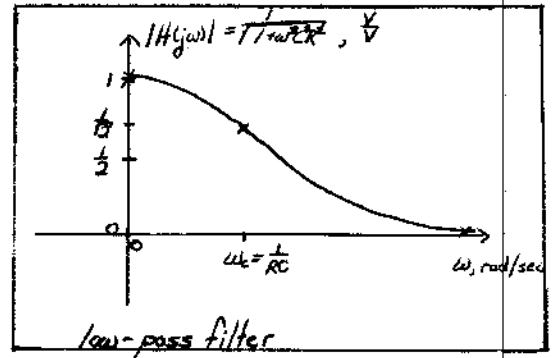@  $\omega = \omega_c = \frac{1}{RC}$ :  $\angle H = -\tan^{-1}\left(\left(\frac{1}{RC}\right)CR\right) = -45^\circ$



## PRIO.4

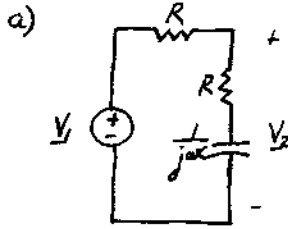

$$V_2 = \frac{V_1 (R + \frac{1}{j\omega C})}{R + R + \frac{1}{j\omega C}} = \frac{V_1 (j\omega CR + 1)}{j\omega C 2R + 1} \Rightarrow H(j\omega) = \frac{1 + j\omega CR}{1 + j\omega C 2R}$$

$$\Rightarrow |H| = \frac{\sqrt{1 + (\omega CR)^2}}{\sqrt{1 + (\omega C 2R)^2}}$$

$$\rightarrow \text{Find } |H|_{\text{max}}: \frac{d|H|^2}{d\omega} = \frac{d}{d\omega} \left( \frac{1 + (\omega CR)^2}{1 + (\omega C 2R)^2} \right):$$

$$= \frac{2\omega C^2 R^2 (1 + (\omega C 2R)^2) - (1 + (\omega CR)^2) (2\omega C^2 2R^2)}{(1 + (\omega C 2R)^2)^2}$$

$$= \frac{2\omega C^2 R^2 + 2\omega C^2 R^2 (\omega C 2R)^2 - 8\omega C^2 R^2 - 8\omega C^2 R^2 (\omega CR)^2}{(1 + (\omega C 2R)^2)^2}$$

$$= \frac{-6\omega C^2 R^2}{(1 + (\omega C 2R)^2)^2} = 0 \Rightarrow |H|^2 = \text{max. when } \omega = 0, \text{ min. when } \omega \rightarrow \infty$$

$$\Rightarrow |H| = \text{max. when } \omega = 0$$

$$\Rightarrow |H|_{\text{max}} = 1$$

$$\rightarrow \text{find } \omega_c: |H(j\omega_c)|^2 = \frac{1}{2} = \frac{1 + \omega_c^2 C^2 R^2}{1 + 4\omega_c^2 C^2 R^2}$$

$$\Rightarrow 1 + 4\omega_c^2 C^2 R^2 = 2 + 2\omega_c^2 C^2 R^2$$



$$\Rightarrow 2\omega_c^2 C^2 R^2 = 1$$

$$\Rightarrow \omega_c = \pm \sqrt{\frac{1}{2C^2 R^2}} = \pm \frac{1}{RC\sqrt{2}}$$

$$\rightarrow \omega = 0: |H| = 1$$

$$\omega = \omega_c = \frac{1}{RC\sqrt{2}}: |H| = \frac{1}{\sqrt{2}}$$

$$\omega \rightarrow \infty: |H| = \frac{1}{2}$$

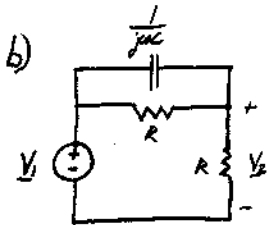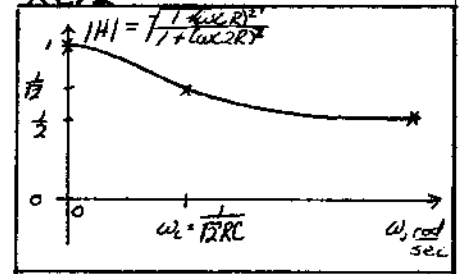

$$V_2 = \frac{V_1 R}{\left( R + \frac{R}{j\omega C} \right) (R + \frac{1}{j\omega C})} = \frac{V_1 R}{R + \frac{R}{j\omega C} + j\omega CR + 1}$$

$$= \frac{V_1 (j\omega CR + 1)R}{(j\omega CR + 1)R + R} \Rightarrow H(j\omega) = \frac{V_2}{V_1} = \frac{j\omega CR^2 + R}{j\omega CR^2 + 2R}$$

$$\Rightarrow |H| = \frac{\sqrt{R^2 + \omega^2 C^2 R^4}}{\sqrt{4R^2 + \omega^2 C^2 R^4}}$$

which is min @  $\omega = 0$ ,  
max @  $\omega \rightarrow \infty$

$$\rightarrow \omega = 0: |H| = \frac{1}{2} \text{ which is min}$$

$$\omega \rightarrow \infty: |H| = 1 \text{ which is max}$$

$$\omega = \omega_c: |H| = \frac{1}{\sqrt{2}} = \frac{R^2 + \omega_c^2 C^2 R^4}{4R^2 + \omega_c^2 C^2 R^4}$$


$$4R^2 + \omega_c^2 C^2 R^4$$

$$\Rightarrow 4R^2 + \omega_c^2 C^2 R^4 = 2(R^2 + \omega_c^2 C^2 R^4)$$


$$\Rightarrow 2R^2 = \omega_c^2 C^2 R^4$$

$$\Rightarrow \frac{2}{C^2 R^2} = \omega_c^2$$

$$\Rightarrow \omega_c = \frac{\sqrt{2}}{RC}$$

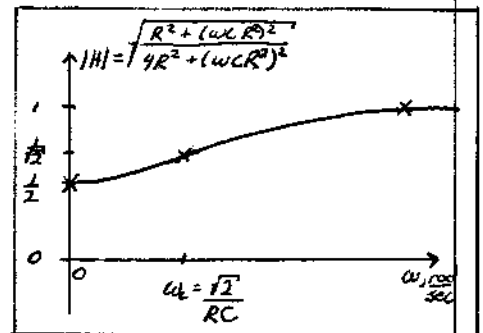

PR 10.5

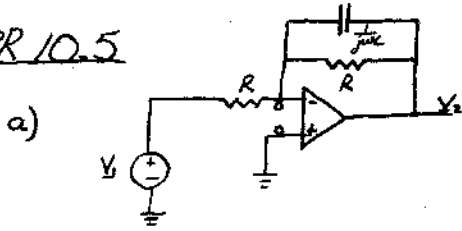

$$e^{-1}: \frac{0-V_1}{R} + \frac{0-V_2}{\frac{1}{j\omega C}} + \frac{0-V_2}{R} = 0$$

$$\Rightarrow -V_1 - j\omega CR V_2 - V_2 = 0$$

$$\Rightarrow V_2(1 + j\omega CR) = -V_1$$



$$\Rightarrow H(j\omega) = \frac{V_2}{V_1} = \frac{-1}{1 + j\omega CR}$$

$\omega = 0, |H| = 1$

$\omega \rightarrow \infty, |H| \rightarrow 0$

$\omega = \omega_c, |H|^2 = \frac{1}{2} = \frac{1}{1 + \omega_c^2 C^2 R^2} \Rightarrow 1 + \omega_c^2 C^2 R^2 = 2 \Rightarrow \omega_c = \frac{1}{RC}$

$\Rightarrow |H(j\omega)| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$

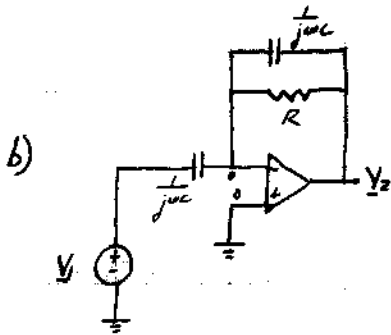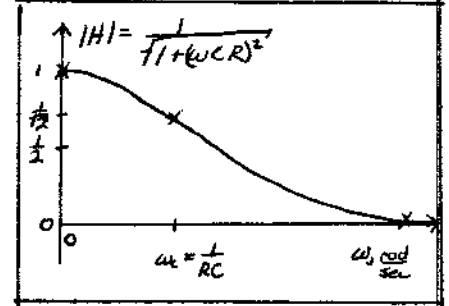

$$e^{-1}: \frac{0-V_1}{\frac{1}{j\omega C}} + \frac{0-V_2}{\frac{1}{j\omega C}} + \frac{0-V_2}{R} = 0$$

$$\Rightarrow j\omega CR V_1 - j\omega CR V_2 - V_2 = 0$$

$$\Rightarrow H(j\omega) = \frac{V_2}{V_1} = \frac{-j\omega CR}{1 + j\omega CR}$$

$\Rightarrow |H| = \frac{\omega CR}{\sqrt{1 + (\omega CR)^2}}$  which is min @  $\omega = 0$ , max @  $\omega \rightarrow \infty$


$\omega = 0, |H| = 0$

$\omega \rightarrow \infty, |H| \rightarrow 1$


$\omega = \omega_c, |H|^2 = \frac{1}{2} = \frac{\omega_c^2 R^2 C^2}{1 + \omega_c^2 R^2 C^2} \Rightarrow 1 + \omega_c^2 R^2 C^2 = 2\omega_c^2 R^2 C^2$

$\Rightarrow 1 = \omega_c^2 R^2 C^2$

$\Rightarrow \omega_c = \frac{1}{RC}$

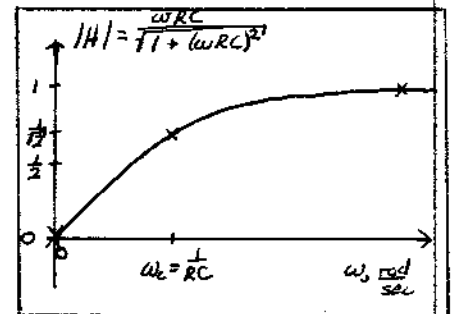

10.7

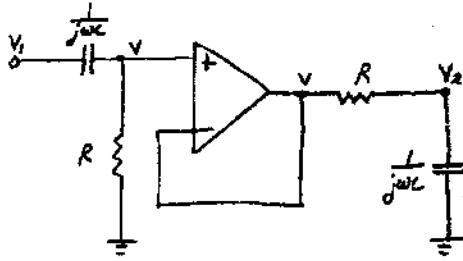

$$e^+ : \frac{V - V_1}{\frac{1}{j\omega C}} + \frac{V - 0}{R} = 0$$

$$\Rightarrow j\omega C V - j\omega C V_1 + \frac{V}{R} = 0$$

$$\Rightarrow V(1 + j\omega C R) = j\omega C R V_1$$

$$e^- : \frac{V_2 - V}{R} + \frac{V_2 - 0}{\frac{1}{j\omega C}} = 0$$

$$\Rightarrow V_2 - V + j\omega C R V_2 = 0$$

$$\Rightarrow V_2(1 + j\omega C R) = V$$

$$= \frac{j\omega C R V_1}{1 + j\omega C R}$$

$$\Rightarrow H(j\omega) = \frac{V_2}{V_1} = \frac{j\omega C R}{(1 + j\omega C R)^2} \Rightarrow \frac{\omega R C}{1 + \omega^2 C^2 R^2} = |H(j\omega)|$$

$$\rightarrow \text{find max } \frac{d|H(j\omega)|}{d\omega} = \frac{RC(1 + \omega^2 C^2 R^2) - \omega RC(2\omega C^2 R^2)}{(1 + \omega^2 C^2 R^2)^2} = 0$$

$$\Rightarrow RC + \omega^2 C^3 R^3 - 2\omega^2 C^3 R^3 = 0 \quad \leftarrow \text{max occurs here, min when } \omega \rightarrow \infty$$

$$\Rightarrow RC = \omega^2 C^3 R^3$$

$$\Rightarrow \omega^2 = \frac{1}{C^2 R^2} \Rightarrow \omega = \frac{1}{RC} = \text{freq of max}$$

$$|H(j\frac{1}{RC})| = \text{max} = \frac{1}{1+1} = \frac{1}{2}$$

\(\rightarrow\) find half-power freq. \(\omega\_c\)

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} = \frac{\omega_c RC}{1 + \omega_c^2 R^2 C^2}$$

$$\Rightarrow 1 + \omega_c^2 R^2 C^2 = \omega_c RC \sqrt{2}$$

$$\Rightarrow R^2 C^2 \omega_c^2 - RC \sqrt{2} \omega_c + 1 = 0$$

$$\Rightarrow \omega_c = \frac{RC \sqrt{2} \pm \sqrt{(RC \sqrt{2})^2 - 4R^2 C^2}}{2R^2 C^2}$$

$$= \frac{\sqrt{2} \pm 2}{2RC} = \frac{\sqrt{2} \pm 1}{RC}$$

$$= \frac{\sqrt{2}-1}{RC}, \frac{\sqrt{2}+1}{RC}$$

