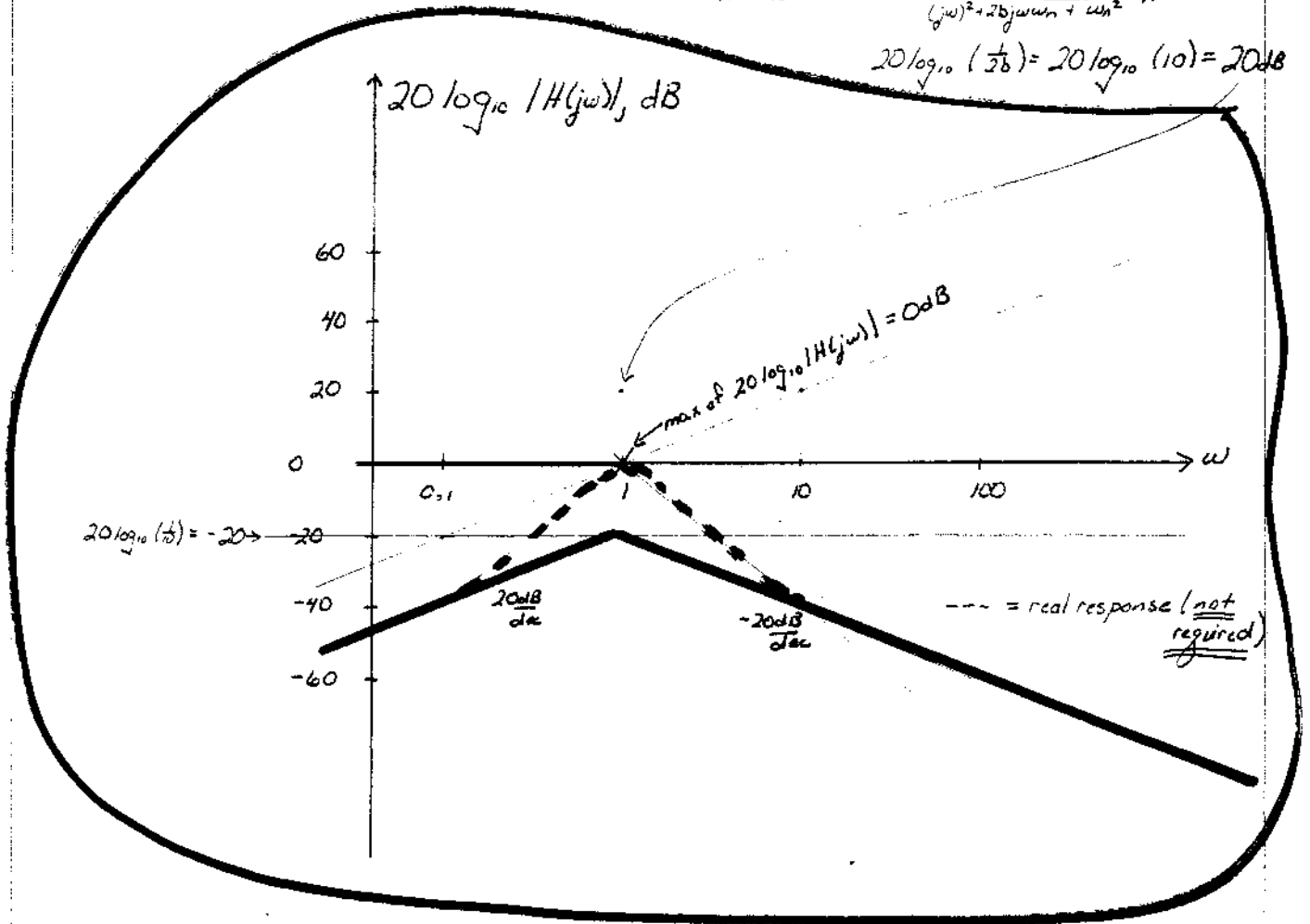


$$\begin{aligned}
 10.15 \text{ from } 10.14, \frac{V_2}{V_1} &= \frac{j\omega(1) \left(\frac{1}{j\omega(1)} \right)}{j\omega(1) + 1} \\
 &= \frac{1}{j\omega + \frac{1}{j\omega}} \\
 &= \frac{1}{10 + j\omega(1) \left(\frac{1}{j\omega(1)} \right)} \\
 &= \frac{1}{10 + \frac{1}{j\omega + \frac{1}{j\omega}}} \\
 &= \frac{1}{10(j\omega + \frac{1}{j\omega}) + 1} = \frac{j\omega}{10(j\omega)^2 + j\omega + 10} \\
 &= \frac{\frac{1}{10} j\omega(1)}{(j\omega)^2 + \frac{1}{10} j\omega + 1} = H(j\omega) \text{ w/ complex poles}
 \end{aligned}$$

$\Rightarrow \omega_n^2 = 1$ for quadratic w/ complex poles
 $2b = \frac{1}{10} \Rightarrow \text{max of } \frac{\omega_n^2}{(j\omega)^2 + 2bj\omega + \omega_n^2}$ is

$$20 \log_{10} \left(\frac{1}{2b} \right) = 20 \log_{10} (10) = 20 \text{ dB}$$



SEE MATLAB AMP/MAG PLOTS ON NEXT PAGE



Commands Typed At MATLAB Prompt:

```

>> clear all; close all;

w = linspace(0.01,10,1000);
H = j*w./(10*j*w*j.*w + j*w + 10);



figure(1);

subplot(2,1,1);
plot(w,abs(H));
grid; ylabel('|H(j\omega)|'); title('Magnitude Response');

w = logspace(-2,3,1000);
H = j*w./(10*j*w*j.*w + j*w + 10);

subplot(2,1,2);
semilogx(w,20*log10(abs(H)));
grid; ylabel('|H(j\omega)|, dB'); title('Bode Plot: Magnitude Response');
xlabel('\omega, (rad/sec)');
>>

```

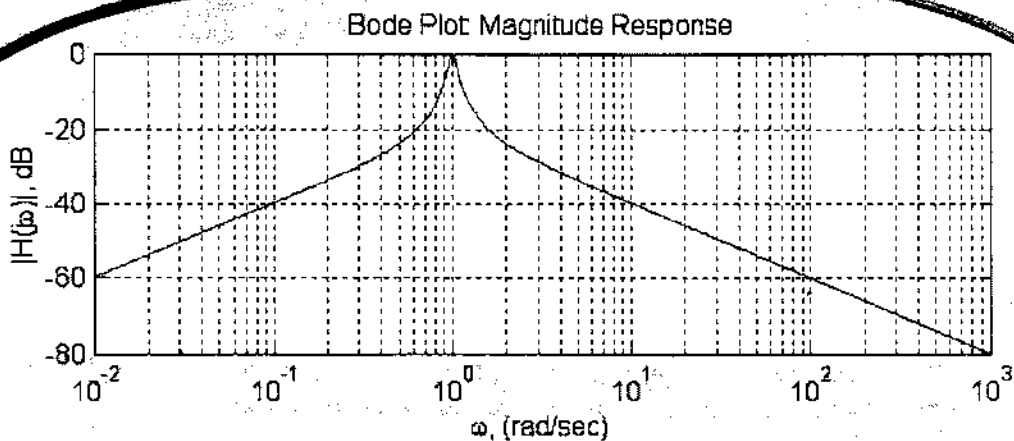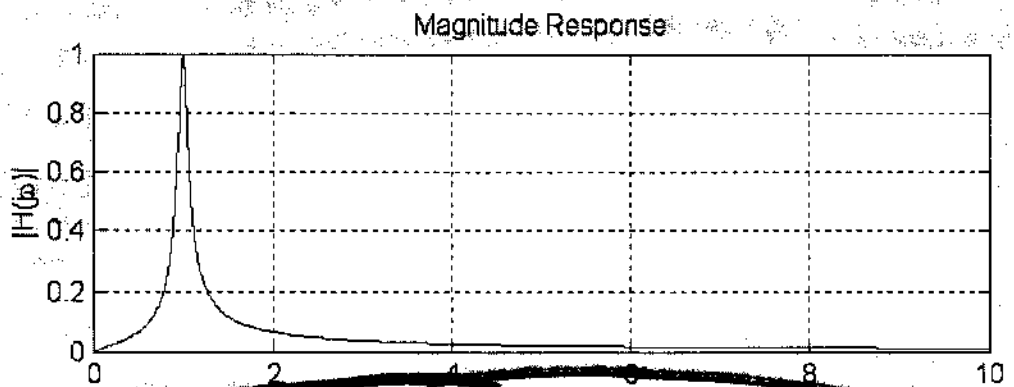Plot Generated:

10.17 from 10.16: $(4+j\omega 2)V - 2V_1 - V_2 = 0$ from node eqn $\approx V$

e^{-1} : $\frac{0-V}{2} + \frac{0-V_2}{\frac{100}{j\omega}} = 0 \Rightarrow -200V - j\omega V_2 = 0 \Rightarrow V = \frac{-j\omega V_2}{200}$



$(4+j\omega 2)\left(\frac{-j\omega V_2}{200}\right) + 2V_1 + V_2 = 0$

$\Rightarrow (4j\omega + (j\omega)^2 2 + 200)V_2 = -400V_1$

$\Rightarrow \frac{V_2}{V_1} = \frac{-400}{2(j\omega)^2 + 4j\omega + 200} = \frac{-200}{(j\omega)^2 + j\omega 2 + 100} = \frac{-2(100)}{(j\omega)^2 + 2j\omega + 100}$

which has complex poles $\omega/\omega_n = 10 \text{ rad/sec}$, max of $\frac{100}{(j\omega)^2 + 2j\omega + 100}$

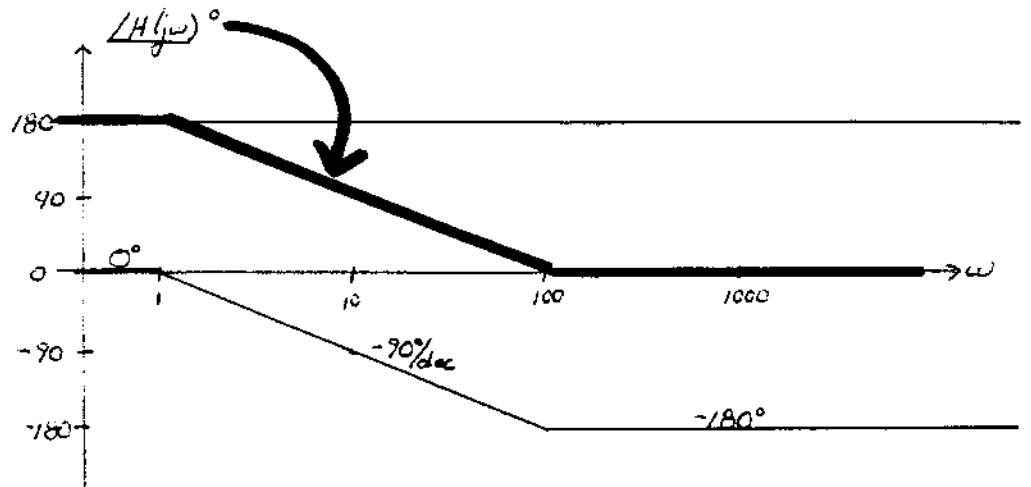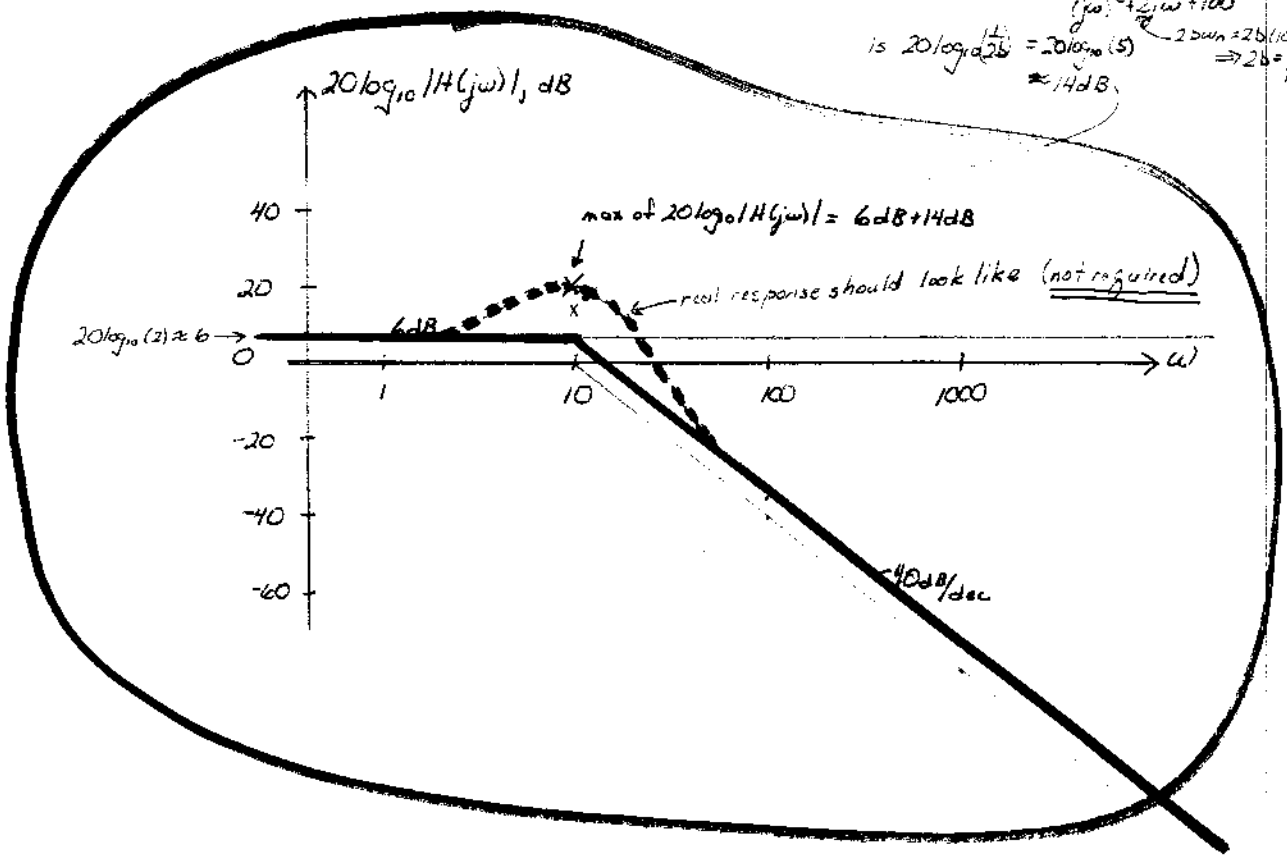is $20 \log_{10} \frac{1}{25} = 20 \log_{10} (5) \approx 14 \text{ dB}$
 $20 \log_{10} (2) \approx 6$
 $\Rightarrow 20 \log_{10} (2) \approx 6$
 $\Rightarrow 20 \log_{10} (5) \approx 14$
 $\Rightarrow 20 \log_{10} (10) \approx 20$



→ see matlab plots on next page

22-141 50 SHEETS
 22-142 100 SHEETS
 22-143 150 SHEETS
 22-144 200 SHEETS

Commands Typed At MATLAB Prompt:

```
>> clear all; close all;



w = linspace(0.1,50,500);
H = -200./(j*w*j.*w + j*w*2 + 100);

figure(1);
subplot(2,1,1);
plot(w,abs(H));
grid; ylabel('|H(j\omega)|'); title('Magnitude Response');
subplot(2,1,2);
plot(w,unwrap(angle(H))*180/pi);
grid; xlabel('\omega (rad/sec)'); ylabel('\angle H(j\omega) (\circ)'); title('Phase Response');


w = logspace(-1,3,1000);
H = -200./(j*w*j.*w + j*w*2 + 100);

figure(2);
subplot(2,1,1);
semilogx(w,20*log10(abs(H)));
grid; ylabel('|H(j\omega)|, dB'); title('Bode Plot: Magnitude Response');
subplot(2,1,2);
semilogx(w,unwrap(angle(H))*180/pi);
grid; xlabel('\omega (rad/sec)'); ylabel('\angle H(j\omega) (\circ)'); title('Bode Plot: Phase Response');
```

Plots Generated:

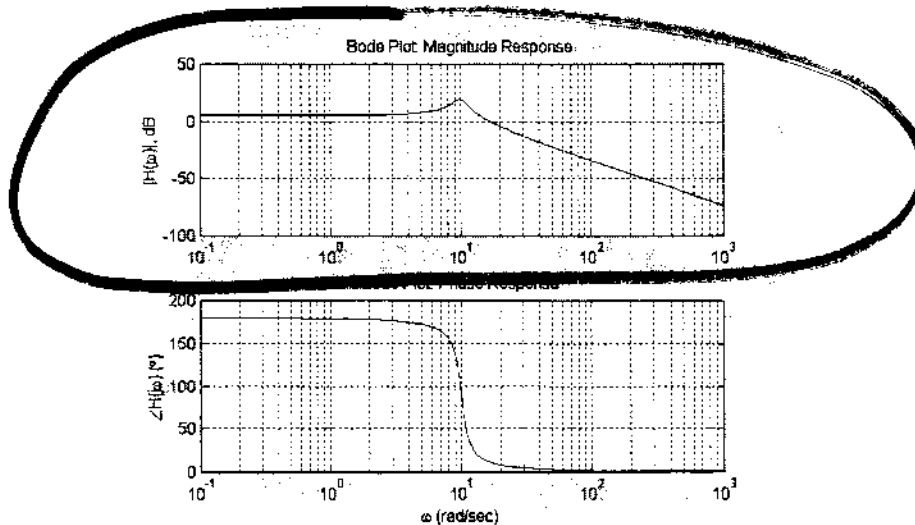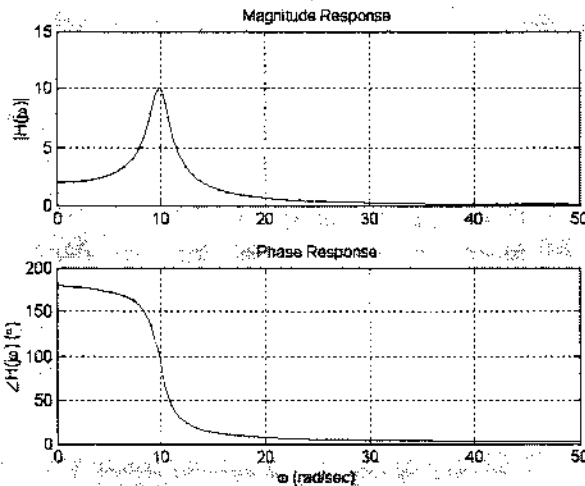

PR10.22

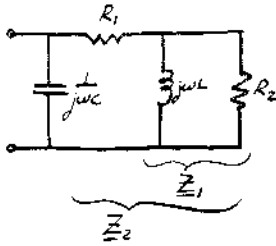

$$\begin{aligned} Z_1 &= \frac{j\omega L R_2}{R_2 + j\omega L}, & Z_2 &= Z_1 + R_1 \\ & & &= \frac{j\omega L R_2}{R_2 + j\omega L} + \frac{R_1(j\omega L + R_2)}{j\omega L + R_2} \\ & & &= \frac{j\omega L(R_1 + R_2) + R_1 R_2}{j\omega L + R_2} \end{aligned}$$

$$Z_{eq} = \frac{\frac{1}{j\omega C} \left(\frac{j\omega L(R_1 + R_2) + R_1 R_2}{j\omega L + R_2} \right)}{\frac{1}{j\omega C} + \frac{j\omega L(R_1 + R_2) + R_1 R_2}{j\omega L + R_2}}$$

$$= \frac{j\omega L(R_1 + R_2) + R_1 R_2}{j\omega L + R_2 + (j\omega)^2 LC(R_1 + R_2) + j\omega C R_1 R_2}$$

$$\Rightarrow \angle Z_{eq} = \tan^{-1} \left(\frac{\omega L(R_1 + R_2)}{R_1 R_2} \right) - \tan^{-1} \left(\frac{\omega C R_1 R_2 + \omega L}{R_2 - \omega^2 LC(R_1 + R_2)} \right) = 0$$

$$\Rightarrow \frac{\omega L(R_1 + R_2)}{R_1 R_2} = \frac{\omega C R_1 R_2 + \omega L}{R_2 - \omega^2 LC(R_1 + R_2)}$$

$$\Rightarrow \omega L R_2 (R_1 + R_2) - \omega^3 L^2 C (R_1 + R_2)^2 = \omega C (R_1 R_2)^2 + \omega L R_1 R_2$$

$$\Rightarrow L R_2 (R_1 + R_2) - \omega^2 L^2 C (R_1 + R_2)^2 = C (R_1 R_2)^2 + L R_1 R_2$$


$$\Rightarrow \omega^2 L^2 C (R_1 + R_2)^2 = L R_1 R_2 + L R_2^2 - C (R_1 R_2)^2 - L R_1 R_2$$

$$\Rightarrow \omega^2 = \frac{R_2^2 (L - C R_1^2)}{L^2 C (R_1 + R_2)^2}$$

$$\Rightarrow \omega = \oplus \sqrt{\frac{\left(\frac{R_2}{R_1 + R_2}\right)^2 (L - C R_1^2)}{L^2 C}}$$

$$\Rightarrow \omega_r = \frac{R_2}{R_1 + R_2} \sqrt{\frac{L - C R_1^2}{L^2 C}}$$

PR10.23

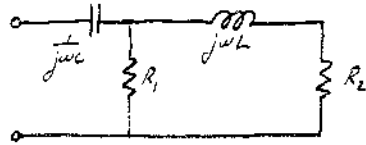

$$Z_{eq} = \frac{1}{jwc} + \frac{R_1(jwL + R_2)}{R_1 + R_2 + jwL}$$

$$= \frac{(R_1 + R_2 + jwL) + (jw)^2 L R_1 + jw C R_1 R_2}{jwC(R_1 + R_2) + (jw)^2 LC}$$

$$\Rightarrow \angle Z_{eq} = \tan^{-1} \left(\frac{wL + wC R_1 R_2}{R_1 + R_2 - w^2 L C R_1} \right) - \tan^{-1} \left(\frac{wC(R_1 + R_2)}{-w^2 LC} \right) = 0$$

$$\Rightarrow \frac{wL + wC R_1 R_2}{R_1 + R_2 - w^2 L C R_1} = \frac{wC(R_1 + R_2)}{-w^2 LC}$$

$$\Rightarrow -w^2 L^2 - w^2 L C R_1 R_2 = (R_1 + R_2)^2 - w^2 L C R_1 (R_1 + R_2)$$

$$\Rightarrow w^2 (L C R_1^2 - L^2) = (R_1 + R_2)^2$$

$$\Rightarrow w^2 = \frac{(R_1 + R_2)^2}{L C R_1^2 - L^2}$$

$$\Rightarrow \boxed{w = w_r = (R_1 + R_2) \sqrt{\frac{1}{L(C R_1^2 - L)}} = \left(\frac{R_1 + R_2}{R_1} \right) \frac{1}{\sqrt{LC - L^2/R_1^2}}}$$

