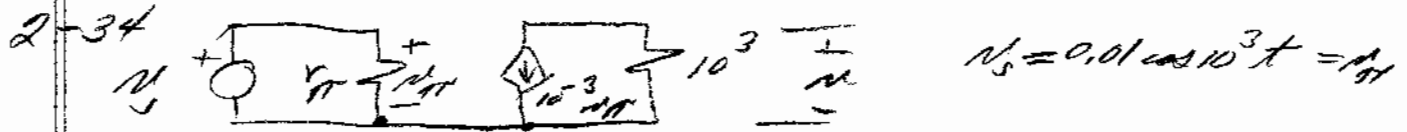


2-28 2mA $470\Omega \pm 5\%$


$P_{\text{max}} = I^2 R = 2 \times 10^{-6} \times 493.5 = \frac{1.974 \text{ mW}}{2}$

$\frac{1}{4}$ watt resistor would be fine. (200mW resistor would work)




dependent source current $= 10^{-5} \cos 10^3 t$

$\therefore N = -10^{-8} \cos 10^3 t$

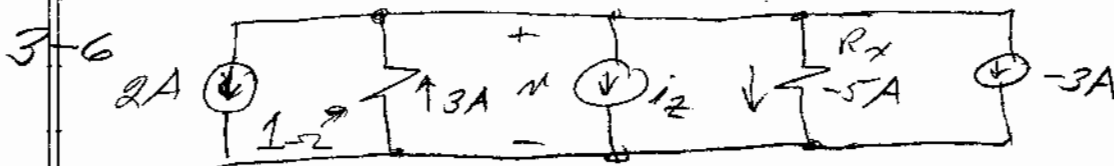

a) $2 - 3 + i_2 - 5 - 3 = 0 \quad \therefore i_2 = 9\text{A}$

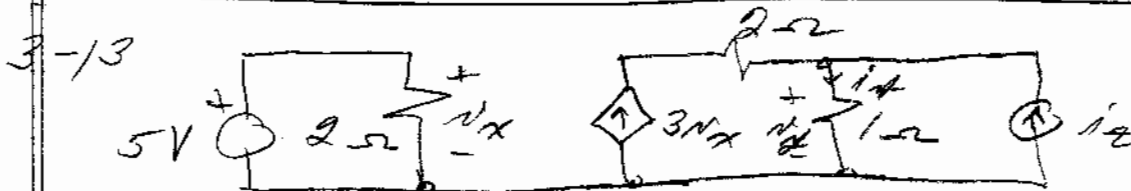b) $N = -3 \quad \therefore R_x = \frac{N}{-5} = \frac{3}{5} \Omega$



a) $i_2 = -3\text{A}$; $N_x = 5\text{V}$ \therefore dependent current source $= 15\text{A}$


$i_y = 3N_x + i_2 = 15 - 3 = 12\text{A}$; $\therefore N_y = i_y \times 2 = 12\text{V}$

b) $i_2 = \frac{1}{2}\text{A}$; $N_x = -6\text{V}$ $\therefore i_y = -6\text{A}$

KCL and $3N_x + i_2 = -6$ or $N_x = -\frac{i_2}{3} - 2 = -\frac{1}{6} - 2$

$N_y = -\frac{13}{6} = -2.167\text{V}$

3-16 a)

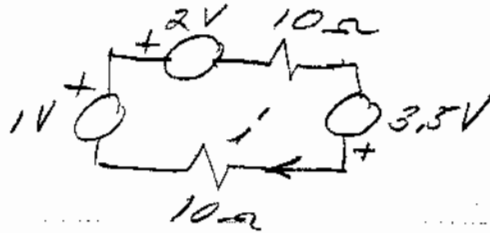


$$-1 + 2 + 10i - 3i + 10i = 0$$

$$20i = 2.5$$

$$i = \frac{2.5}{20} = 0.125$$

b)

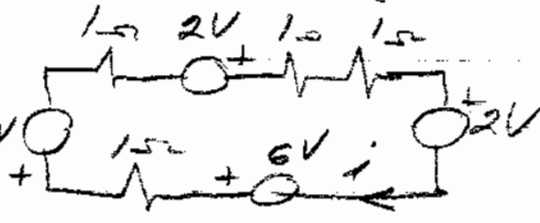


$$10 + i - 2 + i + i + 2 - 6 + i = 0$$

$$4i = -4$$

$$i = -1$$

3-43

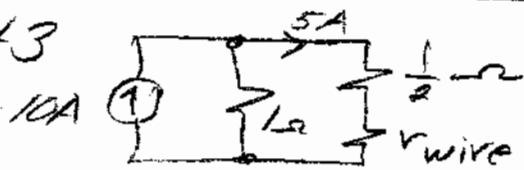


$$r_{wire} = \frac{1}{2} \Omega$$

(28 gauge wire 65.3 Ω / 1000 ft)

$$\frac{65.3}{1000} = \frac{0.5}{x}$$

$$x = \frac{0.5 \times 1000}{65.3} = 7.657 \text{ ft} = 145 \times 10^{-3} \text{ miles}$$

3-65

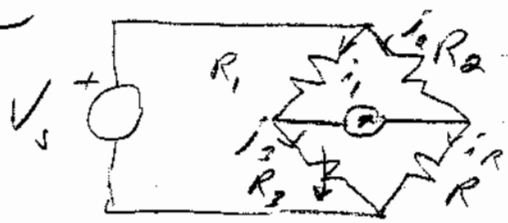


for balance $i_1 R_1 = i_2 R_2$ (1)
and $i_3 R_3 = i_R R$ (2)

but $i_1 = i_3 + i_2 = i_R$

∴ dividing

(1) by (2) gives $\frac{R_1}{R_3} = \frac{R_2}{R}$ or $R = \frac{R_2 R_3}{R_1}$

4-4

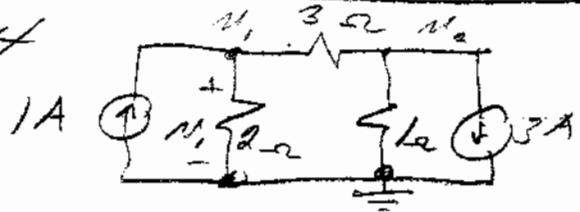

$$\frac{N_1}{2} + \frac{N_2}{3} = 1$$


$$\frac{N_2 - N_1}{3} + \frac{N_2}{1} = -3$$

$$\left. \begin{aligned} \frac{5}{6} N_1 - \frac{1}{3} N_2 &= 1 \\ -\frac{1}{3} N_1 + \frac{4}{3} N_2 &= -3 \end{aligned} \right\}$$

$$\left. \begin{aligned} 5N_1 - 2N_2 &= 6 \\ -N_1 + 4N_2 &= -9 \end{aligned} \right\}$$

$$N_1 = \frac{\begin{vmatrix} 6 & -2 \\ -9 & 4 \end{vmatrix}}{\begin{vmatrix} 5 & -2 \\ -1 & 4 \end{vmatrix}} = \frac{24 - 18}{20 - 2} = \frac{6}{18} = \frac{1}{3} \text{ V}$$

4-9

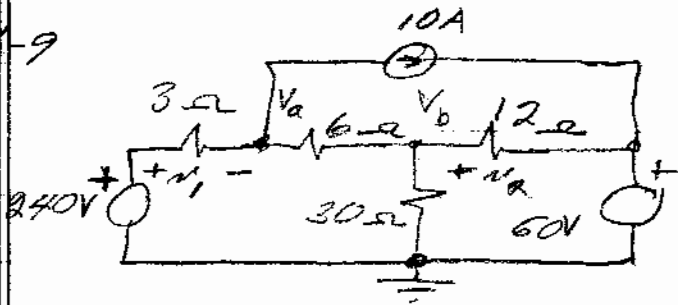

$$\frac{V_a - 240}{3} + \frac{V_a - V_b}{6} = -10$$

$$\frac{V_b - V_a}{6} + \frac{V_b}{30} + \frac{V_b - 60}{12} = 0$$

$$\frac{1}{6} + \frac{1}{30} + \frac{1}{12} = \frac{10 + 2 + 5}{60} = \frac{17}{60}$$

$$\left. \begin{aligned} \frac{1}{2} V_a - \frac{1}{6} V_b &= -10 + 80 \\ \frac{1}{6} V_a + \frac{17}{60} V_b &= 5 \end{aligned} \right\} \begin{aligned} 3V_a - V_b &= 420 \\ -10V_a + 17V_b &= 300 \end{aligned}$$


$$V_a = \frac{\begin{vmatrix} 420 & -1 \\ 300 & 17 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -10 & 17 \end{vmatrix}} = \frac{420(17) + 300}{3(17) - 10} = \frac{7140}{41} = 181.46V$$

$$V_b = \frac{\begin{vmatrix} 3 & 420 \\ -10 & 300 \end{vmatrix}}{41} = \frac{900 + 4200}{41} = 124.39V$$

$V_1 = 240 - V_a = 58.54V$; $V_2 = V_b - 60 = 64.39V$ ←

$$P_{6\Omega} = \frac{(V_b - V_a)^2}{6} = 542.83 \text{ Watts} \leftarrow$$

Super Node

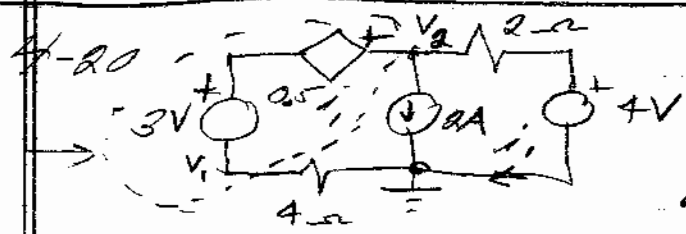

$$V_2 - V_1 = 0.5i_1 + 3$$

$$\text{but } i_1 = \frac{V_2 - 4}{2}$$

$$\therefore V_2 - V_1 = \frac{V_2}{4} - 1 + 3 \quad (1)$$


@ super node $\frac{V_1}{4} + \frac{V_2 - 4}{2} = -2$ ←

$$\text{from (1)} \quad \left. \begin{aligned} \frac{V_1}{4} + \frac{V_2 - 4}{2} &= -2 \\ -V_1 + \frac{3}{4}V_2 &= 2 \end{aligned} \right\} \begin{bmatrix} V_1 + 2V_2 = 0 \\ -4V_1 + 3V_2 = 8 \end{bmatrix}$$

$$V_1 = \frac{\begin{vmatrix} 0 & 2 \\ 8 & 3 \end{vmatrix}}{\begin{vmatrix} 1 & 2 \\ -4 & 3 \end{vmatrix}} = \frac{-16}{3+8} = -\frac{16}{11} ; V_2 = \frac{\begin{vmatrix} 1 & 0 \\ -4 & 8 \end{vmatrix}}{11} = \frac{8}{11}V$$

$$i_1 = \frac{V_2 - 4}{2} = \frac{\frac{8}{11} - \frac{44}{11}}{2} = -\frac{36}{22} = -\frac{18}{11} = -1.636A$$

4-29

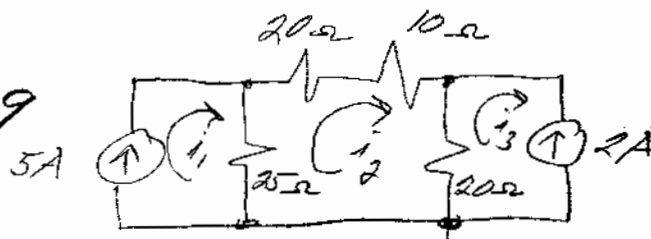

$$i_1 = 5$$

$$i_3 = -2$$


$$(5 - i_1)25 + 30i_2 + (i_2 - i_3)20 = 0$$

$$75i_2 = 125 - 40$$

$$i_2 = \frac{85}{75} = \frac{17}{15} = 1.133A$$

$$P_{25\Omega} = (i_1 - i_2)^2 \cdot 25 = 373.8 \text{ Watts}$$

4-34

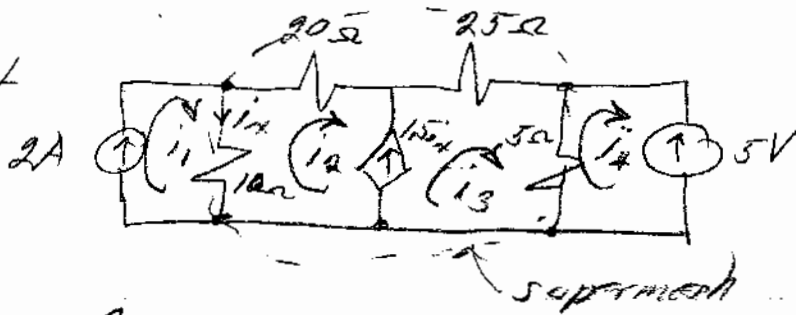

$$\begin{aligned} i_1 &= 2 \\ i_4 &= -5 \end{aligned}$$

$$\begin{aligned} 1.5i_4 &= i_3 - i_2 \quad (1) \\ i_4 &= i_1 - i_2 \quad (2) \end{aligned}$$

$$(i_2 - i_1)10 + 20i_2 + 25i_3 + 5(i_3 - i_4) = 0 \quad (3)$$

combining (1) and (2) gives $\frac{3}{2}(i_1 - i_2) = i_3 - i_2$

$$\text{or } \boxed{i_2 = 6 - 2i_3} \quad \leftarrow \begin{aligned} i_3 - \frac{3}{2}i_2 + i_2 &= -3 + i_3 \\ \frac{1}{2}i_2 &= -3 + i_3 \end{aligned}$$


$$\text{so from (3) } 30(6 - 2i_3) + 25i_3 + 5i_3 = -5$$

$$\begin{aligned} -30i_3 &= -5 - 180 = -185 \\ \boxed{i_3 = \frac{185}{30} = \frac{37}{6} = 6.167 \text{ A}} \leftarrow \end{aligned}$$

$$\text{and } \boxed{i_2 = 6 - 2i_3 = -6.333} \leftarrow$$

$$\text{so } \boxed{i_x = i_1 - i_2 = 2 + 6.333 = 8.333} \leftarrow$$

4-31

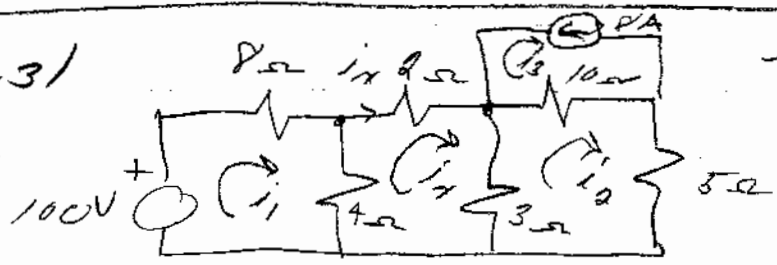

$$i_3 = -8$$

$$\begin{cases} -100 + 8i_1 + 4(i_1 - i_x) = 0 \\ 4(i_x - i_1) + 2i_x + 3(i_x - i_2) = 0 \\ 3(i_2 - i_x) + 10(i_2 + 8) + 5i_2 = 0 \end{cases}$$


$$\begin{aligned} 12i_1 - 4i_x &= 100 \\ -4i_1 + 9i_x - 3i_2 &= 0 \\ -3i_x + 18i_2 &= -80 \end{aligned}$$

4-31 continued

$$i_x = \frac{\begin{vmatrix} 12 & 100 & 0 \\ -4 & 0 & -3 \\ 0 & -10 & 12 \end{vmatrix}}{\begin{vmatrix} 12 & -4 & 0 \\ -4 & 9 & -3 \\ 0 & -3 & 12 \end{vmatrix}} = \frac{12(-240) - 100(-72)}{12(162-9) + 4(-72)}$$

$$i_x = \frac{4320}{1548} = 2.79 \text{ A} \quad \leftarrow$$

5.9 a)

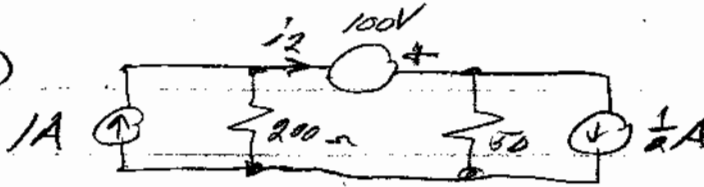



for 1A source $i_{21} = 1 \cdot \frac{200}{200+50} = \frac{4}{5} A$

for 100V source $i_{22} = \frac{100}{250} = \frac{2}{5} A$

for 1/2A source $i_{23} = \frac{1}{2} \cdot \frac{50}{250} = \frac{1}{10} A$

$\therefore i_2 = i_{21} + i_{22} + i_{23} = \frac{13}{10} A = 1.3 A$

5.12 /

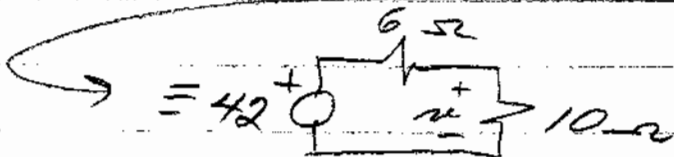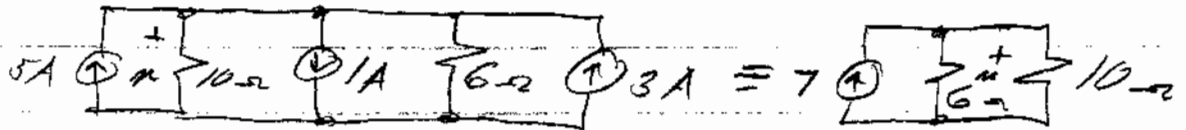


$v = 42 \frac{10}{16} = 26.25 V$

b) If we include 10Ω resistor the voltage v is no longer present!

EE 211

Homework 6


5-42 a)

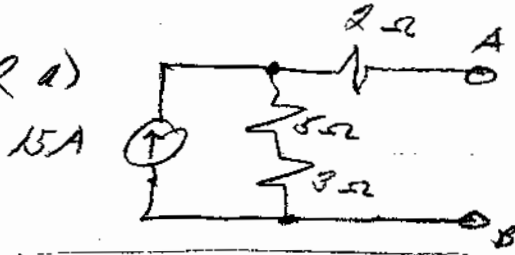


$$V_{oc} = V_{Th} = 15 \times 8 = 120V$$

$$I_{sc} = \frac{3}{8} \times \frac{8}{2} = 12A$$

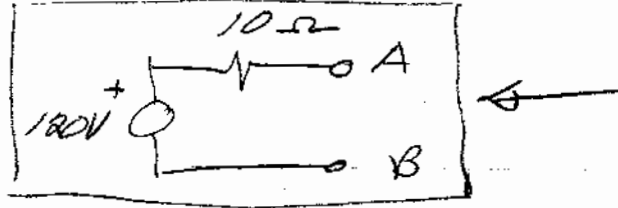
$$\therefore R_{Th} = \frac{V_{oc}}{I_{sc}} = 10\Omega$$




b)

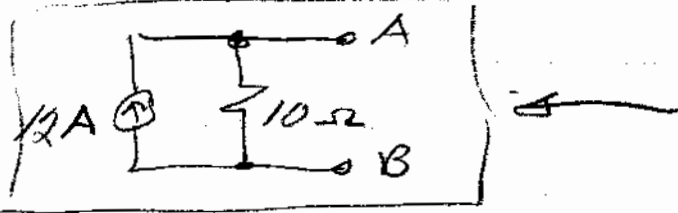

c)

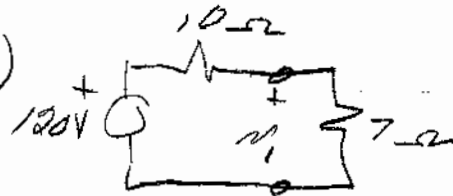

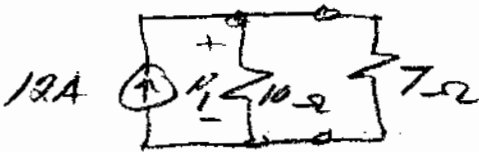
$$V_1 = 120 \times \frac{7}{17} = 49.41V$$




$$V_1 = 12 \times \frac{70}{17} = 49.41V$$

d)

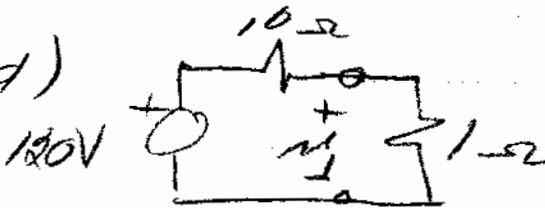


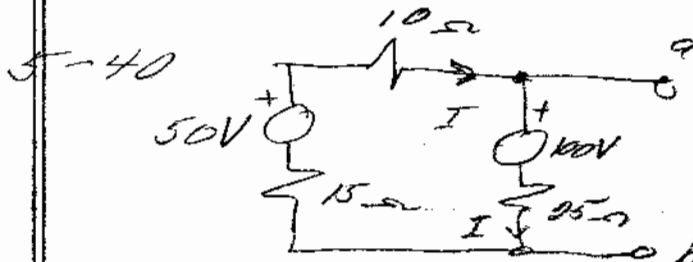
$$V_1 = 200 \times \frac{1}{11} = 18.18V$$



a) for $V_{oc} = V_{Th}$
 $-50 + 100 + I \cdot 50 = 0$


$I = -1$

$\therefore V_{oc} = V_{Th} = 75V$

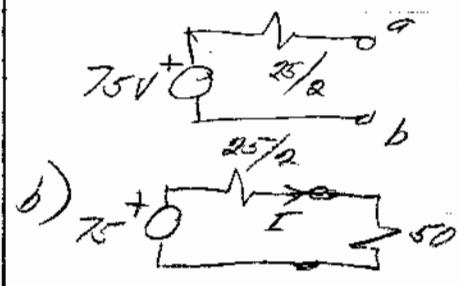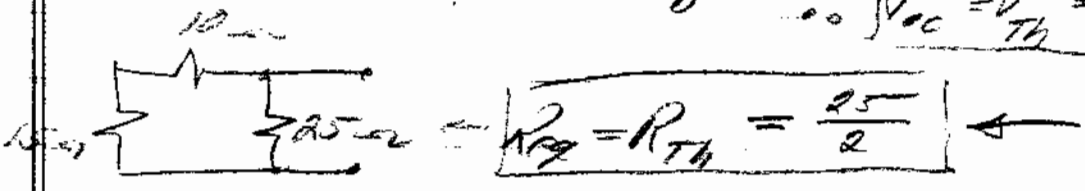


$I = \frac{75}{\frac{125}{2}} = \frac{150}{125} = \frac{30}{25} = \frac{6}{5} A$

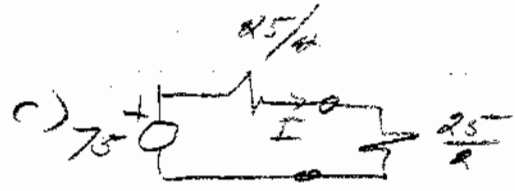$\therefore P_{50\Omega} = \left(\frac{6}{5}\right)^2 \cdot 50 = \frac{36 \cdot 50}{25} = 72W$



$I = \frac{75}{50/2} = \frac{150}{50} = 3$

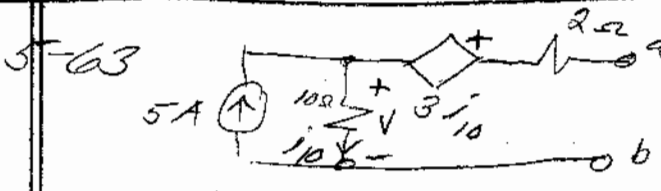$P_{25/2\Omega} = I^2 \cdot \frac{25}{2} = \frac{9 \cdot 25}{2} = 112.5W$



for $V_{oc} \quad V = 30V$

$i_{10} = 3A$

$\therefore V_{oc} = V_{Th} = 3i_{10} + V = 65V$



$(I_{sc} - 5) \cdot 10 - 3(5 - I_{sc}) + I_{sc} \cdot 2 = 0$

$I_{sc}(15) = 65 \quad ; \quad I_{sc} = \frac{65}{15} = \frac{13}{3}$

$\therefore R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{65 \cdot 3}{13} = \frac{195}{13} \Omega = 15 \Omega$

for maximum power $R_L = R_{Th} \quad ; \quad P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{V_{Th}^2}{4R_{Th}}$

$\therefore P_{max} = \frac{65^2}{4 \cdot 15} = 70.4 \text{ Watts}$

7.1 [10 μF]

a) $v = 5V$; $i = C \frac{dv}{dt} = 0$

b) $v = 115\sqrt{2} \cos 120\pi t$; $i = 115\sqrt{2} \cdot 40 \cdot (-1) 120\pi \sin 120\pi t$
or $i = -0.613 \sin 120\pi t$

c) $v = 4e^{-t} \times 10^{-3}$; $i = 4 \times 10^{-8} e^{-t}$

7.13



for $t \geq 0$ $w_c = \frac{1}{2} C v^2 = 20 e^{-10^3 t} \times 10^{-3}$

; $v^2 = \frac{40}{10^6} e^{-10^3 t} \times 10^{-3}$


$v = \pm 200 e^{-500t}$

$i = C \frac{dv}{dt} = \pm 10^{-6} \times (200) \times (-500) e^{-500t} = \mp 0.1 e^{-500t}$

$R = -\frac{v}{i} = + \frac{200}{0.1} = 2 \times 10^3 \Omega$

$w_R = \int_0^{\infty} i v dt = \int_0^{\infty} 20 e^{-10^3 t} dt = \frac{20}{-10^3} e^{-10^3 t} \Big|_0^{\infty} = 0.02 J$

7.15

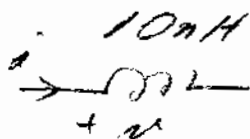


a) $i = 5 \text{ mA}$; $v = L \frac{di}{dt} = 0$

b) $i = 115\sqrt{2} \cos 120\pi t$; $v = 10^{-8} \times 115\sqrt{2} (-1) 120\pi \sin 120\pi t$

$v = 6.13 \times 10^{-4} \sin 120\pi t$

c) $i = 4e^{-6t}$; $v = 10^{-8} \times 4(-6) e^{-6t} = -24 \times 10^{-8} e^{-6t}$


8.6

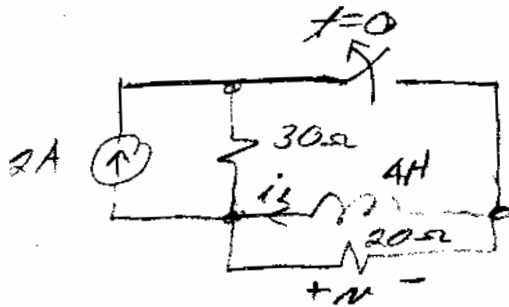

$$a) i_L(0^-) = i_L(0^+) = 2A \leftarrow$$

$$b) v(0^+) = 2 \times 20 = 40V \leftarrow$$

8.8

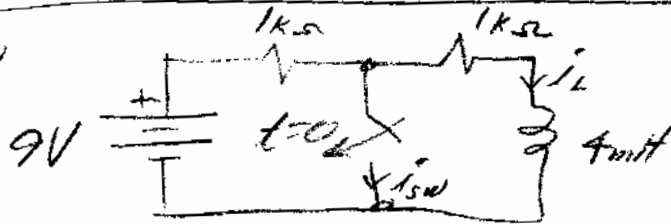

$$i_L(0^-) = i_L(0^+) = \frac{9}{2 \times 10^3}$$

$$\text{for } t > 0 \quad 1 \times 10^3 + 4 \times 10^{-3} \frac{di_L}{dt} = 0$$

$$i_L = A e^{s_1 t} \Rightarrow 10^3 + 4 \times 10^{-3} s_1 = 0$$


$$s_1 = - \frac{10^3}{4 \times 10^{-3}} = - \frac{1}{4} \times 10^6$$

$$\text{so } i_L = \frac{9}{2} \times 10^{-3} e^{-\frac{t \times 10^6}{4}}$$

$$a) t = 5 \mu s \quad i_L = \frac{9}{2} \times 10^{-3} e^{-\frac{5}{4}} = 1.289 \times 10^{-3} \text{ A} \leftarrow$$

$$b) i_{sw}(t = 5 \times 10^{-6}) = -i_L + \frac{9}{10^3} = 7.71 \times 10^{-3} \text{ A} \leftarrow$$

8-35

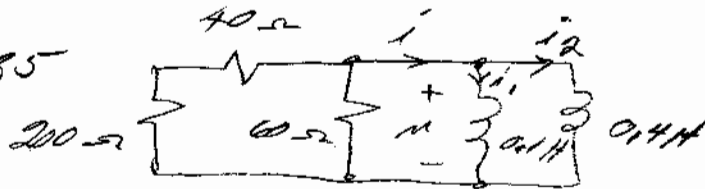


$i_1(0^-) = 10A$

$i_2(0^-) = 20A$

a) $i_1(0^+) = 10A$; $i_2(0^+) = 20A$; $\therefore i(t) = 30A$ ←

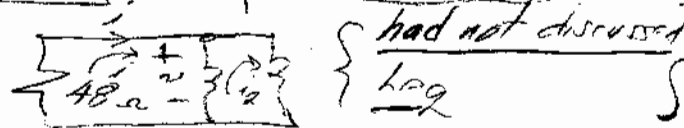b) $R_{eq} = \frac{240 \times 60}{300} = 48 \Omega$



Mesh currents

$48i_1 + 0.1 \frac{d}{dt}(i_1 - i_2) = 0$; $0.1 \frac{di_2}{dt} + 0.1 \frac{d}{dt}(i_2 - i_1) = 0$

$0.5 \frac{di_2}{dt} = +0.1 \frac{di_1}{dt}$

combining these two equations: $48i_1 + 0.1 \frac{di_1}{dt} - 0.1(40.2) \frac{di_1}{dt} = 0$

or $0.08 \frac{di_1}{dt} + 48i_1 = 0$; $i_1 = Ae^{st}$; $0.08s = -48$; $s = -600$

$T = \frac{1}{s} = 1.67 \times 10^{-3} = 1.67 \text{ msec}$ ←

c) $i(t) = 30 e^{-600t}$ ←

d) $v(t) = -48i(t) = -1440 e^{-600t}$ ←

e) $i_1(t) = 10 \int_0^t (-1440) e^{-600t} dt + 10 = \frac{-14400 e^{-600t}}{-600} \Big|_0^t + 10$

or $i_1(t) = 24 e^{-600t} - 14$ ←

$i_2(t) = 2.5 \int_0^t (-1440 e^{-600t}) dt + 20 = 6 e^{-600t} + 14$ ←

f) Energy delivered to $R_{eq} = \int_0^{\infty} i^2 R_{eq} dt = \int_0^{\infty} 900 e^{-1200t} \times 48 dt = W_R$

or $W_R = 36J$ ←


$W_L(t=0) = \frac{1}{2}(0.1) \times 10^2 + \frac{1}{2}(0.14) \times 20^2 = 5 + 80 = 85J$ ←


$W_L(t=\infty) = \frac{1}{2}(0.1) \times 14^2 + \frac{1}{2}(0.14) \times 14^2 = \frac{14^2}{4} = 49J$ ←

? does $W_L(t=0) = W_R + W_L(t=\infty)$?

$85 = 36 + 49$


$85 = 85$

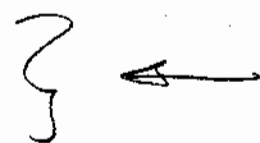

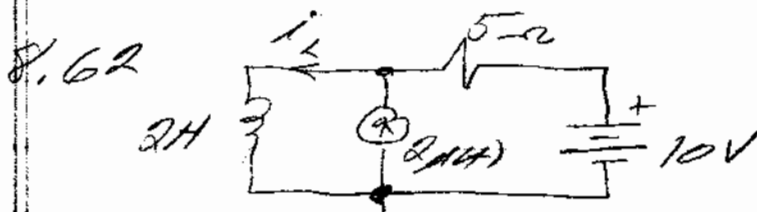

$$i_L(0) = \frac{10}{5} = 2A$$

a) @ $t = 0.5s$; $i_L = 2A$

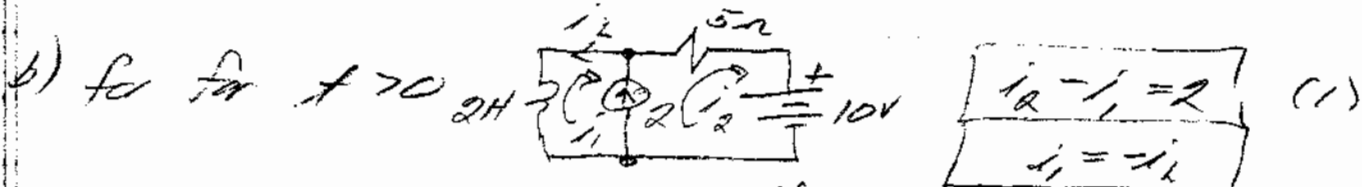

use a supernode equation $2 \frac{di_1}{dt} + 5i_2 = -10$ (2)

combining (1) + (2) gives: $2 \frac{di_1}{dt} + 5(2+i_1) = -10$

$$\text{or } \frac{di_1}{dt} + \frac{5}{2}i_1 = -10$$

$$i_{1, \text{homo}} = Ae^{st} ; s = -\frac{5}{2} \text{ so } i_{1, \text{homo}} = Ae^{-\frac{5}{2}t}$$

$$i_{1, \text{part}} = K \text{ so } \frac{5}{2}K = -10 ; K = -4$$


$$i_L = -i_1 = -i_{1, \text{homo}} - i_{1, \text{part}} = -Ae^{-\frac{5}{2}t} + 4$$

but $i_L(0) = 2 = -A + 4 \therefore A = 2$


and $i_L(t) = -2e^{-\frac{5}{2}t} + 4$ ←

$$i_L(0.5) = 4 - 2e^{-\frac{5}{4}} = 3.427A$$
 ←

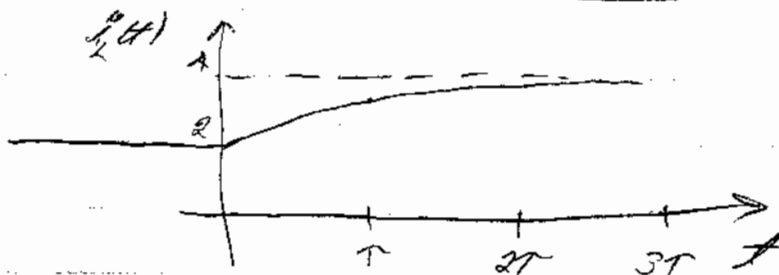c) $i_L(1.5s) = 4 - 2e^{-\frac{15}{4}} = 3.953A$ ←



8-76

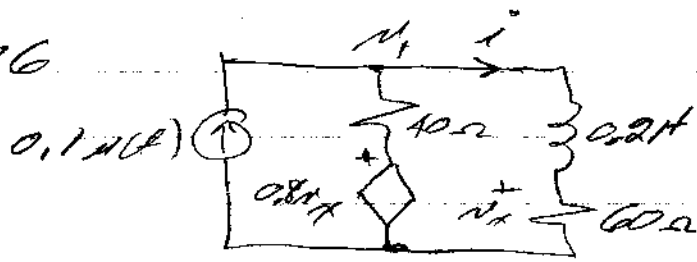for $t < 0$

current source = 0

 $\therefore i_x = 0$ and $i = 0$

for $t > 0$ $\left\{ \begin{array}{l} \frac{i_1 - 0.8i_x}{40} + 5 \int_0^t (i_1 - i_x) dt = 0 \\ 5 \int_0^t (i_x - i_1) dt + \frac{i_x}{60} = 0 \end{array} \right\}$ Node Equations

Mesh $\rightarrow 0.2 \frac{di}{dt} + 60i - 0.8i_x + (5-0.1)40 = 0$
but $i_x = 60i$

so we have $\boxed{\frac{1}{5} \frac{di}{dt} + 52i = 4}$

$i_h = A e^{st}$; $\frac{1}{5}s + 52 = 0$ so $s = -52 \times 5 = -260$

$i_p = K$ so $52K = 4$ or $K = \frac{4}{52}$


$i = i_h + i_p = A e^{-260t} + \frac{4}{52}$ but $i(0) = 0$ so $A = -\frac{4}{52}$

$i = \frac{4}{52} (1 - e^{-260t}) \text{ A}$

$i_x = 60i = \frac{240}{52} (1 - e^{-260t}) \text{ A}$

or $i_x = 4.615 (1 - e^{-260t}) \text{ A}$

9.10

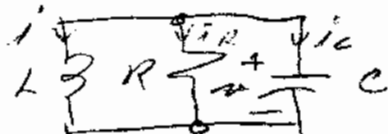

$$L=5, R=8, C=125 \times 10^{-3}$$

$$v(0^+) = 40V$$

$$a) i(0^+) = 8A \quad \frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int_0^t v dt + 8 = 0 \quad (1)$$

$$\text{or } \frac{dv}{dt} + \frac{1}{RC} v + \frac{v}{LC} = 0; \quad v = A e^{st}$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \quad \therefore s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\text{so } s_{1,2} = -\frac{10^3}{2 \times 8 \times 125} \pm \sqrt{25 - 16} = -5 \pm 3 = -2, -8$$

$$\therefore v(t) = A_1 e^{-2t} + A_2 e^{-8t} \quad \text{but } v(0) = 40 \quad \text{so } A_1 + A_2 = 40$$

$$\text{from (1) above } \left. \frac{dv}{dt} \right|_{t=0} = \frac{-8}{C} - \frac{40}{RC} = -640 - 400 = -1040$$

$$\text{so } +2A_1 + 8A_2 = +1040 \quad \text{or } 8(40 - A_2) + 8A_2 = 1040$$

$$6A_2 = 1040 - 80; \quad A_2 = 160 + A_1 = -120$$

$$\text{giving: } \boxed{v(t) = -120 e^{-2t} + 160 e^{-8t}} \quad \leftarrow$$

$$b) i_c(0) = 8A; \quad v(0) = 40; \quad \text{so } i_r(0) = 5$$

$$i(t) = A_3 e^{-2t} + A_4 e^{-8t} \quad \text{but } i(0) = -i_r(0) - i_c(0) = -13$$

$$\text{so } \boxed{-13 = A_3 + A_4} \quad \text{also } v(0) = L \left. \frac{di}{dt} \right|_{t=0} = 40; \quad \left. \frac{di}{dt} \right|_{t=0} = 8$$

$$\text{so } 8 = -2A_3 - 8A_4 = -2(-A_4 + 13) - 8A_4 = -6A_4 + 26$$


$$\therefore A_4 = 3 \quad \text{and} \quad A_3 = -16$$

$$\text{giving: } \boxed{i(t) = -16 e^{-2t} + 3 e^{-8t}} \quad \leftarrow$$

EE 211

Homework 14

9.28

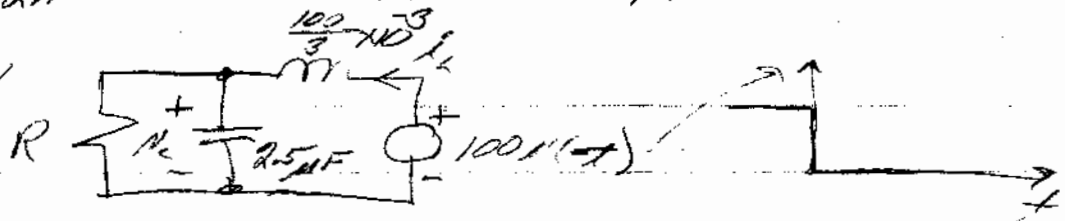

$$i_L(0) = \frac{100}{R} ; v_C(0) = 100$$

for $t > 0$ we have parallel RLC circuit \therefore

$$\frac{dv_C}{dt} + C \frac{dv_C}{dt} + \frac{1}{L} \int_0^t v_C dt - i_L(0) = 0 \quad (1)$$

$$\text{or } \frac{d^2 v_C}{dt^2} + \frac{1}{RC} \frac{dv_C}{dt} + \frac{1}{LC} v_C = 0 ; v_C = A e^{st} ; s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

$$\therefore s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

In critical damping $\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} ; \frac{1}{2RC} = \frac{1}{\sqrt{LC}}$

$$R = \frac{\sqrt{LC}}{2} = \frac{1}{2} \sqrt{\frac{L}{C}} = \frac{1}{2} \sqrt{\frac{0.1 \times 10^{-3}}{3 \times 10^{-6}}} = \boxed{57.73 \Omega}$$

$$s = -\frac{1}{2RC} = -\frac{1}{2 \times 57.735 \times 2.5} = -3464$$

$$\text{so } v_C(t) = A_1 e^{-3464t} + A_2 t e^{-3464t}$$


$$\text{but } v_C(0) = 100 \quad \text{so } \boxed{A_1 = 100}$$

$$\text{from (1) above } \left. \frac{dv_C}{dt} \right|_{t=0} = -\frac{1}{RC} v_C(0) + \frac{100}{RC} = 0!$$

$$\therefore (-3464) \times 100 + A_2 = 0 \quad \text{so } A_2 = +3.464 \times 10^5$$

$$\text{and } \boxed{v_C(t) = 100 e^{-3464t} + 3.464 \times 10^5 t e^{-3464t}}$$

9.60

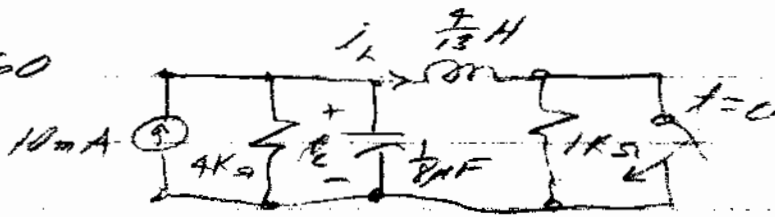

$$v_c(0) = 10^{-2} \times \frac{4}{5} \times 10^3$$

$$\text{or } v_c(0) = 8 \text{ V}$$

$$i_1(0) = 10^{-2} \times \frac{4}{5}$$

for $t > 0$ we have:

$$\frac{v_c}{4 \times 10^3} + \frac{1}{8} \times 10^{-6} \frac{dv_c}{dt} + \frac{13}{4} \int v_c dt + \frac{4}{5} \times 10^{-2} = 10^{-2} \quad (1)$$

differentiating $\times 8 \times 10^6$:

$$\frac{d^2 v_c}{dt^2} + 2 \times 10^3 \frac{dv_c}{dt} + 26 \times 10^6 = 0$$

for $v_c = A e^{st}$ we have $s^2 + 2 \times 10^3 s + 26 \times 10^6 = 0$

$$s_{1,2} = -10^3 \pm \sqrt{10^6 - 26 \times 10^6} = -10^3 \pm j 5 \times 10^3$$

$$\therefore v_c(t) = A_1 e^{-10^3 t} \cos 5 \times 10^3 t + A_2 e^{-10^3 t} \sin 5 \times 10^3 t$$

but $v_c(0) = 8 \therefore A_1 = 8$

from (1) above $\frac{8}{4 \times 10^3} + \frac{1}{8} \times 10^{-6} \left. \frac{dv_c}{dt} \right|_{t=0} + \frac{4}{5} \times 10^{-2} = 10^{-2}$

$$\text{so } \left. \frac{dv_c}{dt} \right|_{t=0} = 8 \times 10^6 \left(10^{-2} - \frac{4}{5} \times 10^{-2} - 2 \times 10^{-3} \right) = 0$$

$0.2 \times 10^{-2} = 2 \times 10^{-3}$

$$\therefore 8(-10^3) + A_2(5 \times 10^3) = 0 ; A_2 = \frac{8 \times 10^3}{5 \times 10^3} = \frac{8}{5}$$

$$\text{and } v_c(t) = 8 e^{-10^3 t} \cos 5 \times 10^3 t + \frac{8}{5} e^{-10^3 t} \sin 5 \times 10^3 t$$


b) see attached plot

EE 211 Hayt problem 9.60

$$t := 0, 10^{-8} .. 2 \times 10^{-3}$$


$$Vc(t) := e^{-1000 \cdot t} \left(\frac{8}{5} \cdot \sin(5000 \cdot t) + 8 \cdot \cos(5000 \cdot t) \right)$$

$$\text{Exp}(t) := \left[\sqrt{8^2 + \left(\frac{8}{5}\right)^2} \right] \cdot e^{-1000 \cdot t} \quad Vc1(t) := \text{Exp}(t) \cdot \cos\left(5000 \cdot t - \text{atan}\left(\frac{1}{5}\right)\right)$$

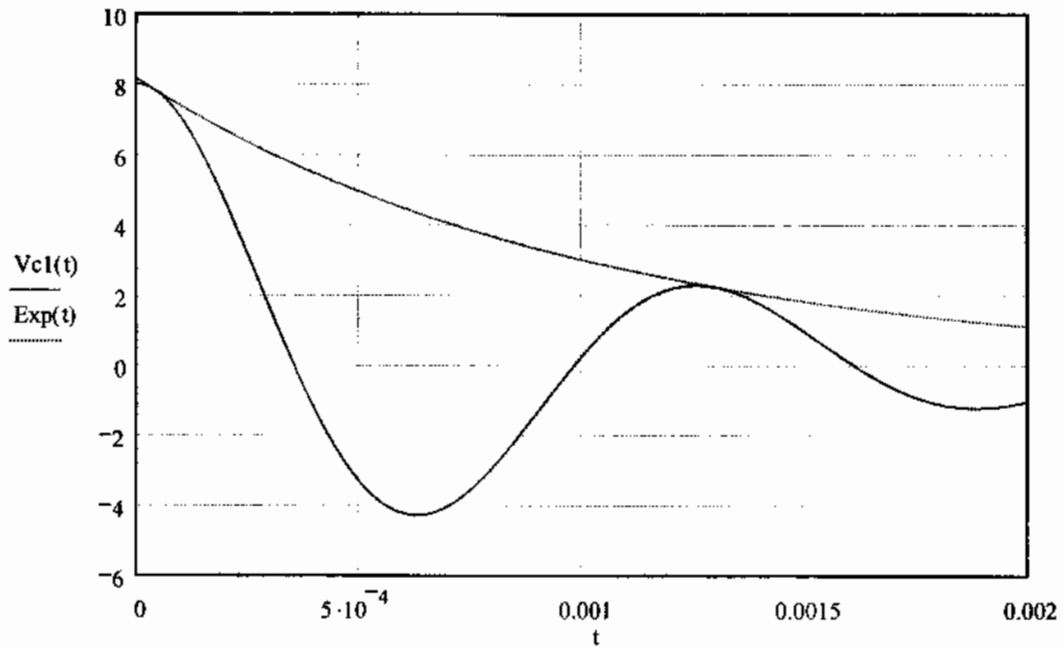

EE 211

Homework 16

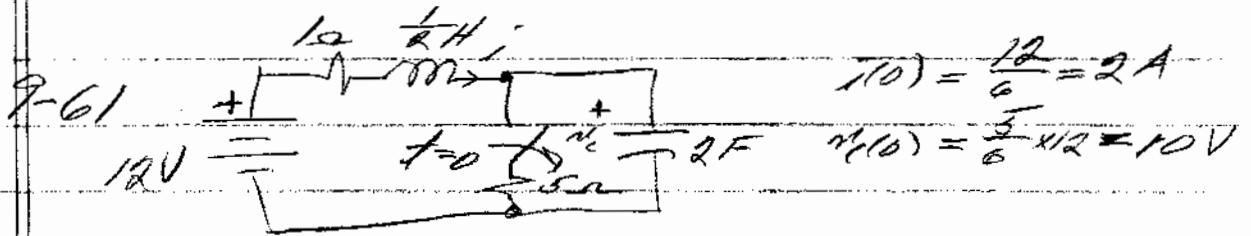

for $t > 0$ $12 = i + \frac{1}{2} \frac{di}{dt} + \frac{1}{2} \int_0^t i dt + 10$ (1)

or $\frac{di}{dt} + 2i + \int_0^t i dt = 0$ let $i = A e^{st}$

we have $s^2 + 2s + 1 = 0$ $s_{1,2} = \frac{-2 \pm \sqrt{4-4}}{2} = -1$

$\therefore i = A_1 e^{-t} + A_2 t e^{-t}$ but $i(0) = 2 \therefore A_1 = 2$

from (1) $\left. \frac{di}{dt} \right|_{t=0} = \frac{12-10-2}{1/2} = 0 = -A_1 + A_2$
 $\therefore A_2 = 2$


and $i(t) = 2e^{-t} + 2te^{-t}$

$v_c(t) = 12 - i - \frac{1}{2} \frac{di}{dt} = 12 - 2e^{-t} - 2te^{-t} - \frac{1}{2} [2e^{-t} + 2t(-1)e^{-t} + 2e^{-t}]$

$v_c(t) = 12 - 2e^{-t} - te^{-t}$

EE 211

Homework 17

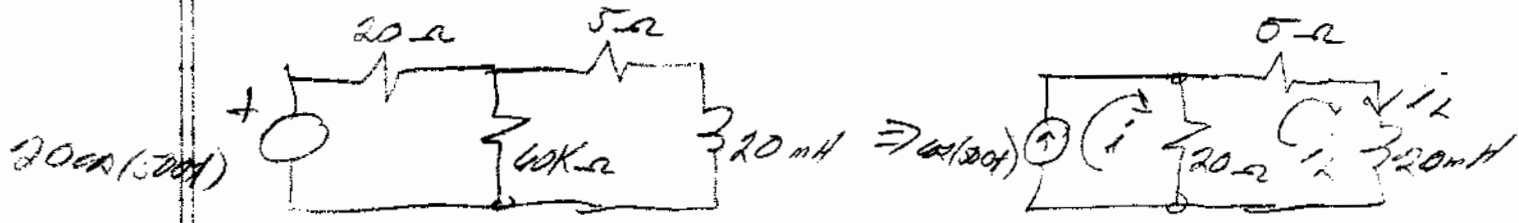

Use current source = $30 \cos 500t$ then all currents and voltages will be of the form $\frac{\tilde{V}}{\tilde{I}} e^{j500t}$

Using mesh currents we have

$$20 \times (\tilde{I}_L - 1) e^{j500t} + 5 \tilde{I}_L e^{j500t} + j10 \tilde{I}_L e^{j500t} = 0$$

$$\tilde{I}_L = \frac{20}{25 + j10} = \frac{20}{26.92 \angle 21.8^\circ}$$


$$\tilde{I}_L = 0.743 \angle -21.8^\circ$$

$$i_L = \text{Re} \{ \tilde{I}_L e^{j500t} \} = 0.743 \cos(500t - 21.8^\circ) \text{ A}$$


EE 211

Homework 18

10.18

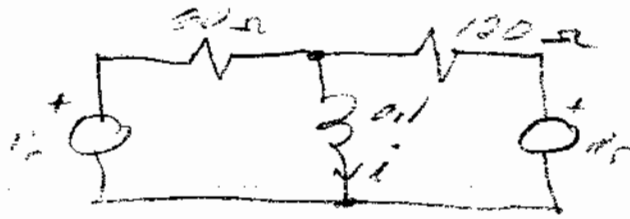
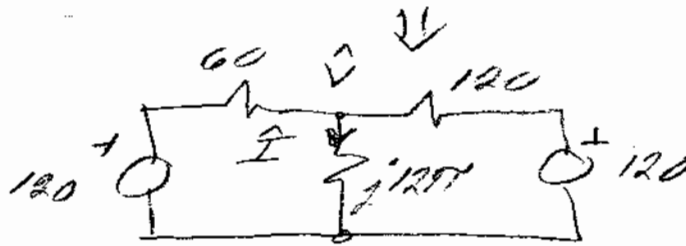
$$\Rightarrow = 120 \angle 120^\circ \text{ V}$$



$$\frac{\hat{V} - 120}{60} + \frac{\hat{V}}{j120} + \frac{\hat{V} - 120}{120} = 0$$

$$\hat{V} \left(\frac{1}{60} + \frac{1}{120} - j \frac{1}{120} \right) = 1 + 2 = 3$$

$$\hat{V} = \frac{3}{\frac{3}{120} - j \frac{1}{120}} = \frac{3 \times 120 \angle 0^\circ}{3 \angle -90^\circ}$$

$$\hat{I} = \frac{\hat{V}}{j120} = \frac{-j30}{3 \angle -90^\circ} = \frac{30}{10 \angle 30^\circ} = \frac{30}{13.74 \angle 43.3^\circ}$$


$$i(t) = 2.183 \text{ A} \angle (120^\circ - 43.3^\circ) \leftarrow$$

$$W_L = \frac{1}{2} L i^2 = 0.238 \text{ J} \angle (120^\circ - 43.3^\circ) \leftarrow$$

$$\text{or } W_L = 0.119 \text{ J} \angle (240^\circ - 86.6^\circ) \leftarrow$$

$$W_{\text{total}} = 0.119 \text{ Joules}$$

10.21

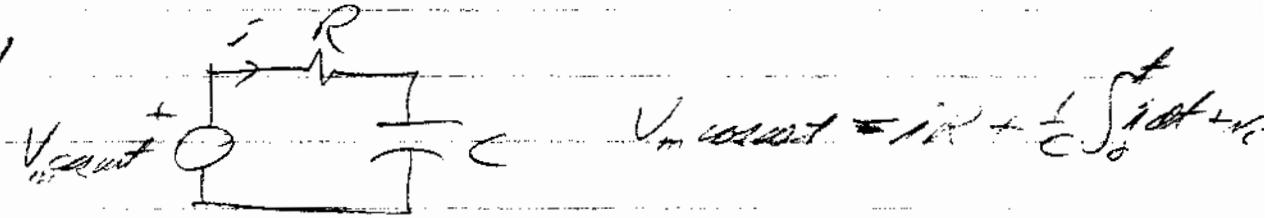

a) or $-V_m \omega \sin \omega t = R \frac{di}{dt} + \frac{1}{C} i$

b) $i_p = A \cos \omega t + B \sin \omega t$

so $-V_m \omega \sin \omega t = R \{ -\omega A \sin \omega t + \omega B \cos \omega t \} + \frac{1}{C} \{ A \cos \omega t + B \sin \omega t \}$

coefficients of \cos & \sin must be equal so:

$$-V_m \omega = -\omega R A + \frac{B}{C} \quad \& \quad 0 = \omega R B + \frac{A}{C}$$

$$B = -\frac{A}{\omega R C}$$

giving $+V_m \omega = +\omega R A + \frac{A}{\omega R C} \Rightarrow A = \frac{V_m \omega}{\omega R + \frac{1}{\omega R C}}$

or $A = \frac{V_m \omega^2 R C^2}{\omega^2 R^2 C^2 + 1}$; $B = -\frac{V_m \omega C}{\omega^2 R^2 C^2 + 1}$

$$i_p = \frac{V_m \omega C}{\omega^2 R^2 C^2 + 1} \{ \omega R C \cos \omega t - \sin \omega t \}$$


but $A \cos \omega t - B \sin \omega t = K \cos(\omega t + \phi) = K \cos \omega t \cos \phi - \sin \omega t \sin \phi$

$$K \cos \phi = A \quad K = \sqrt{A^2 + B^2} ; \phi = \tan^{-1} \frac{B}{A}$$

$$+ K \sin \phi = -B$$

so $i_p = \frac{V_m \omega C}{\omega^2 R^2 C^2 + 1} \sqrt{1 + \frac{1}{R^2 C^2}} \cos \left[\omega t + \tan^{-1} \left(\frac{1}{\omega R C} \right) \right]$

Check on problem 10.21

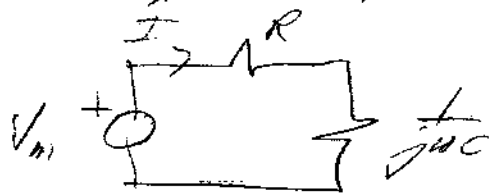

$$\frac{I}{I} = \frac{V_m}{R + \frac{1}{j\omega C}} = \frac{V_m j\omega C}{1 + j\omega RC}$$

$$\therefore i(t) = \frac{V_m \omega C}{\sqrt{1 + \omega^2 R^2 C^2}} \cos \left[\omega t - \underbrace{\tan^{-1}(\omega RC)}_{+\tan^{-1}\left(\frac{1}{\omega RC}\right)} + 90^\circ \right]$$





QED

FE 211

Homework 20

10.65

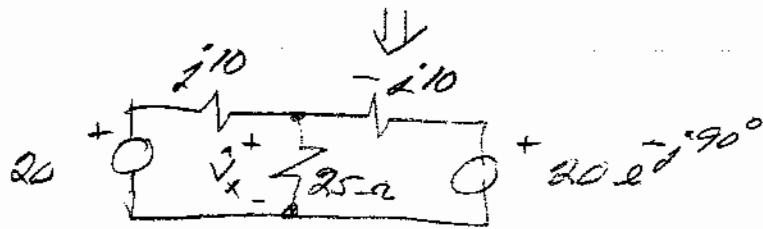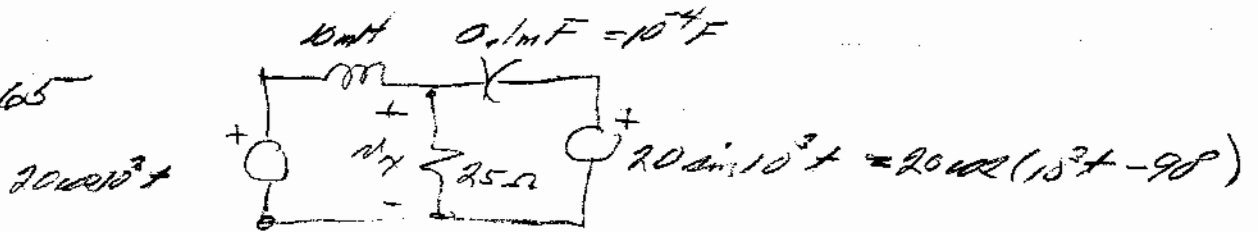

$$\frac{\hat{V}_x - 20}{j10} + \frac{\hat{V}_x}{25} + \frac{\hat{V}_x - 20 e^{-j90^\circ}}{-j10} = 0$$

$$\frac{\hat{V}_x}{25} = \frac{20}{j10} - \frac{20}{j10} e^{-j90^\circ} \Rightarrow \hat{V}_x = 25 \left(\frac{20}{j10} \right) (1 - e^{-j90^\circ})$$


$$\hat{V}_x = 50 \underbrace{(1 - e^{-j90^\circ})}_{-j} = 50(1 - j) = 50\sqrt{2} e^{-j45^\circ}$$

$$\therefore v_x(t) = 50\sqrt{2} \cos(10^3 t - 45^\circ)$$

EE 211

Homework 22

Q13

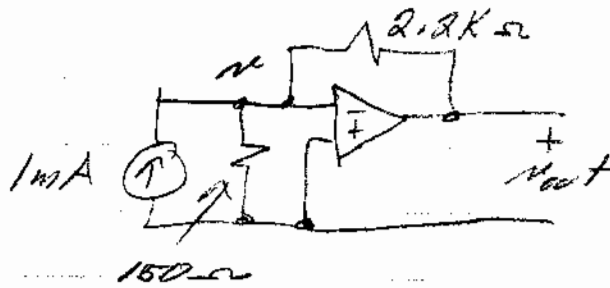


$$\frac{v}{150} + \frac{v - v_{out}}{2.2 \times 10^3} = 10^{-3}$$

$$\boxed{v = 0}$$

$$\therefore \boxed{v_{out} = -2.2 \text{ Volts}}$$

Q16

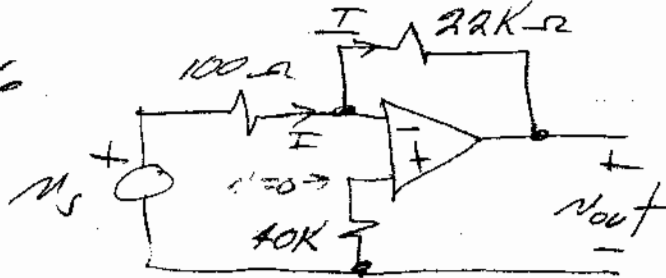


no current through 40K-ohm resistor \therefore voltage of positive input terminal is zero!

$$\text{so } v_s = 100 I \text{ or } I = \frac{v_s}{100}$$

$$\text{and } v_{out} = -I \times 2.2 \times 10^3$$

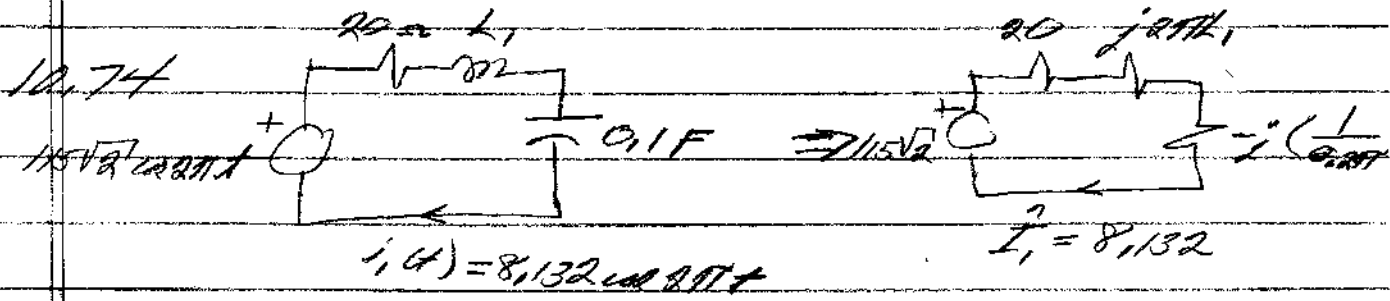
$$\therefore \boxed{v_{out} = -\frac{v_s}{100} \times 2.2 \times 10^3 = -220 v_s}$$



Current $i(t)$ and source are in phase. Therefore, the impedance of the RLC circuit must be real.


$$\therefore 20 \Omega = \frac{1}{0.25} \quad ; \quad j\omega L = \frac{1}{0.472} = 0.2533 \text{ H}$$

Q.17

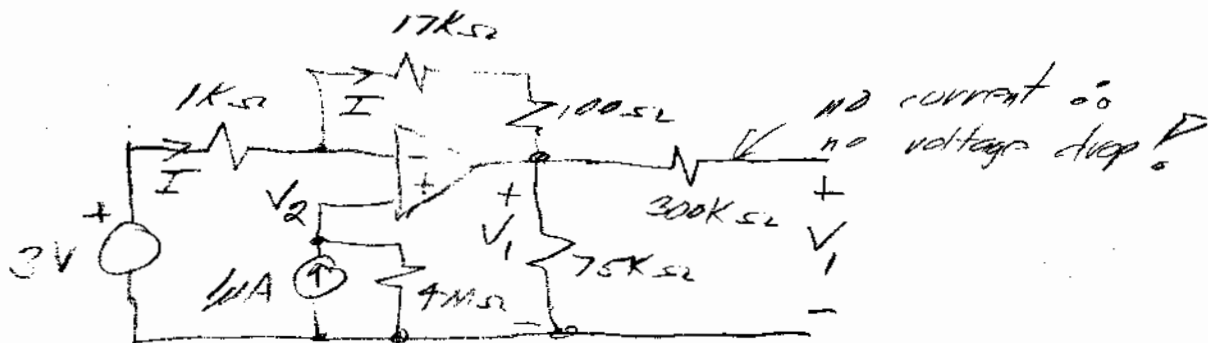

$$V_2 = 10^{-6} \times 4 \times 10^6 = 4 \text{ Volts} ; -3 + 10^3 I - 4 = 0 \text{ or } I = -10^{-3}$$
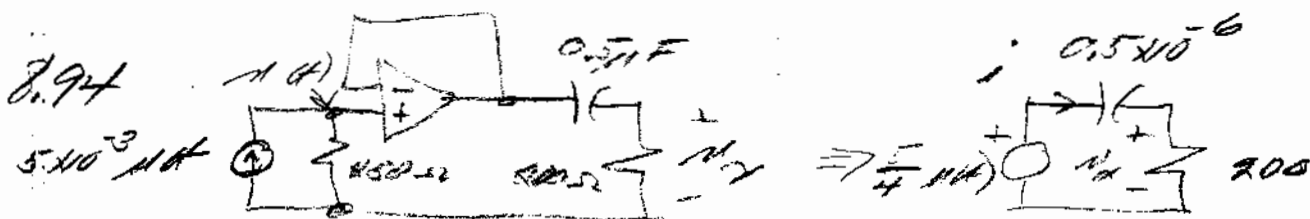
$$V_1 = -I \times 17.1 \times 10^3 + 4 = 17.1 + 4 = \boxed{21.1 \text{ Volts}}$$



$$i(t) = 5 \times 10^{-3} \times 0.25 \times 10^3 = \frac{5}{4} \text{ mA}$$

$$\tau = RC = \frac{1}{2} \times 2 \times 10^{-4}$$

for $t < 0$ $i_{source} = 0 \therefore$

$$i_{cap}(0) = 0$$

$$\rightarrow \text{for } t > 0 \quad \frac{5}{4} = 200i + 2 \times 10^6 \int_0^t i dt \quad (1)$$

$$\text{or } 200 \frac{di}{dt} + 2 \times 10^6 i = 0 \Rightarrow \frac{di}{dt} + 10^4 i = 0$$

$$i = A e^{-10^4 t} \quad ; \quad 5 = -10^4$$



$$\therefore i = A e^{-10^4 t}$$

$$A = 5$$

$$\text{from (1) above } \frac{5}{4} = 200i(0) \text{ or } i(0) = \frac{5}{800} = \frac{1}{160}$$

$$\text{and } i_{200} = 200i = \frac{5}{4} e^{-10^4 t}$$

19.20

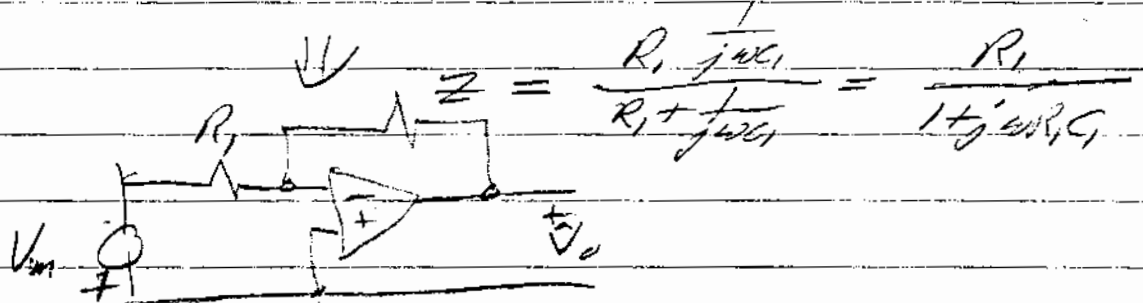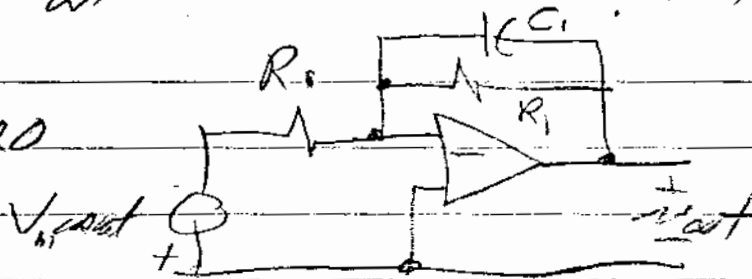

$$\hat{V}_{out} = V_m \left(\frac{1}{1 + j\omega R_1 C_1} \right) \quad \text{inverting amp} \quad \text{Gain} = \frac{Z_f}{Z_{in}}$$

$$\text{or } V_{out} = \frac{V_m e^{j\omega t - \tan^{-1}(\omega R_1 C_1)}}{\sqrt{1 + \omega^2 R_1^2 C_1^2}}$$

$$\text{so } v_{out}(t) = + \frac{V_m}{\sqrt{1 + \omega^2 R_1^2 C_1^2}} \cos[\omega t - \tan^{-1}(\omega R_1 C_1)]$$

$$\text{or } v_{out}(t) = \frac{V_m}{\sqrt{1 + \omega^2 R_1^2 C_1^2}} \cos[\omega t - \tan^{-1}(\omega R_1 C_1)]$$

IF $R_1 C_1 = \frac{L}{R}$ and we multiply by R to get $v_{out}(t) =$

$$v_{out}(t) = \frac{V_m R}{\sqrt{1 + \omega^2 \left(\frac{L}{R}\right)^2}} \cos[\omega t - \tan^{-1}\left(\omega \frac{L}{R}\right)] = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos[\omega t - \tan^{-1}\left(\frac{\omega L}{R}\right)]$$

which is the solution given in equation [4]

page 373

FE 211

Homework 25

10-31

wanted 6-31

$$a) 12e^{j(110^\circ - 90^\circ)} = \boxed{12e^{j20^\circ}} \leftarrow$$

$$b) -7\sin 800t - 3\cos 800t = -K\cos(800t - \phi)$$

$$K = \sqrt{49 + 9} = 7.616; \phi = \tan^{-1}\left(\frac{7}{3}\right) = 66.8^\circ$$

$$\text{so } -7\sin 800t - 3\cos 800t = -7.616\cos(800t - 66.8^\circ)$$

$$\text{or phasor is } \boxed{7.616 \angle 113.2^\circ} \leftarrow$$

$$c) 4e^{j(200t - 30^\circ)} - 5e^{j(200t + 20^\circ)}$$

$$\text{phasor} = 4e^{-j30^\circ} - 5e^{j20^\circ} = 3.464 - j2 - 4.698 - j1.710$$

$$= -1.234 - j3.710 = \boxed{3.91 \angle -109.3^\circ} \leftarrow$$

$$d) \omega = 600; \tau = 5 \text{ msec}$$

$$70e^{j30^\circ} \Rightarrow 70\cos(600t + 30^\circ) \Big|_{t=5\text{msec}} = \boxed{-64.95} \leftarrow$$

$$\vec{V} = -60 + j40 = 78.1 \angle 146.31^\circ$$


$$78.1 \cos(600t + 146.31^\circ) \Big|_{t=5\text{msec}} = \boxed{53.75} \leftarrow$$

6-31



CDS cell
 no light $R = 10^5 \Omega$
 6 candela $R = 10^4 \Omega$

→ 2 candela produces $V_0 = 1.5V$ ←

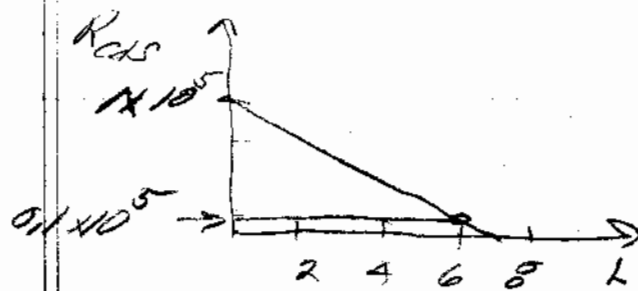

$$\text{slope} = -\frac{0.9}{0.9 \times 10^5} = -0.15 \times 10^5$$

$$\therefore R_{CDS} = -15 \times 10^3 L + 10^5$$

$$I = \frac{N_s}{R_1} ; \left[V_0 = I(R_1 + R_{CDS}) = N_s \left(1 + \frac{R_{CDS}}{R_1} \right) \right]$$


$$\text{For } L = 2 \text{ candela } R_{CDS} = -30 \times 10^3 + 100 \times 10^3 = 70 \times 10^3 \Omega$$

$$\therefore 1.5 = N_s \left(1 + \frac{70 \times 10^3}{R_1} \right)$$

If we pick $R_1 = 10k \Omega$

$$\text{Then } 1.5 = N_s(1+7) \text{ or } N_s = \frac{1.5}{8} = 0.1875V$$

EE 211 Homework 27

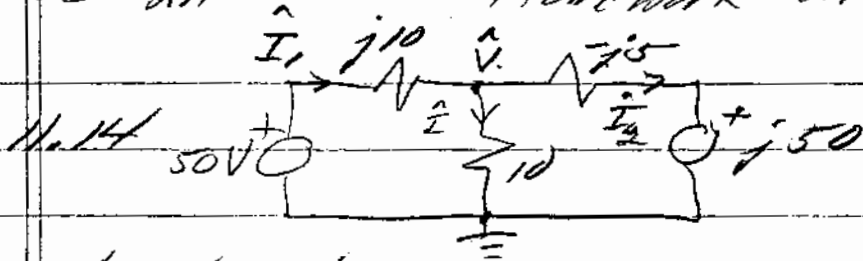

$$\frac{\hat{V} - 50}{j10} + \frac{\hat{V}}{10} + \frac{\hat{V} - j50}{-j5} = 0 \Rightarrow \hat{V} \left(-\frac{j}{10} + \frac{1}{10} + \frac{j}{5} \right) = -j5 - 10$$

$$\therefore \hat{V} = \frac{-10 - j5}{\frac{1}{10} + \frac{j}{10}} = -10 \left\{ \frac{10 + j5}{1 + j} \right\} = \frac{10 \angle 180^\circ \cdot 11.18 \angle 26.56^\circ}{\sqrt{2} \angle 45^\circ}$$

$$\hat{V} = 79.07 \angle 16.56^\circ ; \quad \left\{ 50 \hat{I}_1 = \frac{\hat{V}}{10} = 7.907 \angle 16.56^\circ \right\}$$

$$\hat{I}_1 = \frac{50 - \hat{V}}{j10} = \frac{50(1 + j) + 100 + j50}{j10(1 + j)} = \frac{150 + j100}{-10 + j10} = \frac{15 + j10}{-1 + j} = \frac{18.03 \angle 33.69^\circ}{\sqrt{2} \angle 135^\circ}$$

$$\therefore \hat{I}_1 = 12.75 \angle 101.31^\circ$$

$$\hat{I}_2 = \frac{\hat{V} - j50}{-j5} = \frac{-10 - j50 - j50(1 + j)}{(1 + j)(-j5)} = \frac{-50 - j100}{5 - j5} = \frac{-10 - j20}{1 - j}$$

$$\hat{I}_2 = \frac{22.36 \angle 243.43^\circ}{\sqrt{2} \angle 45^\circ} = 15.81 \angle 71.57^\circ$$

$$P_{ave_{50V}} = -\frac{1}{2} \operatorname{Re} \{ 50 \times 12.75 \angle 101.31^\circ \} = +62.51 \text{ Watts}$$


$$P_{ave_{j50V}} = \frac{1}{2} \operatorname{Re} \{ j50 \times 15.81 \angle 71.57^\circ \} = -374.98 \text{ Watts}$$

$$P_{ave_{10-5}} = \frac{1}{2} |\hat{I}_1|^2 \cdot 10 = 312.05 \text{ Watts}$$

$$P_{ave_{inductor}} = P_{ave_{capacitor}} = 0$$

$$\sum P_s = -0.42 \approx 0$$

11.41

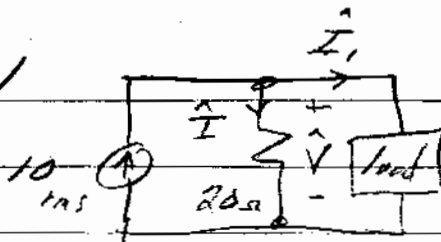

$$a) \hat{I} = 4 e^{j35^\circ}$$

$$\hat{I}_1 = 10 - 4 e^{j35^\circ}$$

$$\therefore \hat{I}_1 = 10 - 3.277 - j2.294 = 6.723 - j2.294 = 7.10 e^{-j18.8^\circ}$$

$$\hat{V} = \hat{I} \times 20 = 80 e^{j35^\circ}$$

$$P_{\text{source}} = P_o \{ 80 e^{j35^\circ} \times 10 \} = 80 \times 10 \times \cos 35^\circ = \boxed{-655.3 \text{ Watts}}$$

$$P_{20\Omega} = P_o \{ \hat{V} \hat{I}^* \} = P_o \{ 320 \} = \boxed{320 \text{ Watts}}$$

$$P_{\text{load}} = P_o \{ \hat{V} \hat{I}_1^* \} = P_o \{ 80 e^{j35^\circ} \times 7.10 e^{-j18.8^\circ} \} = \boxed{335.14 \text{ Watts}}$$


$$\boxed{Z = -0.16 \Omega}$$

$$AP_{\text{source}} = 10 \times 80 = -800 \text{ Volt Amperes}$$

$$AP_{20\Omega} = 320 \text{ Volt Amperes}$$

$$AP_{\text{load}} = 80 \times 7.1 = 568 \text{ Volt Amperes}$$
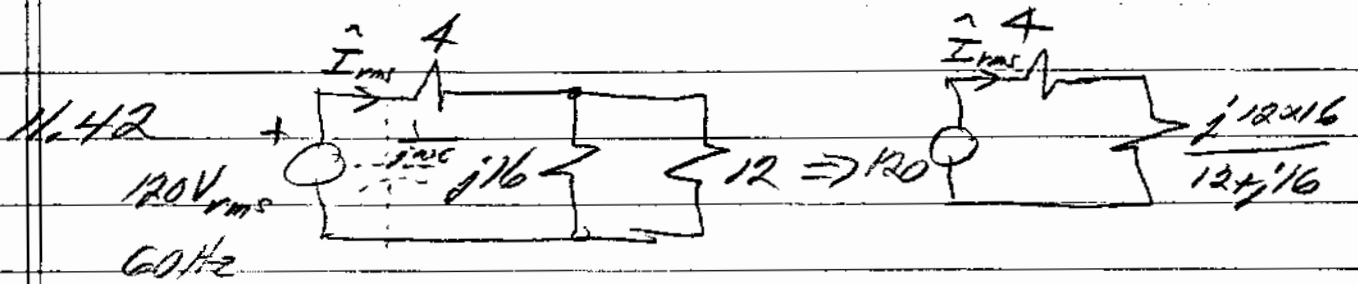
$$pP_{\text{load}} = \frac{P_{\text{avg}}}{AP} = \frac{335.14}{568} = \boxed{0.59} \text{ 1099m}^9$$



$$a) \text{ or } \hat{I}_{rms} = \frac{120}{4 + \frac{j16 \cdot 12}{12 + j16}} = \frac{120(12 + j16)}{48 + j192} = \frac{120(\frac{3}{4} + j)}{3 + j16}$$

$$\hat{I}_{rms} = \frac{90 + j120}{3 + j16} = \frac{150 \angle 53.13^\circ}{16.279 \angle 79.38^\circ} = 9.21 \angle -26.25^\circ$$

∴ source $\text{pf} = 0.897$ lagging ←


$$b) P_{\text{out source}} = -P_o \{120 \times 9.21 \angle -26.25^\circ\} = -991.2 \text{ Watts}$$

$$c) S_{\text{circuit}} = \hat{V}_{rms} \hat{I}_{rms}^* = 120 \times 9.21 \angle 26.25^\circ = 991.2 + j488.82$$

∴ Capacitor Q must be $-j488.82$ for $\text{pf} = 1$

$$Q_{\text{cap}} = 120 \hat{I}_{\text{cap}}^* = 120 \times 120 (-j2\pi \times 60 C)$$
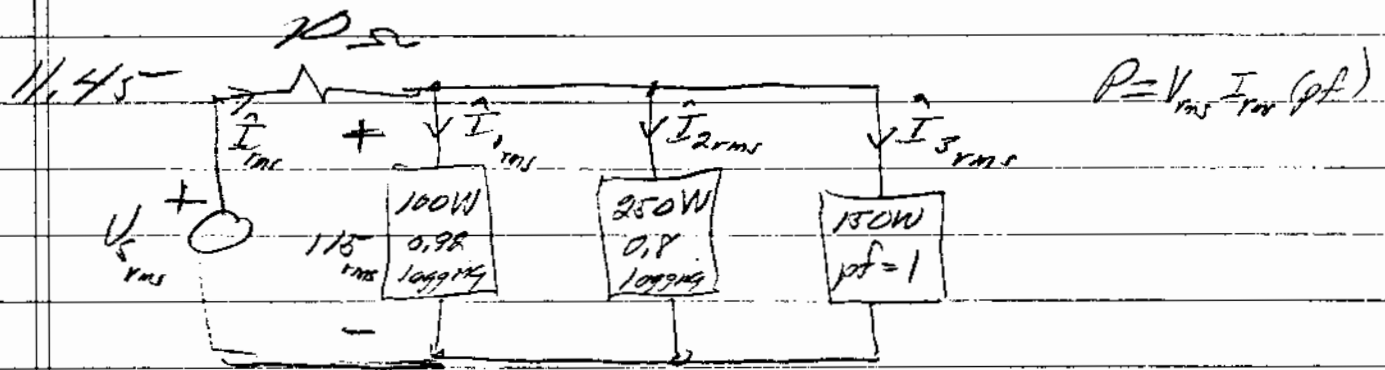
$$C = \frac{488.82}{120^2 \times 2\pi \times 60} = 90 \times 10^{-6} \text{ F} \leftarrow$$



$$\hat{I}_{rms} = \frac{100}{115 \times 0.98} e^{-j23.07^\circ} + \frac{250}{115 \times 0.8} e^{-j36.87^\circ} + \frac{150}{115}$$

$$\hat{I}_{rms} = 0.945 e^{-j23.07^\circ} + 2.717 e^{-j36.87^\circ} + 1.304$$

$$\hat{I}_{rms} = 0.869 - j0.37 + 2.174 - j1.63 + 1.304 = 4.347 - j2$$

$$\text{or } \hat{I}_{rms} = 4.78 e^{-j24.7^\circ}$$

$$pf = \cos 24.7^\circ = 0.9084 \text{ lagging}$$