


a) $v_1 = 30V$ $\therefore i_1 = \frac{30}{5} = 6A$ ←

b) $v_2 = 12V$ $\therefore i_2 = -\frac{12}{4} = -3A$ ←

c) $v_3 = -9V$ $\therefore i_3 = -\frac{-9}{3} = 3A$ ←

d) $v_4 = -3V$ $\therefore i_4 = -3A$

ES 332 Homework 2

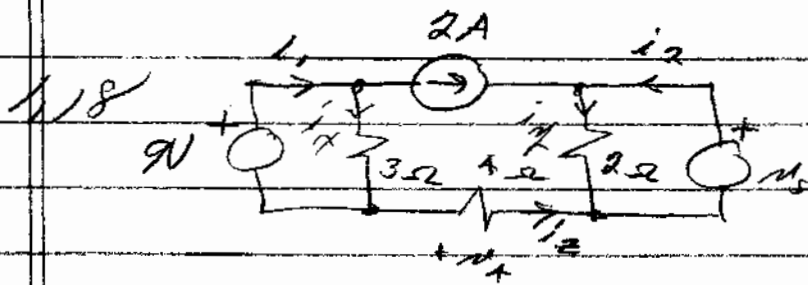

a) $v_5 = 2V$; $i_3 = \frac{9}{3} = 3A$; $i_4 = \frac{2}{2} = 1A$

∴ $i_2 + 2 - i_4 = 0$ or $i_2 = i_4 - 2 = -1$


$i_2 + i_4 - i_3 = 0$ or $i_2 = i_3 - i_4 = 2$ ∴ $v_4 = -8V$

b) $v_5 = 4V$; $i_4 = 2A$, $i_3 = 3A$

again $i_2 = i_4 - 2 = 0$; $i_2 = i_3 - i_4 = -2A$; $v_4 = i_2 \cdot 2 = -8V$

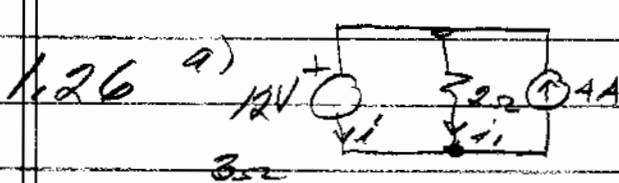
c) $v_5 = 6V$; $i_3 = 3A$, $i_4 = 3A$

again $i_2 = i_4 - 2 = 1A$; $i_2 = i_3 - i_4 = -2A$; ∴ $v_4 = -8V$




$i_1 = \frac{12}{2} = 6A$

$i + i_1 - 4 = 0$ or $i = 4 - 6 = -2A$

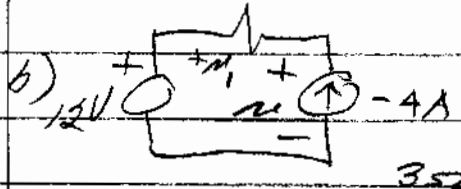

$v_1 = -(-4) \times 3 = 12V$


$-12 + v_1 + v_2 = 0$ ∴ $v_2 = 0$

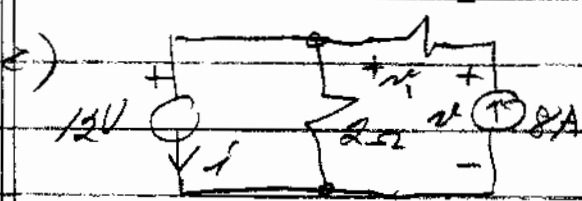

$v_1 = -3 \times 8 = -24V$

$-12 + v_1 + v_2 = 0$ ∴ $v_2 = 36V$

$i = 8 - \frac{12}{2} = 2A$

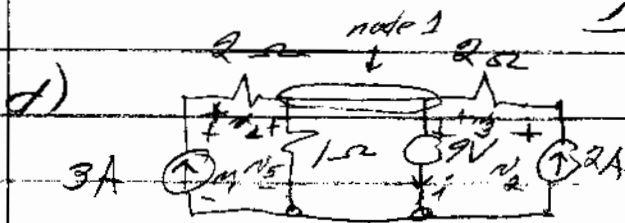

$-9 + v_3 + v_2 = 0$ but $v_3 = -2 \times 2 = -4$


∴ $v_2 = 9 - v_3 = 13V$

KCL @ node 1 $3 - 11 - i + 2 = 0$

$\begin{cases} v_4 = 2 \times 3 = 6V \\ v_5 = 11V \end{cases}$ $-v_1 + v_4 + v_3 + v_2 = 0$ ∴ $v_1 = 15$

$i = -4A$

143 a) $K = -3$

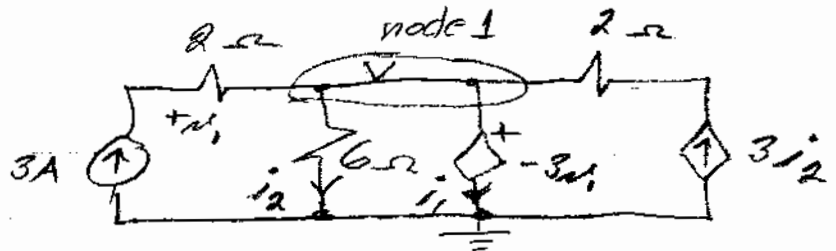

$V_1 = 6V$ $\therefore -3i_1 = -18V$ so $i_2 = \frac{-3i_1}{6} = -3A$

KCL @ node 1 $\begin{cases} -3 + i_2 + i_1 - 3i_2 = 0 \\ -3 - 3 + i_1 - 3(-3) = 0 \end{cases}$


$i_1 = -3A$ ←

Node Voltage Solution

$-3 + \frac{V}{6} + i_1 - 3i_2 = 0 \Rightarrow -3 + \frac{V}{6} + i_1 - 3\frac{V}{6} = 0$

so $i_1 = 3 + V(\frac{1}{6} - \frac{1}{2}) = 3 + (-3i_1)\frac{1}{3}$ but $i_1 = 6$

$\therefore i_1 = 3 - 6 = -3A$ ←

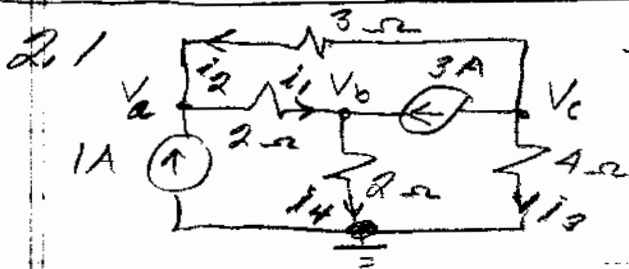

Node Equations

$-1 + \frac{V_a - V_b}{2} + \frac{V_b - V_c}{3} = 0$

$\frac{V_b - V_a}{2} + \frac{V_b}{3} = 3$

$\frac{V_c - V_a}{3} + \frac{V_c}{4} = -3$

or $\begin{cases} \frac{1}{2}(V_a) - \frac{1}{2}V_b - \frac{1}{3}V_c = 1 \\ -\frac{1}{2}V_a + V_b = 3 \\ -\frac{V_a}{3} + V_c(\frac{7}{12}) = -3 \end{cases} \Rightarrow \begin{cases} 5V_a - 3V_b - 2V_c = 6 \\ -V_a + 2V_b = 6 \\ -4V_a + 7V_c = -36 \end{cases}$

$V_a = \frac{1}{33} \begin{vmatrix} 6 & -3 & -2 \\ 6 & 2 & 6 \\ -36 & 0 & 7 \end{vmatrix} = \frac{-36(4) + 7(12+18)}{-4(4) + 7(10-3)} = \frac{-144 + 210}{-16 + 49} = \frac{66}{33} = 2V$

$V_b = \frac{1}{33} \begin{vmatrix} 5 & -3 & -2 \\ -1 & 2 & 0 \\ -4 & 0 & 7 \end{vmatrix} = \frac{-2(36+24) + 7(30+6)}{33} = \frac{-120 + 252}{33} = 4V$

$V_c = \frac{1}{33} \begin{vmatrix} 5 & -3 & 6 \\ -1 & 2 & 6 \\ -4 & 0 & -36 \end{vmatrix} = \frac{-4(-18-12) - 36(10-3)}{33} = \frac{120 - 252}{33} = -4V$

2.1

$$b) i_1 = \frac{V_c - V_b}{2} = \boxed{-1 A}$$


$$i_2 = \frac{V_c - V_a}{3} = \frac{-6}{3} = \boxed{-2 A}$$

$$i_3 = \frac{V_c}{4} = \boxed{-1 A}$$

$$i_4 = \frac{V_b}{2} = \boxed{2 A}$$

ES 332

Homework 4

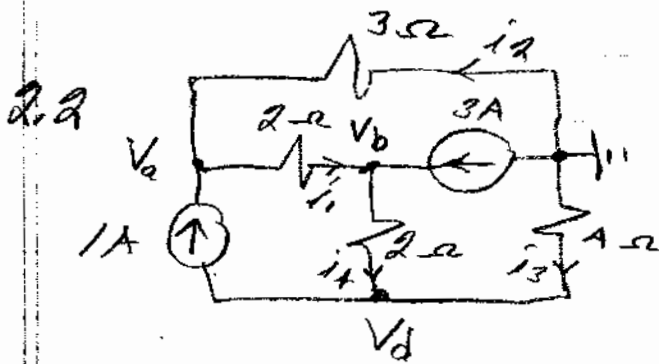

$$\frac{V_a}{3} + \frac{V_b - V_d}{2} = 1$$

$$\frac{V_b - V_d}{2} + \frac{V_b - V_d}{2} = 3$$

$$\frac{V_d - V_b}{2} + \frac{V_d}{4} = -1$$

or

$$\left. \begin{aligned} V_a \frac{5}{6} - V_b \frac{1}{2} &= 1 \\ -V_a \frac{1}{2} + V_b - \frac{V_d}{2} &= 3 \\ -V_b \frac{1}{2} + V_d \frac{3}{4} &= -1 \end{aligned} \right\} \begin{aligned} 5V_a - 3V_b &= 6 \\ -V_a + 2V_b - V_d &= 6 \\ -2V_b + 3V_d &= -4 \end{aligned}$$

$$V_a = \frac{\begin{vmatrix} 6 & -3 & 0 \\ 6 & 2 & -1 \\ -4 & -2 & 3 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & 0 \\ -1 & 2 & -1 \\ 0 & -2 & 3 \end{vmatrix}} = \frac{6(6-2) + 3(18-4)}{5(6-2) + 3(-3)} = \frac{66}{11} = \boxed{6V}$$

$$V_b = \frac{1}{11} \begin{vmatrix} 5 & 6 & 0 \\ -1 & 6 & -1 \\ 0 & -4 & 3 \end{vmatrix} = \frac{1}{11} \{ 5(18-4) - 6(-3) \} = \boxed{8V}$$

$$V_d = \frac{1}{11} \begin{vmatrix} 5 & -3 & 6 \\ -1 & 2 & 6 \\ 0 & -2 & -4 \end{vmatrix} = \frac{1}{11} \{ 5(-8+12) + 1(18+12) \} = \boxed{4V}$$


so

$$i_1 = \frac{V_b - V_d}{2} = \boxed{-1A}$$

$$i_2 = -\frac{V_a}{3} = \boxed{-2A}$$

$$i_3 = -\frac{V_d}{4} = \boxed{-1A}$$
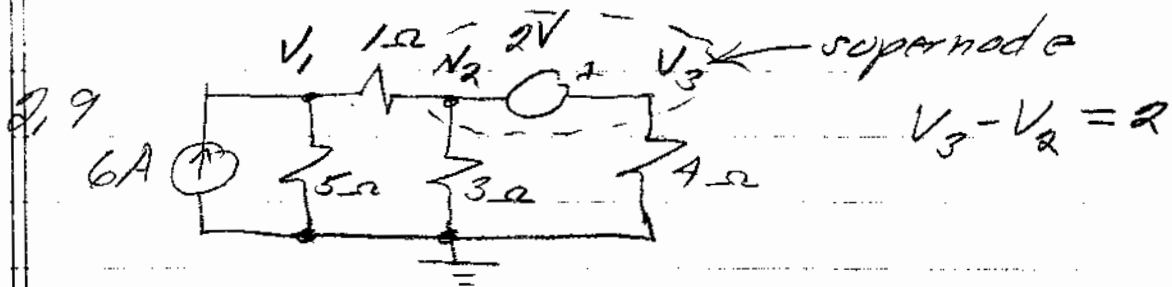
$$i_4 = \frac{V_b - V_d}{2} = \boxed{2A}$$



$$\left. \begin{aligned} \frac{V_1}{5} + \frac{V_1 - V_2}{1} &= 6 \\ \frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_3}{4} &= 0 \end{aligned} \right\} \begin{aligned} \frac{6}{5}V_1 - V_2 &= 6 \\ -V_1 + \left(\frac{1}{3} + \frac{1}{4}\right)V_2 &= -\frac{1}{2} \end{aligned}$$

$\frac{19}{12}$

or

$$\begin{cases} 6V_1 - 5V_2 = 30 \\ -12V_1 + 19V_2 = -6 \end{cases}$$

$$V_1 = \frac{\begin{vmatrix} 30 & -5 \\ -6 & 19 \end{vmatrix}}{\begin{vmatrix} 6 & -5 \\ -12 & 19 \end{vmatrix}} = \frac{540}{54} = \boxed{10V}$$


$$V_2 = \frac{\begin{vmatrix} 6 & 30 \\ -12 & -6 \end{vmatrix}}{54} = \frac{324}{54} = \boxed{6V}$$

$$V_3 = V_2 + 2 = \boxed{8V}$$

FS 332

Homework 5

2.10

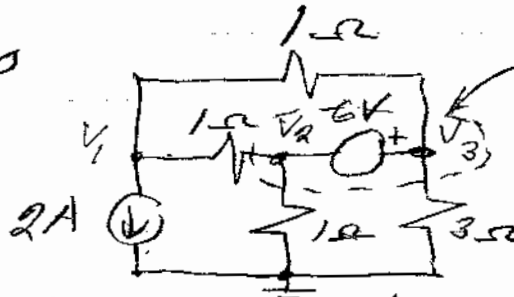

supernode $\Rightarrow V_3 - V_2 = 6$

$$\frac{V_3 - V_2}{1} + \frac{V_1 - V_3}{1} = -2$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{1} + \frac{V_2 - V_1}{1} + \frac{V_3}{3} = 0$$


$$\text{or } \left. \begin{aligned} 2V_1 - V_2 - V_3 &= -2 \\ -2V_1 + 2V_2 + \frac{4}{3}V_3 &= 0 \\ -V_2 + V_3 &= 6 \end{aligned} \right\} \begin{aligned} 2V_1 - 2V_2 &= 4 \\ -2V_1 + \frac{10}{3}V_2 &= -8 \end{aligned}$$

$$V_1 = \frac{\begin{vmatrix} 4 & -2 \\ -8 & \frac{10}{3} \end{vmatrix}}{\begin{vmatrix} 2 & -2 \\ -2 & \frac{10}{3} \end{vmatrix}} = \frac{\frac{40}{3} - 16}{\frac{20}{3} - 4} = \frac{40 - 48}{20 - 12} = \frac{-8}{8} = \boxed{-1V}$$

$$V_2 = \frac{\begin{vmatrix} 2 & 4 \\ -2 & -8 \end{vmatrix}}{\frac{8}{3}} = \frac{-16 + 8}{\frac{8}{3}} = \boxed{-3V}$$

$$V_3 = V_2 + 6 = \boxed{3V}$$

2.19

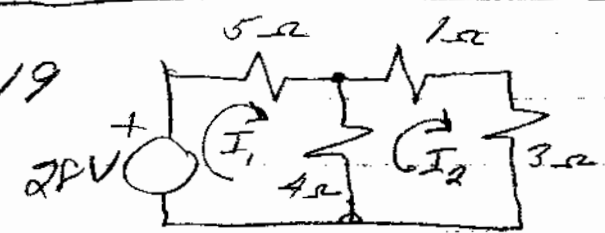

$$5I_1 + 4(I_1 - I_2) = 20$$

$$4(I_2 - I_1) + 4I_2 = 0$$


$$\text{or } \left\{ \begin{aligned} 9I_1 - 4I_2 &= 20 \\ -4I_1 + 8I_2 &= 0 \end{aligned} \right.$$

$$I_1 = \frac{\begin{vmatrix} 20 & -4 \\ 0 & 8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -4 & 8 \end{vmatrix}} = \frac{20 \cdot 8}{72 - 16} = \frac{224}{56} = \boxed{4A}$$

$$I_2 = \frac{\begin{vmatrix} 9 & 20 \\ -4 & 0 \end{vmatrix}}{56} = \frac{4 \cdot 20}{56} = \boxed{2A}$$

ES 332

Homework 6

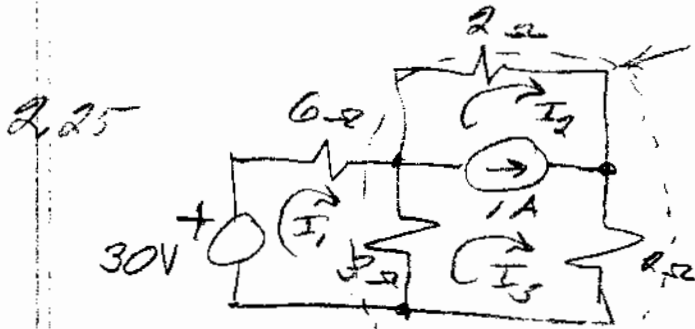

supermesh $\Rightarrow I_3 - I_2 = 1$

$$6I_1 + 3(I_1 - I_3) = 30$$

$$3(I_3 - I_1) + 2I_2 + 2I_3 = 0$$

$$\begin{cases} 9I_1 - 3I_3 = 30 \\ -3I_1 + 2I_2 + 5I_3 = 0 \\ -I_2 + I_3 = 1 \end{cases} \Rightarrow \begin{cases} 9I_1 - 3I_2 = 33 \\ -3I_1 + 7I_2 = -5 \end{cases}$$

$$I_1 = \frac{\begin{vmatrix} 33 & -3 \\ -5 & 7 \end{vmatrix}}{\begin{vmatrix} 9 & -3 \\ -3 & 7 \end{vmatrix}} = \frac{231 - 15}{63 - 9} = \frac{216}{54} = \boxed{4A}$$

$$I_2 = \frac{\begin{vmatrix} 9 & 33 \\ -3 & -5 \end{vmatrix}}{54} = \frac{-45 + 99}{54} = \boxed{1A}$$

$$I_3 = 1 + I_2 = \boxed{2A}$$



$N(0) = 12$

$$\frac{N}{5} + \frac{1}{10} \frac{dN}{dt} = 0$$



or $\frac{dN}{dt} + 2N = 0$; $N = Ae^{st}$; $s = -2$

but $N(0) = 12$

$$N = 12e^{-2t}$$

$$i(t) = C \frac{dN}{dt} = \frac{1}{10} 12(-2)e^{-2t} = \boxed{-\frac{12}{5}e^{-2t}}$$


$N(0) = 12$

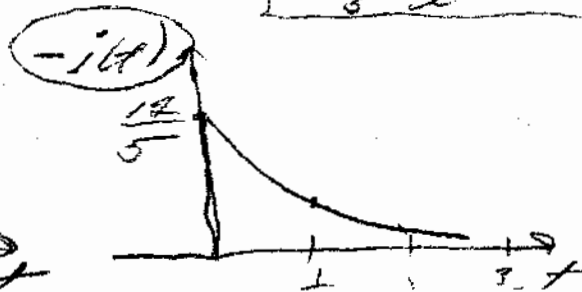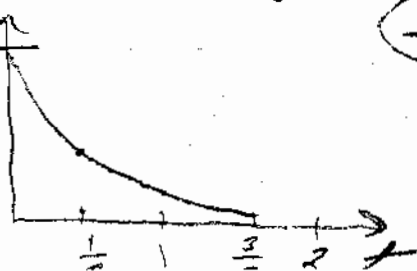

3.29
3.34

ES 332



Homework 7

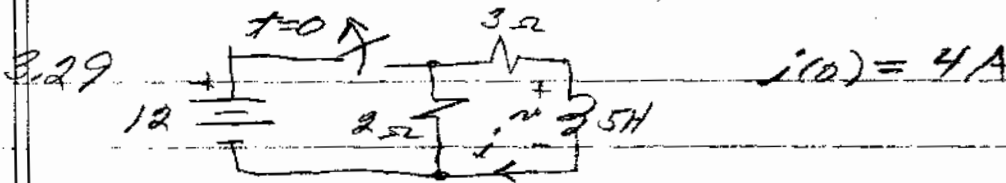

for $t > 0$ $5i + 5 \frac{di}{dt} = 0$; $i = A e^{st}$ so $s = -1$


and since $i(0) = 4$ $i(t) = 4e^{-t}$

$v(t) = -5i(t) = -20e^{-t}$

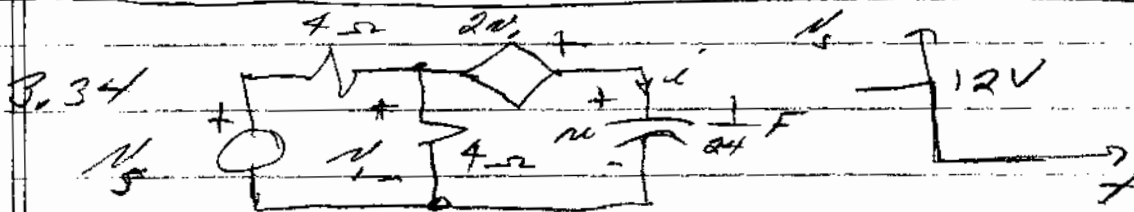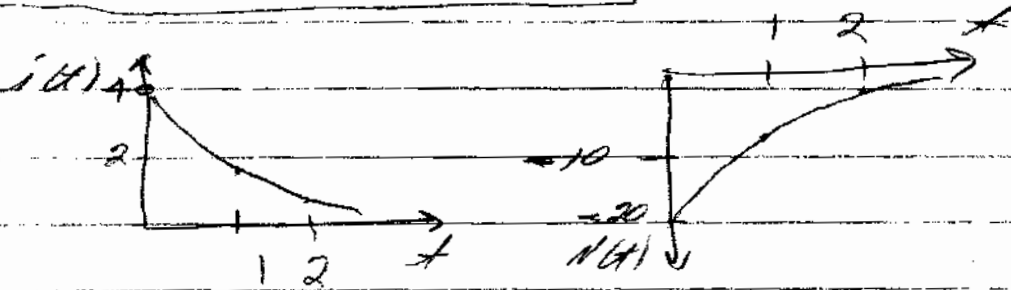

for $t < 0$ $i = 0$ so $v_c = \frac{12}{2} = 6V$

$v(0) = 3v_c(0) = 18V$

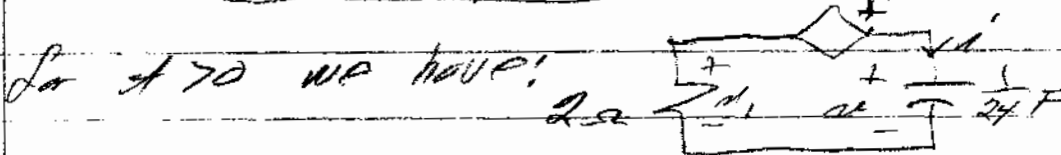


$2i' - 2i' + 24 \int_0^t i' dt + 18 = 0$ but $v_c = -2i'$


(1) so $2i' + 4i' + 24 \int_0^t i' dt + 18 = 0$ or $6 \frac{di'}{dt} + 24i' = 0$

$i' = A e^{st}$; $s = -4$ from (1) $i'(0) = -3$

so $i(t) = -3e^{-4t}$

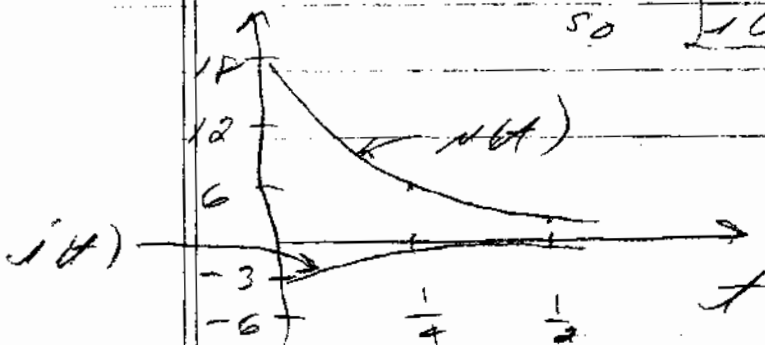

$v(t) = 3v_c = -6i' = 18e^{-4t}$

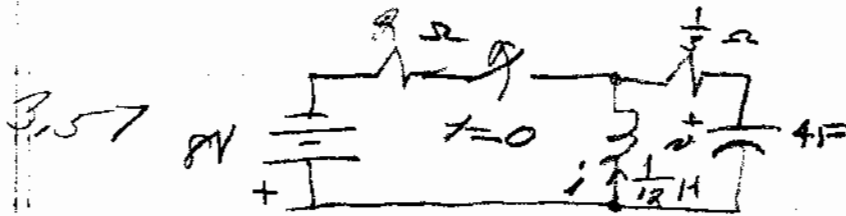

$v(0) = 0$
 $i(0) = 4A$

For $t > 0$ $\frac{1}{3}i + \frac{1}{4} \int_0^t i dt + \frac{1}{12} \frac{di}{dt} = 0$ (1)


or $\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 3i = 0$; $i = A e^{st}$; $s_{1,2} = \frac{-4 \pm \sqrt{16-12}}{2}$

$i = A_1 e^{-3t} + A_2 e^{-t}$ but $i(0) = 4$ so $4 = A_1 + A_2$

From (1) $\left. \frac{di}{dt} \right|_{t=0} = -\frac{4}{2} = -16 = -3A_1 - A_2 = -3A_1 - (4 - A_1)$

$A_1 = 6$ + $A_2 = 4 - 6 = -2$
 $i(t) = 6e^{-3t} - 2e^{-t}$

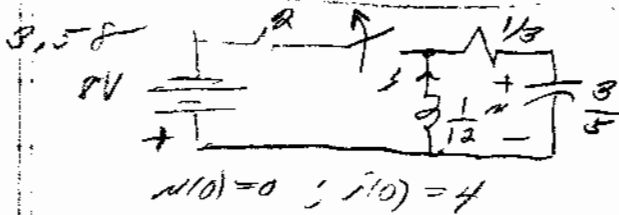$v = -\frac{1}{2}i - \frac{1}{12} \frac{di}{dt}$
 $v = -2e^{-3t} + \frac{2}{3}e^{-t} - \frac{1}{12}(-18e^{-3t} + 2e^{-t}) = -\frac{1}{2}e^{-3t} + \frac{1}{2}e^{-t}$



$v(0) = 0$; $i(0) = 4$

$\frac{1}{3}i + \frac{1}{12} \frac{di}{dt} + \frac{5}{3} \int_0^t i dt = 0$ (1)

$\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 20i = 0$; $i = A e^{st}$

$s_{1,2} = \frac{-4 \pm \sqrt{16-80}}{2} = -2 \pm j4$

so $i(t) = A_1 e^{-2t} \cos 4t + A_2 e^{-2t} \sin 4t$

but $i(0) = 4$ so $4 = A_1$


From (1) $\left. \frac{di}{dt} \right|_{t=0} = -16 = 4(-2) + 4A_2$ so $A_2 = -2$

$i(t) = 4e^{-2t} \cos 4t - 2e^{-2t} \sin 4t$


as above $v(t) = -\frac{1}{3}i - \frac{1}{12} \frac{di}{dt}$

giving $v(t) = \frac{5}{3} e^{-2t} \sin 4t$ A

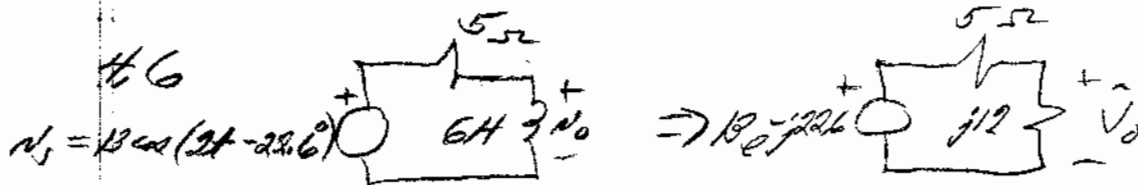- 4.1 a) $4 + j7 = 8.06 e^{j60.25^\circ}$ e) $4 = 4 e^{j0^\circ}$
 b) $3 - j5 = 5.83 e^{j-59.04^\circ}$ f) $-5 = 5 e^{j180^\circ}$
 c) $-2 + j3 = 3.6 e^{j123.7^\circ}$ g) $j7 = 7 e^{j90^\circ}$
 d) $-1 - j6 = 6.08 e^{j260.5^\circ}$ h) $-j2 = 2 e^{-j90^\circ}$



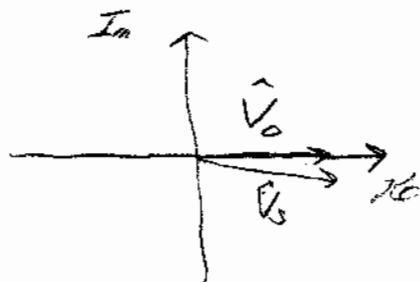
$$\hat{V}_o = \frac{j12}{5 + j12} \cdot 13 e^{-j22.6^\circ} = \frac{156 e^{j67.4^\circ}}{13 e^{j67.38^\circ}} = 12$$



\hat{V}_o leads \hat{V}_s

$i_o(t) = 12 \cos(2t)$

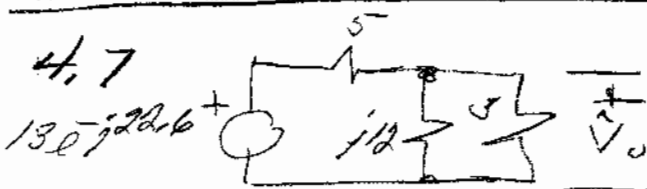


$$Z_{eq} = \frac{j60}{5 + j12}$$

$$\hat{V}_o = \frac{Z_{eq}}{5 + Z_{eq}} \cdot 13 e^{-j22.6^\circ} = \frac{j60 \cdot 13 e^{-j22.6^\circ}}{25 + j60 + j60} = \frac{j60 \hat{V}_s}{25 + j120} = \frac{j12 \hat{V}_s}{5 + j24}$$

$$\hat{V}_o = \frac{12 e^{j90^\circ} 13 e^{-j22.6^\circ}}{24.513 e^{j78.93^\circ}} = 6.36 e^{-j10.83^\circ}$$

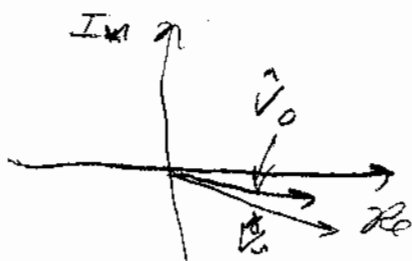
or $i_o(t) = 12 \cos\{2t - 10.83^\circ\}$



\hat{V}_o leads \hat{V}_s

4.9
4.24

ES 332 Homework 10

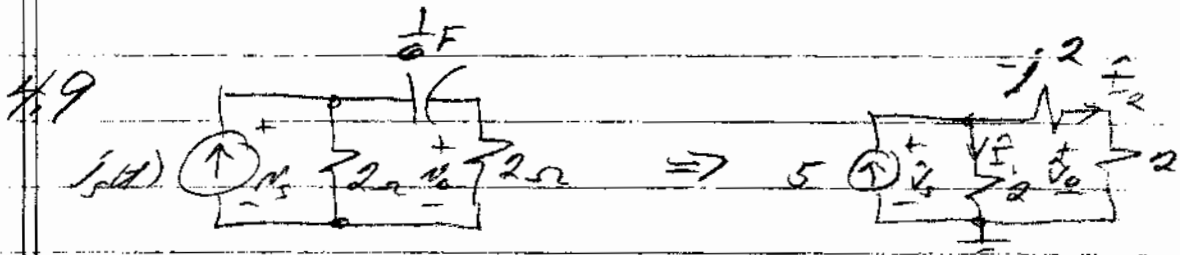


$i_s(t) = 5 \cos 3t$

$\hat{I}_1 = 5 \frac{2-j2}{4-j2} \therefore \hat{V}_s = 10 \frac{1-j}{2-j} = 10 \frac{\sqrt{2} \angle -45^\circ}{\sqrt{5} \angle -63.4^\circ} = 6.32 \angle -18.4^\circ$

or $v_s(t) = 6.32 \cos(3t - 18.4^\circ)$

$\hat{I}_2 = 5 \frac{2}{4-j2} \therefore \hat{V}_s = 10 \frac{1}{2-j} = \frac{10}{\sqrt{5}} \angle 26.56^\circ$

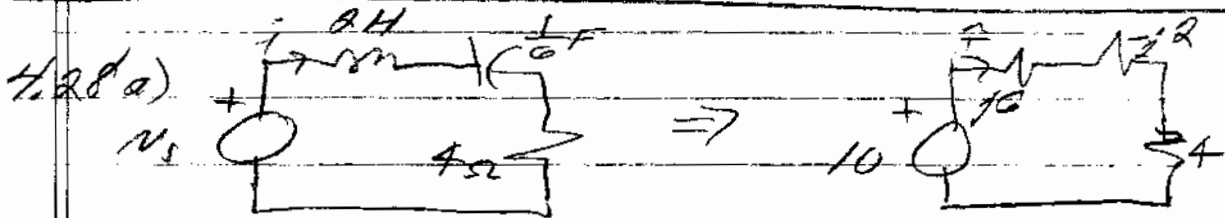or $v_s(t) = 4.472 \cos(3t + 26.56^\circ)$



$i_s(t) = 10 \cos 3t$


$\hat{I} = \frac{10}{4+j4} = \frac{10}{4\sqrt{2} \angle 45^\circ} = 1.767 \angle -45^\circ$

$\therefore P_{avg} = \frac{1}{2} |\hat{I}|^2 4 = 6.25 \text{ Watts}$

ES 332

Homework 11

20 Arms (pf = 0.75 lagging)

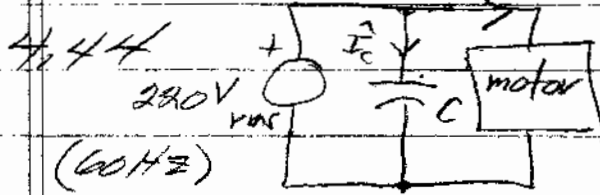

a) $P_{ave} = V_{rms} I_{rms} pf$


$\therefore P_{ave} = 280 \times 20 \times 0.75 = 3,300 W$

b) $I_{rms} = 20 \angle^{-\cos^{-1}(0.75)} = 20 \angle^{-41.41^\circ} = 15 - j13.23$

so for pf = 1 $I_c = +j13.23 = j\omega C \cdot 280$

$\therefore C = \frac{13.23}{2\pi \times 60 \times 280} = 1.595 \times 10^{-4} \approx 160 \mu F$

2.30

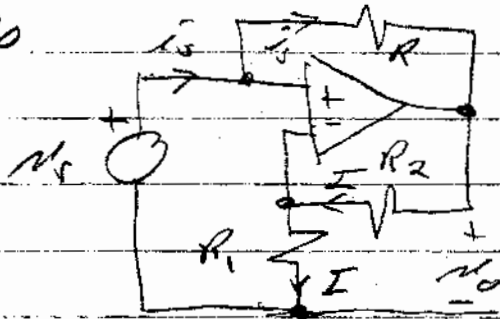

a) $I = \frac{N_s}{R_1}$; $N_o = I(R_1 + R_2)$

$\therefore N_o = \frac{N_s}{R_1} (R_1 + R_2)$

$N_o = N_s \left(1 + \frac{R_2}{R_1}\right)$

b) $I_s = \frac{N_s - N_o}{R} = \frac{N_s}{R} - \frac{N_s \left(1 + \frac{R_2}{R_1}\right)}{R}$


$I_s = N_s \left[\frac{1}{R} - \frac{R_1 + R_2}{RR_1} \right] = N_s \left[\frac{R_1 - R_1 - R_2}{RR_1} \right]$

$\therefore \frac{N_s}{I_s} = - \frac{RR_1}{R_2}$

ES 332

Homework 12

Q-28

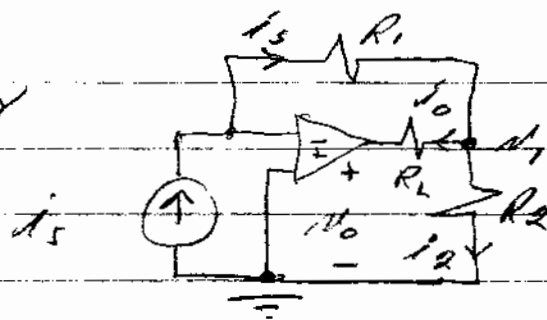


$$v_1 = -i_o R_1$$

$$i_2 = \frac{v_1}{R_2}$$

$$i_o = i_s - i_2 = i_s - \frac{v_1}{R_2} = i_s + i_s \frac{R_1}{R_2} = i_s \left(1 + \frac{R_1}{R_2}\right) \leftarrow$$

$$v_o = -i_o R_2 + v_1 = -i_s R_2 \left(1 + \frac{R_1}{R_2}\right) - i_s R_1 = -i_s \left(R_1 + R_2 + \frac{R_1 R_2}{R_2}\right) \leftarrow$$

Q-35

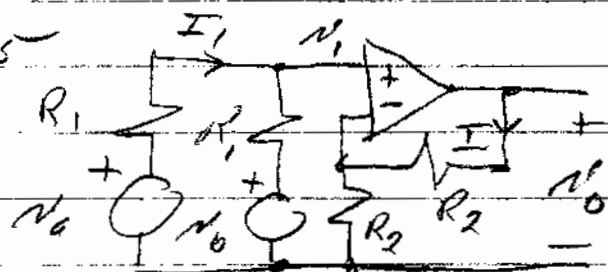

$$I = \frac{v_0'}{2R_2}$$

$$v_1 = \frac{v_0'}{2} \quad (1)$$


$$-v_0 + I R_1 + I R_1 + v_0' = 0 \quad \therefore I = \frac{v_0' - v_0}{2R_1}$$

$$v_1 = I R_1 + v_0' = \frac{v_0' - v_0}{2} + v_0' = \frac{v_0' + v_0}{2}$$


\therefore from (1) above $v_0' = 2v_1 = v_0 + v_0' \leftarrow$

10.67


$$N_1 = V_r > 0$$

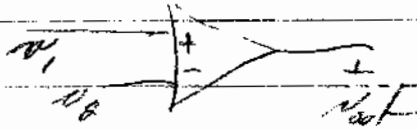

a)

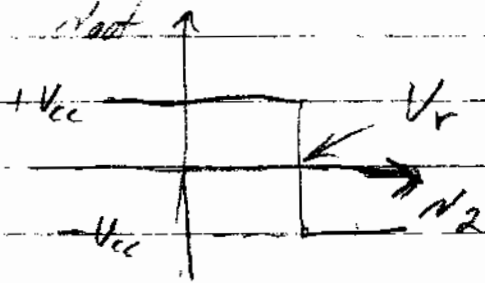


b)

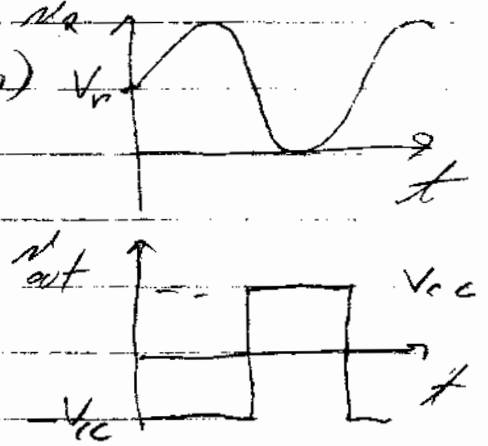

11.26

A	B	$A \oplus B = A + B = F = \overline{A} \overline{B} + AB$
0	0	1
0	1	0
1	0	0
1	1	1

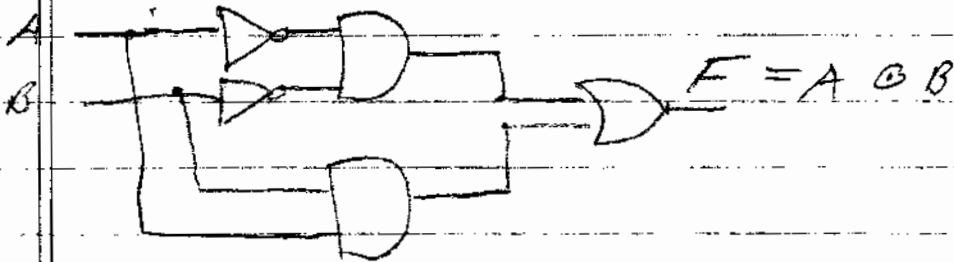


11.44

A	B	C	F	m	M
0	0	0	0	m_0	M_0
0	0	1	0	m_1	M_1
0	1	0	0	m_2	M_2
0	1	1	1	m_3	M_3
1	0	0	0	m_4	M_4
1	0	1	1	m_5	M_5
1	1	0	1	m_6	M_6
1	1	1	1	m_7	M_7

$$F = M_0 \cdot M_1 \cdot M_2 \cdot M_4 = (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (\bar{A}+B+C)$$
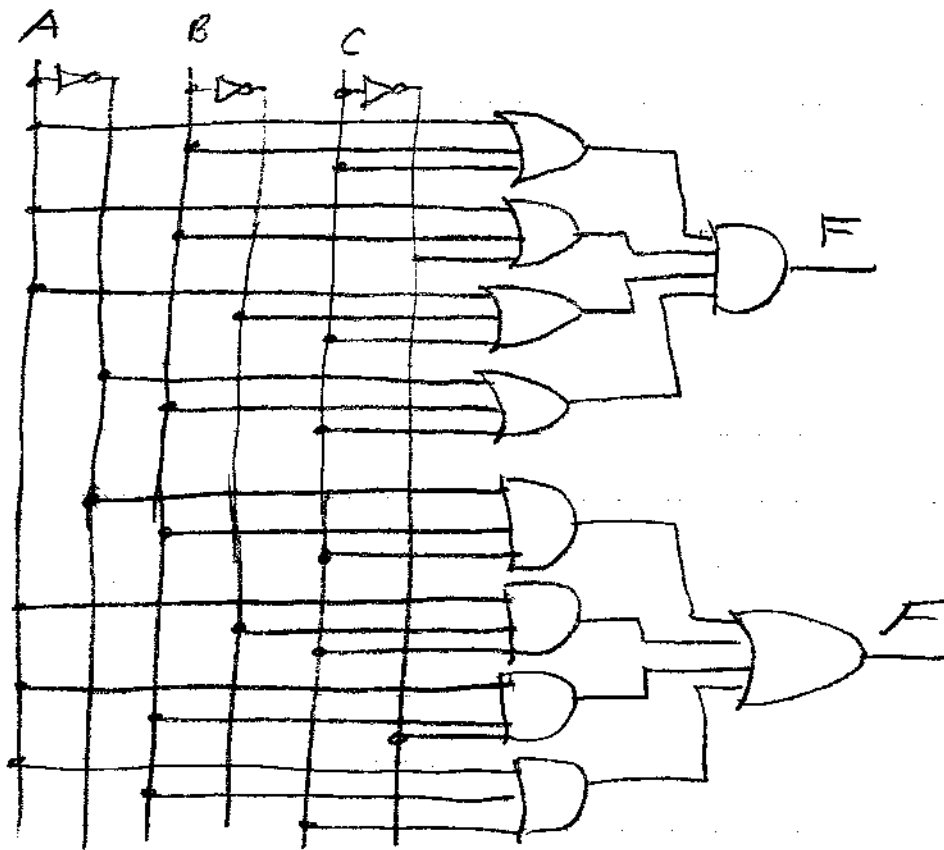
$$F = m_3 + m_5 + m_6 + m_7 = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$



11.53 a) A

	BC			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

$$F = A\bar{B} + \bar{B}C + \bar{A}B$$

b) A

	BC			
	00	01	11	10
0	0	0	0	1
1	1	0	1	1

$$F = A\bar{C} + AB + B\bar{C}$$

c) A

	BC			
	00	01	11	10
0	1	1	1	1
1	0	1	0	1

$$F = \bar{A} + \bar{B}C + B\bar{C}$$

11.54

11.54 a) A

	BC			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

$$F = (\bar{B} + \bar{A})(A + B + C)$$

b)

	BC			
	00	01	11	10
0	0	0	0	1
1	1	0	1	1

$$F = (A + B) \cdot (A + \bar{C}) \cdot (B + \bar{C})$$

c)

	BC			
	00	01	11	10
0	1	1	1	1
1	0	1	0	1

$$F = (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

11.56

a) A

	BC			
	00	01	11	10
0	0	0	0	1
1	1	0	0	0

$$F = B\bar{C} + A\bar{C}$$

b)

	BC			
	00	01	11	10
0	1	0	0	0
1	1	1	1	1

$$F = A + \bar{B}\bar{C}$$

c)

	BC			
	00	01	11	10
0	1	0	1	1
1	1	0	0	0

$$F = \bar{B}\bar{C} + \bar{A}B$$

1157 a)

		CD			
AB		00	01	11	10
00		0	0	0	0
01		1	1	1	1
11		0	1	1	1
10		0	0	0	1

$$F = \bar{A}B + BD + AC\bar{C}$$

b)

		CD			
AB		00	01	11	10
00		0	1	1	1
01		0	0	0	1
11		0	1	0	1
10		0	1	1	1

$$F = \bar{B}D + C\bar{C} + AC\bar{C}$$

c)

		CD			
AB		00	01	11	10
00		1	0	1	0
01		0	0	1	1
11		0	1	0	1
10		1	0	0	1

$$F = \bar{B}\bar{C}\bar{D} + AC\bar{C} + \bar{A}BC + \bar{A}CD + AB\bar{C}D$$

many possible combinations

12.17

ABC	D	E	F
000	0	0	0
001	0	0	1
010	0	1	1
011	0	1	0
100	1	1	0
101	1	1	1
110	1	0	1
111	1	0	0

D)

		BC			
A		00	01	11	10
0		0	0	0	0
1		1	1	1	1

$$D = A$$

E)

		BC			
A		00	01	11	10
0		0	0	1	1
1		1	1	0	0

$$E = \bar{A}B + A\bar{B}$$


$$E = A \oplus B$$

F)

		BC			
A		00	01	11	10
0		0	1	0	1
1		0	1	0	1


$$F = \bar{B}C + B\bar{C}$$

$$F = B \oplus C$$

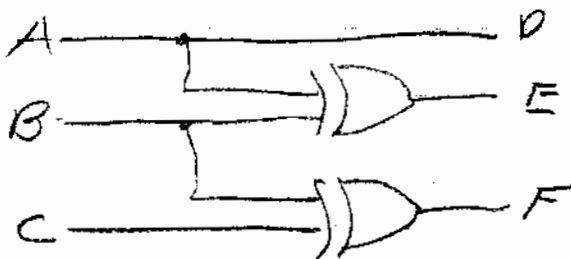

Assignment 17

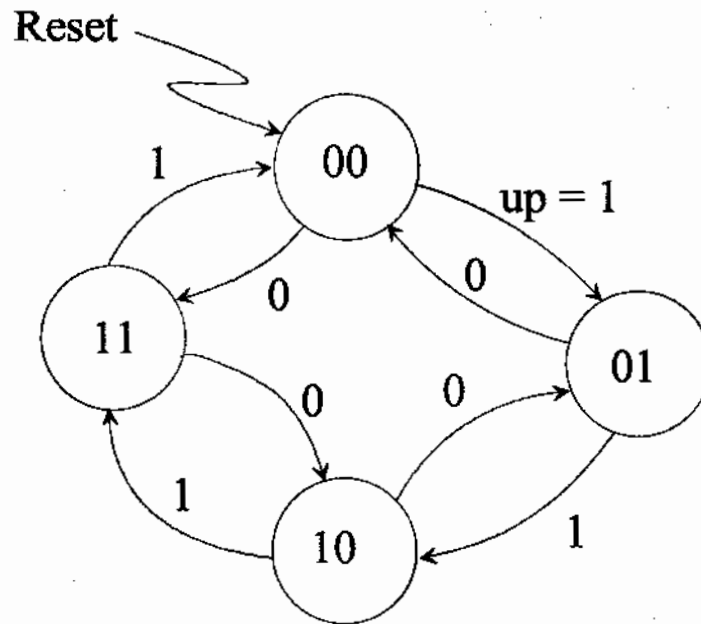- a) Draw a state transition table for the two bit up-down counter described by the state diagram shown below.
- b) If this counter is to be realized using D flip-flops add the D inputs necessary to produce the proper state transitions to your transition table.
- c) Find minimized Boolean expressions that will produce the necessary D inputs found in b).
- d) Draw a logic circuit that realizes this two bit up down counter.



a)

Up	Present		Next		D ₀	D ₁
	Q ₀	Q ₁	Q ₀ ⁺	Q ₁ ⁺		
1	0	0	0	1	0	1
1	0	1	1	0	1	0
1	1	0	1	1	1	0
1	1	1	0	0	0	0
0	0	0	1	1	1	1
0	1	0	1	0	1	0
0	1	1	0	1	0	1
0	0	1	0	0	0	0

(D₀)

Up	Q ₀ Q ₁			
	00	01	11	10
0	1	0	1	0
1	0	1	0	1

(D₁)


Up	Q ₀ Q ₁			
	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$$D_0 = \bar{U}_p \bar{Q}_0 \bar{Q}_1 + \bar{U}_p Q_0 Q_1 + U_p \bar{Q}_0 Q_1 + U_p Q_0 \bar{Q}_1$$

$$D_1 = \bar{Q}_1$$

$$D_0 = \bar{U}_p (\bar{Q}_0 \bar{Q}_1 + Q_0 Q_1) + U_p (\bar{Q}_0 Q_1 + Q_0 \bar{Q}_1)$$


$$D_0 = \bar{U}_p (\overline{Q_0 \oplus Q_1}) + U_p (Q_0 \oplus Q_1) = U_p \oplus (Q_0 \oplus Q_1) \leftarrow$$

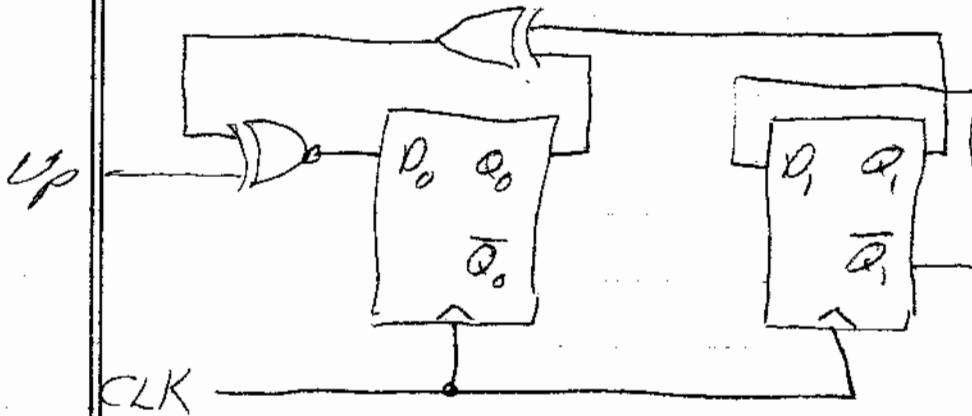

ES 332




Homework 18

18.3

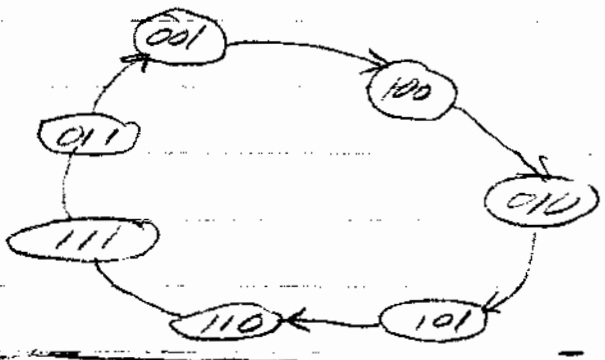

Present Next

Q_0	Q_1	Q_2	Q_0^+	Q_1^+	Q_2^+	D_0, D_1, D_2
0	0	0	0	0	0	0 0 0
0	0	1	1	0	0	1 0 0
1	0	0	0	1	0	0 1 0
0	1	0	1	0	1	1 0 1
1	0	1	1	1	0	1 1 0
1	1	0	1	1	1	1 1 1
1	1	1	0	1	1	0 1 1
0	1	1	0	0	1	0 0 1

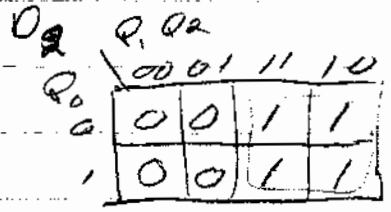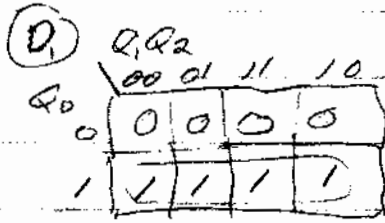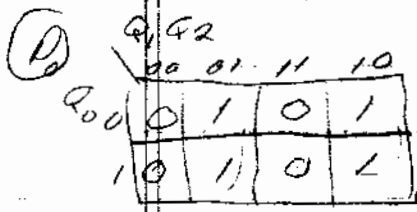

$D_0 = \bar{Q}_1 Q_2 + Q_1 \bar{Q}_2$

$D_1 = Q_0$

$D_2 = Q_1$

$D_0 = Q_1 \oplus Q_2$

