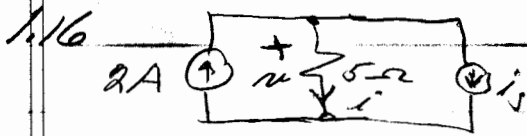


1.7 a) $v_1 = 5i_1 = 20 \text{ Volts}$ ✓

b) $v_2 = -4i_2 = 8 \text{ Volts}$ ✓

c) $v_3 = -3i_3 = -6 \text{ Volts}$

d) $v_4 = i_4 = -2 \text{ Volts}$




a) $i_s = 1 \Rightarrow i = 1$ and $v = 5V$

b) $i_s = 2 \Rightarrow i = 0$ and $v = 0V$

c) $i_s = 3 \Rightarrow i = -1$ and $v = -5V$

$i = 2 - i_s$

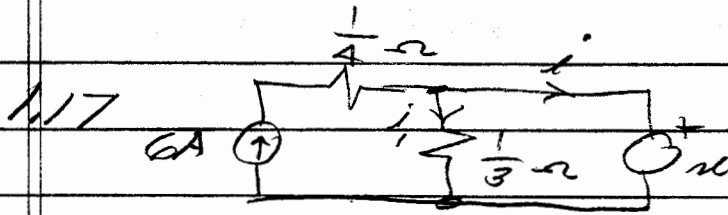

a) $n=1$

$i = 6 - i_1 = 6 - 3A$

$\therefore i = 3 \text{ Amperes}$ ←

b) $n=2$


\therefore

$i = 6 - 6 = 0 \text{ Amperes}$ ←

c) $n=3$

\therefore

$i = 6 - 9 = -3 \text{ Amperes}$ ←

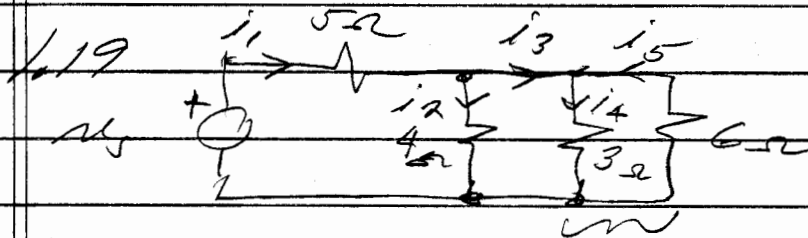

$i_1 = 6$


$R_{eq} = \frac{3 \times 6}{9} = 2 \Omega$

$\therefore i_2 = 6 \frac{2}{6} = 2 \text{ Amperes}$ ←

$i_3 = 6 \frac{4}{6} = 4 \text{ Amperes}$ ←

$i_4 = i_3 \frac{6}{9} = \frac{8}{3} \text{ Amperes}$ ←

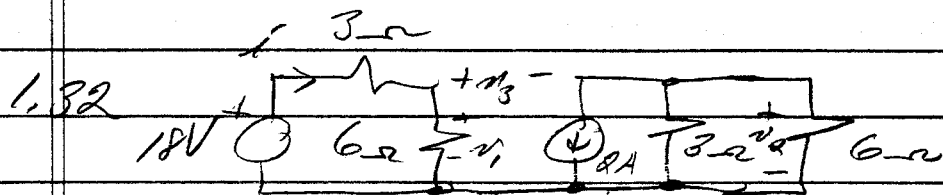$i_5 = -i_3 \frac{3}{9} = -\frac{4}{3}$ ←




a) $i = \frac{18}{9} = 2A$

$v_1 = 2 \times 6 = 18V$

$v_2 = -2 \times \frac{18}{9} = -4V$

$v_3 = v_1 - v_2 = 22V$

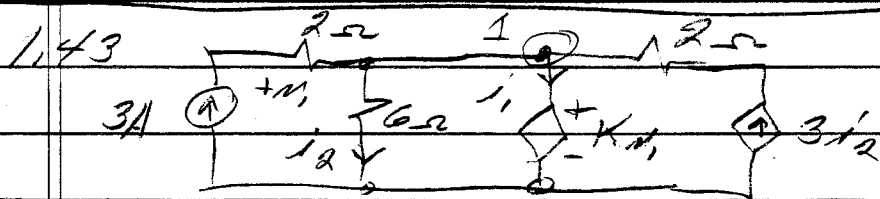b) $i, v_1, \text{ and } v_2$ are the same!




a) $K = -3$; $v_1 = 6 \text{ Volts}$ $\therefore K v_1 = -18$

so $i_2 = \frac{K v_1}{6} = -3$; KCL @ node 1 $-3 + i_2 + i_1 - 3i_2 = 0$

$\therefore i_1 = 2i_2 + 3 = -6 + 3 = -3A$

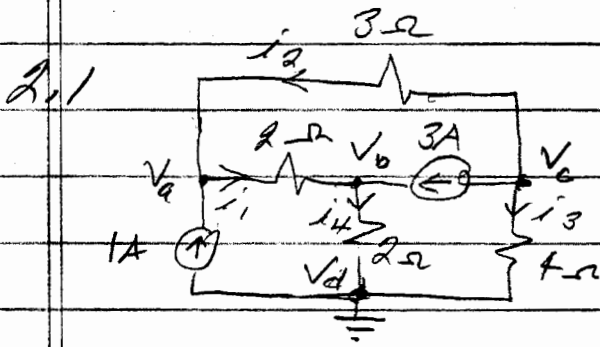Node Voltages $-3 + i_2 + i_1 - 3i_2 = 0$
 or $i_1 = 3 + 2i_2 = 3 + 2 \frac{K v_1}{6} = 3 + \frac{(-3) 6}{3}$
 $i_1 = -3A$



$$\frac{V_a - V_b}{2} + \frac{V_a - V_c}{3} = 1$$

$$\frac{V_b - V_a}{2} + \frac{V_b}{2} = 3$$

$$\frac{V_c - V_a}{3} + \frac{V_c}{4} = -3$$

$$\text{or } V_a \left(\frac{5}{6}\right) - V_b \left(\frac{1}{2}\right) - V_c \left(\frac{1}{3}\right) = 1$$

$$-V_a \left(\frac{1}{2}\right) + V_b = 3$$

$$-V_a \left(\frac{1}{3}\right) + V_c \left(\frac{7}{12}\right) = -3$$

$$5V_a - 3V_b - 2V_c = 6$$

$$-V_a + 2V_b = 6$$

$$-4V_a + 7V_c = -36$$

a)
$$V_b = \frac{\begin{vmatrix} 5 & 6 & -2 \\ -1 & 6 & 0 \\ -4 & -36 & 7 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & -2 \\ -1 & 2 & 0 \\ -4 & 0 & 7 \end{vmatrix}} = \frac{-2(36+24) + 7(30+6)}{-2(8) + 7(10-3)} = \frac{132}{33} = 4 \text{ V}$$

$$V_a = \frac{\begin{vmatrix} 6 & -3 & -2 \\ 0 & 2 & 0 \\ -36 & 0 & 7 \end{vmatrix}}{33} = \frac{-2(72) + 7(12+48)}{33} = \frac{210}{33} = 2 \text{ V}$$


$$V_c = \frac{\begin{vmatrix} 5 & -3 & 6 \\ -1 & 2 & 6 \\ -4 & 0 & -36 \end{vmatrix}}{33} = \frac{-4(-18-12) - 36(10-3)}{33} = \frac{-4}{33} \text{ V}$$

b)
$$i_1 = \frac{V_a - V_b}{2} = -1 \text{ A}$$

$$i_2 = \frac{V_c - V_a}{2} = -2 \text{ A}$$

$$i_3 = \frac{V_c}{4} = -1 \text{ A}$$

$$i_4 = \frac{V_b}{2} = 2 \text{ A}$$

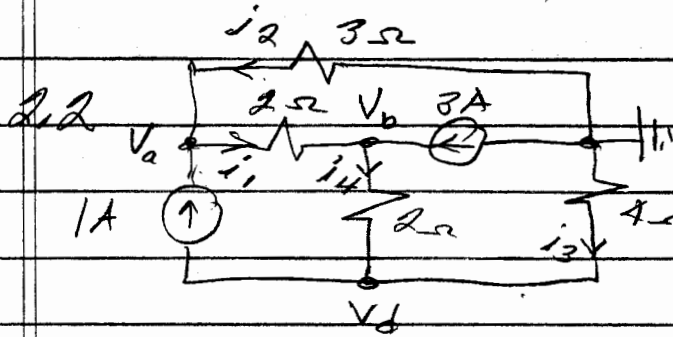

$$\textcircled{V_a} \quad \frac{V_a - V_b}{2} + \frac{V_a}{3} = 1$$

$$\textcircled{V_b} \quad \frac{V_b - V_a}{2} + \frac{V_b - V_d}{2} = 3$$

$$\textcircled{V_d} \quad \frac{V_d - V_b}{2} + \frac{V_d}{4} = -1$$

$$\left. \begin{aligned} \frac{5}{6}V_a - \frac{1}{2}V_b &= 1 \\ -\frac{1}{2}V_a + V_b - \frac{1}{2}V_d &= 3 \\ -\frac{1}{2}V_b + \frac{3}{4}V_d &= -1 \end{aligned} \right\} \begin{aligned} 5V_a - 3V_b &= 6 \\ -V_a + 2V_b - V_d &= 6 \\ -2V_b + 3V_d &= -4 \end{aligned}$$

$$V_a = \frac{\begin{vmatrix} 6 & -3 & 0 \\ 6 & 2 & -1 \\ -4 & -2 & 3 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & 0 \\ -1 & 2 & -1 \\ 0 & -2 & 3 \end{vmatrix}} = \frac{6(6-2) + 3(18-4)}{5(6-2) + 3(-3)} = \frac{66}{11} = 6V$$

$$V_b = \frac{\begin{vmatrix} 5 & 6 & 0 \\ -1 & 6 & -1 \\ 0 & -4 & 3 \end{vmatrix}}{11} = \frac{5(18-4) - 6(-3)}{11} = 8V$$


$$V_d = \frac{\begin{vmatrix} 5 & -3 & 6 \\ -1 & 2 & 6 \\ 0 & -2 & -4 \end{vmatrix}}{11} = \frac{5(-8+2) + (12+2)}{11} = 4V$$

$$i_1 = \frac{V_a - V_b}{2} = -1A$$

$$i_2 = -\frac{V_a}{3} = -2A$$

$$i_3 = -\frac{V_d}{4} = -1A$$

$$i_4 = \frac{V_b - V_d}{2} = 2A$$

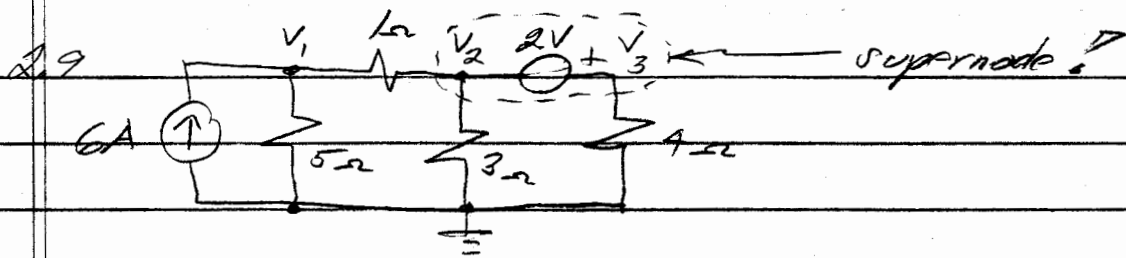

node 1 $\frac{V_1}{5} + \frac{V_1 - V_2}{1} = 6$

supernode $\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_3}{4} = 0$

$V_3 - V_2 = 2 \Rightarrow V_3 = V_2 + 2$


$$\left. \begin{array}{l} \frac{6}{5}V_1 - V_2 = 6 \\ -V_1 + \frac{4}{3}V_2 + \frac{V_2}{4} = -\frac{1}{2} \end{array} \right\} \begin{array}{l} \frac{6}{5}V_1 - V_2 = 6 \\ -V_1 + \frac{19}{12}V_2 = -\frac{1}{2} \end{array}$$

or $\begin{bmatrix} 6V_1 - 5V_2 = 30 \\ -12V_1 + 19V_2 = -6 \end{bmatrix}$

$$V_1 = \frac{\begin{vmatrix} 30 & -5 \\ -6 & 19 \end{vmatrix}}{\begin{vmatrix} 6 & -5 \\ -12 & 19 \end{vmatrix}} = \frac{540}{54} = 10 \text{ Volts}$$

$$V_2 = \frac{\begin{vmatrix} 6 & 30 \\ -12 & -6 \end{vmatrix}}{54} = \frac{324}{54} = 6 \text{ Volts}$$

$$V_3 = V_2 + 2 = 8 \text{ Volts}$$

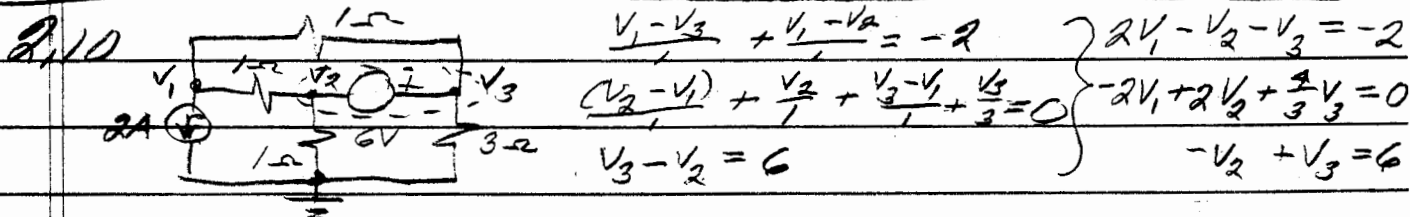


$$\left. \begin{array}{l} \frac{V_1 - V_2}{1} + \frac{V_1 - V_2}{1} = -2 \\ \frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_3 - V_1}{1} + \frac{V_3}{3} = 0 \\ V_3 - V_2 = 6 \end{array} \right\} \begin{array}{l} 2V_1 - V_2 - V_3 = -2 \\ -2V_1 + 2V_2 + \frac{2}{3}V_3 = 0 \\ -V_2 + V_3 = 6 \end{array}$$

$$V_1 = \frac{\begin{vmatrix} -2 & -1 & -1 \\ 0 & 2 & 2/3 \\ 0 & -1 & 1 \end{vmatrix}}{\begin{vmatrix} 2 & -1 & -1 \\ -2 & 2 & 2/3 \\ 0 & -1 & 1 \end{vmatrix}} = \frac{-2(2 + \frac{4}{3}) + 6(-\frac{4}{3} + 2)}{2(2 + \frac{4}{3}) + 2(-1 - 1)} = \frac{-\frac{8}{3}}{\frac{20}{3} - \frac{12}{3}} = -1 \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 2 & -2 & -1 \\ -2 & 0 & 2/3 \\ 0 & 0 & 1 \end{vmatrix}}{\frac{20}{3} - \frac{12}{3}} = \frac{-16 + 8}{\frac{8}{3}} = \frac{-8 \times 3}{8} = -3$$


$$V_3 = 6 + V_2 = 3 \text{ V}$$

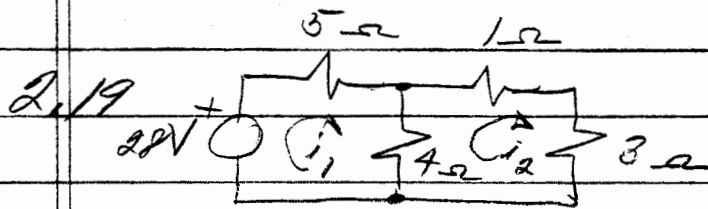

$$\begin{cases} 5i_1 + 4(i_1 - i_2) = 28 \\ 4(i_2 - i_1) + i_2 + 3i_2 = 0 \end{cases} \Rightarrow \begin{cases} 9i_1 - 4i_2 = 28 \\ -4i_1 + 8i_2 = 0 \end{cases} \Rightarrow \begin{cases} 9i_1 - 4i_2 = 28 \\ -i_1 + 2i_2 = 0 \end{cases}$$

$$i_1 = \frac{\begin{vmatrix} 28 & -4 \\ 0 & 2 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -1 & 2 \end{vmatrix}} = \frac{2 \times 28}{18 - 4} = \frac{2 \times 28}{14} = \boxed{4A} \quad \triangleleft$$
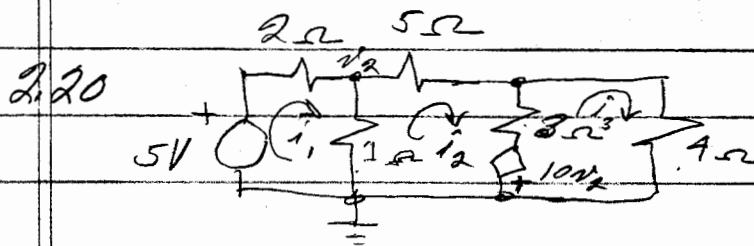
$$i_2 = \frac{\begin{vmatrix} 9 & 28 \\ -1 & 0 \end{vmatrix}}{14} = \frac{28}{14} = \boxed{2A} \quad \triangleleft$$



$$2i_1 + (i_1 - i_2) = 5$$

$$(i_2 - i_1) + 5i_2 + 3(i_2 - i_3) - 10i_2 = 0$$

$$10i_2 + 3(i_3 - i_2) + 4i_3 = 0$$

giving: $3i_1 - i_2 = 5$

$$i_2 = i_1 - i_2$$


$$-11i_1 + 19i_2 - 3i_3 = 0$$

$$10i_1 - 13i_2 + 7i_3 = 0$$

$$i_1 = \frac{\begin{vmatrix} 5 & -1 & 0 \\ 0 & 19 & -3 \\ 0 & -13 & 7 \end{vmatrix}}{\begin{vmatrix} 3 & -1 & 0 \\ -11 & 19 & -3 \\ 10 & -13 & 7 \end{vmatrix}} = \frac{5(133 - 39)}{3(133 - 39) + (-77 + 30)} = \frac{470}{582 - 47} = 2A \leftarrow$$

$$i_2 = \frac{\begin{vmatrix} 3 & 5 & 0 \\ -11 & 0 & -3 \\ 10 & 0 & 7 \end{vmatrix}}{235} = \frac{-5(-77 + 30)}{235} = 1A \leftarrow$$
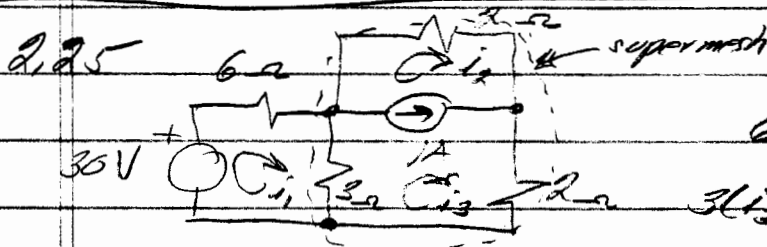
$$i_3 = \frac{\begin{vmatrix} 3 & -1 & 5 \\ -11 & 19 & 0 \\ 10 & -13 & 0 \end{vmatrix}}{235} = \frac{5(143 - 190)}{235} = -1A \leftarrow$$



$$i_3 - i_2 = 1 \Rightarrow i_3 = 1 + i_2$$

$$6i_1 + 3(i_1 - i_3) = 30$$

$$3(i_2 - i_1) + 2i_2 + 2i_3 = 0$$


giving: $9i_1 - 3i_2 = 30$

$$-3i_1 + 7i_2 = -5$$

$$i_1 = \frac{\begin{vmatrix} 30 & -3 \\ -5 & 7 \end{vmatrix}}{\begin{vmatrix} 9 & -3 \\ -3 & 7 \end{vmatrix}} = \frac{231 - 15}{63 - 9} = \frac{216}{54} = 4A \leftarrow$$

$$i_2 = \frac{\begin{vmatrix} 9 & 30 \\ -3 & 5 \end{vmatrix}}{54} = \frac{-45 + 99}{54} = 1A \leftarrow$$

$$i_3 = 1 + i_2 = 2A \leftarrow$$

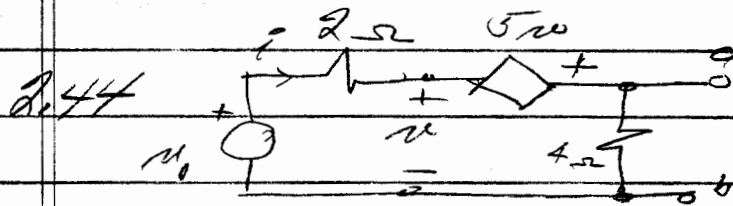

$$v_1 = 6i - 5v$$

$$v = v_1 - 2i$$




$$\therefore v_1 = 6i - 5(v_1 - 2i) \Rightarrow 6v_1 = 16i; i = \frac{3}{8} v_1$$

$$\text{so } \boxed{V_{oc} = V_{th} = 4i = \frac{3}{2} v_1}$$

for I_{sc} $v_1 = 2I_{sc} - 5v = 2I_{sc} - 5(v_1 - 2I_{sc})$



$$6v_1 = 12I_{sc} \Rightarrow \boxed{I_{sc} = \frac{1}{2} v_1}$$

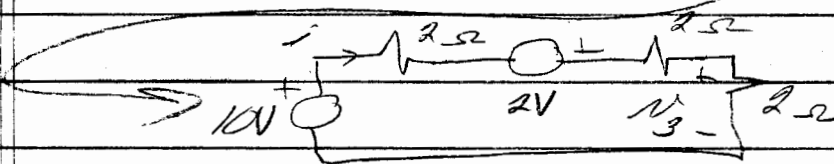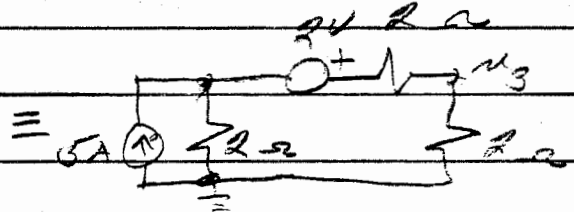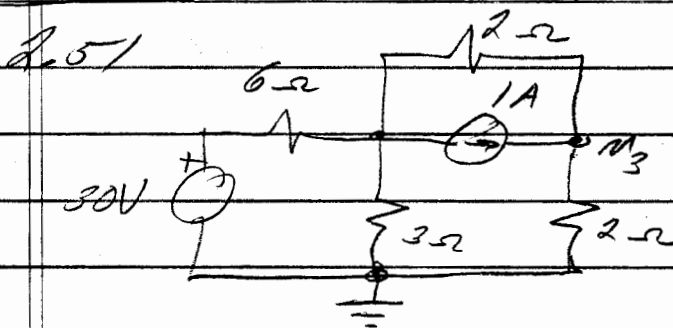thus $\boxed{R_{th} = \frac{V_{oc}}{I_{sc}} = 3 \Omega}$



$$i = \frac{12}{6} = 2$$

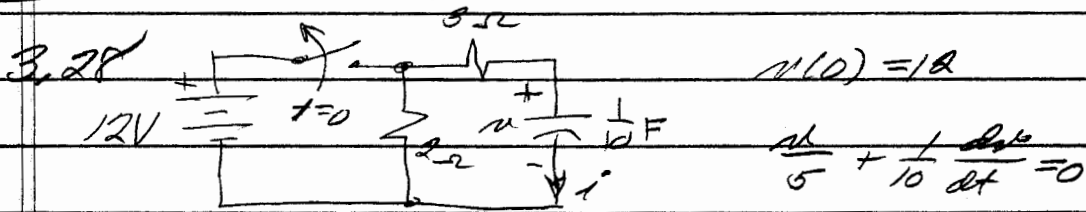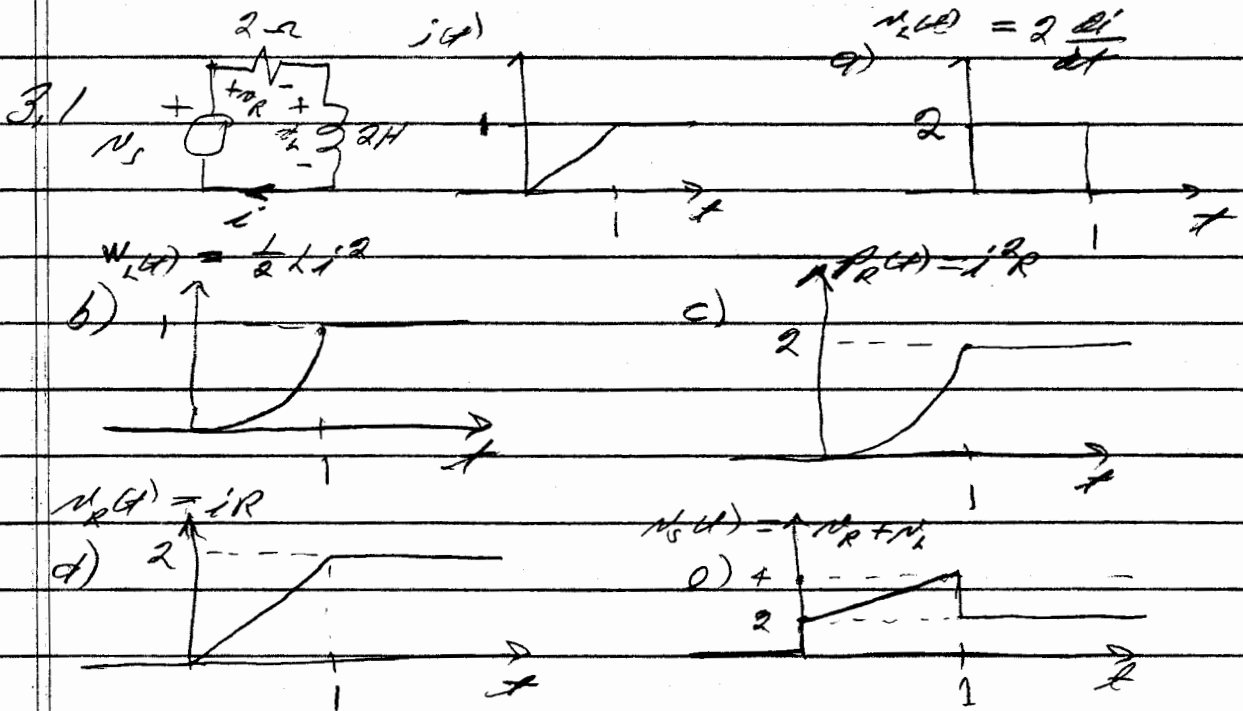
$$\therefore \boxed{v_3 = 4 \text{ Volts}}$$




or $\frac{dv}{dt} + 2v = 0 \Rightarrow v = Ae^{st} \Rightarrow s = -2$

so $v = Ae^{-2t}$ but $v(0) = 12 \Rightarrow v = 12e^{-2t}$

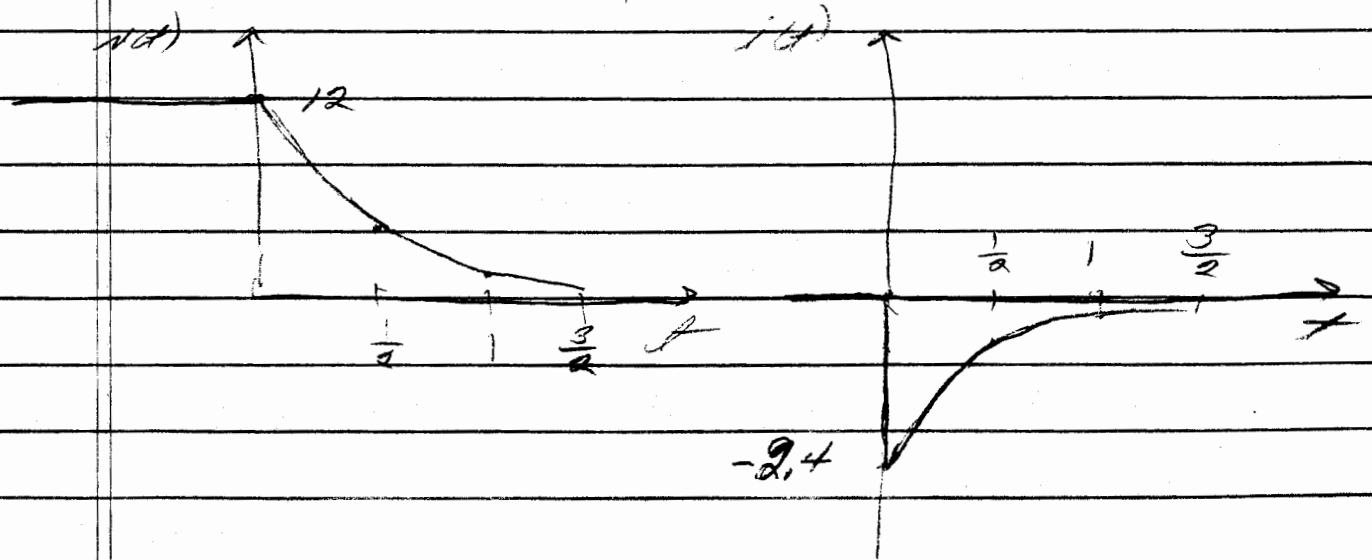$i = C \frac{dv}{dt} = \frac{1}{10} (-24) e^{-2t} = -2.4 e^{-2t}$




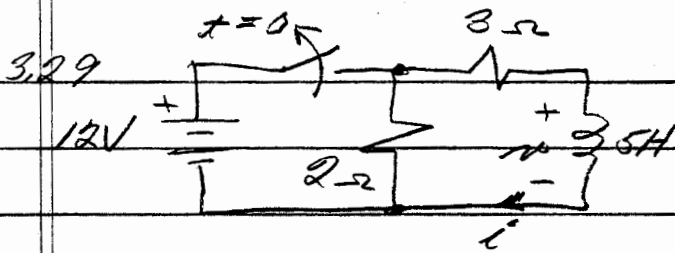


$$i(0) = \frac{12}{3} = 4A$$

for $t > 0$ $5i + 5 \frac{di}{dt} = 0$; $i = Ae^{st} \Rightarrow s = -1$

so $i(t) = Ae^{-t}$ but $i(0) = 4$ so $i(t) = 4e^{-t}$ ←

$v(t) = L \frac{di}{dt} = -20e^{-t}$ ←

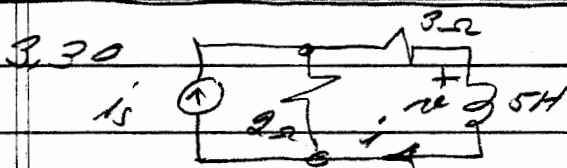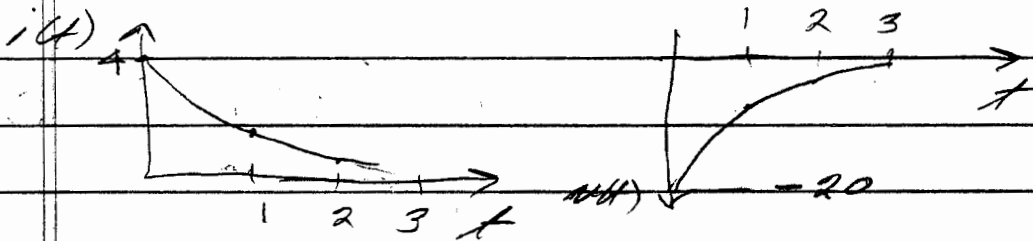


$$i_s(t) = 10 \text{ for } t < 0$$

$$i_s(t) = 0 \text{ for } t \geq 0$$

$$\text{so } i(0) = 10 \frac{2}{5} = 4$$


so we see that for $t > 0$ this is the same as problem 3.29 ✓

3.34

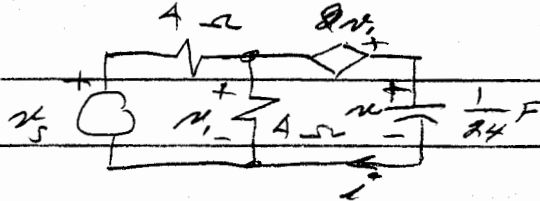

$v_s(t) = 18 \text{ for } t < 0$
 $v_s(t) = 0 \text{ for } t \geq 0$


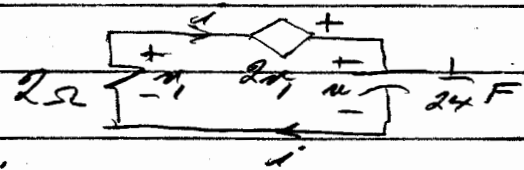
$v_1(t) = 6$ for $t \geq 0$ we have
 so $v_1(t) = 18 \text{ Volts}$



$v_1 = -2i$

(1) $2i - 2v_1 + 24 \int_0^t i dt + 18 = 0 \Rightarrow 6 \frac{di}{dt} + 24i = 0$
 $i = A e^{-4t}$

from (1) $6i(0) = -18$ or $i(0) = -3$

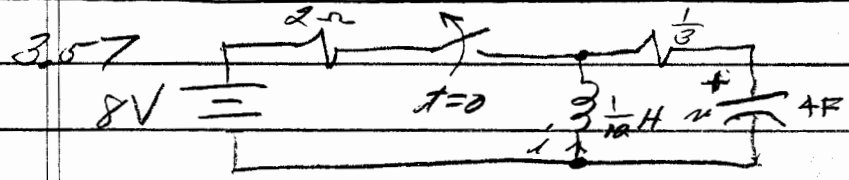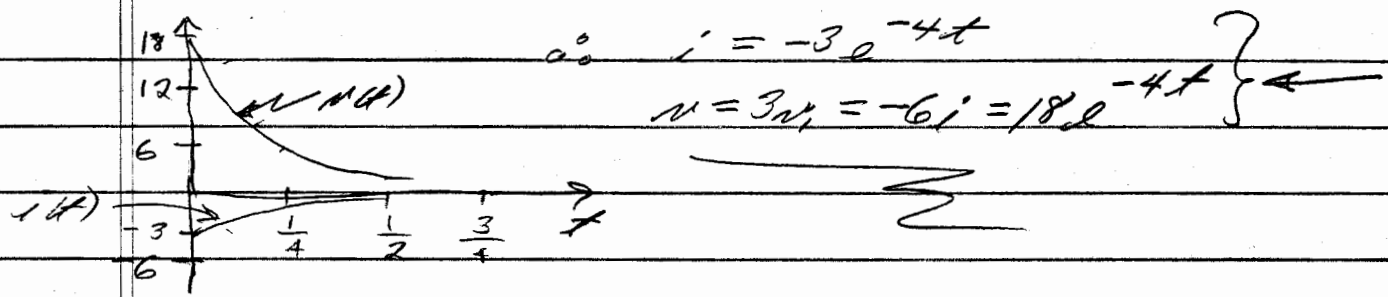

$v(0) = 0$
 $i(0) = -4$

for $t > 0$ $\frac{1}{12} \frac{di}{dt} + \frac{1}{3}i + \frac{1}{4} \int_0^t i dt = 0$ (1)

or $\frac{di}{dt} + 4i + 3 \int_0^t i dt = 0$; $i = A e^{st}$

$s^2 + 4s + 3 = 0$ or $s_{1,2} = -2 \pm \sqrt{4-3} = -3, -1$


so $i(t) = A_1 e^{-3t} + A_2 e^{-t}$ but $i(0) = -4$ so $-4 = A_1 + A_2$

from (1) $\frac{di}{dt} = -4i(0) = 16 = -3A_1 - A_2$

so $16 = -3(-4 - A_2) - A_2 = 12 + 2A_2$ or $A_2 = 2$ and $A_1 = -6$

$i(t) = -6e^{-3t} + 2e^{-t}$

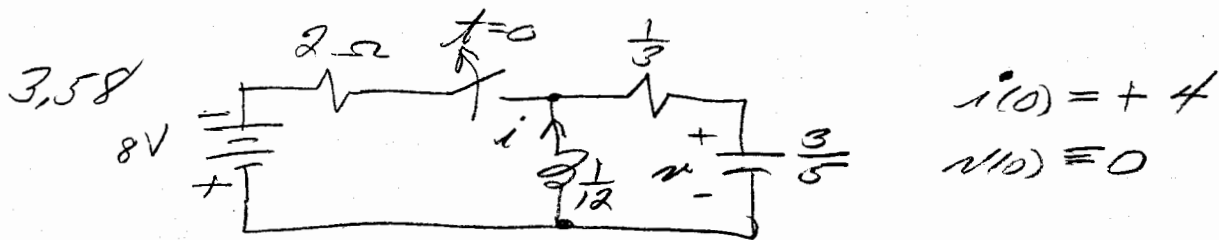$v(t) = -\frac{1}{3}i - \frac{1}{12} \frac{di}{dt} = 2e^{-3t} - \frac{2}{3}e^{-t} - \frac{3}{2}e^{-3t} + \frac{1}{6}e^{-t} = \frac{1}{2}e^{-3t} - \frac{1}{2}e^{-t}$



For $t > 0$ $\frac{1}{12} \frac{di}{dt} + \frac{1}{3} i + \frac{5}{3} \int_0^t i dt = 0$ (1)

or $\frac{d^2 i}{dt^2} + 4 \frac{di}{dt} + 20i = 0$ For $i = A e^{st}$

$s^2 + 4s + 20 = 0$, $s_{1,2} = \frac{-4 \pm \sqrt{16 - 80}}{2} = -2 \pm j4$

$\therefore i(t) = A_1 e^{-2t} \cos 4t + A_2 e^{-2t} \sin 4t$

but $i(0) = +4$ $\therefore \boxed{+4 = A_1}$

from (1) $\left. \frac{di}{dt} \right|_{t=0} = -4i(0) = -16$

so $-16 = +4 \left[-2 \times e^{-2t} \cos 4t - 4 \times e^{-2t} \sin 4t \right] + \left[-2A_2 e^{-2t} \sin 4t + 4A_2 e^{-2t} \cos 4t \right]$

$t=0$

$-16 = -8 + 4A_2$ or $\boxed{A_2 = -2}$

giving: $\underline{i(t) = +4 e^{-2t} \cos 4t - 2 e^{-2t} \sin 4t}$ ←


$v = -\frac{1}{3} i - \frac{1}{12} \frac{di}{dt} = -\frac{4}{3} e^{-2t} \cos 4t + \frac{2}{3} e^{-2t} \sin 4t$

$+ \frac{2}{3} e^{-2t} \cos 4t + \frac{4}{3} e^{-2t} \sin 4t - \frac{1}{3} e^{-2t} \sin 4t + \frac{2}{3} e^{-2t} \cos 4t$



$\boxed{v(t) = \frac{5}{3} e^{-2t} \sin 4t}$ ←

- 4.1 a) $4+j7 = 8,06 e^{j69,25^\circ}$
- b) $3-j5 = 5,83 e^{-j59,04^\circ}$
- c) $-2+j3 = 3,6 e^{j123,7^\circ}$
- d) $-1-j6 = 6,08 e^{j260,5^\circ}$

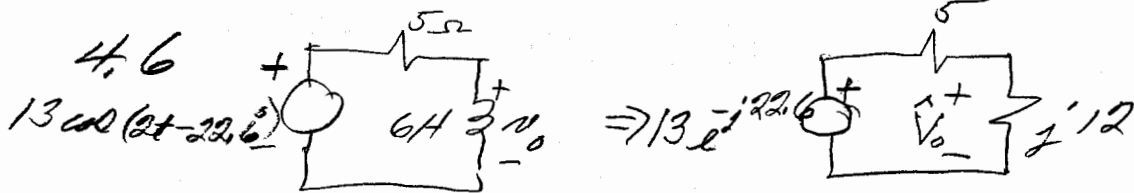- e) $4 = 4 e^{j0^\circ}$
- f) $-5 = 5 e^{j180^\circ}$
- g) $j7 = 7 e^{j90^\circ}$
- h) $-j2 = 2 e^{-j90^\circ}$



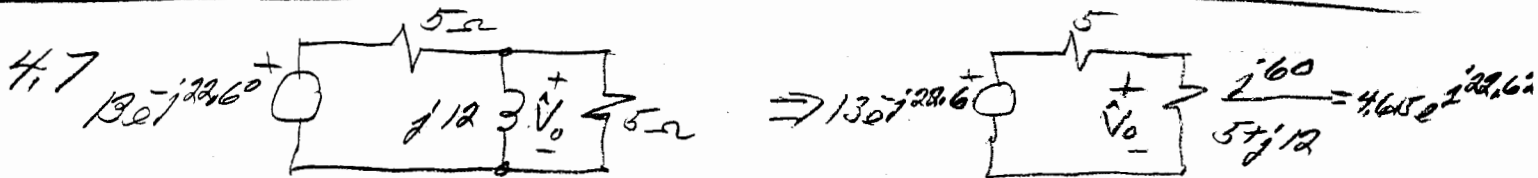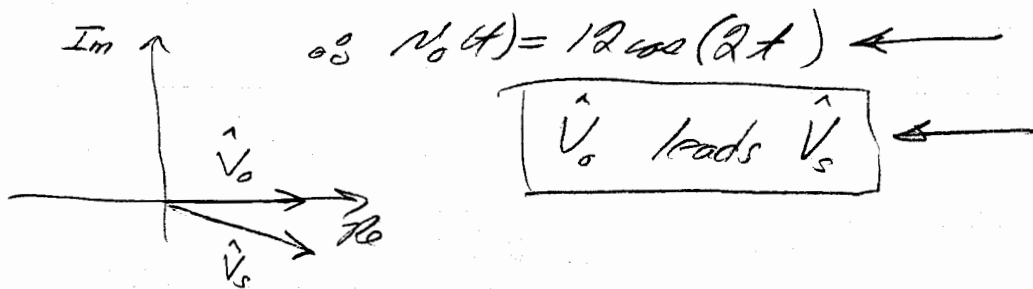
$$\hat{V}_o = 13 e^{-j22,6^\circ} \frac{j12}{5+j12} = \frac{13 \times 12 e^{j(90^\circ - 22,6^\circ)}}{13 e^{j67,38^\circ}} = 12 e^{j0,02^\circ}$$




$$\hat{V}_o = 13 e^{-j22,6^\circ} \frac{4,615 e^{j22,6^\circ}}{5 + 4,615 e^{j22,6^\circ}} = \frac{60}{9,26 + j1,775} = \frac{60}{9,428 e^{j10,85^\circ}} = 6,36 e^{-j10,85^\circ}$$

$i_m(t) = 6,36 \cos(2t - 10,85^\circ)$

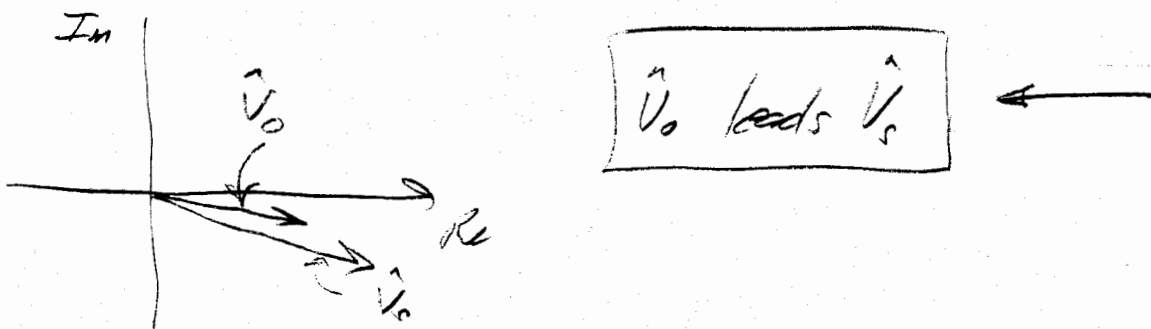

4.9


$i_s = 5 \cos 3t$

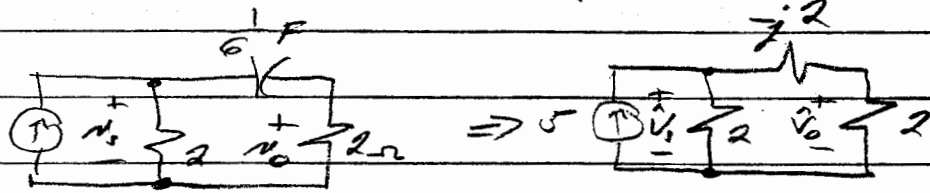

$$\hat{V}_o = 5 \frac{2 \times 2}{2 - j2 + 2} = \frac{20}{4 + j2} = 4.472 \angle -26.56^\circ \Rightarrow i_o(t) = 4.472 \cos(3t - 26.56^\circ)$$

$$\hat{V}_1 = \frac{10(2 - j2)}{4 - j2} = \frac{10 \times 2 \times 1.414 \angle -45^\circ}{4.472 \angle -26.56^\circ} = 6.32 \angle -18.4^\circ \Rightarrow i_o(t) = 6.32 \cos(3t - 18.4^\circ)$$

4.17

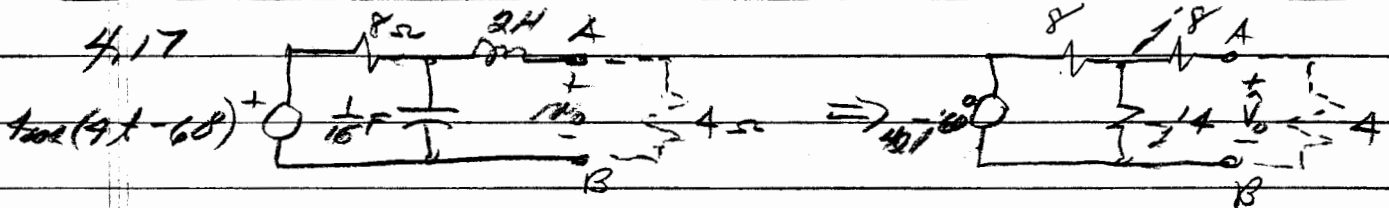

@ A-B $\hat{V}_{Th} = \frac{40 \angle -60^\circ (-j4)}{8 - j4} = \frac{160 \angle -90^\circ}{8.256 \angle -26.56^\circ} = 1.789 \angle -123.44^\circ$

$$Z_{Th} = j8 + \frac{8(-j4)}{8 - j4} = \frac{64j + 32 - j32}{8 - j4} = \frac{32 + j32}{8 - j4} = \frac{32 \times 1.414 \angle 45^\circ}{8.944 \angle -26.56^\circ} = 5.059 \angle 71.56^\circ$$


OR $Z_{Th} = 1.6 + j4.799$

SO $\hat{V}_o = \frac{1.789 \angle -123.44^\circ \times 4}{(5.6 + j4.799)} = \frac{4 \times 1.789 \angle -123.44^\circ}{7.375 \angle 40.6^\circ} = 0.97 \angle -164^\circ$

OR $i_o(t) = 0.97 \cos(4t - 160^\circ)$


4.28

Power

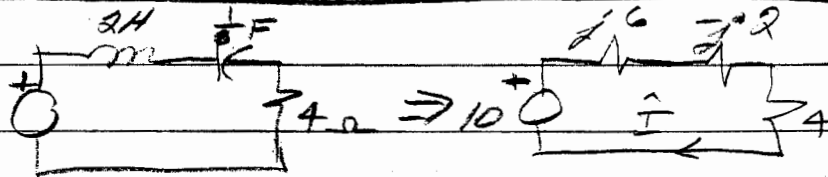

$$\hat{I} = \frac{10}{4 + j4} = \frac{5}{2 + j2} = \frac{5 \angle -45^\circ}{2\sqrt{2}}$$

$$P_{ave} = \frac{1}{2} |\hat{I}|^2 \times 4 = 2 \times \frac{25}{8} = \frac{25}{4} = 6.25 \text{ Watts}$$

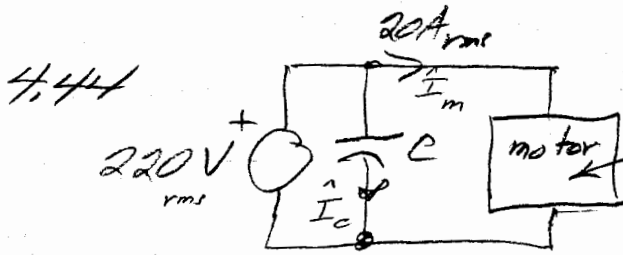

(60Hz)

pf = 0.75 lagging


a) $P_{ave} = 220 \times 20 \times 0.75 = 3,300 \text{ Watts}$

b) $\vec{I}_m = 20 \angle -\phi \cos^{-1}(0.75) = 20 \angle -41.41^\circ = 15 - j13.23$

∴ need $\vec{I}_c = +j13.23 = \frac{220}{\sqrt{j2\pi 60 C}} = j2\pi 60 \times 220 C$

so $C = \frac{13.23}{2\pi \times 60 \times 220} \approx 1.6 \times 10^{-4} \text{ F} = \boxed{160 \mu\text{F}}$

2.30

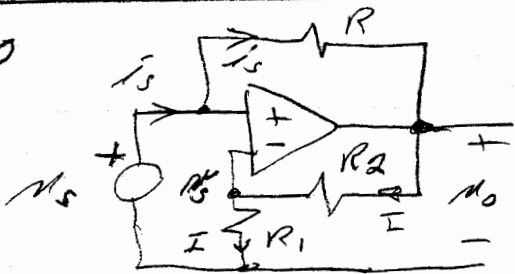

a) $I = \frac{N_s}{R_1}$; $N_o = I(R_1 + R_2)$


∴ $N_o = N_s \frac{R_1 + R_2}{R_1}$

b) $i_s = \frac{N_s - N_o}{R} = \frac{N_s}{R} - N_s \frac{R_1 + R_2}{R R_1} = \frac{N_s}{R} \left(1 - \frac{R_1 + R_2}{R_1} \right)$

or $i_s = \frac{N_s}{R} \left(\frac{-R_2}{R_1} \right)$

and $\frac{N_s}{i_s} = -\frac{R_1 R}{R_2}$

2.28

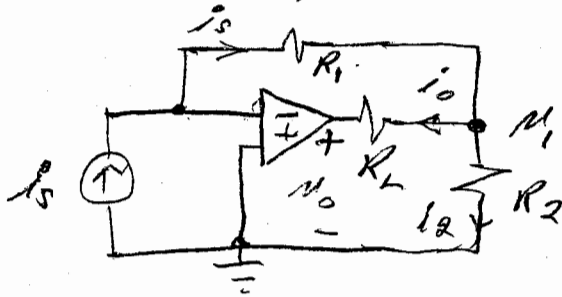


$$v_1 = -i_s R_1$$

$$i_2 = \frac{v_1}{R_2}$$

$$i_o = i_s - i_2 = i_s - \frac{v_1}{R_2} = i_s - \frac{(-i_s R_1)}{R_2} = i_s \left(1 + \frac{R_1}{R_2}\right) \leftarrow$$

$$v_o = -i_o R_L + v_1 = -i_s \left(1 + \frac{R_1}{R_2}\right) R_L - i_s R_1 = -i_s \left(R_L + \frac{R_1 R_L}{R_2} + R_1\right) \leftarrow$$

2.35

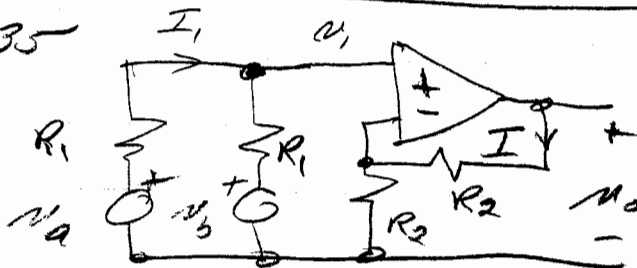

$$I = \frac{v_o}{2R_2}$$


$$v_1 = \frac{v_o}{2} \quad (1)$$

$$-v_a + I_1 R_1 + I_1 R_1 + v_b = 0 \quad \text{so} \quad I_1 = \frac{v_a - v_b}{2R_1}$$

$$v_1 = I_1 R_1 + v_b = \frac{v_a - v_b}{2} + v_b = \frac{v_a + v_b}{2}$$



so from (1) $\boxed{v_o = 2v_1 = v_a + v_b} \leftarrow$

10.67

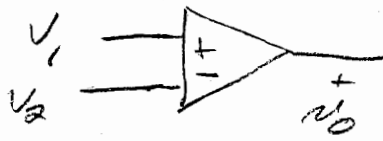

$$V_1 = V_2 > 0$$

$$V_2 = \mu_{11} V_1$$

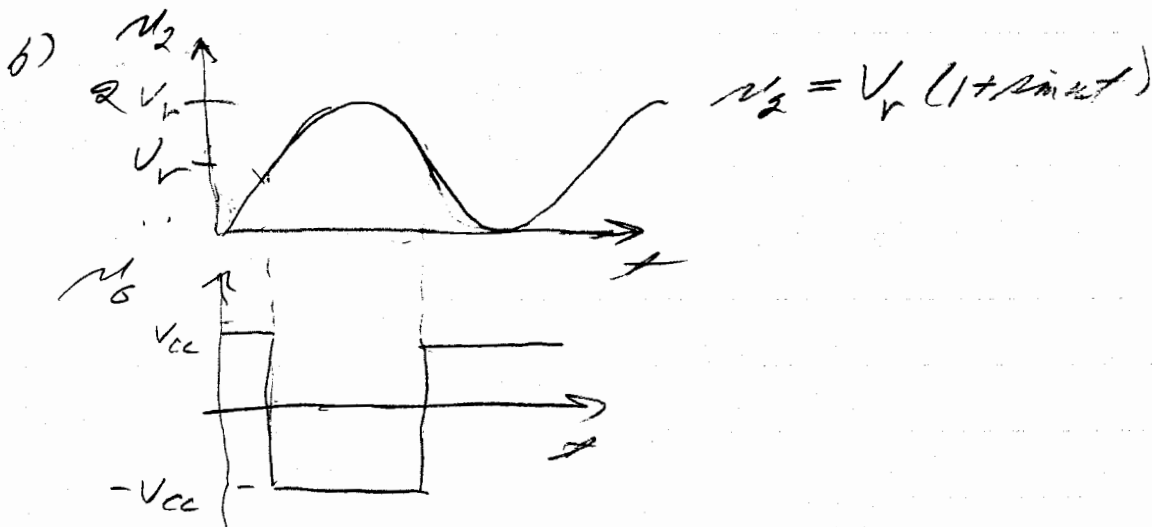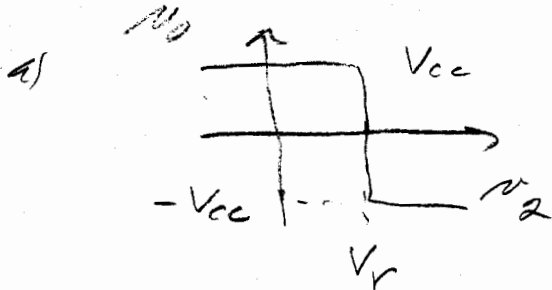

10-79 for a 555 timer $f_0 = \frac{1.44}{(R_1 + 2R_2)C}$

a) $f_0 = \frac{1.44}{15 \times 10^3 \times 10^{-7}} = \boxed{960 \text{ Hz}}$ ←

b) $1.6 \times 10^3 = \frac{1.44}{15 \times 10^3 \times C}$; $C = \frac{1.44}{15 \times 10^3 \times 1.6 \times 10^3} = \boxed{0.06 \mu\text{F}}$ ←


c) $10^4 = \frac{1.44}{(R_1 + 2 \times 10^4) 5 \times 10^{-9}}$; $R_1 \times 5 \times 10^{-5} = 1.44 - 1$; $R_1 = \frac{0.44}{5 \times 10^{-5}} = \boxed{8.8 \times 10^3 \Omega}$ ←

d) $10^4 = \frac{1.44}{(10^4 + 2R_2) 5 \times 10^{-9}}$; $R_2 \times 10^{-4} = 1.44 - 0.5$; $R_2 = \boxed{9.4 \times 10^3 \Omega}$ ←

11.26

A	B	$A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

$A \odot B = \bar{A}\bar{B} + AB$

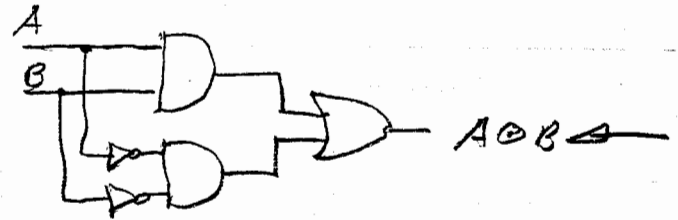

11.44


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$

or $F = m_3 + m_5 + m_6 + m_7$

$F = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)$

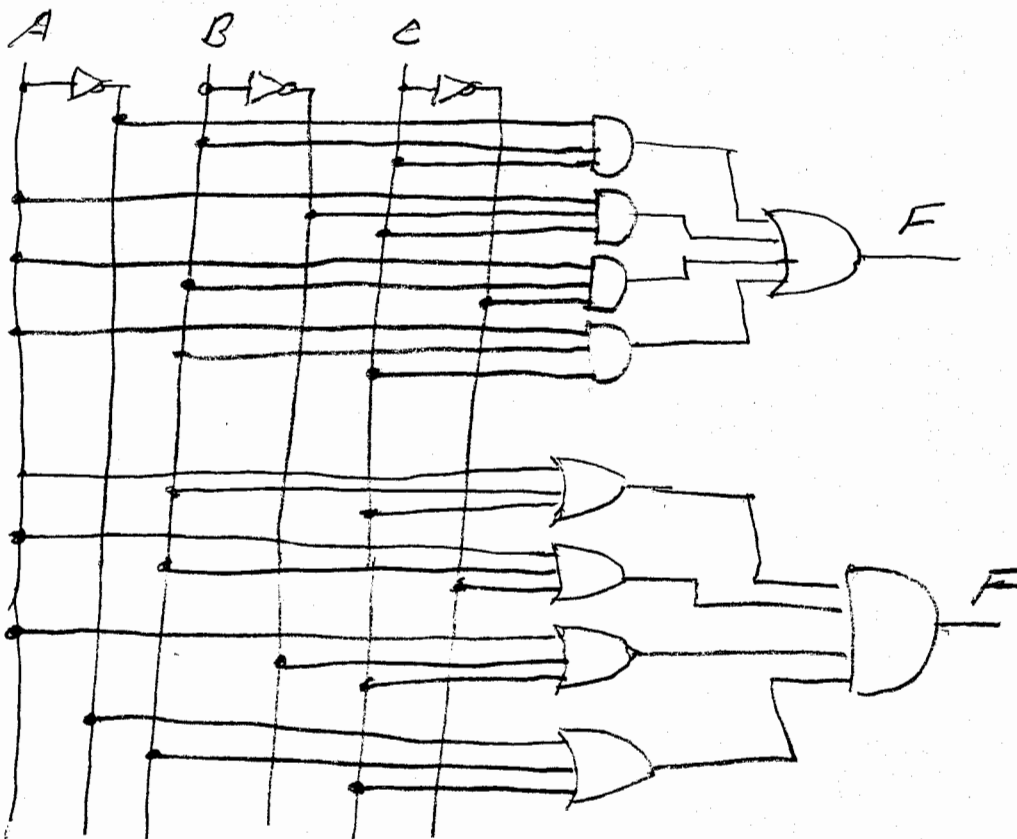or $F = M_0 \cdot M_1 \cdot M_2 \cdot M_4$



11.53 a)

		BC			
A		00	01	11	10
0	0	0	1	1	1
1	1	1	0	0	0

$$F = \underline{A\bar{B} + \bar{B}C + \bar{A}C + \bar{A}B}$$

b)

		BC			
A		00	01	11	10
0	0	0	0	0	1
1	1	1	0	1	1

$$F = \underline{B\bar{C} + AB + AC}$$

c)

		BC			
A		00	01	11	10
0	1	1	1	1	1
1	0	1	0	1	1

$$F = \underline{\bar{A} + \bar{B}C + B\bar{C}}$$

11.54 a)

		BC			
	A	00	01	11	10
0		0	1	1	1
1		1	1	0	0

$$F = \overline{A} \overline{B} C + AB$$

$$F = (A+B+C) \cdot (\overline{A} + \overline{B})$$

b)

		BC			
	A	00	01	11	10
0		0	0	0	1
1		1	0	1	1

$$F = \overline{A} \overline{B} + \overline{A} C + \overline{B} C$$

$$F = (A+B) \cdot (A+\overline{C}) \cdot (B+\overline{C})$$

c)

		BC			
	A	00	01	11	10
0		1	1	1	1
1		0	1	0	1

$$F = A \overline{B} \overline{C} + ABC$$

$$F = (\overline{A} + B + C) \cdot (\overline{A} + \overline{B} + \overline{C})$$

11.56 a)

		BC			
	A	00	01	11	10
0		0	0	0	1
1		1	0	0	1

$$F = B \overline{C} + A \overline{C}$$

b)

		BC			
	A	00	01	11	10
0		1	0	0	0
1		1	1	1	1

$$F = A + \overline{B} \overline{C}$$

c)

		BC			
	A	00	01	11	10
0		1	0	1	1
1		1	0	0	0

$$F = \overline{B} \overline{C} + \overline{A} B$$

11.57

a)

		CD			
AB		00	01	11	10
00		0	0	0	0
01		1	1	1	1
11		0	1	1	1
10		0	0	0	1

$$F = \bar{A}B + BD + BC + AC\bar{D}$$

b)

		CD			
AB		00	01	11	10
00		0	1	1	1
01		0	0	0	1
11		0	1	0	1
10		0	1	1	1

$$F = C\bar{D} + \bar{B}D + A\bar{C}D$$

c)

		CD			
AB		00	01	11	10
00		1	0	1	0
01		0	0	1	1
11		0	1	0	1
10		1	0	0	1

$$F = \bar{B}\bar{C}\bar{D} + \bar{A}CD + BC\bar{D} + AC\bar{D} + ABC\bar{D}$$




many possible combinations

12.14

A	B	C	D	E	F	G	H	F ₁	F ₂	F ₃
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	0
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	0
0	0	0	0	0	0	1	0	0	1	0
0	0	0	0	0	0	0	1	0	0	1

$F_1 = E + F + G + H$; $F_2 = C + D + G + H$; $F_3 = B + D + F + H$

B C D E F G H

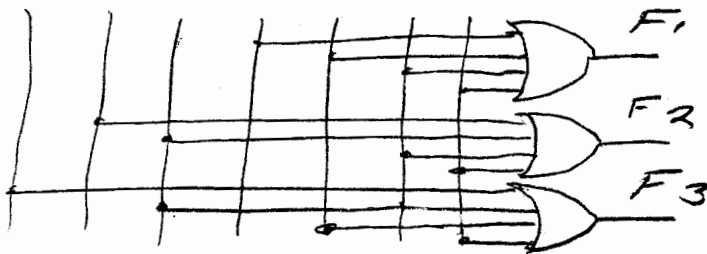

12.17

A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

Ⓓ

A	BC	00	01	11	10
0	0	0	0	0	0
1	1	1	1	1	1

$D = A$

Ⓔ


A	BC	00	01	11	10
0	0	0	0	1	1
1	1	1	1	0	0

$E = \bar{A}B + A\bar{B}$
 $E = A \oplus B$

Ⓕ

A	BC	00	01	11	10
0	0	0	1	0	1
1	0	1	0	0	1

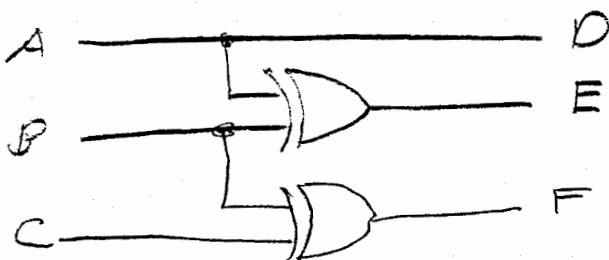$F = \bar{B}C + B\bar{C}$
 $F = B \oplus C$





12.19


A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$
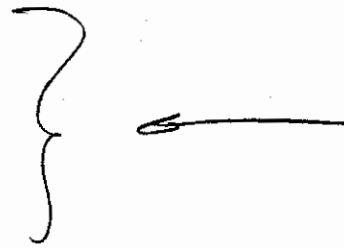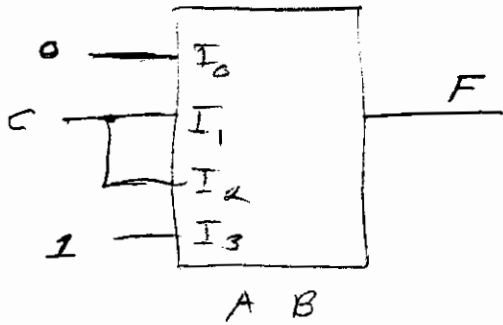
$$F = \bar{A}B \cdot C + A\bar{B} \cdot C + AB \cdot 1 + \bar{A}\bar{B} \cdot 0$$



12.42 no-outputs

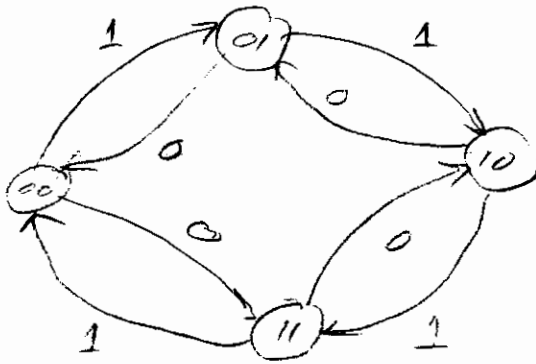

In	Present state	Next state	D_0	D_1
	$Q_0 Q_1$	$Q_0^+ Q_1^+$		
0	0 0	1 1	1	1
0	0 1	0 0	0	0
0	1 0	0 1	0	1
0	1 1	1 0	1	0
1	0 0	1 0	0	1
1	0 1	1 0	1	0
1	1 0	1 1	1	1
1	1 1	0 0	0	0

D_0

I_n	$Q_0 Q_1$	01	11	10
0	1	0	1	0
1	0	1	0	1

D_1

I_n	$Q_0 Q_1$	00	01	11	10
0	1	0	0	0	1
1	1	0	0	0	1

$$D_0 = \bar{I}_n \bar{Q}_0 \bar{Q}_1 + \bar{I}_n Q_0 Q_1 + I_n \bar{Q}_0 Q_1 + I_n Q_0 \bar{Q}_1 = \bar{I}_n (Q_0 \oplus Q_1) + I_n (Q_0 \oplus Q_1)$$

$$D_0 = \bar{I}_n \oplus (Q_0 \oplus Q_1) \quad ; \quad D_1 = \bar{Q}_0 \bar{Q}_1 + Q_0 \bar{Q}_1 = \bar{Q}_1$$

