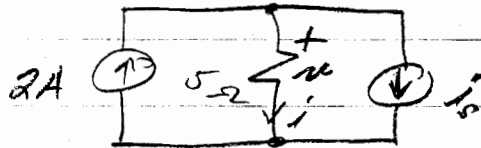


- 1.17 a) $v_1 = 5i_1 = 20V$
 b) $v_2 = -4i_2 = 8V$
 c) $v_3 = -3i_3 = -6V$
 d) $v_4 = 1 \times i_4 = -2V$

1.16



a) $i_s = 1 \implies v = 5V$


b) $i_s = 2 \implies v = 0$

$2 = i + i_s \implies i = 2 - i_s$ c) $i_s = 3 \implies v = -5V$

$\therefore v = 5i = 10 - 5i_s$

Homework 2

1.17

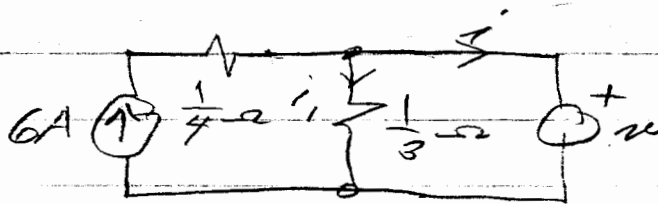

$6 = i + i_1$

$i_1 = 3v$


$\therefore i = 6 - i_1 = 6 - 3v$

a) $i = 6 - 3(0) = 3A$

b) $i = 6 - 3(2) = 0A$

c) $i = 6 - 3(3) = -3A$

1.19

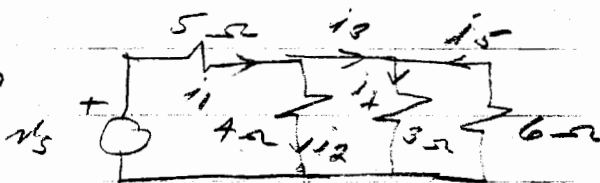

for $i_1 = 6A$

Using current division


$R_{eq} = \frac{3(6)}{9} = 2$

$i_2 = 6 \frac{2}{6} = 2A$

$i_3 = 6 \frac{4}{6} = 4A$

$i_4 = 13 \frac{6}{9} = \frac{24}{9} = \frac{8}{3}A$

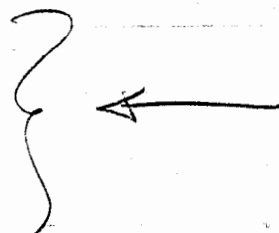$i_5 = -i_3 \frac{3}{9} = -\frac{12}{9} = -\frac{4}{3}A$



ES 332 Homework 3




a) $v_1 = 2V$; $i_1 = 2A$
 $v_2 = 6V$; $i_2 = 2A$
 $i_1 = i_2 = 4A$
 $v_5 = v_1 + v_2 = 4 + 6 = 10V$

$i = i_1 + i_5 = 4 + 2 = 6A$ $\therefore V_s = 6 + 10 = 16V$ ←

b) $i_3 = 3A$; $v_3 = 9V$; $i_2 = 3A$; $i_1 = 6A$; $v_5 = 6 + 9 = 15V$
 $i = 6 + 3 = 9A$ $\therefore V_s = 9 + 15 = 24V$ ←

c) $i_5 = 4A$; $v_5 = 20V$; $i_1 = \frac{20}{1+1.5} = 8$; $i = 12$
 $V_s = 12 + 20 = 32V$ ←

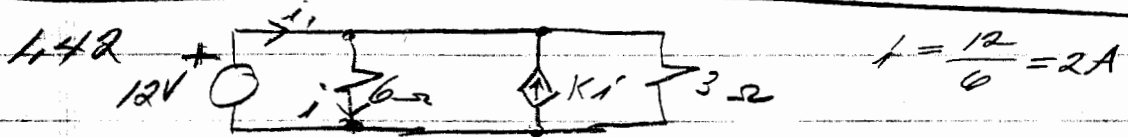
d) $\left\{ \begin{array}{l} a) R_{eq} = \frac{V_s}{i} = \frac{8}{3} \Omega \\ b) R_{eq} = \frac{8}{9} \Omega \\ c) R_{eq} = \frac{8}{3} \Omega \end{array} \right.$



a) $K=2$ KCL $i_1 = 2 + 4 - 4 = 2A$ ←

b) $K=3$ $i_1 = 2 + 4 - 6 = 0A$ ←

c) $K=4$ $i_1 = 2 + 4 - 8 = -2A$ ←

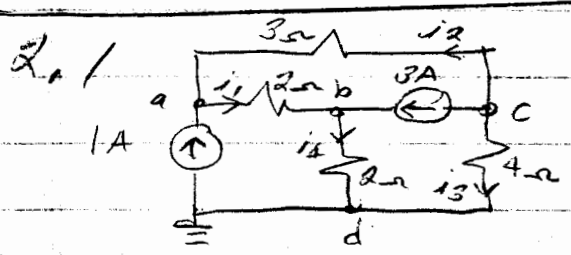

a) $\frac{V_a - V_b}{2} + \frac{V_b - V_c}{3} = 1$
 $\frac{V_b - V_a}{2} + \frac{V_b}{2} = 3$
 $\frac{V_c - V_b}{3} + \frac{V_c}{4} = -3$

$V_b(\frac{1}{2} + \frac{1}{3}) - V_a \frac{1}{2} - V_c \frac{1}{3} = 1$
 or $-V_a \frac{1}{2} + V_b = 3$
 $-V_a \frac{1}{3} + V_c(\frac{1}{3} + \frac{1}{4}) = -3$
 $-4V_a + 7V_c = -36$

$5V_a - 3V_b - 2V_c = 6$
 $V_b = 3 + V_a \frac{1}{2}$
 $V_c = \frac{-36 + 4V_a}{7}$

$$\text{From above: } 5V_a - 3\left(3 + \frac{V_a}{2}\right) - 2\left(\frac{-36 + 4V_a}{7}\right) = 6$$

$$V_a\left(5 - \frac{3}{2} - \frac{8}{7}\right) = 6 + 9 - \frac{72}{7}$$

$$V_a\left(\frac{70 - 21 - 16}{14}\right) = \frac{210 - 144}{14} \Rightarrow V_a = \frac{66}{33} = \underline{2} \text{ A}$$

$$V_b = 3 + \frac{V_a}{2} = \underline{4} \text{ A}$$


$$V_c = \frac{-36 + 8}{7} = \underline{-4} \text{ A}$$

$$i_1 = \frac{V_a - V_b}{2} = -1 \text{ A}$$

$$i_2 = \frac{V_c - V_a}{3} = -2 \text{ A}$$

$$i_3 = \frac{V_c}{4} = -1 \text{ A}$$

$$i_4 = \frac{V_b}{2} = 2 \text{ A}$$

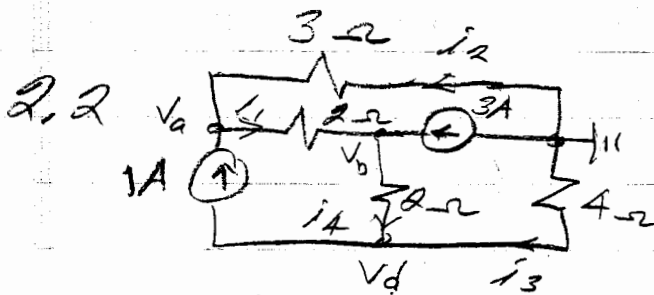

$$\frac{V_a}{3} + \frac{V_a - V_b}{2} = 1$$

$$\frac{V_b - V_a}{2} + \frac{V_b - V_d}{2} = 3$$

$$\frac{V_d - V_b}{2} + \frac{V_d}{4} = -1$$

or

$$\begin{cases} V_b(\frac{1}{3} + \frac{1}{2}) - V_a \frac{1}{2} = 1 \\ -V_a \frac{1}{2} + V_b - \frac{V_d}{2} = 3 \\ -V_b \frac{1}{2} + V_d(\frac{3}{4}) = -1 \end{cases}$$

$$5V_a - 3V_b = 6$$

$$-V_a + 2V_b - V_d = 6$$

$$-2V_b + 3V_d = -4$$

$$V_a = \frac{\begin{vmatrix} 6 & -3 & 0 \\ 6 & 2 & -1 \\ -4 & -2 & 3 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & 0 \\ -1 & 2 & -1 \\ 0 & -2 & 3 \end{vmatrix}} = \frac{6(6-2) + 3(18-4)}{5(6-2) + 3(-3)} = \frac{24 + 42}{20-9} = \frac{66}{11} = 6$$

$$V_b = \frac{\begin{vmatrix} 5 & 6 & 0 \\ -1 & 6 & -1 \\ 0 & -4 & 3 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & 0 \\ -1 & 2 & -1 \\ 0 & -2 & 3 \end{vmatrix}} = \frac{5(18-4) - 6(-3)}{20-9} = \frac{70+18}{11} = \frac{88}{11} = 8V$$


$$V_d = \frac{\begin{vmatrix} 5 & -3 & 6 \\ -1 & 2 & 6 \\ 0 & -2 & -4 \end{vmatrix}}{\begin{vmatrix} 5 & -3 & 0 \\ -1 & 2 & -1 \\ 0 & -2 & 3 \end{vmatrix}} = \frac{5(-8+12) + (12+12)}{20-9} = \frac{4V}{11}$$

$$i_1 = \frac{V_a - V_b}{2} = -1$$


$$i_2 = -\frac{V_a}{3} = -2$$

$$i_3 = -\frac{V_d}{4} = -1$$

$$i_4 = \frac{V_b - V_d}{2} = 2$$

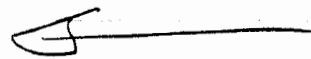

2.9

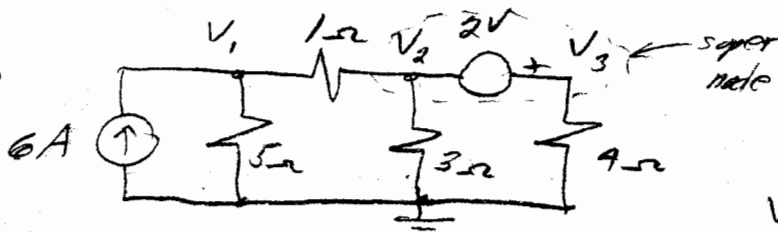

$$V_3 = V_2 + 2$$

$$\frac{V_1}{5} + \frac{V_1 - V_2}{1} = 6$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_3}{4} = 0$$

giving:

$$\frac{6}{5}V_1 - V_2 = 6$$

$$-V_1 + V_2(1 + \frac{1}{3} + \frac{1}{4}) = -\frac{1}{2}$$


$$\left. \begin{aligned} 6V_1 - 5V_2 &= 30 \\ -12V_1 + 19V_2 &= -6 \end{aligned} \right\}$$

$$V_1 = \frac{\begin{vmatrix} 30 & -5 \\ -6 & 19 \end{vmatrix}}{\begin{vmatrix} 6 & -5 \\ -12 & 19 \end{vmatrix}} = \frac{570 - 30}{114 - 60} = \frac{540}{54} = 10 \text{ Volts}$$

$$V_2 = \frac{\begin{vmatrix} 6 & 30 \\ -12 & -6 \end{vmatrix}}{54} = \frac{-36 + 360}{54} = \frac{324}{54} = 6 \text{ Volts}$$

$$V_3 = V_2 + 2 = 8 \text{ Volts}$$

2.10

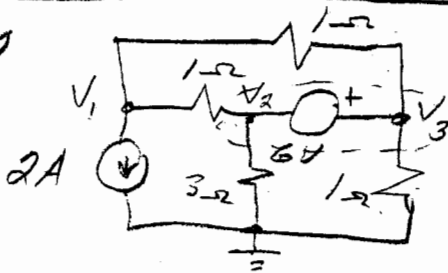

$$\frac{V_1 - V_3}{1} + \frac{V_1 - V_2}{1} = -2$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{3} + \frac{V_3 - V_1}{1} + \frac{V_3}{1} = 0$$

$$V_3 - V_2 = 6$$

giving:

$$2V_1 - V_2 - V_3 = -2$$

$$-2V_1 + V_2(1 + \frac{1}{3}) + 2V_3 = 0$$


$$-V_2 + V_3 = 6$$

$$\left. \begin{aligned} 2V_1 - V_2 - V_3 &= -2 \\ -6V_1 + 4V_2 + 6V_3 &= 0 \\ -V_2 + V_3 &= 6 \end{aligned} \right\}$$

$$V_1 = \frac{\begin{vmatrix} -2 & -1 & -1 \\ 0 & 4 & 6 \\ 0 & -1 & 1 \end{vmatrix}}{\begin{vmatrix} 2 & -1 & -1 \\ -6 & 4 & 6 \\ 0 & -1 & 1 \end{vmatrix}} = \frac{-2(4+6) + 6(-6+4)}{2(4+6) + 6(-1-1)} = \frac{-20 - 12}{20 - 12} = -\frac{32}{8} = -4V$$

$$V_2 = \frac{\begin{vmatrix} 2 & -2 & -1 \\ -6 & 0 & 6 \\ 0 & 6 & 1 \end{vmatrix}}{8} = \frac{2(-36) + 6(-2+6)}{8} = \frac{-72 + 36}{8} = \frac{24}{8} = 3V$$

$$V_3 = V_2 + 6 = 9V$$

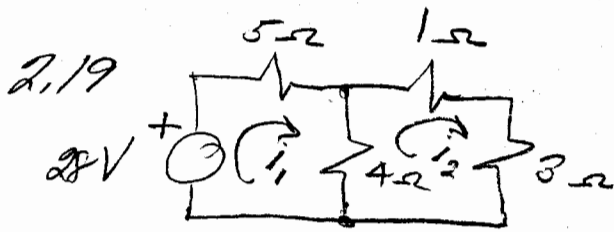

$$5i_1 + 4(i_1 - i_2) = 28$$


$$4(i_2 - i_1) + 4i_2 = 0$$

$$\text{or } \left. \begin{array}{l} 9i_1 - 4i_2 = 28 \\ -4i_1 + 8i_2 = 0 \end{array} \right\} \begin{array}{l} 9i_1 - 4i_2 = 28 \\ -i_1 + 2i_2 = 0 \end{array}$$

$$i_1 = \frac{\begin{vmatrix} 28 & -4 \\ 0 & 2 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -1 & 2 \end{vmatrix}} = \frac{56}{18-4} = \frac{56}{14} = 4 \text{ A} \quad \leftarrow$$

$$i_2 = \frac{\begin{vmatrix} 9 & 28 \\ -1 & 0 \end{vmatrix}}{14} = \frac{28}{14} = 2 \text{ A} \quad \leftarrow$$

2.10 (corrected)

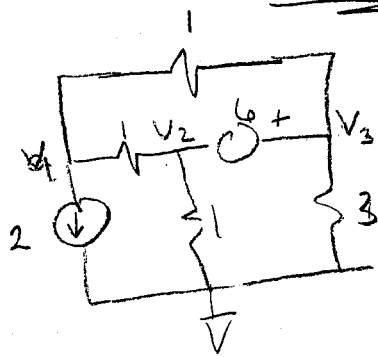

$$\frac{V_1 - V_3}{1} + \frac{V_1 - V_2}{1} = -2$$

$$V_3 - V_2 = 6$$

$$\frac{V_2 - V_1}{1} + \frac{V_2}{1} + \frac{V_3 - V_1}{1} + \frac{V_3}{3} = 0$$

$$2V_1 - V_2 - V_3 = -2$$

$$-2V_1 + 2V_2 + \frac{4}{3}V_3 = 0$$

$$2V_1 - V_2 + V_3 = 6$$

$$\Delta = \begin{vmatrix} 2 & -1 & -1 \\ -2 & 2 & 4/3 \\ 0 & -1 & 1 \end{vmatrix} = \frac{8}{3}$$

$$\Delta_1 = \begin{vmatrix} -2 & -1 & -1 \\ 0 & 2 & 4/3 \\ 6 & -1 & 1 \end{vmatrix} = -\frac{8}{3}$$


$$\Delta_2 = \begin{vmatrix} 2 & -2 & -1 \\ -2 & 0 & 4/3 \\ 0 & 6 & 1 \end{vmatrix} = -8$$

$$\Delta_3 = \begin{vmatrix} 2 & -1 & -2 \\ -2 & 2 & 0 \\ 0 & -1 & 6 \end{vmatrix} = 8$$

$$V_1 = \frac{\Delta_1}{\Delta} = -1$$

$$V_2 = \frac{\Delta_2}{\Delta} = -3$$

$$V_3 = \frac{\Delta_3}{\Delta} = 3$$

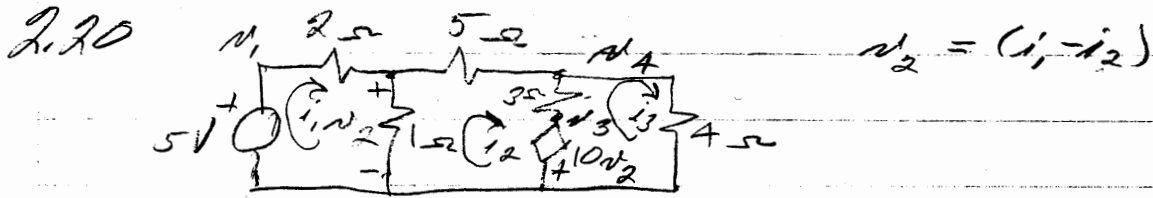


$$\left. \begin{aligned} i_1 \cdot 2 + (i_1 - i_2) \cdot 1 &= 5 \\ (i_2 - i_1) \cdot 1 + i_2 \cdot 5 + (i_2 - i_3) \cdot 3 - 10i_2 &= 0 \\ 10i_2 + (i_3 - i_2) \cdot 3 + i_3 \cdot 4 &= 0 \end{aligned} \right\} \begin{aligned} 3i_1 - i_2 &= 5 \\ -11i_1 + 19i_2 - 3i_3 &= 0 \\ 10i_1 - 13i_2 + 7i_3 &= 0 \end{aligned}$$

$$i_1 = \frac{\begin{vmatrix} 5 & -1 & 0 \\ 0 & 19 & -3 \\ 0 & -13 & 7 \end{vmatrix}}{\begin{vmatrix} 3 & -1 & 0 \\ -11 & 19 & -3 \\ 10 & -13 & 7 \end{vmatrix}} = \frac{5(133 - 39)}{3(133 - 39) + 1(-77 + 30)} = \frac{470}{235} = 2 \text{ A} \leftarrow$$

$$i_2 = \frac{\begin{vmatrix} 3 & -1 & 0 \\ -11 & 0 & -3 \\ 10 & 0 & 7 \end{vmatrix}}{235} = \frac{-5(-77 + 30)}{235} = 1 \text{ A} \leftarrow$$
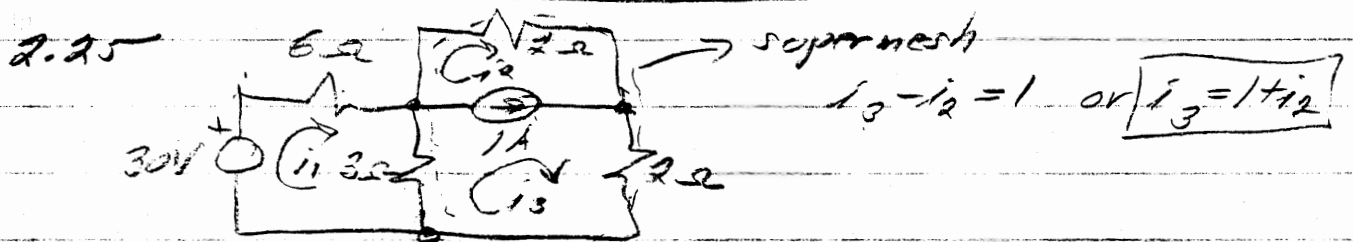
$$i_3 = \frac{\begin{vmatrix} 3 & -1 & 5 \\ -11 & 19 & 0 \\ 10 & -13 & 0 \end{vmatrix}}{235} = \frac{5(143 - 110)}{235} = -1 \text{ A} \leftarrow$$




$$\left. \begin{aligned} i_1 \cdot 6 + (i_1 - i_2) \cdot 3 &= 30 \\ (i_2 - i_1) \cdot 3 + i_2 \cdot 2 + i_3 \cdot 2 &= 0 \end{aligned} \right\} \begin{aligned} 9i_1 - 3i_2 &= 33 \\ -3i_1 + 7i_2 &= -5 \end{aligned}$$

$$i_1 = \frac{\begin{vmatrix} 33 & -3 \\ -5 & 7 \end{vmatrix}}{\begin{vmatrix} 9 & -3 \\ -3 & 7 \end{vmatrix}} = \frac{231 - 15}{63 - 9} = \frac{216}{54} = 4 \text{ A} \leftarrow$$


$$i_2 = \frac{\begin{vmatrix} 9 & 33 \\ -3 & -5 \end{vmatrix}}{54} = \frac{-45 + 99}{54} = 1 \text{ A} \leftarrow$$

$$i_3 = 2 \text{ A} \leftarrow$$

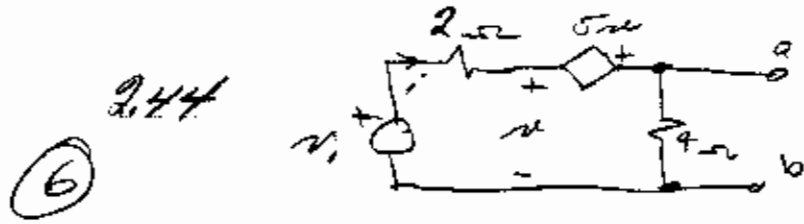



$v = v_1 - 2i$ ✓
 $v_1 = 2i - 5u + 4i$ ✓

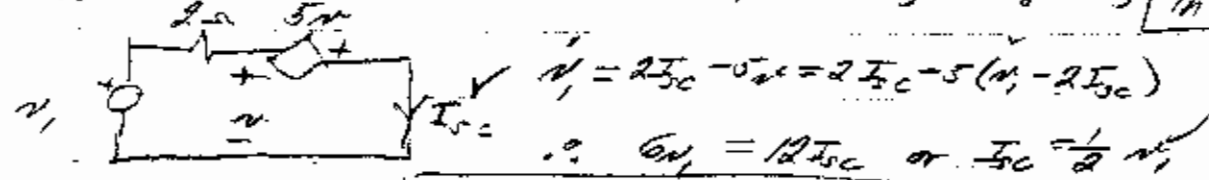∴ $v_1 = 6i - 5(u - 2i)$ V or $Gv_1 = 16i$; $i = \frac{3}{8}v_1$; $V_{Th} = 4i = \frac{3}{2}v_1$





∴ $Gv_1 = 12I_{sc}$ or $I_{sc} = \frac{1}{2}v_1$

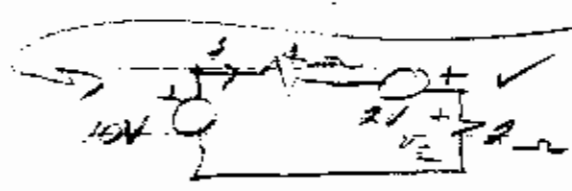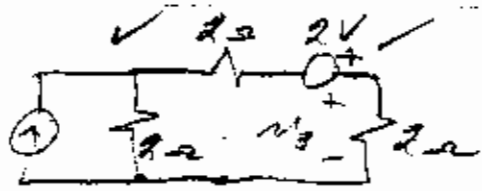$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{\frac{3}{2}v_1}{\frac{1}{2}v_1} = 3 \Omega$ ✓








$12 = 6i$ or $i = 2A$


∴ $v_3 = 2i = 4V$ ✓

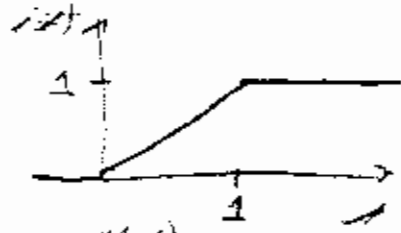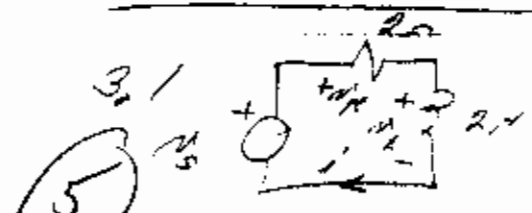

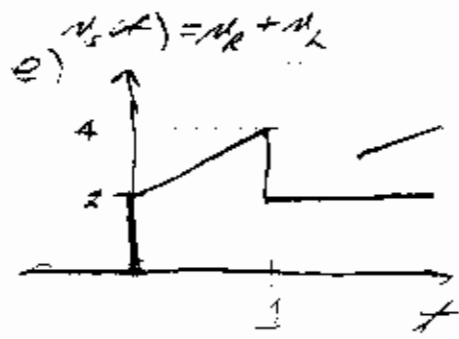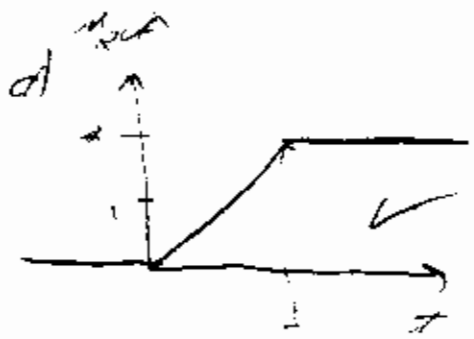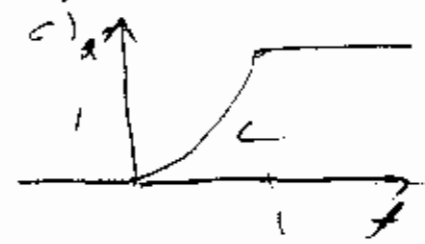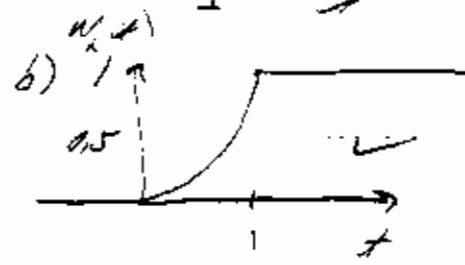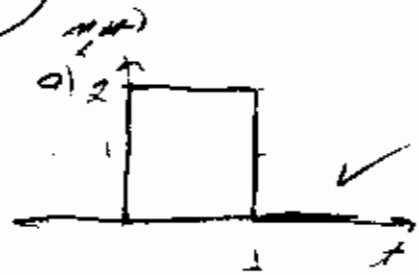$v_L(t) = L \frac{di}{dt}$
 $w_L = \frac{1}{2} L i^2$
 Power = $i^2 R$



2.44 again

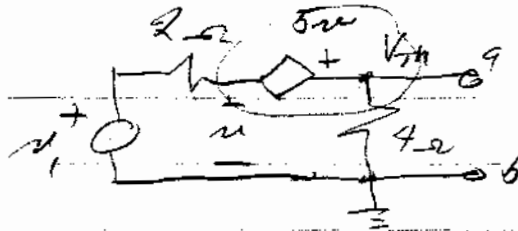


$$\frac{v - v_1}{2} + \frac{V_{Th}}{4} = 0$$

$$5v = V_{Th} - v \Rightarrow 6v = V_{Th}$$

$$\frac{0}{12} - \frac{v_1}{2} + \frac{V_{Th}}{4} = 0$$
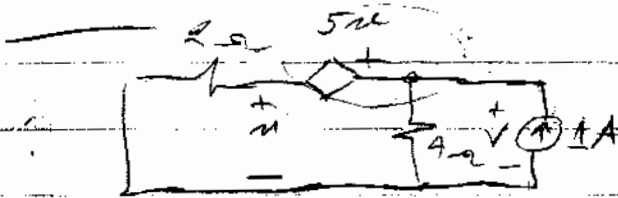
$$; V_{Th} \left(\frac{1}{3}\right) = \frac{v_1}{2} \Rightarrow \boxed{V_{Th} = \frac{3}{2} V_1}$$



$$\frac{v}{2} + \frac{V}{4} = 1$$

$$v - v = 5v \Rightarrow v = 6v$$

$$\frac{V}{12} + \frac{V}{4} = 1$$

$$; \frac{1}{3}V = 1 ; V = 3 ; \boxed{R_{Th} = \frac{V}{1} = 3 \Omega}$$

3.15 a) $i \rightarrow \frac{L_1}{n} \frac{di_1}{dt} + \frac{L_2}{n} \frac{di_2}{dt} \equiv \frac{L_{eq}}{n} \frac{di}{dt}$ $n = L_{eq} \frac{di}{dt}$

but $n = n_1 + n_2 = L_1 \frac{di_1}{dt} + L_2 \frac{di_2}{dt} = (L_1 + L_2) \frac{di}{dt} \therefore L_{eq} = L_1 + L_2$

b) $\frac{i}{n} \frac{L_1}{n} \frac{di_1}{dt} + \frac{i}{n} \frac{L_2}{n} \frac{di_2}{dt} \equiv \frac{i}{n} L_{eq} \frac{di}{dt}$ $i = \frac{1}{L_{eq}} \int_0^t n dt + i(0)$

$i_1 = \frac{1}{L_1} \int_0^t n dt + i_1(0)$; $i_2 = \frac{1}{L_2} \int_0^t n dt + i_2(0)$

$\therefore i = i_1 + i_2 = \left(\frac{1}{L_1} + \frac{1}{L_2}\right) \int_0^t n dt + i(0)$ so $\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$


c) $\frac{i}{n} \frac{C_1}{n} \frac{di_1}{dt} + \frac{i}{n} \frac{C_2}{n} \frac{di_2}{dt} \equiv \frac{i}{n} C_{eq} \frac{di}{dt}$ $i = C_{eq} \frac{di}{dt}$

$i = i_1 + i_2 = C_1 \frac{di_1}{dt} + C_2 \frac{di_2}{dt} = (C_1 + C_2) \frac{di}{dt} \therefore C_{eq} = C_1 + C_2$

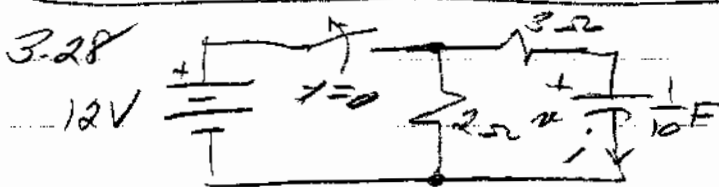d) $\frac{i}{n} \frac{C_1}{n} \frac{di_1}{dt} + \frac{i}{n} \frac{C_2}{n} \frac{di_2}{dt} \equiv \frac{i}{n} C_{eq} \frac{di}{dt}$ $n = C_{eq} \int_0^t i dt + n(0)$

$n = n_1 + n_2 = C_1 \int_0^t i dt + n_1(0) + C_2 \int_0^t i dt + n_2(0) = \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int_0^t i dt + n(0)$

$\therefore \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$



$v_c(0) = 12 \text{ Volts}$

a) $\frac{n}{5} + \frac{1}{10} \frac{dn}{dt} = 0$ for $t > 0$


$n = A e^{st}$ so $2 + 5 = 0 \Rightarrow s = -2$; $n = 12 e^{-2t}$

$i = C \frac{dn}{dt} = \frac{1}{10} (-24) e^{-2t} = -2.4 e^{-2t}$

ES 332

Homework 8

3.29

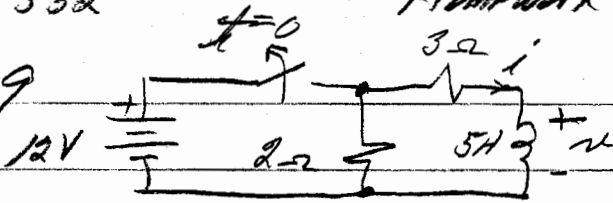

$$i(0) = \frac{12 \times 5}{8} \cdot \frac{2}{5} = 4$$

$$5i + 5 \frac{di}{dt} = 0$$

$$i = A e^{-t}$$

$$\therefore s = -1$$

$$i(t) = A_1 e^{-t}$$


$$\text{but } i(0) = 4$$

$$\therefore \boxed{i(t) = 4e^{-t}}$$

$$\boxed{M(t) = -5i = -20e^{-t}}$$

$$\text{or } M(t) = 5 \frac{di}{dt} = -20e^{-t} \quad \text{check}$$

3.34

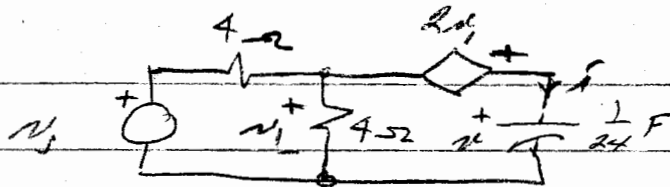


$$v_s(t) = 12 \text{ for } t < 0$$

$$v_s(t) = 0 \text{ for } t > 0$$

for $t < 0$ $v_s = 6$ and $v = 3v_s = 18V$

for $t > 0$ circuit becomes

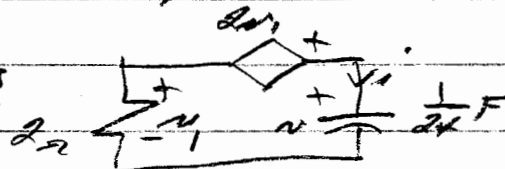

$$(1) \quad 2i - 2v + 24 \int_0^t i dt + 18 = 0 \quad \text{but } v = -2i$$

$$\therefore 6i + 24 \int_0^t i dt + 18 = 0$$

$$\text{or } \frac{di}{dt} + 4i = 0 \quad ; \quad i = A e^{st} \Rightarrow s = -4$$

$$i(t) = A e^{-4t}$$

$$\text{from (1)} \quad 6i(0) = -18 \quad \text{or } i(0) = -3$$

$$\therefore i(t) = -3 e^{-4t} \quad \leftarrow$$

$$v = 3v_s = -6i = 18 e^{-4t} \quad \leftarrow$$

4.1 a) $4+j7 = 8.06 e^{j'60.25^\circ}$

b) $3-j5 = 5.83 e^{-j'59.04^\circ}$

c) $-2+j3 = 3.6 e^{j'113.7^\circ}$



d) $-1-j6 = 6.08 e^{-j'26.5^\circ}$

e) $4 = 4 e^{j'0^\circ}$

f) $-5 = 5 e^{j'180^\circ}$

g) $j7 = 7 e^{j'90^\circ}$

h) $-j2 = 2 e^{-j'90^\circ}$

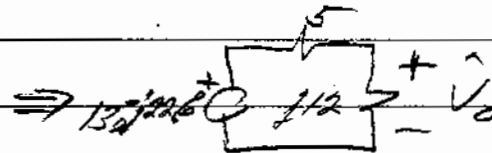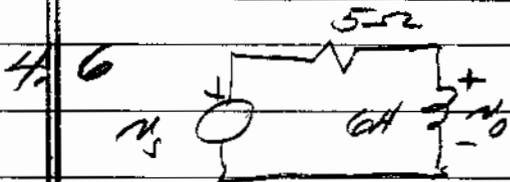


$N_o(t) = 13 \cos(2t - 22.6^\circ)$



$\hat{V}_o = \frac{j12}{5+j12} \cdot 13 e^{-j'22.6^\circ}$

or $\hat{V}_o = \frac{156 e^{j'67.4^\circ}}{13 e^{j'67.38^\circ}} = 12 e^{j'0.02^\circ} \approx 12$

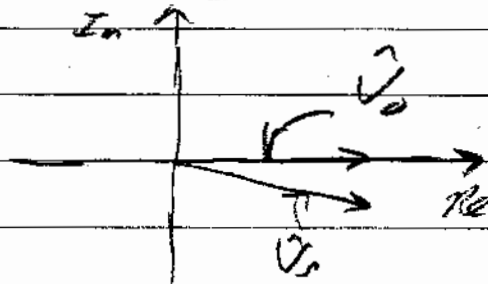$\therefore N_o(t) = 12 \cos(2t + 0^\circ)$




\hat{V}_o leads \hat{V}_s

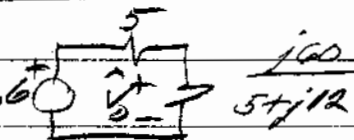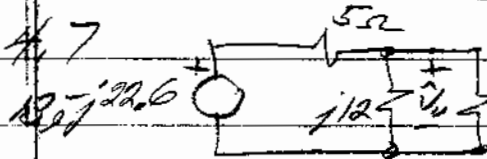

$\hat{V}_o = \frac{j160}{5+j12} \cdot 13 e^{-j'22.6^\circ} = \frac{j608 e^{-j'22.6^\circ}}{122.58 e^{j'78.23^\circ}} = 7.82 e^{j'67.4^\circ}$

$\hat{V}_o = 6.36 e^{j'10.83^\circ}$

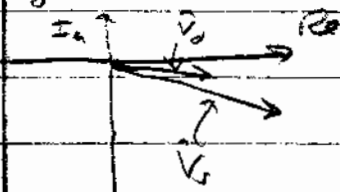
so $N_o(t) = 6.36 \cos(2t - 10.83^\circ)$



\hat{V}_o leads \hat{V}_s

4.9


$i_s = 5 \cos 3t$

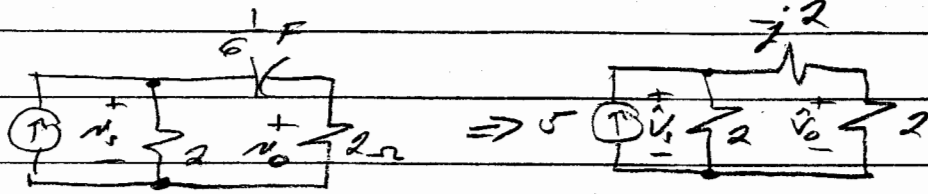

$$\hat{V}_0 = 5 \frac{2 \times 2}{2 - j2 + 2} = \frac{20}{4 + j2} = 4.472 \angle -26.56^\circ \quad i_0(t) = 4.472 \cos(3t - 26.56^\circ)$$

$$\hat{V}_1 = \frac{10(2 - j2)}{4 - j2} = \frac{10 \times 2 \times 1.414 \angle -45^\circ}{4.472 \angle -26.56^\circ} = 6.32 \angle -18.4^\circ \quad i_1(t) = 6.32 \cos(3t - 18.4^\circ)$$

4.17

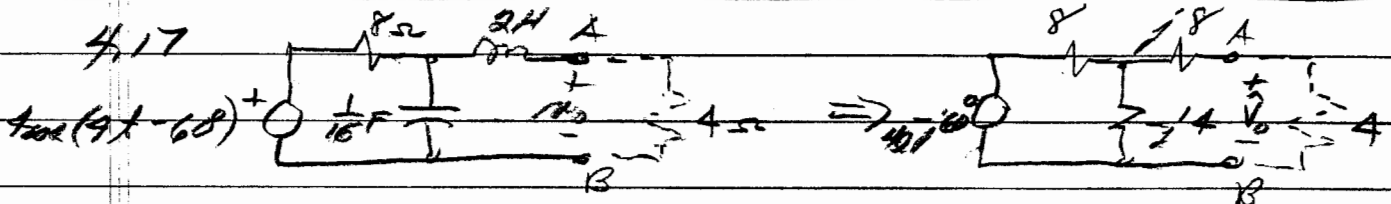

$$\text{@ A-B } \hat{V}_{Th} = \frac{401 \angle 60^\circ (-j4)}{8 - j4} = \frac{e^{j60^\circ} 4 e^{-j90^\circ}}{8.236 \angle -26.56^\circ} = 1.789 e^{-j123.44^\circ}$$

$$Z_{Th} = j8 + \frac{8(-j4)}{8 - j4} = \frac{64j + 32 - j32}{8 - j4} = \frac{32 + j32}{8 - j4} = \frac{32 \times 1.414 \angle 45^\circ}{8.944 \angle -26.56^\circ} = 5.059 \angle 71.56^\circ$$


or $Z_{Th} = 1.6 + j4.799$

$$\text{so } \hat{V}_0 = \frac{1.789 e^{-j123.44^\circ} \times 4}{(5.6 + j4.799)} = \frac{4 \times 1.789 e^{-j123.44^\circ}}{7.375 \angle 40.6^\circ} = 0.97 e^{-j164^\circ}$$

or $i_0(t) = 0.97 \cos(4t - 160^\circ)$


4.28

Power

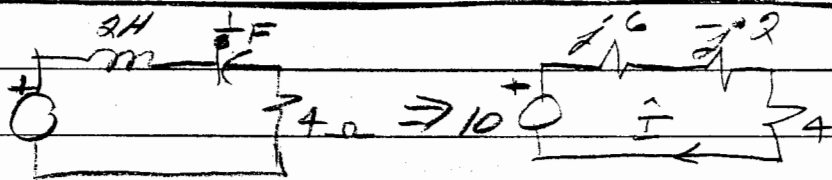

$$\hat{I} = \frac{10}{4 + j6} = \frac{5}{2 + j2} = \frac{5 \angle -45^\circ}{2\sqrt{2}}$$

$$P_{ave} = \frac{1}{2} |\hat{I}|^2 \times 4 = 2 \times \frac{25}{8} = \frac{25}{4} = 6.25 \text{ Watts}$$

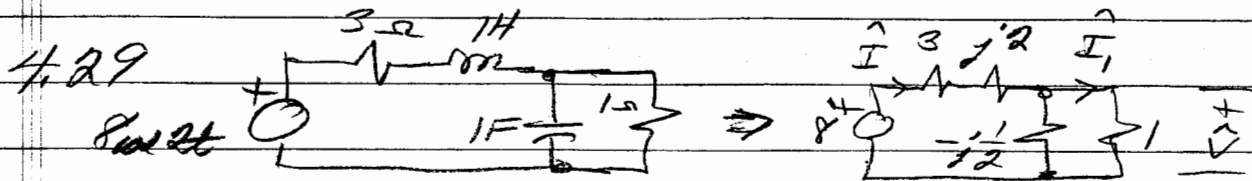

$$\hat{I} = \frac{8}{3 + j2 + \frac{-j2}{1-j2}} = \frac{8(1-j2)}{3 - j\frac{3}{2} + j2 + 1 - j2} = \frac{8-j4}{4} = 2-j$$

$$\text{or } \hat{I} = \sqrt{5} \angle -26.56^\circ$$

$$\hat{I}_1 = \hat{I} \frac{-j2}{1-j2} = (2-j) \frac{-j}{2-j} = -j$$

$$P_{3\Omega} = \frac{1}{2} |\hat{I}|^2 \cdot 3 = \frac{15}{2} \text{ W} \quad \leftarrow$$


$$P_{1\Omega} = \frac{1}{2} |\hat{I}_1|^2 \cdot 1 = \frac{1}{2} \text{ W} \quad \leftarrow$$

$$P_{1H} = P_{1F} = 0 \quad \leftarrow$$

$$P_{\text{SOURCE}} = -8 \times \frac{\sqrt{5}}{2} \cos(26.56^\circ) = -8 \text{ Watts} \quad \leftarrow$$

ES 332 R1 V Homework 13

2.28

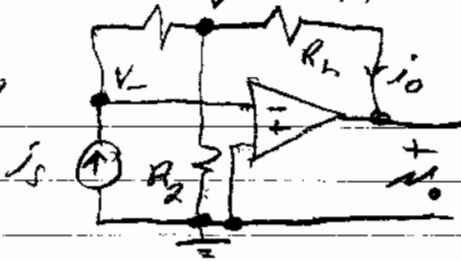

KCL @ V gives:

$$\frac{V}{R_1} + \frac{V}{R_2} + \frac{V - v_o}{R_1} = 0$$

but $\frac{V}{R_1} = -i_s \quad \therefore -i_s R_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_1} \right) = \frac{v_o}{R_1}$


or $v_o = -i_s R_1 R_2 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_1} \right)$ ←

$$v_o = -i_s \left(\frac{R_2 R_1 + R_1 R_2 + R_1 R_2}{R_1 R_2 R_1} \right) R_1 R_2$$

$$v_o = -i_s \left(R_2 + \frac{R_1}{R_2} R_2 + R_1 \right)$$
 ←

$$i_o = \frac{V - v_o}{R_2} = \frac{-i_s R_1 - v_o}{R_2} = i_s \left(1 + \frac{R_1}{R_2} \right)$$
 ←

2.30

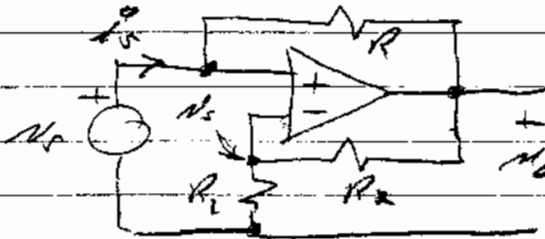

$$\frac{v_s}{R_1} + \frac{v_s - v_o}{R_2} = 0$$


$$v_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_o}{R_2}$$

$$\therefore v_o = v_s \left(1 + \frac{R_2}{R_1} \right)$$
 ←

$$i_s = \frac{v_s - v_o}{R} \quad \therefore i_s = \frac{v_s}{R} - \frac{v_s}{R} \left(1 + \frac{R_2}{R_1} \right) = -v_s \frac{R_2}{R_1 R}$$

$$\frac{v_o}{i_s} = - \frac{R_1}{R_2} (R)$$
 ←


2.45

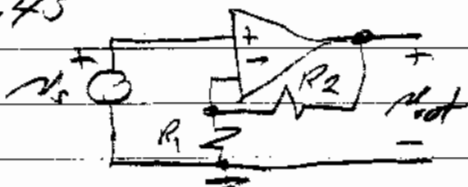

$$\frac{v_s}{R_1} + \frac{v_s - v_{out}}{R_2} = 0$$

$$v_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_{out}}{R_2}$$
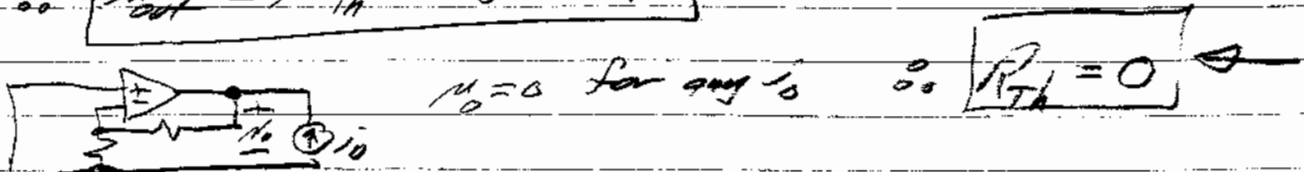
$$\therefore v_{out} = v_{Th} = v_s \left(1 + \frac{R_2}{R_1} \right)$$
 ←




$$v_o = 0 \text{ for any } i_o \quad \therefore R_{Th} = 0$$
 ←

ES 332 Spring 2007
Assignment 14

A temperature sensor has an output of 0.01 volts per degree Fahrenheit from $T = 0$ to $T = 100^\circ\text{F}$ (at $T = 0$ $V_{\text{out}} = 0$). Design an Op-Amp circuit using this sensor that will provide an output voltage of 0 to 10 Volts for a temperature variation of 0 to 100°F .

$$0.01 \times 100 = 1 \text{ volt from sensor @ } T = 100^\circ\text{F}$$

\therefore need a gain of +10

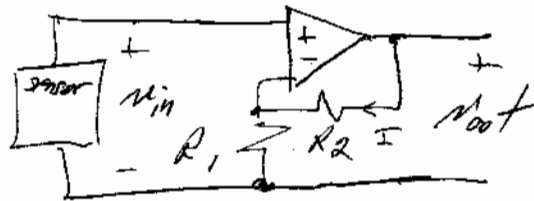


$$I = \frac{V_{\text{out}}}{R_1 + R_2} ; V_{\text{in}} = I R_1$$

$$\therefore V_{\text{out}} = (R_1 + R_2) \frac{V_{\text{in}}}{R_1} = \frac{R_1 + R_2}{R_1} V_{\text{in}}$$


$$\text{so for our design } \frac{R_1 + R_2}{R_1} = 10 \leftarrow$$

$$\text{or } \frac{R_2}{R_1} = 9 \leftarrow$$

10.67

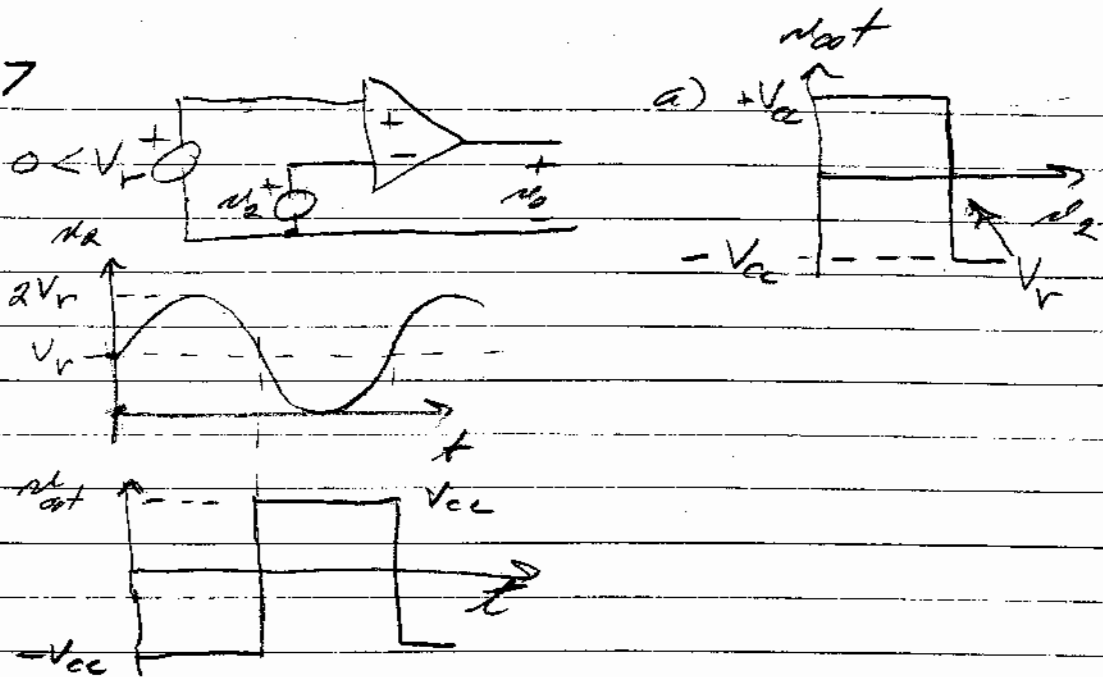

P. 68

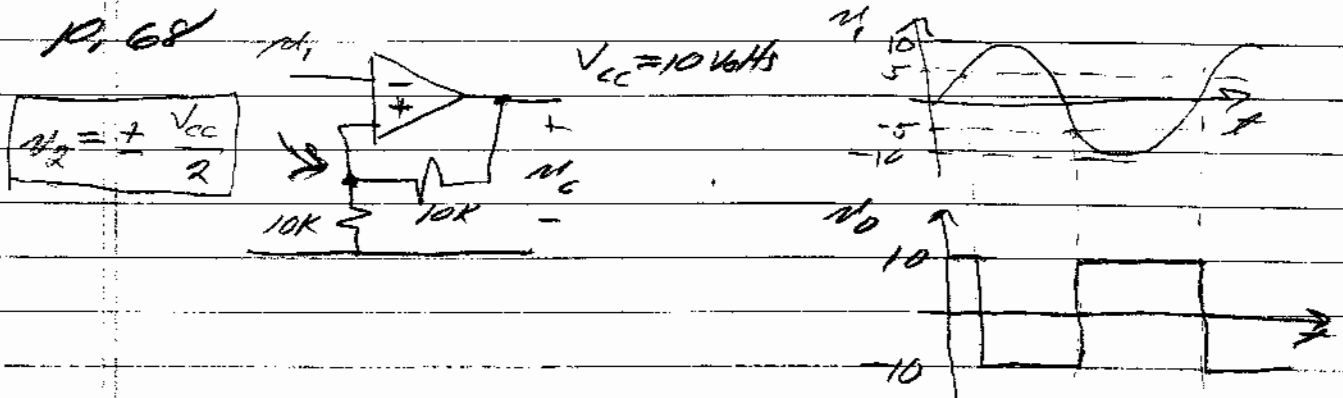

10.79 for 555 timer $f = \frac{1.44}{(R_1 + 2R_2)C}$

a) $f_0 = \frac{1.44}{(15 \times 10^3) \times 10^{-7}} = 960 \text{ Hz}$

b) $1.6 \times 10^3 = \frac{1.44}{15 \times 10^3 C} \therefore C = \frac{1.44}{15 \times 10^3 \times 1.6 \times 10^3} = 0.06 \mu\text{F}$

c) $10^4 = \frac{1.44}{(R_1 + 2 \times 10^4) 5 \times 10^{-9}} \therefore R_1 = \frac{1.44}{5 \times 10^{-5}} - 2 \times 10^4 = 8.8 \text{ k}\Omega$

d) $10^4 = \frac{1.44}{(10^4 + 2R_2) 5 \times 10^{-9}} \therefore R_2 = \left(\frac{1.44}{5 \times 10^{-5}} - 10^4 \right) \frac{1}{2} = 9.4 \text{ k}\Omega$

11.2 a) $11011_2 = 16 + 8 + 2 + 1 = 27$

b) $101011 = 32 + 8 + 2 + 1 = 43$

c) $0,11011_2 = \frac{1}{2} + \frac{1}{4} + \frac{1}{16} + \frac{1}{32} = 0,84375$

d) $0,10101_2 = \frac{1}{2} + \frac{1}{8} + \frac{1}{32} = 0,65625$

e) $10100,011_2 = 16 + 4 + \frac{1}{4} + \frac{1}{8} = 20,375$

f) $10011,101_2 = 16 + 2 + 1 + \frac{1}{2} + \frac{1}{8} = 19,625$

11.3 a) $43 = 101011$

b) $27 = 11011$

c) $0,84375 = 0,11011$ see above


d) $0,65625 = 0,10101$ " "

e) $19,625 = 10011,101$ " "

f) $20,375 = 10100,011$

11.26	A	B	$A \odot B$
	0	0	1
	0	1	0
	1	0	0
	1	1	1
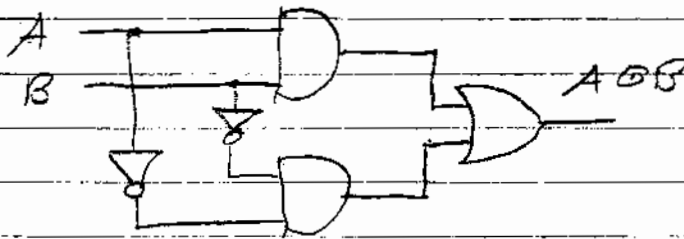
$$A \odot B = \bar{A} \cdot \bar{B} + AB$$




11.44

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

a) $F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
 $F = m_3 + m_5 + m_6 + m_7$

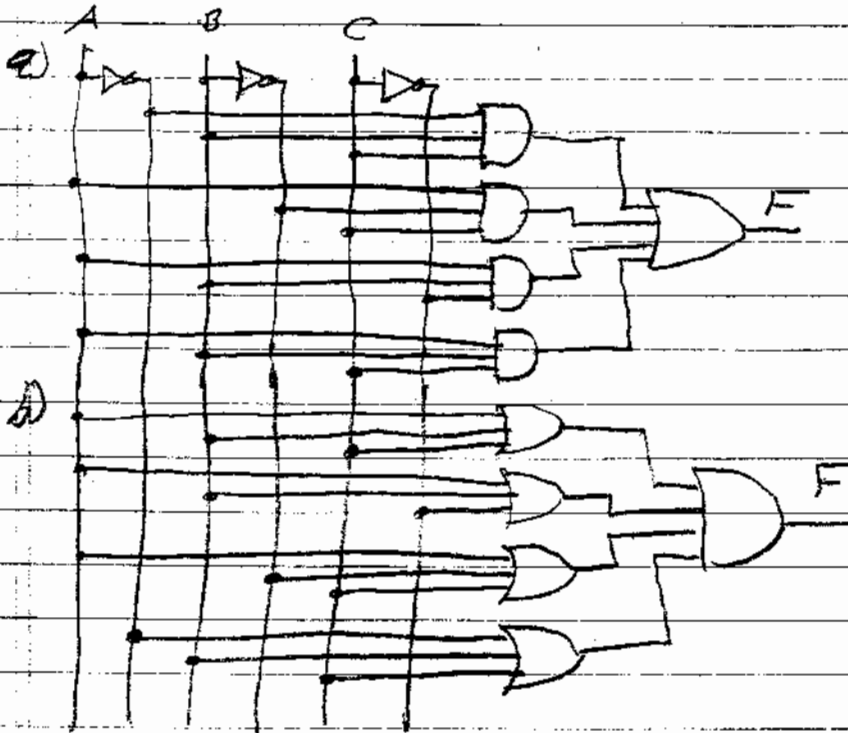b) $\bar{F} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$
 $F = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)$
 or $F = M_0 M_1 M_2 M_4$



11.53

a)

A	BC			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

$F = AB + \bar{B}C + \bar{A}B$

b)

A	BC			
	00	01	11	10
0	0	0	0	1
1	1	1	0	1

$F = A\bar{C} + AB + B\bar{C}$

c)

A	BC			
	00	01	11	10
0	1	1	1	1
1	0	1	0	1

$F = \bar{A} + \bar{B}C + B\bar{C}$


12.14 8x3 encoder

A_1	A_2	A_3	A_4	A_5	A_6	A_7	A_8	B_1	B_2	B_3
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	1	0	0	0
0	0	1	1	0	0	0	0	1	0	0
0	1	0	0	1	0	0	1	0	1	0
1	0	0	0	0	1	0	0	0	0	1
1	0	1	0	0	0	1	0	1	0	0
1	1	0	0	0	0	0	1	1	0	0
1	1	1	0	0	0	0	1	1	1	1

$$B_1 = A_5 + A_6 + A_7 + A_8$$

$$B_2 = A_3 + A_4 + A_7 + A_8$$

$$B_3 = A_2 + A_4 + A_6 + A_8$$

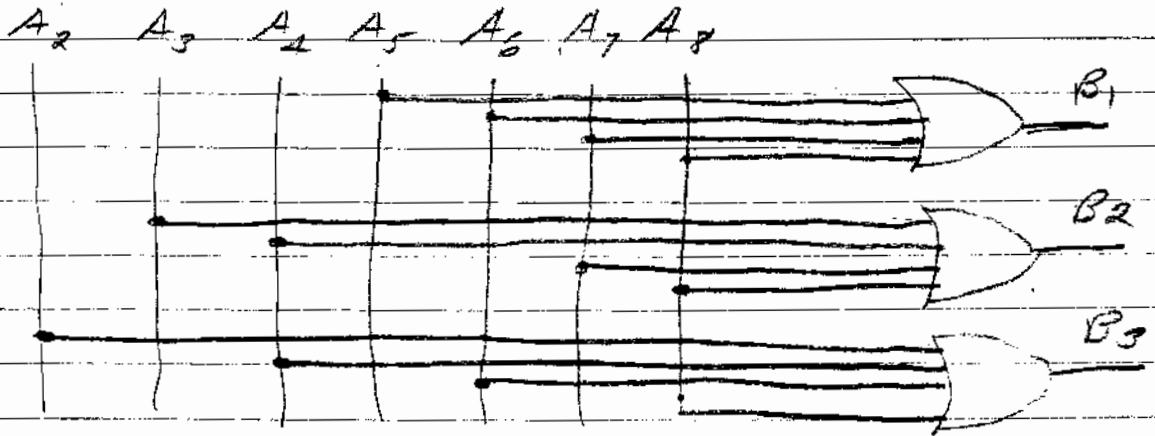

12.17

A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	0	1	0	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	0	0	0

(D)

	BC			
A	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$\therefore D = A$

(E)

	BC	
A	00	01
0	0	1
1	1	0

$E = A\bar{B} + \bar{A}B$

(F)

	BC	
A	00	01
0	0	1
1	1	0


$F = \bar{B}C + B\bar{C}$

have results of form $F = X\bar{Y} + \bar{X}Y$
truth table for this function is:

X	Y	F
0	0	0
0	1	1
1	0	1
1	1	0

} This is exclusive OR $X \oplus Y$

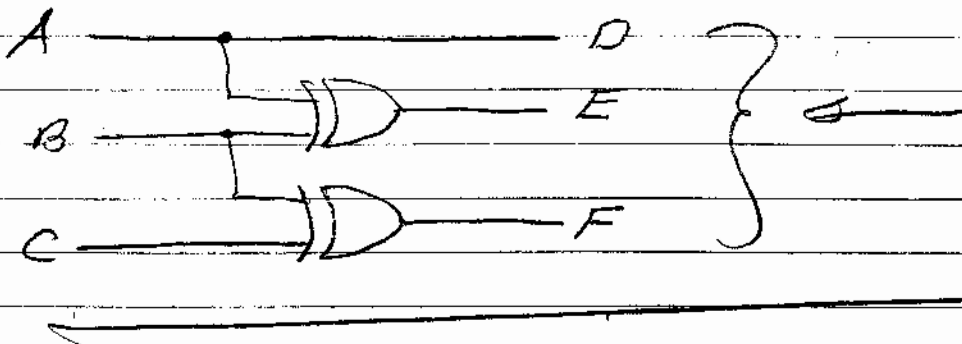so we can realize our converter as follows



12.4	A_i	B_i	R_i	D_i	R_{i+1}	$B_i \oplus R_i$
	0	0	0	0	0	0
	0	0	1	1	0	1
	0	1	0	1	1	1
	0	1	1	0	1	0
	1	0	0	0	0	0
	1	0	1	0	0	1
	1	1	0	0	0	1
	1	1	1	1	1	0

D_i

A_i	$B_i R_i$			
	00	01	11	10
0	0	1	0	1
1	1	0	1	0


$$D_i = \bar{A}_i \bar{B}_i R_i + \bar{A}_i B_i \bar{R}_i + A_i \bar{B}_i \bar{R}_i + A_i B_i R_i$$

$$D_i = \bar{A}_i \cdot (B_i \oplus R_i) + A_i \cdot (\overline{B_i \oplus R_i}) = A_i \oplus (B_i \oplus R_i)$$

R_{i+1}

A_i	$B_i R_i$			
	00	01	11	10
0	0	1	1	1
1	0	0	1	0
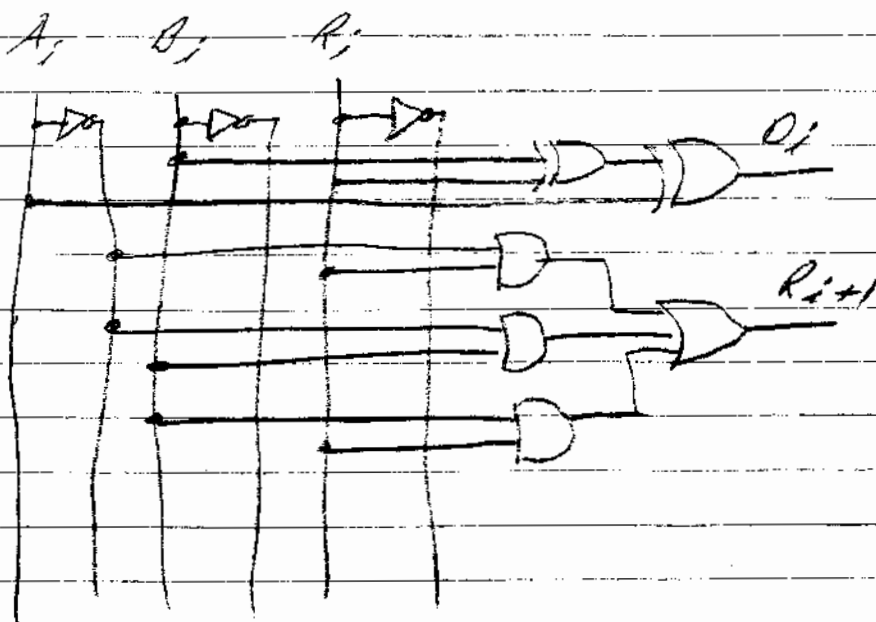
$$R_{i+1} = \bar{A}_i R_i + \bar{A}_i B_i + B_i R_i$$



12/19

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$F = \bar{A}BC + A\bar{B}C + AB \cdot 1 + \bar{A}\bar{B} \cdot 0$$

