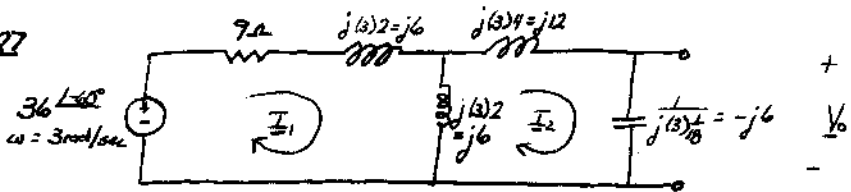


EE212

HW3 Soln

PR. 8.27, 8.29, 8.33, 8.34, 8.36, 8.44

PR. 8.27



$$a) e_{I_1}: -36 \angle 60^\circ + 9I_1 + j6I_1 + j6(I_1 - I_2) = 0$$

$$\Rightarrow (9 + j12)I_1 - j6I_2 = 36 \angle 60^\circ$$

$$e_{I_2}: j6(I_2 - I_1) + j12I_2 - j6I_2 = 0$$

$$\Rightarrow -j6I_1 + j12I_2 = 0$$

$$\Rightarrow j12I_2 = j6I_1$$

$$\Rightarrow 2I_2 = I_1$$

$$\Rightarrow (9 + j12)2I_2 - j6I_2 = 36 \angle 60^\circ$$

$$\Rightarrow (18 + j24 - j6)I_2 = 36 \angle 60^\circ$$

$$\Rightarrow (18 + j18)I_2 = 36 \angle 60^\circ$$

$$\Rightarrow 18\sqrt{2} \angle 45^\circ I_2 = 36 \angle 60^\circ$$

$$\Rightarrow I_2 = \frac{36}{18\sqrt{2}} \angle 60^\circ - 45^\circ$$

$$= \frac{2}{\sqrt{2}} \angle 105^\circ = \sqrt{2} \angle 105^\circ$$

$$* V_0 = -j6I_2 = 6 \angle -90^\circ (\sqrt{2} \angle 105^\circ) = 6\sqrt{2} \angle 195^\circ$$

$$\Rightarrow V_0(t) = 6\sqrt{2} \cos(3t - 195^\circ) \text{ V}$$

$$= 8.49 \cos(3t + 165^\circ) \text{ V}$$

b) for $Z_{\text{seen by source}}$, can either reduce circuit to right of source to equivalent impedance or use $Z_{\text{seen by source}} = \frac{V_s}{I_1}$

$$Z_{\text{seen by source}} = \frac{V_s}{I_1} = \frac{36 \angle 60^\circ}{2\sqrt{2} \angle 105^\circ} = 9\sqrt{2} \angle 45^\circ = 9 + j9$$


$$\Rightarrow Z_{\text{seen by source}} = 9\sqrt{2} \angle 45^\circ \Omega$$

$$= 9 + j9 \Omega$$

EE212

HW3 Soln

PR 8.29

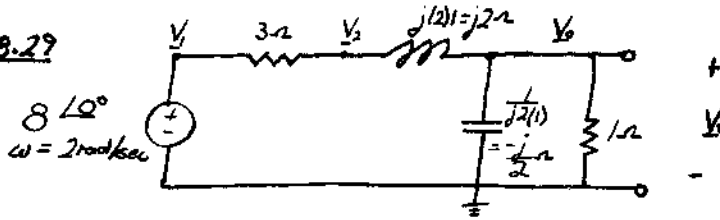

a) e V_1 : $V_1 = 8\angle 0^\circ$

e V_2 : $\frac{V_2 - V_1}{3} + \frac{V_2 - V_0}{j2} = 0$

$$\Rightarrow j2V_2 - j2V_1 + 3V_2 - 3V_0 = 0$$

$$\Rightarrow (3+j2)V_2 - j2V_1 - 3V_0 = 0$$

e V_0 : $\frac{V_0 - V_2}{j2} + \frac{V_0 - 0}{1} + \frac{V_0 - 0}{1} = 0$

$$\Rightarrow V_0 - V_2 - 4V_0 + j2V_0 = 0$$

$$\Rightarrow (-3+j2)V_0 = V_2$$

$$(3+j2)(-3+j2)V_0 - j2(8\angle 0^\circ) - 3V_0 = 0$$

$$\Rightarrow (-9+j6-j6-4-3)V_0 = 16\angle 90^\circ$$

$$\Rightarrow -16V_0 = 16\angle 90^\circ$$

$$\Rightarrow V_0 = \frac{16\angle 90^\circ}{-16}$$

$$= 1\angle -90^\circ$$

$$\Rightarrow V_0(t) = \cos(2t - 90^\circ) \text{ V}$$

$$= \sin 2t \text{ V}$$

b) can find impedance seen by source by reducing circuit to right of source or use $\frac{V_s}{I_s}$

$$Z_{\text{seen by source}} = \frac{V_s}{I_s} = \frac{8\angle 0^\circ}{\frac{V_1 - V_0}{3}} = \frac{8\angle 0^\circ}{\frac{8\angle 0^\circ - (-3+j2)(1\angle -90^\circ)}{3}} = \frac{24}{8 - (-3+j2)(-j)}$$

$$= \frac{24}{8 - j3 - 2} = \frac{24}{6 - j3} \cdot \frac{(6+j3)}{(6+j3)} = \frac{24(6+j3)}{36+9}$$


$$= \frac{24}{45}(6+j3) = 3.2 + j1.6$$

$$Z_{\text{seen by source}} = 3.2 + j1.6 \Omega$$

EE212


HW3 SOLN

PR8.33

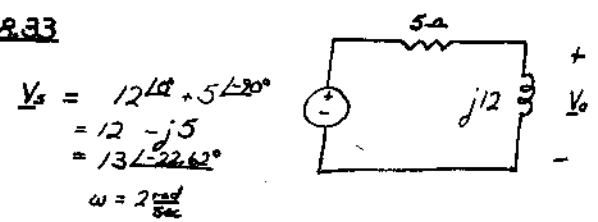

$$\begin{aligned} \underline{V}_s &= 12\angle 0^\circ + 5\angle -90^\circ \\ &= 12 - j5 \\ &= 13\angle -22.62^\circ \\ \omega &= 2 \frac{\text{rad}}{\text{sec}} \end{aligned}$$
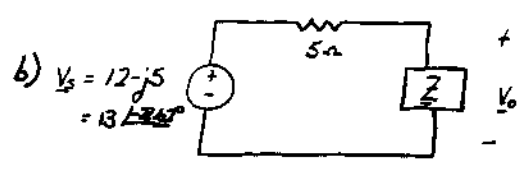
$$a) \underline{V}_o = \frac{(13\angle -22.62^\circ)(j12)}{5+j12} = \frac{(12-j5)(j12)}{5+j12} = 12 \Rightarrow \underline{V}_o(t) = 12\cos 2t \text{ V}$$




$$b) \underline{V}_s = 12 - j5 = 13\angle -22.62^\circ$$

$$\underline{Z} = \frac{5(j12)}{5+j12} = \frac{j60}{5+j12}$$

$$\underline{V}_o = \frac{(12-j5)(j60)}{5 + \frac{j60}{5+j12}} = \frac{(12-j5)(j60)}{5 + \frac{j60}{5+j12}} = 6.25 - j1.2 = 6.36\angle -10.9^\circ$$

$$\Rightarrow \underline{V}_o(t) = 6.36\cos(2t - 10.9^\circ) \text{ V}$$

PR8.34

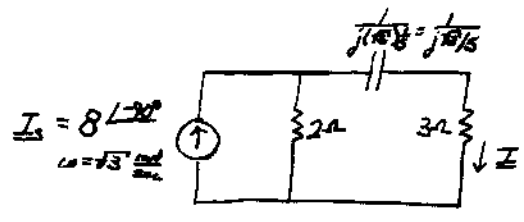

$$\underline{I}_s = 8\angle 90^\circ = j8$$


$$\underline{I} = \frac{(8\angle 90^\circ)(2)}{2 + (3 + \frac{j16}{5})} = \frac{-j16}{5 - j5/5} = 1.385 - j2.4 = 2.77\angle -60^\circ$$

$$\Rightarrow \underline{i}(t) = 2.77\cos(3t - 60^\circ) \text{ A}$$

EE212

HW3 Soln

PR8.36

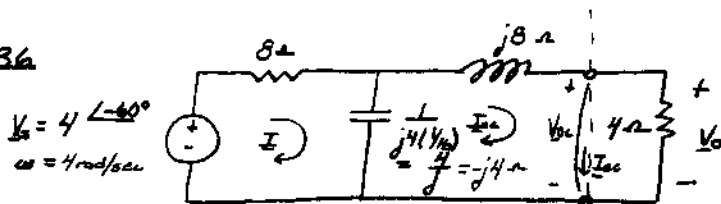

* V_{oc} : $V_{oc} = \frac{(4\angle-40^\circ)(-j4)}{8-j4} = \frac{4\angle-40^\circ \cdot 4\angle90^\circ}{8.944\angle-26.57^\circ} = 1.79\angle-123.4^\circ = \frac{4}{\sqrt{5}}\angle-123.4^\circ$

* I_{sc} : mesh currents $eI: -4\angle-40^\circ + 8I - j4(I - I_{sc}) = 0$

$\Rightarrow (8-j4)I + j4I_{sc} = 4\angle-40^\circ$

$eI_{sc}: -j4(I_{sc} - I) + j8I_{sc} = 0$

$\Rightarrow j4I + j4I_{sc} = 0$

$\Rightarrow -I_{sc} = I$

$(8-j4)(-I_{sc}) + j4I_{sc} = 4\angle-40^\circ$

$\Rightarrow (8+j8)I_{sc} = 4\angle-40^\circ$



$\Rightarrow I_{sc} = \frac{4\angle-40^\circ}{8\sqrt{2}\angle45^\circ}$

$= \frac{\sqrt{2}}{4}\angle-85^\circ$

* Z_{Th} can be found by turning off source or $Z_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{1.79\angle-123.4^\circ}{\frac{\sqrt{2}}{4}\angle-85^\circ}$

$= 5.06\angle-38.4^\circ$

$= 1.6 + j4.8\Omega$

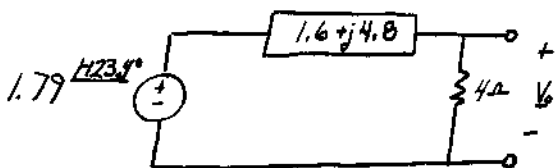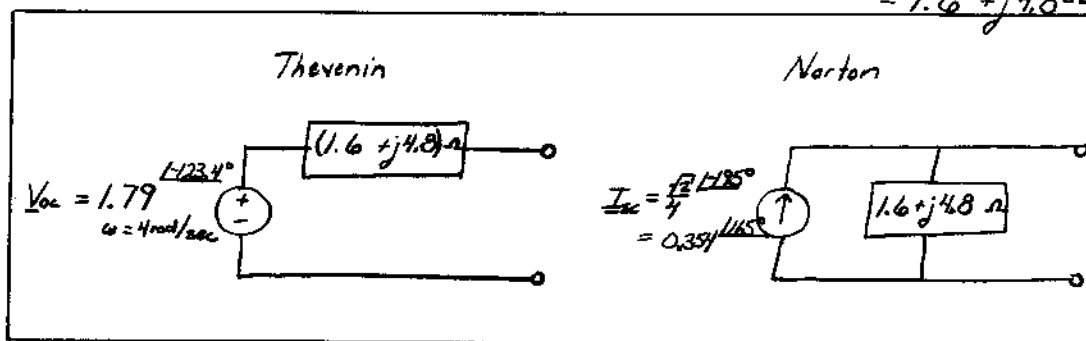


$V_o = \frac{(1.79\angle-123.4^\circ)(4)}{4 + 1.6 + j4.8}$
 $= -0.933 - j0.267$
 $= 0.97\angle-164^\circ$

$\Rightarrow v_o(t) = 0.97 \cos(4t - 164^\circ) \text{ V}$

EE212

HW3 SOLN

PR 8.44

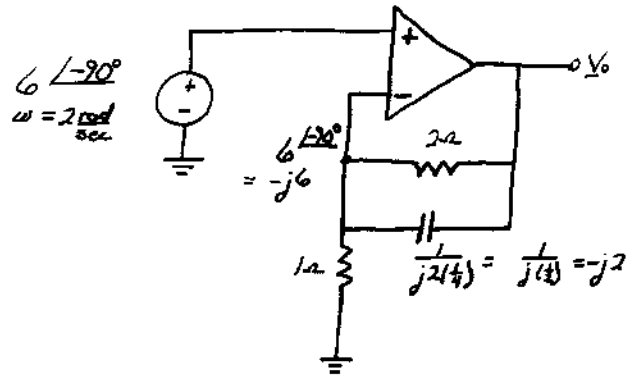

$$\text{KCL: } \frac{(-j6 - v_o)}{2} + \frac{(-j6 - v_o)}{-j2} + \frac{-j6 - 0}{1} = 0$$

$$\Rightarrow -6 + jv_o - j6 - v_o - 12 = 0$$

$$\Rightarrow v_o(-1 + j) = 18 + j6$$

$$\Rightarrow v_o = \frac{18 + j6}{-1 + j} = 13.42 \angle -116.6^\circ$$

$$\Rightarrow v_o(t) = \frac{13.42}{6\sqrt{5}} \cos(2t - 116.6^\circ) \text{ V}$$