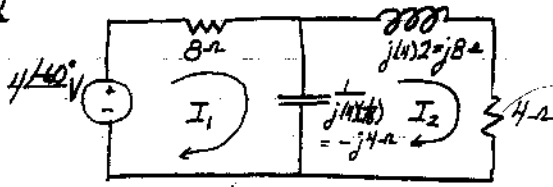


PR 9.2, 9.3, 9.4

9.2



$$I_{1, \text{mesh}}: -4\angle -60^\circ + 8I_1 + (-j4)(I_1 - I_2) = 0$$

$$\Rightarrow I_1(8 - j4) + I_2(j4) = 4\angle -60^\circ$$

$$I_{2, \text{mesh}}: (-j4)(I_2 - I_1) + j8I_2 + 4I_2 = 0$$

$$\Rightarrow I_1(j4) + I_2(j4 + j8 + 4) = 0$$

$$\Rightarrow I_1(j4) + I_2(4 + j4) = 0$$

$$\Rightarrow I_1 = \frac{I_2(4 + j4)}{-j4}$$

$$= \frac{I_2(4 + j4)j4}{(-j4)(j4)}$$

$$= \frac{I_2(16j - 16)}{16}$$

$$= I_2(-1 + j)$$

$$I_2(-1 + j8 - j4) + I_2j4 = 4\angle -60^\circ$$

$$\Rightarrow I_2(-8 + j4 + j8 + 4 + j4) = 4\angle -60^\circ$$

$$\Rightarrow I_2(-4 + j16) = 4\angle -60^\circ$$

$$\Rightarrow I_2 = \frac{4\angle -60^\circ}{16.49\angle 109^\circ}$$

$$= 0.243\angle -164^\circ \text{ A}$$

$$\Rightarrow I_1 = (\sqrt{2}\angle 135^\circ)(0.243\angle -164^\circ)$$

$$= 0.343\angle -29^\circ \text{ A}$$

$$\Rightarrow P_{8\Omega} = \frac{1}{2}(0.343)^2 8 = 0.471 \text{ W} = 471 \text{ mW}$$

$$P_{4\Omega} = \frac{1}{2}(0.243)^2 4 = 0.118 \text{ W} = 118 \text{ mW}$$

$$P_{2H} = 0 \text{ W}$$

$$P_{\text{cap}} = 0 \text{ W}$$

$$P_{\text{source}} = -\frac{1}{2}(4)(0.343) \cos(-60^\circ - (-29^\circ))$$


$$= -0.588 = -588 \text{ mW}$$

$P_{\text{source}} = -588 \text{ mW}$
$P_{8\Omega} = 471 \text{ mW}$
$P_C = 0 \text{ W}$
$P_L = 0 \text{ W}$
$P_{4\Omega} = 118 \text{ mW}$

22-111 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS



9.3

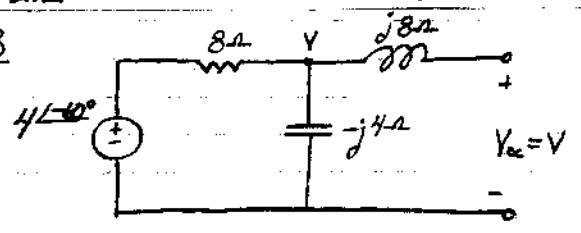

→ find Thevenin equivalent circuit

node eqn @ $V = V_o$: $\frac{V - 4\angle -60^\circ}{8\Omega} + \frac{V - 0}{-j4} = 0$


$\Rightarrow jV - j4\angle -60^\circ - 2V = 0$

$\Rightarrow V(-2 + j) = 4\angle 130^\circ$

$\Rightarrow V = \frac{4\angle 130^\circ}{\sqrt{2^2 + 1^2} \angle \tan^{-1}(1/-2)} = 1.789\angle 123.4^\circ$

$Z_o = \frac{8(-j4)}{8-j4} + j8 = \frac{-j32}{8-j4} + j8 = \frac{-j32(8+j4)}{8^2 + 4^2} + j8$
 $= \frac{128(-j2+1)}{80} + j8 = 1.6 + j4.8\Omega$

⇒ Thevenin equivalent:

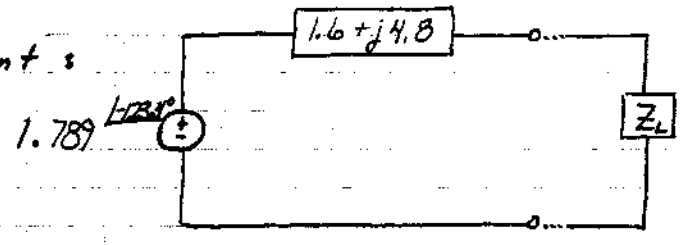

a) for max. power transfer $Z_L = 1.6 - j4.8\Omega$

$P_{max} = \frac{|V_{oc}|^2}{8R_o} = \frac{1.789^2}{8 \cdot 1.6} = 0.25W$

$Z_L = 1.6 - j4.8\Omega$
 $P_{max} = 0.25W$

b) $R_L = \sqrt{1.6^2 + 4.8^2} = 5.06\Omega$

$P_{max} = \frac{1/2 (1.789)^2 (5.06)}{(1.6 + 5.06)^2 + 4.8^2} = 0.12W$


$R_L = 5.06\Omega$
 $P_{max} = 0.12W$

22-141 50 SHEETS
 22-142 100 SHEETS
 22-144 200 SHEETS

EE212

HW4 SOLN

94

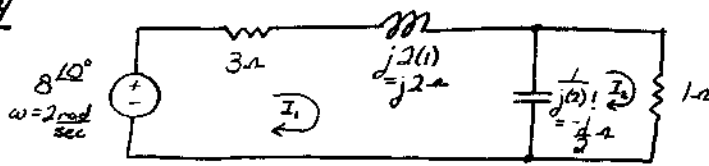

$$\text{mesh } I_1: -8 + 3I_1 + j2I_1 + \left(\frac{1}{2}\right)(I_1 - I_2) = 0$$

$$\Rightarrow (3 + j2 - \frac{1}{2})I_1 + \frac{1}{2}I_2 = 8$$

$$\Rightarrow (6 + j4 - j)I_1 + jI_2 = 16$$

$$\Rightarrow (6 + 3j)I_1 + jI_2 = 16$$

$$\text{mesh } I_2: \left(\frac{1}{2}\right)(I_2 - I_1) + I_2 = 0$$

$$\Rightarrow \frac{1}{2}I_1 + \left(1 - \frac{1}{2}\right)I_2 = 0$$

$$\Rightarrow jI_1 + (2 - j)I_2 = 0$$

$$\Rightarrow I_1 = \frac{1}{j}(j - 2)I_2$$

$$= (1 + j2)I_2$$

$$(6 + 3j)(1 + j2)I_2 + jI_2 = 16$$

$$\Rightarrow (6 + j12 + j3 - 6 + j)I_2 = 16$$

$$\Rightarrow j16I_2 = 16$$

$$\Rightarrow I_2 = \frac{1}{j} = -j = 1 \angle -90^\circ$$

$$\Rightarrow I_1 = (1 + j2)(-j) = -j + 2 = \sqrt{5} \angle 26.6^\circ$$

$$P_{\text{source}} = -\frac{1}{2}(8)(\sqrt{5})\cos(0^\circ - (-26.6^\circ)) = -8W$$

$$P_{3\Omega} = \frac{1}{2}(\sqrt{5})^2(3) = 7.5W$$

$$P_{j2} = 0W$$

$$P_{1/2} = 0W$$

$$P_{1\Omega} = \frac{1}{2}(1)^2(1) = \frac{1}{2} = 0.5W$$