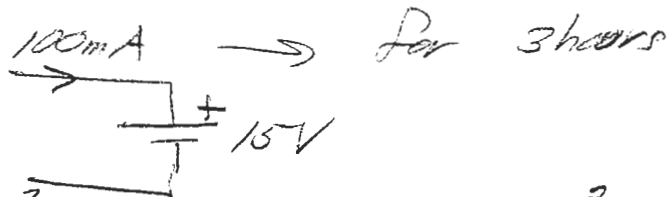


4.




$$W = \int_{t=0}^{3 \times 60^2} 0.1 \times 15 dt = 1.5 t \Big|_0^{3 \times 60^2} = 1.5 \times 3 \times 60^2 = 16.2 \times 10^3 \text{ Joules}$$

14.

$$2.86 \text{ Volts}$$

20.

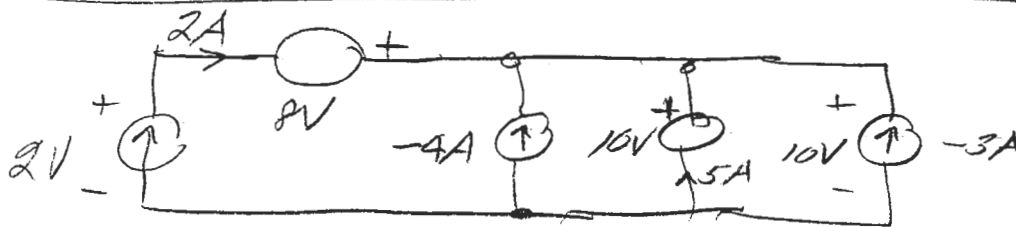

$$P_{2V} = -4W$$

$$P_{8V} = -16W$$

$$P_{4A} = -(-4)(10) = 40W \text{ absorbing}$$

$$P_{10V} = -50W$$

$$P_{3A} = -(-3)(10) = 30W \text{ absorbing}$$


$$\Sigma = 0!$$

2-28 $470\Omega \pm 5\%$ ($446.5 \rightarrow 493.5\Omega$)

for 2mA $P_{max} = (2 \times 10^{-3})^2 493.5 = 1.974 \times 10^{-3}$

resistor must be able to dissipate $\approx 2mW$

2-34

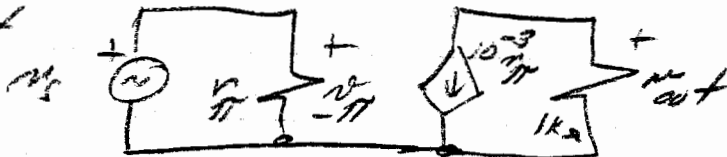


$N_1 = 0.01 \times 1000 = 10^{-3} A$

\therefore dependent current source $= 10^{-5} \text{ or } 10^3 A$

and $N_{out} = -10^3 \times 10^{-5} \text{ or } 10^3 A = -10^{-2} \text{ or } 10^3 A$

3-6

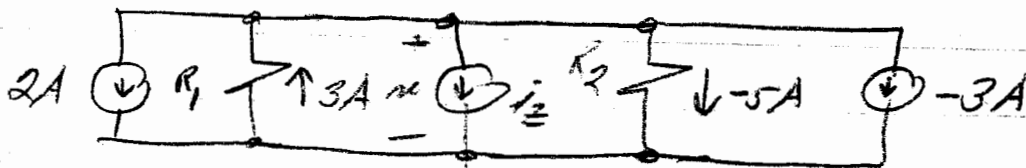


a) $\sum i's = 0$ $\therefore 2 - 3 + i_2 - 5 - 3 = 0$

$i_2 = 9A$

b) if $R_1 = 1\Omega$ then $v = -3R_1 = -3 \text{ Volts}$

so $-5R_2 = -3$ or $R_2 = \frac{3}{5} \Omega$

3-13

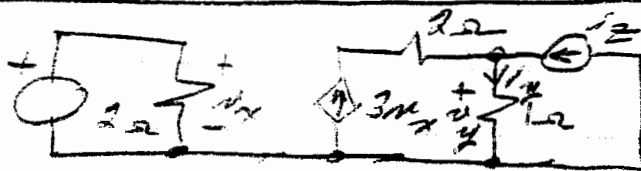



$N_x = 5 \text{ Volts}$


a) $i_2 = -3A$; $i_y = 3N_x + i_2 = 15 - 3 = 12A$ $\therefore \frac{N_x}{4} = 1 \times i_y = 12 \text{ Volts}$


b) $i_2 = 0.5A$, $N_y = -6V$, $N_x = ?$; $i_y = -6 = 3N_x + i_2 = 3N_x + \frac{1}{2}$

$N_x = \frac{-6 - \frac{1}{2}}{3} = -\frac{13}{6} = -2.167$

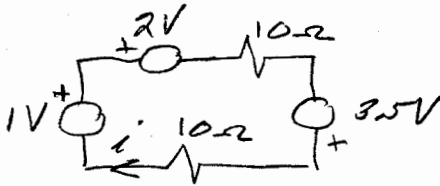3-16 a)  (KVL) $-1 + 2 + 10i - 3.5 + 10i = 0$
 $20i = 2.5$
 $i = 0.125 \text{ A}$

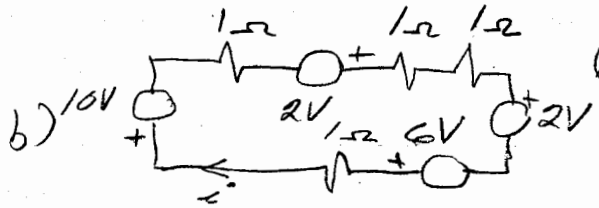b)  (KVL) $10 + 4i - 2 + 2 - 6 = 0$
 $i = -1$

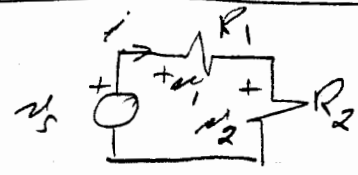3-18  $i = \frac{v_s}{R_1 + R_2} \therefore v_1 = iR_1 = v_s \frac{R_1}{R_1 + R_2}$
 and $v_2 = iR_2 = v_s \frac{R_2}{R_1 + R_2}$

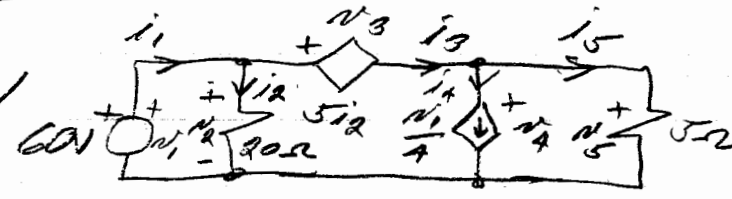3-21  $v_1 = 60 \text{ V} = v_2$
 $i_4 = \frac{60}{4} = 15$

a) $i_2 = \frac{60}{20} = 3 \text{ A}$ $\therefore v_3 = 5i_2 = 15 \text{ V}$

(KVL) $-60 + v_3 + v_4 = 0 \therefore v_4 = 60 - 15 = 45 \text{ V} = v_5$

$i_5 = \frac{v_4}{5} = 9 \text{ A}$

$i_3 = i_4 + i_5 = \frac{v_1}{4} + i_5 = 15 + 9 = 24 \text{ A}$

$i_1 = i_2 + i_3 = 3 + 24 = 27 \text{ A}$

b) $P_{60V} = -60i_1 = -60 \times 27 = -1620 \text{ W}$

$P_{30\Omega} = v_2 i_2 = 60 \times 3 = 180 \text{ W}$


$P_{5\Omega \text{ source}} = v_3 i_3 = 15 \times 24 = 360 \text{ W}$

$P_{\frac{4}{\Omega} \text{ source}} = v_4 i_4 = 45 \times 15 = 675 \text{ W}$

$P_{5\Omega} = v_5 i_5 = 45 \times 9 = 405 \text{ W}$

$\Sigma = 0 !$

3-48

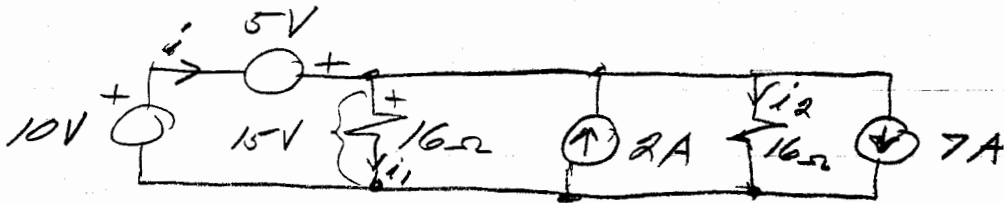

$$P_{16\Omega} = \frac{15^2}{16} = \frac{225}{16} \text{ W} \leftarrow \text{(Two of these)}$$

$$P_{2A} = -15 \times 2 = -30$$

$$P_{7A} = 15 \times 7 = 105$$


$$i = i_1 + i_2 + 7 - 2 = \frac{15}{8} + 5 = \frac{55}{8} \text{ A}$$

$$\therefore P_{10V} = -\frac{550}{8}$$

$$P_{5V} = -\frac{275}{8}$$

$$P_{\text{total}} = \frac{225 - 480 + 1680 - 1100 - 550 + 225}{16} = 0$$

3-43

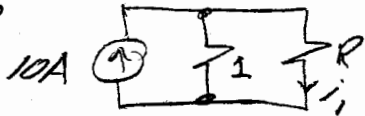


$$i_1 = 10 \frac{1}{1+R} = 5 \quad \therefore R = 1$$

28 AWG solid resistance = 0.5Ω ($65.3 \Omega / 1000'$)


$$\therefore \text{length} = \frac{0.5}{65.3} \times 10^3 \times \frac{1 \text{ mile}}{5280 \text{ ft}} = 1.45 \times 10^{-3} \text{ miles}$$

3-57

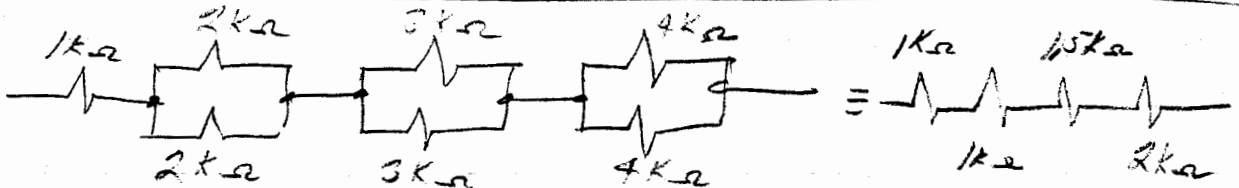

$$R_{eq} = 5.5 \text{ k}\Omega$$

3-65

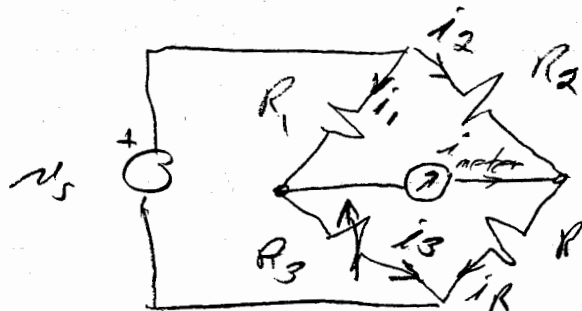


@ balance $i_{meter} = 0$

so $i_2 = i_R$ and $i_1 = i_3$

so $i_1 R_1 = i_2 R_2$ and $i_1 R_3 = i_2 R \Rightarrow \frac{R_1}{R_3} = \frac{R_2}{R}$

or $R = \frac{R_2 R_3}{R_1}$

3-77

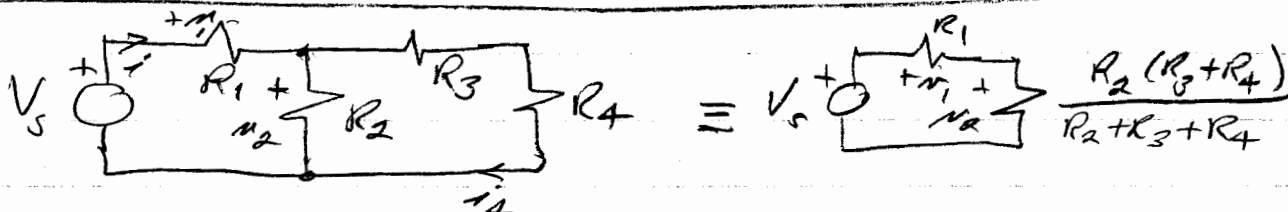


a) $v_2 = v_s \frac{\frac{R_2(R_3+R_4)}{R_2+R_3+R_4}}{R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4}} = v_s \frac{R_2(R_3+R_4)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$

b) $v_1 = v_s \frac{R_1}{R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4}} = v_s \frac{R_1(R_2+R_3+R_4)}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$

c) $i_4 = i \frac{R_2}{R_2+R_3+R_4} = \frac{v_s}{R_1 + \frac{R_2(R_3+R_4)}{R_2+R_3+R_4}} \cdot \frac{R_2}{R_2+R_3+R_4} = v_s \frac{R_2}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$

3-80

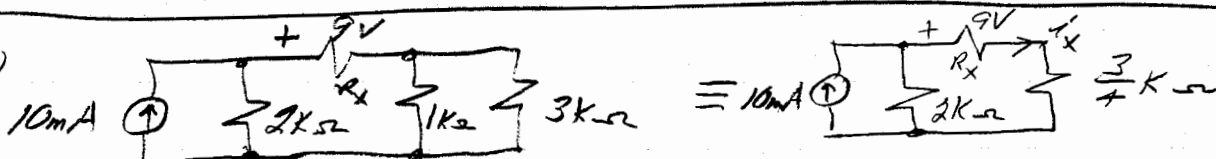


$i_x = \frac{2 \times 10^3}{2.75 \times 10^3 + R_x} \times 10 \text{mA}$ but $i_x R_x = 9 = \frac{20 R_x}{2.75 \times 10^3 + R_x}$

or $R_x = 2,250 \Omega$

$P_{R_x} = \frac{9^2}{R_x} = 0.036 = 36 \text{mW}$


4-9

4-4

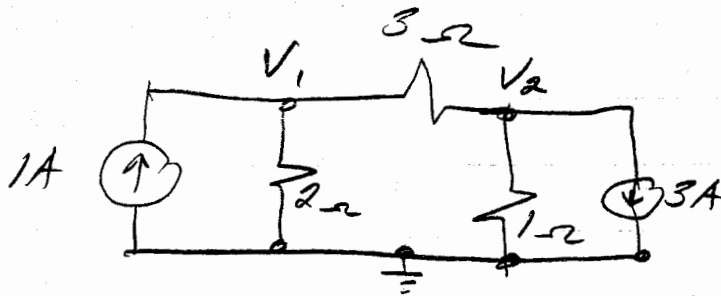

$$\left. \begin{aligned} \frac{V_1}{2} + \frac{V_1 - V_2}{3} &= 1 \\ \frac{V_2 - V_1}{3} + \frac{V_2}{1} &= -3 \end{aligned} \right\} \begin{aligned} V_1 \left(\frac{5}{6} \right) - \frac{V_2}{3} &= 1 \\ -V_1 \left(\frac{1}{3} \right) + V_2 \left(\frac{4}{3} \right) &= -3 \end{aligned} \Rightarrow \begin{bmatrix} 5 & -2 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -9 \end{bmatrix}$$
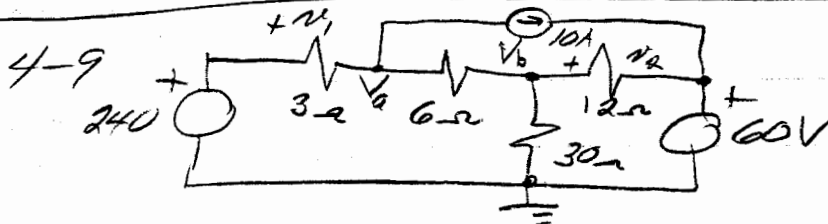
$$V_1 = \frac{\begin{vmatrix} 6 & -2 \\ -9 & 4 \end{vmatrix}}{\begin{vmatrix} 5 & -2 \\ -1 & 4 \end{vmatrix}} = \frac{24 - 18}{20 - 2} = \frac{6}{18} = \frac{1}{3} \text{ V}$$



$$\begin{aligned} \frac{V_a - 240}{3} + \frac{V_a - V_b}{6} &= -10 \\ \frac{V_b - V_a}{6} + \frac{V_b}{30} + \frac{V_b - 60}{12} &= 0 \end{aligned}$$

$$\text{or } \left. \begin{aligned} V_a \left(\frac{1}{3} \right) - V_b \left(\frac{1}{6} \right) &= 70 \\ -V_a \left(\frac{1}{6} \right) + V_b \left(\frac{1}{6} + \frac{1}{30} + \frac{1}{12} \right) &= 5 \end{aligned} \right\} \begin{aligned} 3V_a - V_b &= 420 \\ -10V_a + 17V_b &= 300 \end{aligned}$$


$$V_a = \frac{\begin{vmatrix} 420 & -1 \\ 300 & 17 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -10 & 17 \end{vmatrix}} = \frac{7440}{41} = 181.46 \text{ V}; \quad V_b = \frac{\begin{vmatrix} 3 & 420 \\ -10 & 300 \end{vmatrix}}{41} = \frac{5700}{41} = 139.02 \text{ V}$$

$$V_1 = 240 - V_a = 58.54 \text{ V}$$

$$V_2 = V_b - 60 = 79.02 \text{ V}$$

$$P_{6\Omega} = \frac{(V_a - V_b)^2}{6} = 542.89 \text{ Watts}$$

4-13

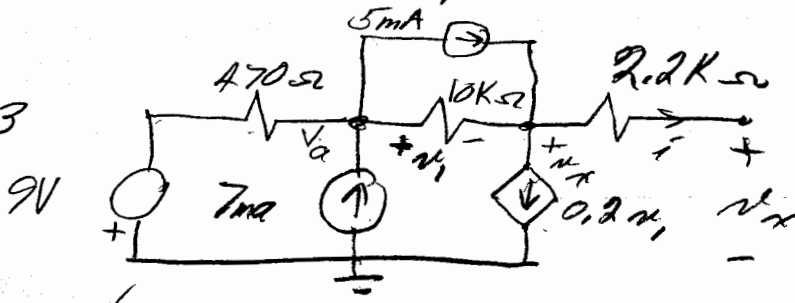

$i = 0$
 ∞ $v_x =$ voltage across the dependent source

@ V_a

$$\frac{V_a + 9}{470} + \frac{V_a - v_x}{10,000} = 2 \times 10^{-3}$$

@ v_x

$$\frac{v_x - V_a}{10,000} + 0.2(V_a - v_x) = 5 \times 10^{-3}$$

$$V_a \cdot 10,470 - 470v_x = -9 \times 10^4 + 20 \times 470$$


$$V_a(2 \times 10^3 - 1) + v_x(1 - 2 \times 10^3) = 50$$

$$10,470V_a - 470v_x = -80,600$$

or $1.999 \times 10^3 V_a - 1.999 \times 10^3 v_x = 50$


$$v_x = \frac{\begin{vmatrix} 10.470 \times 10^3 & -80.6 \times 10^3 \\ 1.999 \times 10^3 & 50 \end{vmatrix}}{\begin{vmatrix} 10.470 \times 10^3 & -470 \\ 1.999 \times 10^3 & -1.999 \times 10^3 \end{vmatrix}} = \frac{161.64 \times 10^6}{-20.93 \times 10^6 + 9395 \times 10^3 - 19.99 \times 10^6} = -8.086V$$

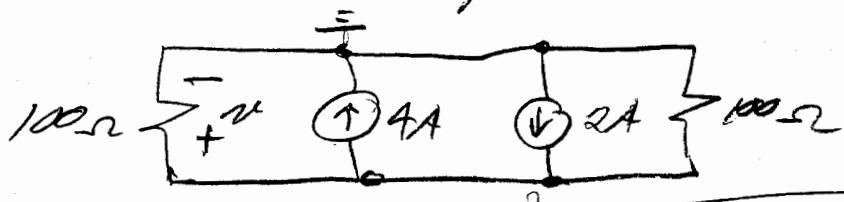4-14 no current flows from top to bottom part of circuit ∞ problem reduces to



$$\frac{v}{100} + \frac{v}{100} = 2 - 4$$
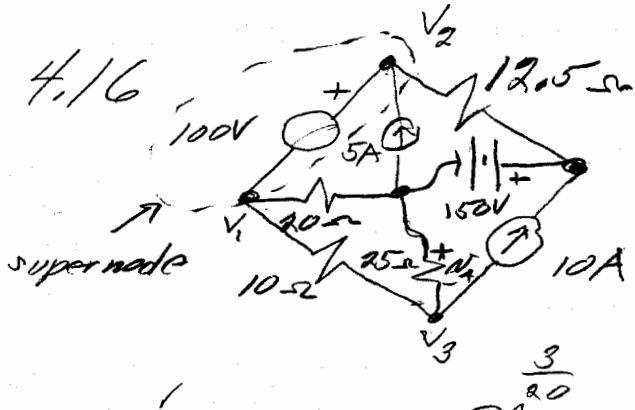
$$50v = \frac{-2 \times 100}{2} = -100V$$



Use center as reference

$$V_1 - V_2 = -100 \Rightarrow V_1 = V_2 - 100$$


$$\frac{V_2 - 150}{12.5} + \frac{V_1}{20} + \frac{V_1 - V_3}{10} = 5$$

$$\frac{V_2 - V_1}{10} + \frac{V_3}{25} = -10$$

$$\text{or } \frac{V_2}{12.5} + (V_2 - 100) \left(\frac{1}{20} + \frac{1}{10} \right) - \frac{V_3}{10} = 5 + 12 \quad \left. \begin{array}{l} V_2^{0.23} - V_3^{0.1} = 32 \\ -V_2^{0.1} + V_3^{0.14} = -20 \end{array} \right\}$$

$$-(V_2 - 100) \frac{1}{10} + \frac{V_3}{25} \left(\frac{1}{10} + \frac{1}{25} \right) = -10$$
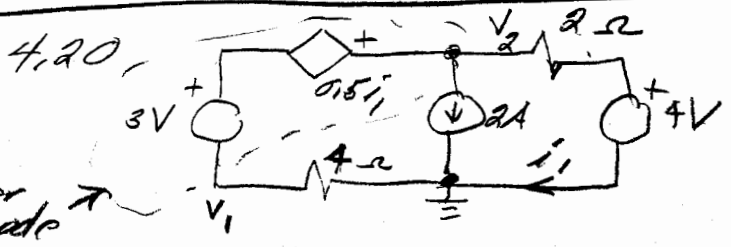
$$V_3 = -N_A = \frac{\begin{vmatrix} 0.23 & 32 \\ -0.1 & -20 \end{vmatrix}}{\begin{vmatrix} 0.23 & -0.1 \\ -0.1 & 0.14 \end{vmatrix}} = \frac{-14}{0.0322} = -63.06V \quad \text{or } N_A = 63.06V$$



$$V_2 - V_1 = 0.5i_1 + 3 = 0.5 \left(\frac{V_2 - 4}{2} \right) + 3$$

@ supernode

$$\frac{V_1}{4} + \frac{V_2 - 4}{2} = -2$$

$$\left. \begin{array}{l} V_2 \left(1 - \frac{1}{4} \right) - V_1 = 2 \\ \frac{V_1}{4} + \frac{V_2}{2} = 0 \end{array} \right\} \begin{array}{l} -V_1 + \frac{3}{4}V_2 = 2 \\ V_1 + 2V_2 = 0 \end{array} \quad \left. \begin{array}{l} -4V_1 + 3V_2 = 8 \\ V_1 + 2V_2 = 0 \end{array} \right\}$$


$$V_2 = \frac{\begin{vmatrix} -4 & 8 \\ 1 & 0 \end{vmatrix}}{\begin{vmatrix} -4 & 3 \\ 1 & 2 \end{vmatrix}} = \frac{-8}{-8-3} = \frac{8}{11}$$

$$i_1 = \frac{V_2 - 4}{2} = \frac{\frac{8}{11} - \frac{44}{11}}{2} = -\frac{36}{22} = -1.636A$$

EE 211

Assignment 9

4.26, 4.29

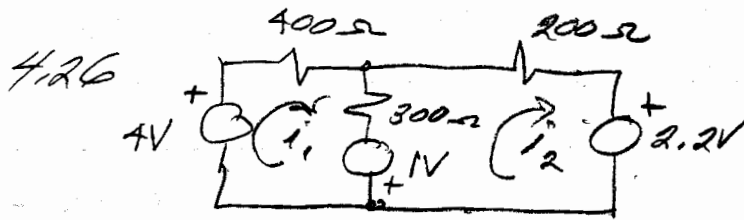

$$400i_1 + 300(i_1 - i_2) = 5$$

$$300(i_2 - i_1) + 200i_2 = -3.2$$


$$700i_1 - 300i_2 = 5$$

$$\text{OR } -300i_1 + 500i_2 = -3.2$$

$$i_1 = \frac{\begin{vmatrix} 5 & -300 \\ -3.2 & 500 \end{vmatrix}}{\begin{vmatrix} 700 & -300 \\ -300 & 500 \end{vmatrix}} = \frac{2500 - 960}{350,000 - 90,000} = \frac{1540}{260,000} = 5.92 \times 10^{-3} \text{ A}$$

$$i_2 = \frac{\begin{vmatrix} 700 & 5 \\ -300 & -3.2 \end{vmatrix}}{260,000} = \frac{-2240 + 1500}{260,000} = -\frac{740}{260,000} = -2.85 \times 10^{-3} \text{ A}$$

4.29

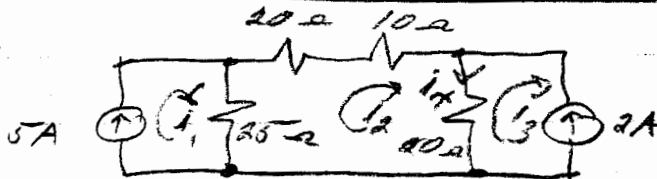

$$i_1 = 5$$


$$i_3 = -2$$

$$25(i_2 - i_1) + 30i_2 + 20(i_2 - i_3) = 0 \Rightarrow 75i_2 = 125 - 40$$

$$i_2 = 1.133 \text{ A}$$

$$\text{So } i_x = i_2 - i_3 = 3.133 \text{ A}$$
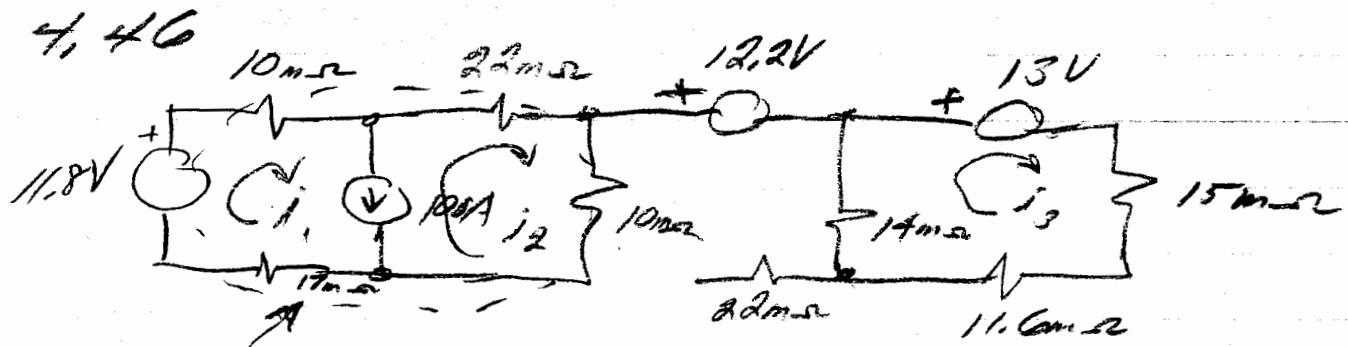
$$P_{25\Omega} = (i_1 - i_2)^2 \cdot 25 = (5 - 1.133)^2 \cdot 25 = 373.77 \text{ Watts}$$



supermesh

$$i_1 \cdot 10 \times 10^{-3} + i_2 \cdot 32 \times 10^{-3} + 17 \times 10^{-3} i_1 = 11.8; \quad i_1 - i_2 = 100$$

$$i_3 (14 + 15 + 11.6) \times 10^{-3} = -13 \Rightarrow i_3 = -\frac{13}{40.6 \times 10^{-3}} = -0.32 \times 10^3$$


$$i_3 = -320 \text{ A} \leftarrow$$

$$\rightarrow 27 \times 10^{-3} i_1 + 32 \times 10^{-3} i_2 = 11.8$$

$$i_1 - i_2 = 100 \Rightarrow i_1 = i_2 + 100$$

$$\text{so } (27 \times 10^{-3} + 32 \times 10^{-3}) i_2 = 11.8 - 2.7$$
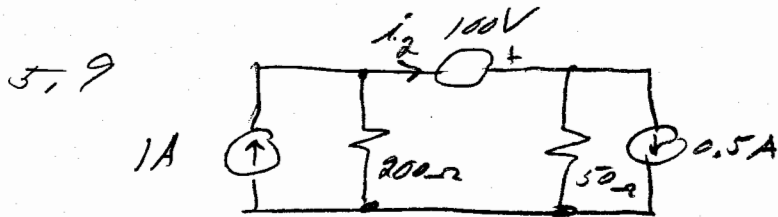
$$\left. \begin{aligned} i_2 &= \frac{9.1}{59 \times 10^{-3}} = 154.2 \text{ A} \\ i_1 &= 254.2 \text{ A} \end{aligned} \right\}$$



Voltage source only

$$i_{2V} = \frac{100}{250} = \frac{2}{5} A$$

left current source



$$i_{2A_1} = 1 \times \frac{200}{250} = \frac{4}{5} A$$

right current source

$$i_{2A_2} = \frac{1}{2} \times \frac{50}{250} = \frac{25}{250} = \frac{1}{10} A$$

$$\therefore i_2 = i_{2V} + i_{2A_1} + i_{2A_2} = \frac{13}{10} A = 1.3A \quad \leftarrow$$


5.21

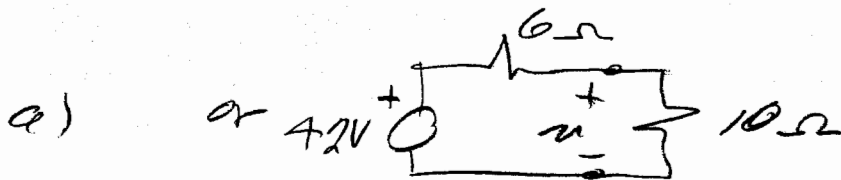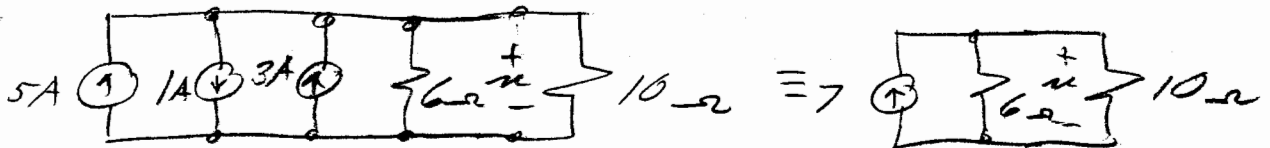




b)

$$n = 42 \frac{10}{16} = \frac{420}{16} = 26.25 V$$


c) If we include 10Ω resistor we lose n!

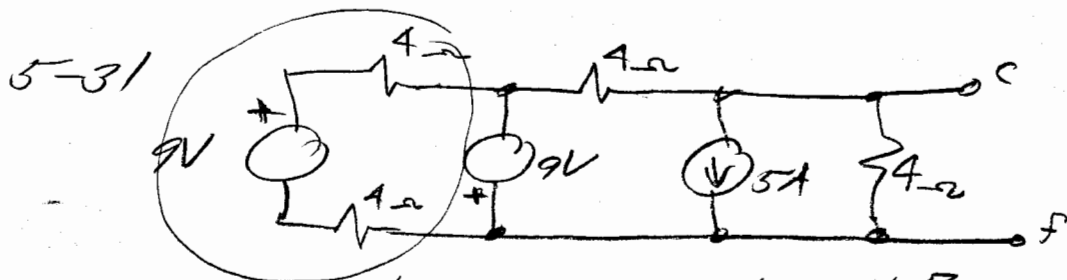

no effect on circuit to the right!

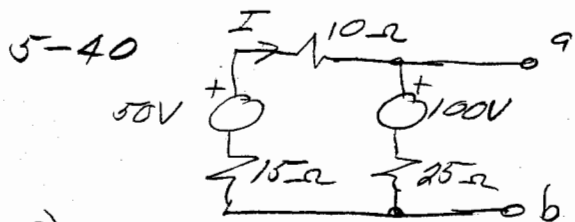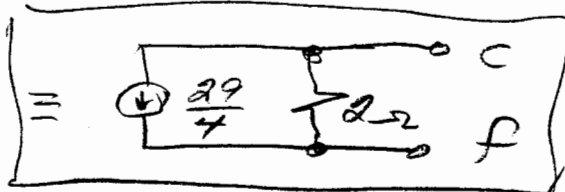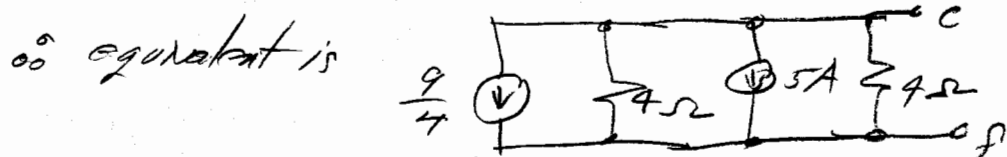


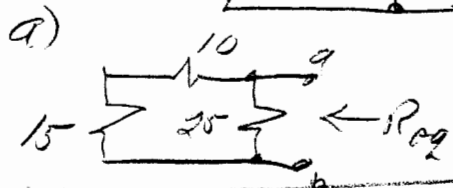KVL $15I - 50 + 10I + 100 + 25I = 0$
 $50I = -50$
 $I = -1A$




∞ $V_{oc} = V_{Th} = 100 - 25 = 75V$

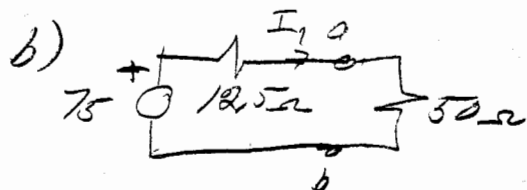$R_{Th} = R_{eq} = \frac{25(15)}{50} = 7.5\Omega$




$I_1 = \frac{75}{62.5}$

$P_{50\Omega} = I_1^2 50 = 72W$

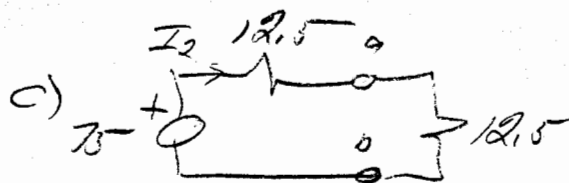


$I_2 = \frac{75}{25} = 3$

$P_{12.5} = 9 \times 12.5 = 112.5$

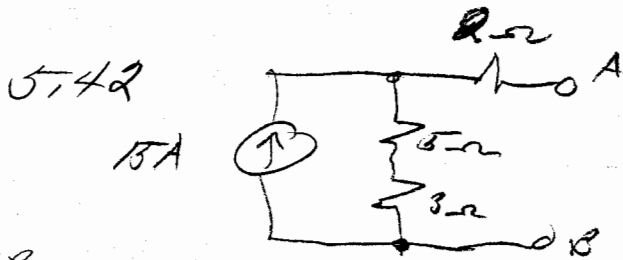


a)
$$\left\{ \begin{aligned} V_{Th} &= V_{oc} = 15 \times 8 = 120V \\ R_{Th} &= R_{eq} = 10\Omega \end{aligned} \right\}$$

$V=IR$

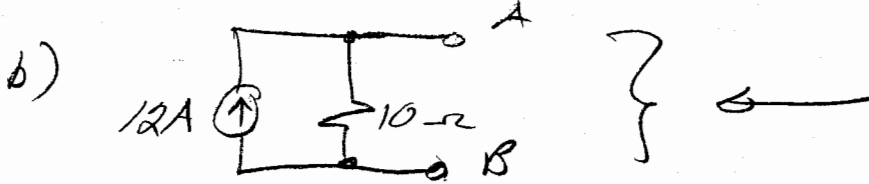

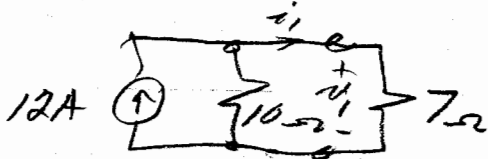
$$V_1 = \frac{7}{17} \times 120 = 49.41V$$




$$i_1 = \frac{10}{17} \times 12$$
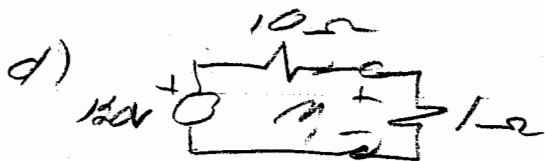
$$V_1 = \frac{10}{17} \times 12 \times 7 = \frac{7}{17} \times 120 = 49.41V$$


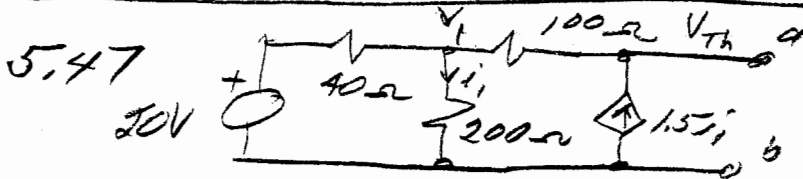
$$V_1 = \frac{1}{11} \times 120 = 10.9V$$



$$\frac{V_1 - 20}{40} + \frac{V_1}{200} + \frac{V_1 - V_{Th}}{100} = 0 \quad \frac{3}{2} \times \frac{1}{200} = \frac{3}{400}$$

$$\frac{V_{Th} - V_1}{100} - 1.5i_1 = 0 \quad \text{but } i_1 = \frac{V_1}{200}$$

$$\left\{ \begin{aligned} V_1 \left(\frac{1}{40} + \frac{1}{200} + \frac{1}{100} \right) - \frac{1}{100} V_{Th} &= \frac{1}{2} \\ V_1 \left(-\frac{1}{100} - \frac{3}{400} \right) + \frac{1}{100} V_{Th} &= 0 \end{aligned} \right.$$

$$8V_1 - 2V_{Th} = 100$$

$$-7V_1 + 4V_{Th} = 0$$

$$V_{Th} = \frac{\begin{vmatrix} 8 & 100 \\ -7 & 0 \end{vmatrix}}{\begin{vmatrix} 8 & -2 \\ -7 & 4 \end{vmatrix}} = \frac{700}{32-14} = \frac{700}{18} = 38.89V$$

$$\overset{I_{sc}}{=} \frac{V_1 - 20}{40} + \frac{V_1}{200} + \frac{V_1}{100} = 0$$

$$V_1 \left(\frac{8}{200} \right) = \frac{1}{2}; V_1 = \frac{100}{8} = \frac{25}{2}$$


$$-\frac{V_1}{100} - \frac{3}{2} \left(\frac{V_1}{200} \right) + I_{sc} = 0$$

$$I_{sc} = V_1 \left(\frac{1}{400} + \frac{3}{400} \right) = \frac{25}{2} \cdot \frac{7}{400} = \frac{7}{32}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{700}{18} \cdot \frac{32}{7} = \frac{1600}{9} = 177.8\Omega$$

$$P_{100\Omega @ ab} = V^2/R = \left[38.89 \frac{100}{177.8} \right]^2 \times \frac{1}{100} = 1.96W$$

5.57

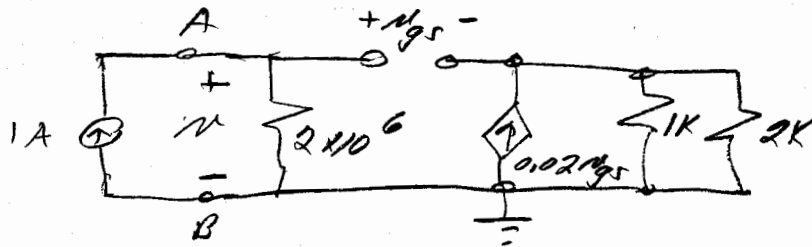


$$R_{Th} = \frac{2K}{1}$$

$$M = 2 \times 10^6$$

$$\therefore R_{Th} = 2 \times 10^6 \Omega$$


5.63

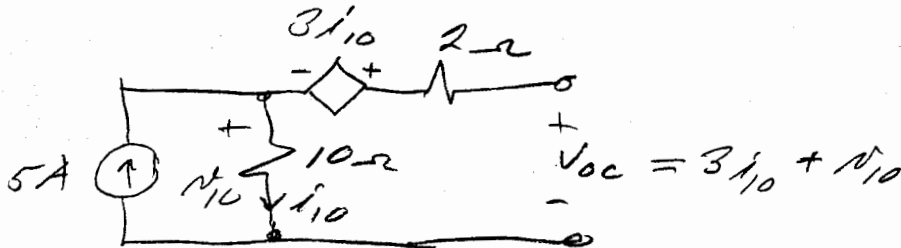

$$\text{but } i_{10} = 5$$

$$i_{10} = 5$$
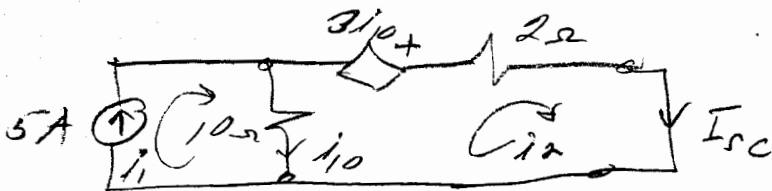
$$\therefore V_{oc} = V_{Th} = 15 + 50 = 65V$$



$$i_2 = I_{sc}$$


$$i_1 = 5$$

$$10(i_2 - i_1) - 3i_{10} + 2i_2 = 0$$

$$\text{but } i_{10} = i_1 - i_2$$

$$\therefore 15i_2 - 13i_1 = 0 \text{ giving } i_2 = \frac{13 \times 5}{15} = \frac{13}{3} = I_{sc}$$
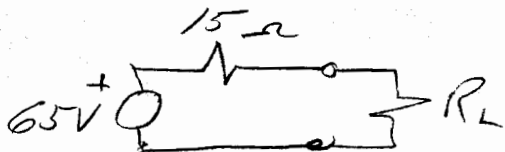
$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{65 \times 3}{13} = 15 \Omega$$



b) maximum power to R_L for $R_L = 15 \Omega$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{65^2}{60} = 70.42 \text{ Watts}$$

7.1 $10 \mu F$

a) $v = 5V$ $\therefore i = C \frac{dv}{dt} = 0$

b) $v = 115\sqrt{2} \cos 120\pi t$ $i = 115\sqrt{2} \times 10^{-5} \times (-120\pi \sin 120\pi t)$
or $i = -0.613 \sin 120\pi t$

c) $v = 4e^{-t} \times 10^{-3}$; $i = 4 \times 10^{-8} e^{-t}$

7.13



For $t > 0$ $w_c = \frac{1}{2} C v^2 = 20 e^{-10^3 t} \times 10^{-3}$

$\therefore w = \frac{40}{10^6} e^{-10^3 t} = 4 \times 10^{-8} e^{-10^3 t}$


$w = \pm 200 e^{-500t}$

$i = C \frac{dv}{dt} = \pm 10^{-6} \times (200) \times (-500) e^{-500t} = \mp 0.1 e^{-500t}$

$R = -\frac{v}{i} = + \frac{200}{0.1} = 2 \times 10^3 \Omega$

$w_R = \int_0^{\infty} i v dt = \int_0^{\infty} 20 e^{-10^3 t} dt = \frac{20}{-10^3} e^{-10^3 t} \Big|_0^{\infty} = 0.02 J$

7.15

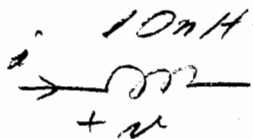


a) $i = 5mA$; $v = L \frac{di}{dt} = 0$

b) $i = 115\sqrt{2} \cos 120\pi t$; $v = 10^{-2} \times 115\sqrt{2} (-1) 120\pi \sin 120\pi t$



$i = 6.13 \times 10^{-4} \sin 120\pi t$

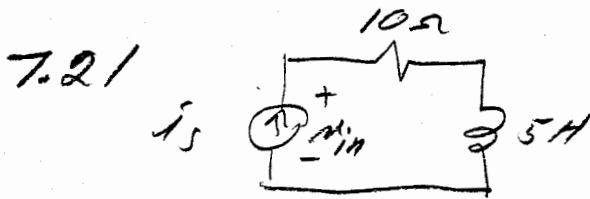c) $i = 4e^{-6t}$; $v = 10^{-2} \times 4(-6) e^{-6t} = -24 \times 10^{-2} e^{-6t}$



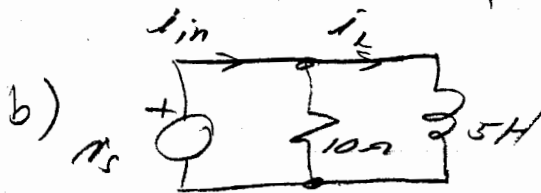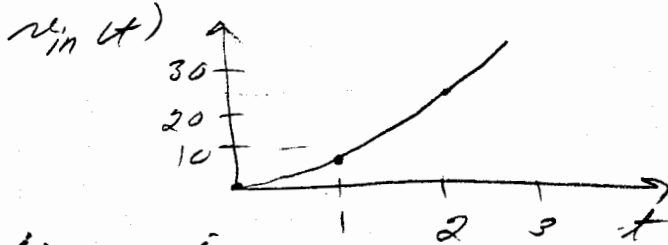a) $i_s = 0.4t^2$

$$v_{in} = 10i_s + 5 \frac{di_s}{dt} = 4t^2 + 4t$$





$v_L = 40t$; $i_L(0) = 5$

$$i_{in} = \frac{v_L}{10} + \frac{1}{5} \int_0^t v_L dt + 5$$


or $i_{in} = 4t + 4t^2 + 5$

[Sketch same as above shifted up by 5]

7.33

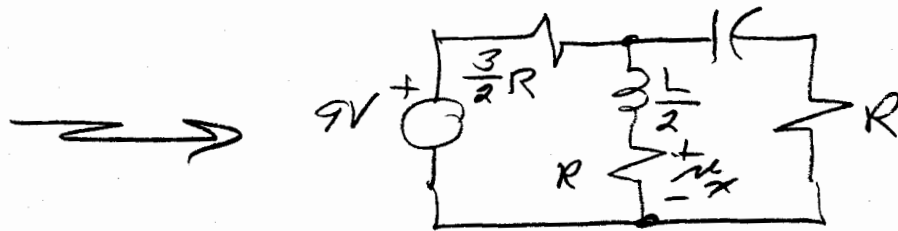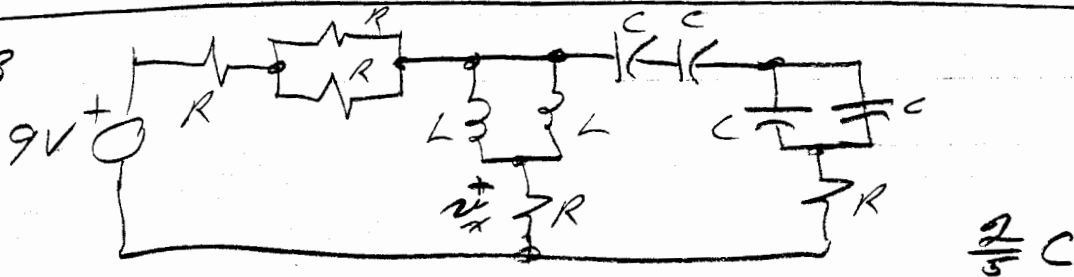


@ dc reduces to:

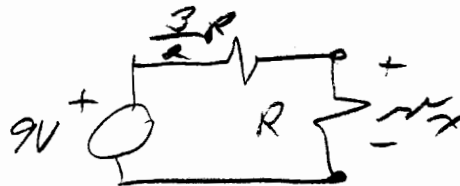

so $v_x = 9 \frac{R}{\frac{3}{2}R + R} = \frac{18}{5} V$


8.6

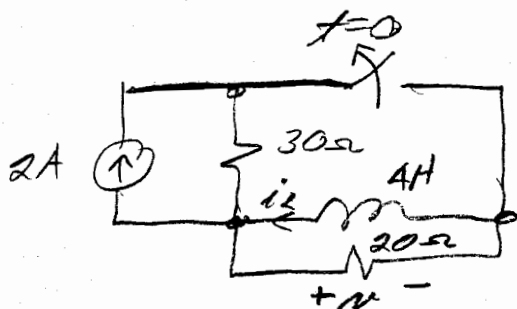

$$a) i_L(0^-) = i_L(0^+) = 2A \leftarrow$$

$$b) v(0^+) = 2 \times 20 = 40V \leftarrow$$

8.8

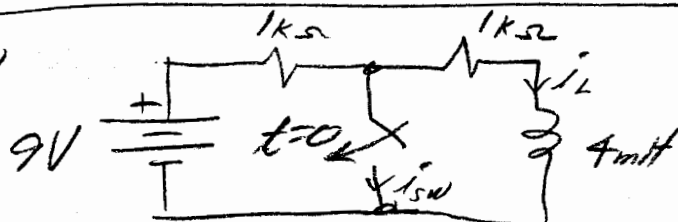

$$i_L(0^-) = i_L(0^+) = \frac{9}{2 \times 10^3}$$

$$\text{for } t > 0 \quad i_L \times 10^3 + 4 \times 10^{-3} \frac{di_L}{dt} = 0$$

$$i_L = A e^{s_1 t} \Rightarrow 10^3 + 4 \times 10^{-3} s_1 = 0$$

$$s_1 = - \frac{10^3}{4 \times 10^{-3}} = - \frac{1}{4} \times 10^6$$

$$\therefore i_L = \frac{9}{2} \times 10^{-3} e^{-\frac{t \times 10^6}{4}}$$


$$a) t = 5 \mu s \quad i_L = \frac{9}{2} \times 10^{-3} e^{-\frac{5}{4}} = 1.289 \times 10^{-3} \leftarrow$$

$$b) i_{sw}(t = 5 \times 10^{-6}) = -i_L + \frac{9}{10^3} = 7.71 \times 10^{-3} \leftarrow$$


EE 211

Assignment 18

8.22

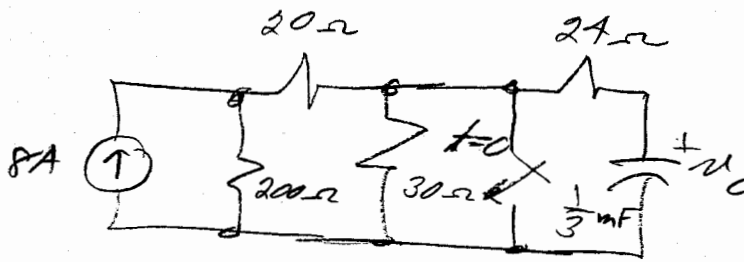

a) before $t=0$

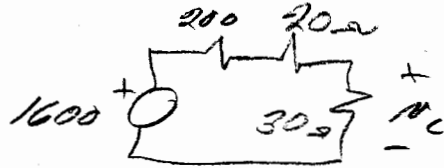

$$v_C(t) = 1600 \frac{30}{250} = 192V$$


for $t > 0$

$$v_C(t) = 192e^{-\frac{t}{\tau}} = 192e^{-\frac{t}{8 \times 10^{-3}}} = 192e^{-125t}$$

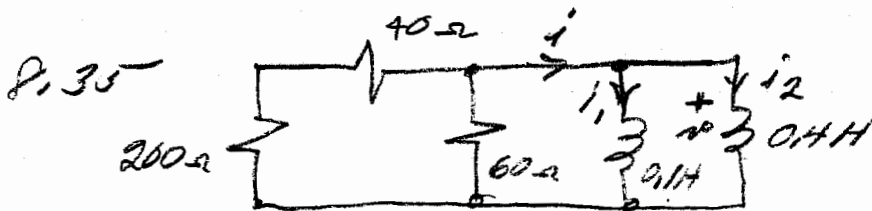b) $0.1 = e^{-125t}$

$\ln 0.1 = -125t$

$$t = -\frac{1}{125} \ln 0.1 = 0.0184 \text{ sec} = 18.4 \text{ msec} \leftarrow$$



$$i_1(0^-) = 10 \text{ A}$$

$$i_2(0^-) = 20 \text{ A}$$

a) $i_1(0^+) = 10 \text{ A}$; $i_2(0^+) = 20 \text{ A}$; $i(0^+) = 30 \text{ A}$ ←

b) $T = \frac{L_{eq}}{R_{eq}} = \frac{\frac{0.04}{0.5}}{\frac{2+10(60)}{300}} = \frac{0.04 \times 300}{0.5 \times 240 \times 60} = \frac{0.4}{240} = \frac{5}{3} \times 10^{-3}$ ←

c) $i(t) = 30 e^{-\frac{3 \times 10^3}{5} t} = 30 e^{-600t}$ ← for $t > 0$

d) $v(t) = -R_{eq} i(t) = -1440 e^{-600t}$ ←

e) $i_1(t) = 10 \int_0^t (-1440) e^{-600t} dt + 10 = \frac{+14 \times 1440}{+600} e^{-600t} + 10$

$i_1(t) = 24 e^{-600t} + 14$ ←

$i_2(t) = 20 \int_0^t (-1440) e^{-600t} dt + 20 = 6 e^{-600t} + 14$ ←

f) Energy delivered to resistor = $\int_0^{\infty} i^2 R_{eq} dt = \int_0^{\infty} 900 e^{-1200t} 48 dt$


$$W_R = \frac{48 \times 900}{-1200} e^{-1200t} \Big|_0^{\infty} = 36 \text{ Joules}$$

$$W_L(t=\infty) = \left[\frac{1}{2} (0.1) + \frac{1}{2} (0.4) \right] 14^2 = 49 \text{ Joules}$$

$$W_L(t=0) = \frac{1}{2} (0.1) 10^2 + \frac{1}{2} (0.4) 20^2 = 5 + 80 = 85 \text{ Joules}$$

$W_L(t=0) - W_L(t=\infty) = 85 - 49 = 36 \text{ Joules} = W_R$ ✓

P.62

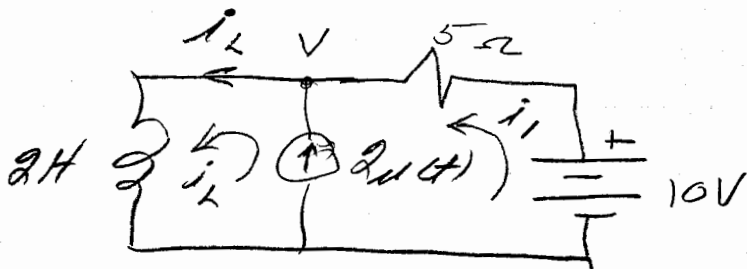

a) $t = -0.5 \text{ sec}$ for $t < 0$ $i_L = \frac{10}{5} = 2 \text{ A}$

b) + c) for $t > 0$ super mesh eq. is:

$$-10 + 5i_1 + 2 \frac{di_L}{dt} = 0 \quad ; \quad i_L - i_1 = 2 \quad \text{or} \quad i_1 = i_L - 2$$

$$\therefore \quad \boxed{5i_L + 2 \frac{di_L}{dt} = 20}$$

$$i_L = A e^{st} \quad ; \quad s = -\frac{5}{2} \quad (\tau = \frac{2}{5} = 0.4 \text{ sec})$$


$$i_{Lp} = K = 4$$

so $i_L = A e^{-\frac{5}{2}t} + 4$ but $i_L(0) = 2$


$$\therefore \quad \boxed{i_L = 4 - 2e^{-\frac{5}{2}t}}$$

$$i_L(t=0.5) = 4 - 2e^{-\frac{5}{4}} = 3.427 \text{ A}$$
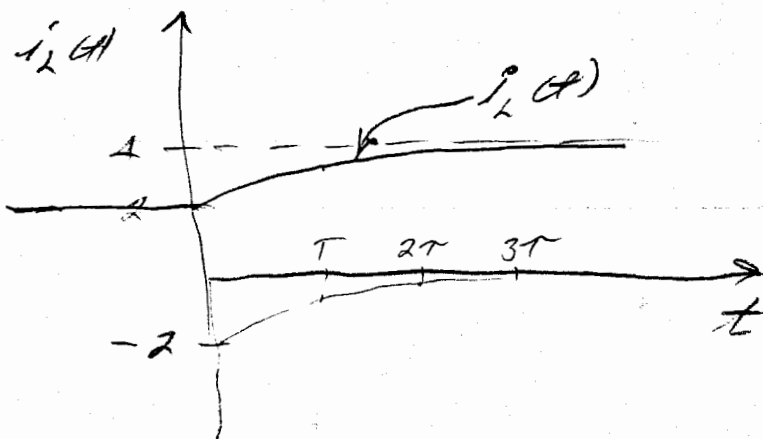
$$i_L(t=1.5) = 4 - 2e^{-\frac{15}{4}} = 3.95 \text{ A}$$



8.76

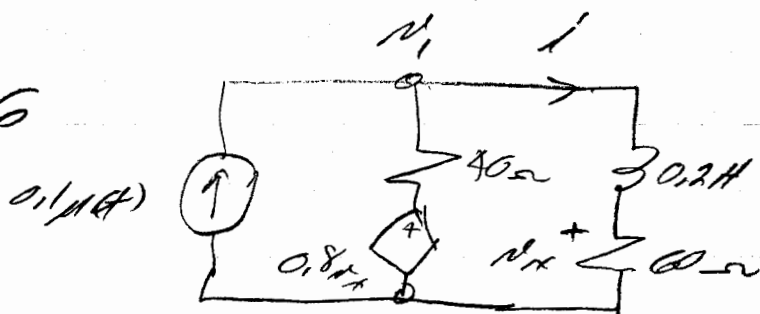

For $t < 0$
 current source = ϕ
 $\therefore v_x = 0 ; i = 0$

For $t > 0$

$$\text{Node } \left\{ \begin{array}{l} \frac{v_1 - 0.8v_x}{40} + 5 \int_0^t (v_1 - v_x) dt = \frac{1}{10} \\ 5 \int_0^t (v_x - v_1) dt + \frac{v_x}{60} = 0 \end{array} \right. \left. \begin{array}{l} \text{could solve} \\ \text{but not} \\ \text{straight forward} \end{array} \right.$$

$$\text{Mesh } \left\{ \begin{array}{l} 40(i - \frac{1}{10}) + \frac{1}{5} \frac{di}{dt} + 60i = \frac{4}{5} v_x \\ v_x = 60i \end{array} \right.$$

$$\therefore \frac{1}{5} \frac{di}{dt} + 52i = 4$$

$$i_h = A e^{st} ; s = -52 \times 5 = -260$$

$$\therefore \boxed{i_h = A e^{-260t}}$$


$$i_p = K = \frac{4}{52}$$

$$\text{so } i = i_h + i_p = \frac{4}{52} + A e^{-260t}$$

$$\text{but } i(0) = 0 \quad \therefore A = -\frac{4}{52}$$

$$\text{so } i = \frac{4}{52} (1 - e^{-260t}) \mu\text{A}$$
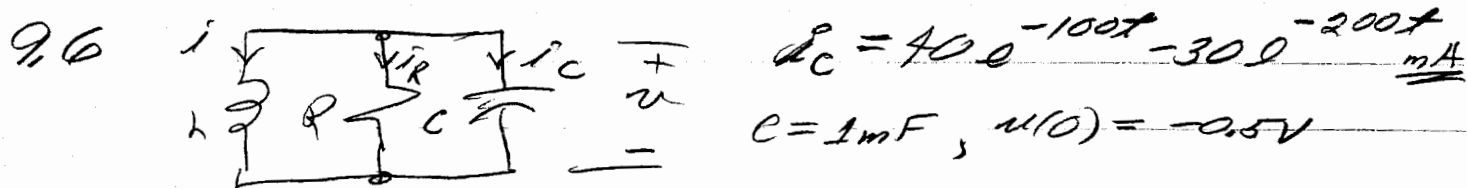
$$\text{and } v_x(t) = 60i = 4.615 (1 - e^{-260t}) \mu\text{V}$$



$$a) v = \frac{1}{C} \int_0^t i dt + v(0) = \left[-\frac{2}{5}e^{-100t} + \frac{3}{20}e^{-200t} \right]_0^t - 0.5$$

$$v(t) = -\frac{2}{5}e^{-100t} + \frac{3}{20}e^{-200t} + \frac{2}{5} - \frac{3}{20} - \frac{1}{2} \leftarrow$$

$$b) i_R(t) = \frac{v}{R} \quad \text{need } R$$

$$s_{1,2} = -100, -200$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -100$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -200$$

$$\left[s_1 + s_2 = -2\alpha = -300 \quad \text{or} \quad \frac{2}{RC} = 300 \right]$$

$$R = \frac{1}{300 \times 10^{-3}} = 3.33 \Omega \leftarrow$$

$$\therefore i_R(t) = \frac{v(t)}{3.33} \leftarrow$$


$$c) i(t) = -i_R(t) - i_C(t) \leftarrow$$

[Extra credit if they realize $v(0)$ must equal $-\frac{1}{4}$]

could find L $s_1 - s_2 = 2\sqrt{\alpha^2 - \omega_0^2} = 100$

$$\alpha^2 - \omega_0^2 = 50^2 \Rightarrow \omega_0^2 = \frac{1}{LC} = \alpha^2 - 50^2$$
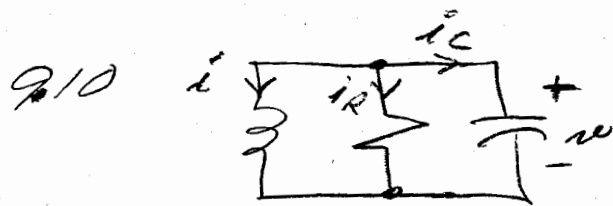
$$L = \frac{1}{C(\alpha^2 - 50^2)} = \frac{1}{10^{-3}(150^2 - 50^2)} = \frac{10^3}{20 \times 10^3} = 0.05 \text{ H}$$



$$L=5\text{H}, R=8\Omega, C=12.5\text{mF}$$

$$v(10^+) = 40\text{V}$$

a) $i(0^+) = 8\text{A}$ find $v(t)$

$$\frac{v}{R} + C \frac{dv}{dt} + \frac{1}{L} \int_0^t v dt + i(0) = 0 \Rightarrow \frac{dv}{dt} + \frac{1}{RC} v + \frac{1}{LC} \int v dt = 0$$

$$v = Ae^{st} \quad \text{so} \quad s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \quad \text{or} \quad s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\frac{1}{2RC} = \frac{1}{16 \times 12.5 \times 10^{-3}} = 5, \quad \frac{1}{LC} = \frac{1}{5 \times 12.5 \times 10^{-3}} = 16$$

$$\therefore s_{1,2} = -5 \pm \sqrt{25 - 16} = -5 \pm 3 = -2, -8$$

$$v = A_1 e^{-2t} + A_2 e^{-8t}; \quad v(0) = 40 = A_1 + A_2$$

$$i(t) = -i_R - i_C = -\frac{A_1 e^{-2t}}{8} - \frac{A_2 e^{-8t}}{8} - 12.5 \times 10^{-3} (-2A_1 e^{-2t} - 8A_2 e^{-8t})$$

$$i(0) = 8 = \frac{1}{25} \times 10^{-3} A_1 - 0.125 A_1 + 0.1 A_2 - 0.125 A_2 = -0.1 A_1 - 0.025 A_2$$

$$\therefore 8 = -\frac{1}{10} (40 - A_2) - \frac{1}{40} A_2 = -4 + A_2 \left(\frac{1}{10} - \frac{1}{40} \right); \quad A_2 = \frac{4 \times 12 \times 40}{3} = 160$$

$$v(t) = -120 e^{-2t} + 160 e^{-8t}$$

b) $i_C(10) = 8\text{A}$; find $i(t)$; $v(10) = 40 \therefore i_R(10) = 5$

$$i(t) = A_3 e^{-2t} + A_4 e^{-8t} \quad \text{but} \quad i(0) = -i_C(0) - i_R(0) = -13$$

$$\text{so} \quad -13 = A_3 + A_4$$

$$\text{but} \quad v(10) = L \left. \frac{di}{dt} \right|_{t=0} = 0 \quad \text{so} \quad \left. \frac{di}{dt} \right|_{t=0} = \frac{+0}{5} = 8 = -2A_3 - 8A_4$$

$$\therefore 8 = -2(-13 - A_4) - 8A_4 \quad \text{or} \quad 8 = 26 - 6A_4 \Rightarrow A_4 = 3$$

$$A_3 = -13 - 3 = -16$$

$$\text{so} \quad i(t) = -16 e^{-2t} + 3 e^{-8t}$$


EE 211

Assignment 24

$$v_c(0) = 100$$

$$i_L(0) = \frac{100}{R}$$

for $t > 0$ we have
all RLC circuit

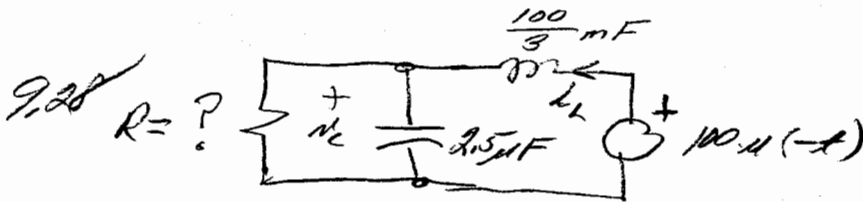

$$a) \alpha = \omega_0 \quad \text{if} \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} \quad \text{or} \quad \frac{1}{4R^2C^2} = \frac{1}{LC} ; R^2 = \frac{L}{4C}$$

$$\therefore R = \sqrt{\frac{0.1 \times 10^{-6}}{3 \times 4 \times 2.5}} = 75.59 \Omega$$

$$\omega_0 = \alpha = \sqrt{\frac{1}{LC}} = \sqrt{\frac{3 \times 10^6}{0.1 \times 2.5}} = 3464$$


$$\text{so } v_c(t) = A_1 e^{-3464t} + A_2 t e^{-3464t}$$

$$\therefore 100 = A_1$$

$$\frac{v_c}{R} + C \frac{dv_c}{dt} + \frac{1}{L} \int_0^t v_c dt - i_L(0) = 0 \quad \therefore \left. \frac{dv_c}{dt} \right|_{t=0} = -\frac{100}{RC} + \frac{100}{RC} = 0!$$

$$\text{giving } -100 \times 3464 + A_2 = 0 ; \text{ or } A_2 = 3.464 \times 10^5$$
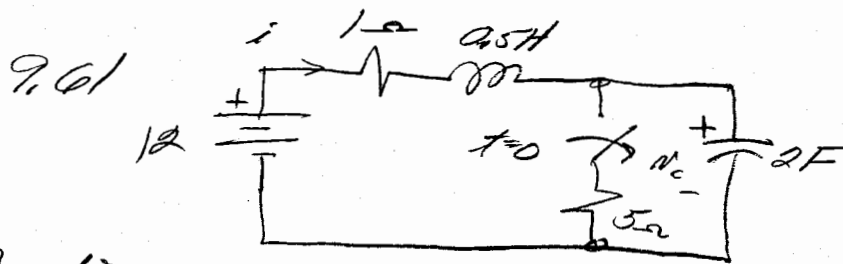
$$v_c(t) = 100 e^{-3464t} + 3.464 \times 10^5 t e^{-3464t}$$



$$i(0) = \frac{12}{6} = 2A$$

$$v_C(0) = 12 \frac{5}{6} = 10V$$

for $t > 0$

$$12 = i + \frac{1}{2} \frac{di}{dt} + \frac{1}{2} \int_0^t i dt + 10 \quad (1)$$

$$\therefore \frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + i = 0 \quad i = A e^{s t}; \quad s_{1,2} = \frac{-2 \pm \sqrt{4-4}}{2} = -1$$

$$i(t) = A_1 e^{-t} + A_2 t e^{-t}$$

$$i(0) = 2 = A_1$$

and from (1) $2 + \frac{1}{2} \frac{di}{dt} \Big|_{t=0} = 2 \Rightarrow \frac{di}{dt} \Big|_{t=0} = 0$



$$\frac{di}{dt} \Big|_{t=0} = -A_1 + A_2 = 0 \Rightarrow A_1 = A_2$$

$$i(t) = 2e^{-t} + 2t e^{-t}$$

$$v_C(t) = 12 - i - \frac{1}{2} \frac{di}{dt} = 12 - 2e^{-t} - 2t e^{-t} - \frac{1}{2} \{-2e^{-t} - 2t e^{-t} + 2e^{-t}\}$$

$$v_C(t) = 12 - 2e^{-t} - t e^{-t} \quad t > 0$$

9.60

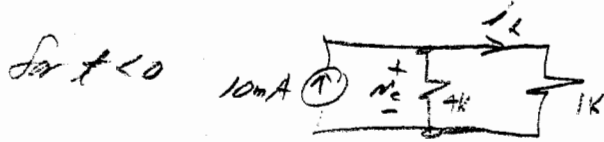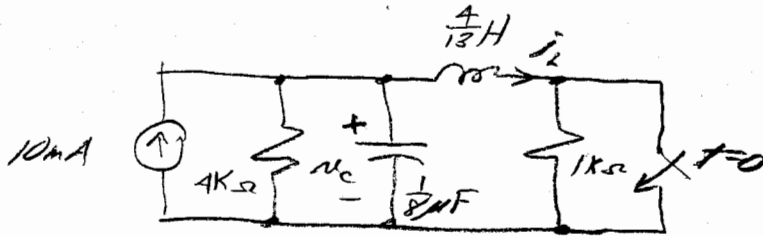

so $n_c(0) = 10^{-2} \frac{4}{5} \times 10^3 = 8$

$i_L(0) = 10^{-2} \frac{4}{5} = 8 \text{ mA}$

$$10^{-2} = \frac{n_c}{4 \times 10^3} + \frac{1}{5} \times 10^{-6} \frac{dn_c}{dt} + \frac{13}{4} \int_0^t n_c dt + 8 \times 10^{-3} \quad (1)$$

$$\infty \quad 0 = \frac{2n_c}{dt} + 2 \times 10^{-3} \frac{dn_c}{dt} + 26 \times 10^{-6} n_c$$

$$s_{1,2} = -1 \times 10^3 \pm \sqrt{10^6 - 26 \times 10^6} = -10^3 \pm j 5 \times 10^3$$

$$n_c(t) = A_1 e^{-10^3 t} \cos 5 \times 10^3 t + A_2 e^{-10^3 t} \sin 5 \times 10^3 t$$

but $n_c(0) = 8 = A_1$

from (1) $10^{-2} = 2 \times 10^{-3} + \frac{1}{5} \times 10^{-6} \frac{dn_c}{dt} + 8 \times 10^{-3} \Rightarrow \frac{dn_c}{dt} = 0$

$$\text{so } \left[-8 \times 5 \times 10^3 e^{-10^3 t} \sin 5 \times 10^3 t - 8 \times 10^3 e^{-10^3 t} \cos 5 \times 10^3 t + A_2 5 \times 10^3 e^{-10^3 t} \cos 5 \times 10^3 t - A_2 10^3 e^{-10^3 t} \sin 5 \times 10^3 t \right]_{t=0} = 0$$

giving $-8 \times 10^3 + 5 \times 10^3 A_2 = 0 \Rightarrow A_2 = \frac{8}{5}$

$$n_c(t) = e^{-10^3 t} \left[8 \cos(5 \times 10^3 t) + \frac{8}{5} \sin(5 \times 10^3 t) \right]$$

$$\left[\begin{aligned} \tau = \frac{1}{f} = \frac{2\pi}{5 \times 10^3} = 1.26 \text{ msec} \\ \tau = 1 \text{ msec} \end{aligned} \right]$$

see attached plot


$$\text{or } n_c(t) = \sqrt{8^2 + \left(\frac{8}{5}\right)^2} e^{-10^3 t} \cos(5000t - \tan^{-1} \frac{1}{5})$$

EE 211 Hayt problem 9.60


$$t := 0, 10^{-8} .. 2 \times 10^{-3}$$

$$Vc(t) := e^{-1000 \cdot t} \left(\frac{8}{5} \cdot \sin(5000 \cdot t) + 8 \cdot \cos(5000 \cdot t) \right)$$
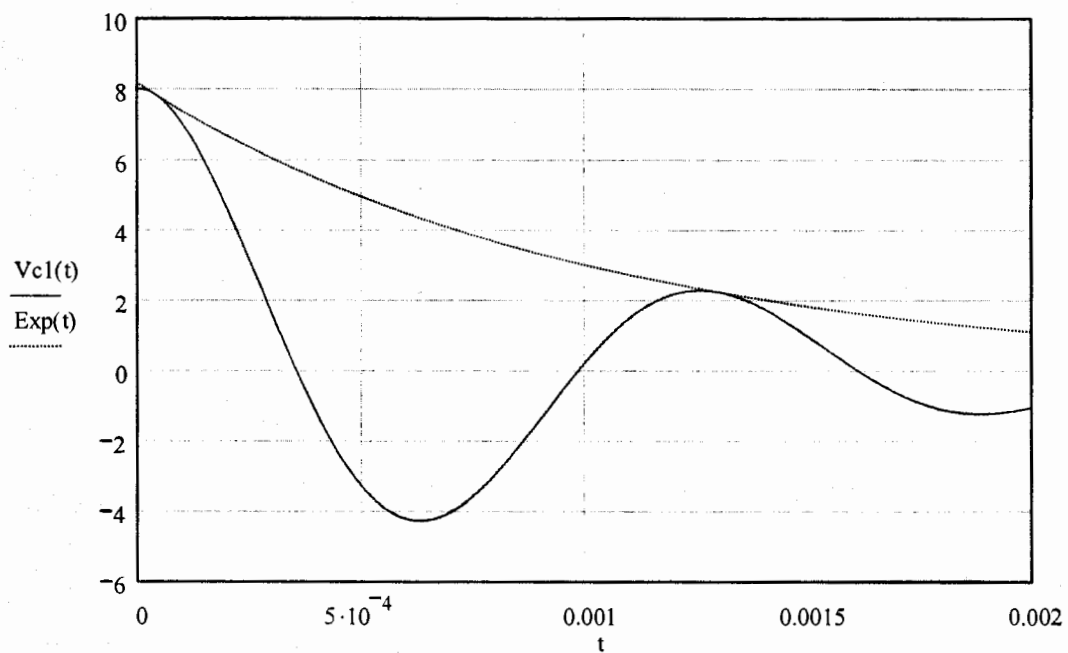
$$\text{Exp}(t) := \left[\sqrt{8^2 + \left(\frac{8}{5} \right)^2} \right] \cdot e^{-1000 \cdot t} \quad Vc1(t) := \text{Exp}(t) \cdot \cos \left(5000 \cdot t - \text{atan} \left(\frac{1}{5} \right) \right)$$




9.62

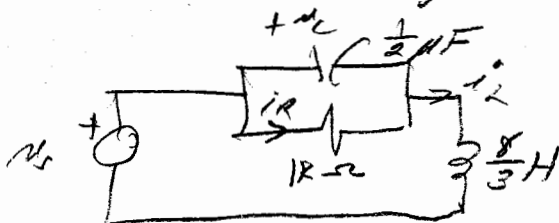

$v_c(0) = 10$

$i_L(0) = \frac{10}{10^3} = 10^{-2}$

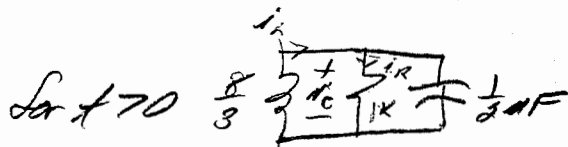a) $i_L = 10^{-2} e^{-t}$ or for $t < 0, i_L = 10^{-2}$
 for $t > 0, i_L = 0$



$\frac{d v_c}{dt} + \frac{v_c}{10^3} + \frac{10^{-6} v_c}{2 dt} + \frac{3}{8} \int v_c dt - 10^{-2} = 0 \quad (1)$

or $\frac{d^2 v_c}{dt^2} + 2 \times 10^3 \frac{d v_c}{dt} + \frac{3}{4} \times 10^6 v_c = 0$; $s^2 + 2 \times 10^3 s + \frac{3}{4} \times 10^6 = 0$

$s_{1,2} = \frac{-2 \times 10^3 \pm \sqrt{4 \times 10^6 - 3 \times 10^6}}{2} = -1 \times 10^3 \pm \frac{1}{2} \times 10^3$

$s_{1,2} = -\frac{3}{2} \times 10^3, -\frac{1}{2} \times 10^3$

$v_c(t) = A_1 e^{-\frac{3}{2} \times 10^3 t} + A_2 e^{-\frac{1}{2} \times 10^3 t}$ but $v_c(0) = 10$

so $10 = A_1 + A_2$

from (1) $10^{-2} + \frac{10^{-6}}{2} \frac{d v_c}{dt} \Big|_{t=0} - 10^{-2} = 0$ so $\frac{d v_c}{dt} \Big|_{t=0} = 0$


giving $0 = A_1 (-\frac{3}{2} \times 10^3) + A_2 (-\frac{1}{2} \times 10^3)$ or $0 = -3A_1 - A_2$

so $0 = -3(10 - A_2) - A_2 = -30 + 2A_2$ so $A_2 = 15$

and $A_1 = 10 - A_2 = -5$

so $i_L = \frac{v_c(t)}{10^3} = -5 \times 10^{-3} e^{-\frac{3}{2} \times 10^3 t} + 15 \times 10^{-3} e^{-\frac{1}{2} \times 10^3 t}$

10.11
 find $v_c(t)$

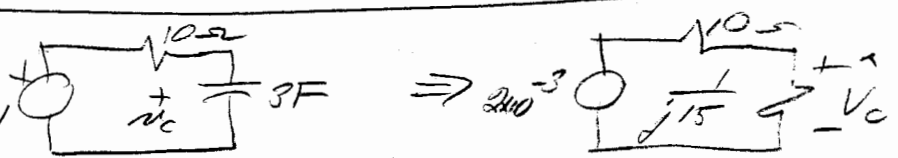

$V_c = \frac{2 \times 10^{-3} \frac{1}{j15}}{10 + \frac{1}{j15}} = 2 \times 10^{-3} \frac{1}{1 + j150} = \frac{2 \times 10^{-3}}{150 \angle 89.6^\circ} = 1.33 \times 10^{-5} \angle -89.6^\circ$




so $v_c(t) = 13.33 \times 10^{-6} \cos(5t - 89.6^\circ)$

EE 211

Assignment 28

10.13

$20 \mu A \cdot 500 \mu s = 10 \mu s$

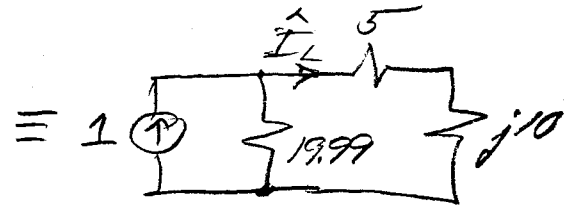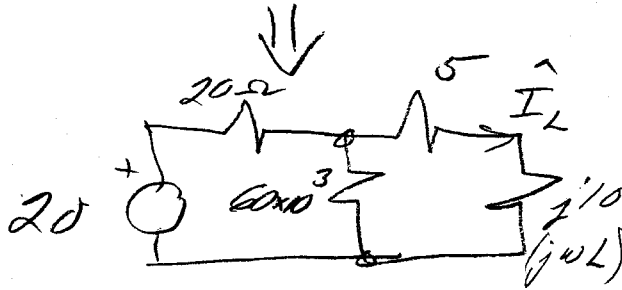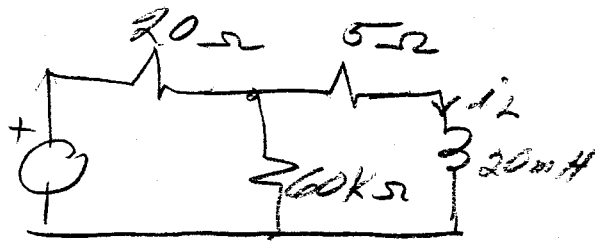


so by current division $\hat{I}_L = 1 \cdot \frac{19.99}{24.99 + j10} = \frac{19.99}{26.92 \angle 21.8^\circ}$


$$\hat{I}_L = 0.7426 \angle -21.8^\circ$$

$i_L(t) = 0.7426 \cos(500t - 21.8^\circ)$

10.18

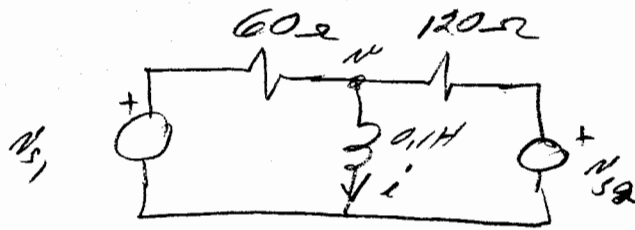

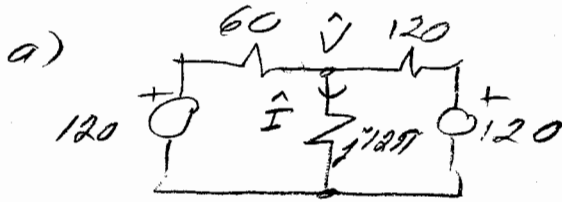$N_{s1} = N_{s2} = 120 \text{ or } 120 \text{ V}$
 $j\omega L = j^{\circ} 120 \pi \times 0.1$



$$\frac{\hat{V} - 120}{60} + \frac{\hat{V}}{j120\pi} + \frac{\hat{V} + 120}{120} = 0$$

$$\hat{V} \left(\frac{1}{60} + \frac{1}{120} - j \frac{1}{120\pi} \right) = 1 + 2 = 3$$

or $\hat{V} (3\pi - j10) = 360\pi$; $\hat{V} = \frac{360\pi}{3\pi - j10}$; $\hat{I} = \frac{\hat{V}}{j120\pi} = \frac{-j30}{3\pi - j10}$


$\hat{I} = \frac{30}{10 + j3\pi} = 13.74 \text{ or } 43.3^{\circ}$; $2.183 \text{ or } (120\pi - 43.3^{\circ}) = j4$

$W_L = \frac{1}{2} L i^2 = 0.05 \times 4.765 \text{ or } (120\pi - 43.3^{\circ})$

or $W_L = 0.2383 \text{ or } (120\pi - 43.3^{\circ}) \text{ J}$

b) $W_{\text{Loss}} = \frac{1}{2} \times 0.2383 = 0.119 \text{ J}$

10.21

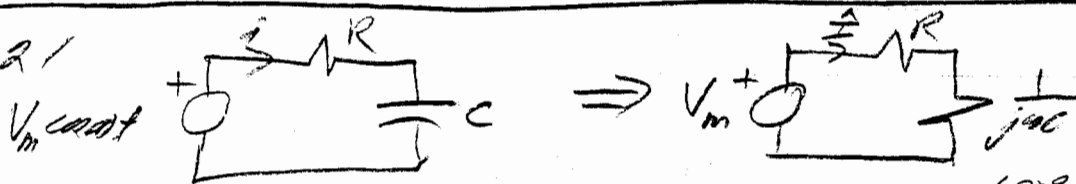

$$\hat{I} = \frac{V_m}{R + j\omega C} = \frac{V_m j\omega C}{1 + j\omega RC} = \frac{\omega C V_m e^{j90^{\circ}}}{\sqrt{1 + (\omega RC)^2} e^{j \tan^{-1}(\omega RC)}}$$

$$\hat{I} = \frac{\omega C V_m}{\sqrt{1 + (\omega RC)^2}} e^{j[90^{\circ} - \tan^{-1}(\omega RC)]}$$

so $i(t) = \frac{\omega C V_m}{\sqrt{1 + (\omega RC)^2}} \cos[wt + 90^{\circ} - \tan^{-1}(\omega RC)]$

or $i(t) = \frac{\omega C V_m}{\sqrt{1 + (\omega RC)^2}} \cos[wt + \tan^{-1}(\frac{1}{\omega RC})]$

$$10.26 \ a) \ 5 \angle^{-110^\circ} = -1.71 - j4.698 \quad \leftarrow$$

$$b) \ 6 \angle^{160^\circ} = -5.638 + j2.052 \quad \leftarrow$$

$$c) \ (3+j6)(2 \angle^{50^\circ}) = (3+j6)(1.285 + j1.532) = -5.337 + j12.31 \quad \leftarrow$$

$$d) \ -100 - j40 = \underline{107.7 \angle^{201.8^\circ}} = \underline{107.7 \angle^{158.2^\circ}} \quad \leftarrow$$


$$e) \ 2 \angle^{50^\circ} + 3 \angle^{120^\circ} = 1.2856 + j1.532 - 1.5 - j2.598 = -0.2144 - j1.066 \\ = \underline{1.087 \angle^{-101.37^\circ}} \quad \leftarrow$$

$$10.27 \ a) \ 40 \angle^{50^\circ} - 18 \angle^{25^\circ} = 25.712 - j30.64 - 16.31 - j7.607 \\ = \underline{9.402 - j38.247} = \underline{39.39 \angle^{-76.19^\circ}} \quad \leftarrow$$


$$b) \ 3 - j2 + \frac{2 - j5}{1 + j2} = \frac{3 + j6 - j2 + 4 + 2 - j5}{1 + j2} = \frac{9 - j}{1 + j2} = \frac{(9 - j)(1 - j2)}{5} \\ = \underline{\frac{7 - j19}{5}} = \underline{1.4 - j3.8} = \underline{4.05 \angle^{-69.78^\circ}} \quad \leftarrow$$

$$c) \ [2.1 \angle^{25^\circ}]^3 = 9.261 \angle^{75^\circ} = \underline{2.397 + j8.945} \quad \leftarrow$$
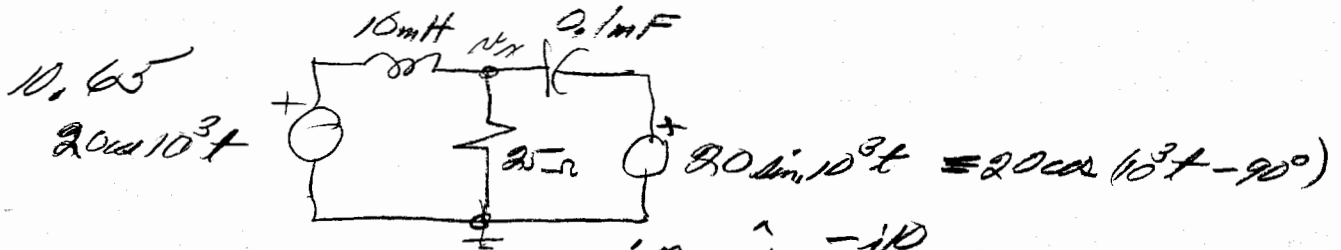
$$d) \ 0.7 \angle^{10.3^\circ} = \underline{0.669 + j0.207} \quad \leftarrow$$



so we have:

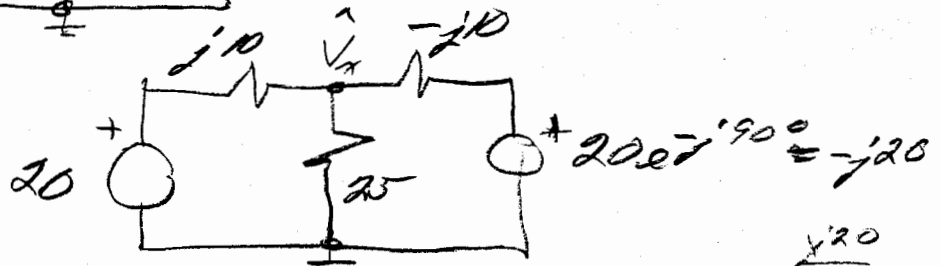


$$\frac{\hat{V}_x - 20}{j10} + \frac{\hat{V}_x}{25} + \frac{\hat{V}_x - 20 \sqrt{2} e^{j90^\circ}}{-j10} = 0$$

$$\frac{j20}{-j10}$$

$$\hat{V}_x \left(-\frac{1}{j10} + \frac{1}{25} + \frac{1}{j10} \right) = -j2 + 2 \Rightarrow \hat{V}_x = 50 (1 + j)$$


$$\hat{V}_x = 50 \sqrt{2} e^{-j45^\circ}$$

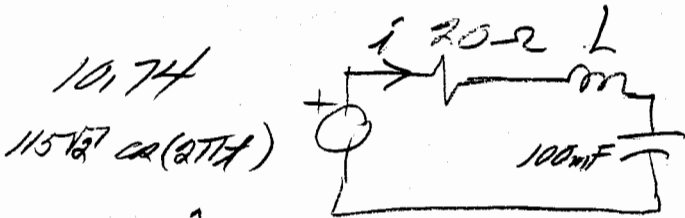so $v_x(t) = \underbrace{50 \sqrt{2}}_{70.71} \cos(10^3 t - 45^\circ)$ ←



$$i = 8.132 \angle 271^\circ$$
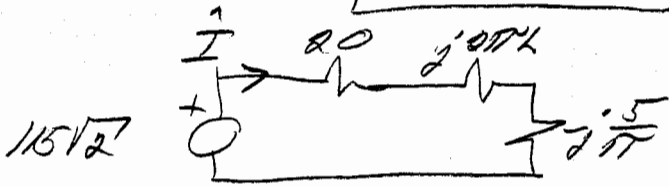
$$\frac{1}{j\omega C} = \frac{1}{j2\pi \times 0.1} = -j\frac{5}{\pi}$$




$$\hat{I} = \frac{115\sqrt{2}}{20 + j(271k - \frac{5}{\pi})}$$

$$|\hat{I}| = 8.132 = \frac{115\sqrt{2}}{\sqrt{400 + (271k - \frac{5}{\pi})^2}}$$


$$\text{or } 400 + (271k - \frac{5}{\pi})^2 = \left(\frac{115\sqrt{2}}{8.132}\right)^2 = 400$$

$$\text{or } (271k - \frac{5}{\pi})^2 = 0 ; \boxed{L = \frac{5}{271k} = 0.253 \mu\text{H}}$$

6.13

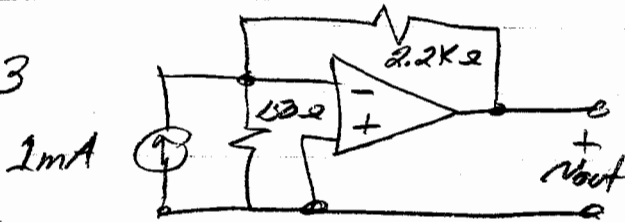


Inverting amp

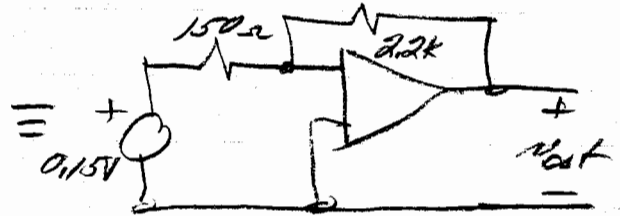

$$V_{out} = -\frac{2.2 \times 10^3}{150} \times 0.15 = -2.2 \text{ volts}$$


6.16

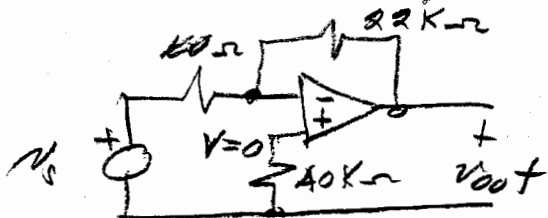

$40\text{K}\Omega$ resistor has no current so it has no effect on the circuit.

$$V_{out} = - \frac{22 \times 10^3}{10^2} V_s = -220 V_s$$

6.17

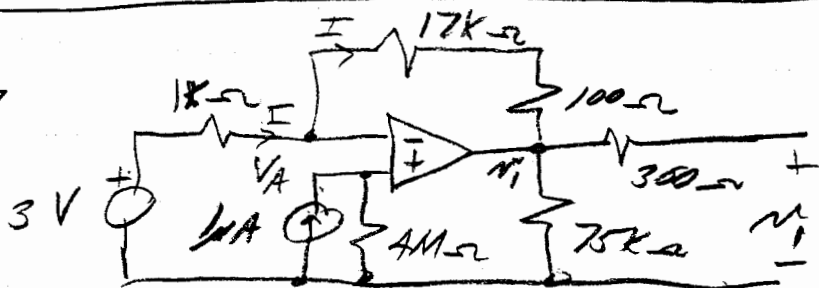

$$V_A = 10^{-6} \times 4 \times 10^6 = 4\text{V} \quad \therefore -3 + 10^3 I + 4 = 0$$

OR $I = -10^{-3}\text{A}$

$$\text{and } \frac{4-3}{10^3} + \frac{4-V_1}{17.1 \times 10^3} = 0$$

$$\frac{1}{10^3} + \frac{4}{17.1 \times 10^3} = \frac{V_1}{17.1 \times 10^3}$$

$$V_1 = 4 + 17.1 = 21.1\text{V}$$


$$\text{could find } V_1 = -I (17.1 \times 10^3) + 4 = 17.1 + 4 = 21.1\text{V}$$

↑
2nd method

EE 211

Assignment 3#

6.22

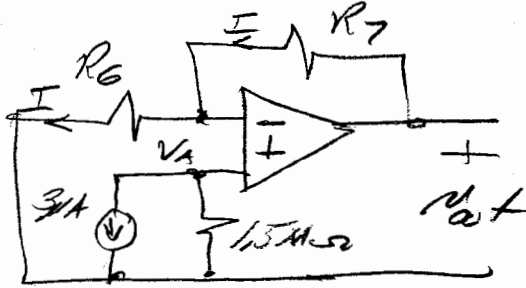

$$-V_A = 3 \times 10^{-6} \times 1.5 \times 10^6 = -4.5$$


$$\therefore I = \frac{-4.5}{R_6}$$

$$\text{and } v_{out} = IR_7 - 4.5 = \frac{-4.5}{R_6} R_7 - 4.5 = -4.5 \left(1 + \frac{R_7}{R_6}\right) \leftarrow$$

Special problem ... need a non-inverting amplifier with a gain of:

$$0.01 \text{ V/degree} \times 100 \text{ degrees} = 1 \text{ V}$$

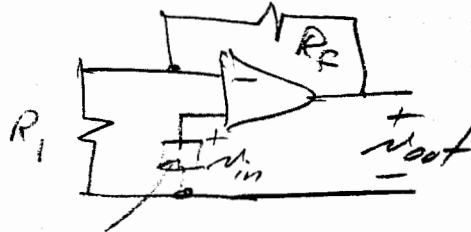
\therefore 1 volt in should give 10 volts out or a gain of 10.



Thermal sensor

$$\frac{v_{out}}{v_{in}} = 10 = 1 + \frac{R_f}{R_1} ; \text{ so } \boxed{\frac{R_f}{R_1} = 9} \leftarrow$$

8.94


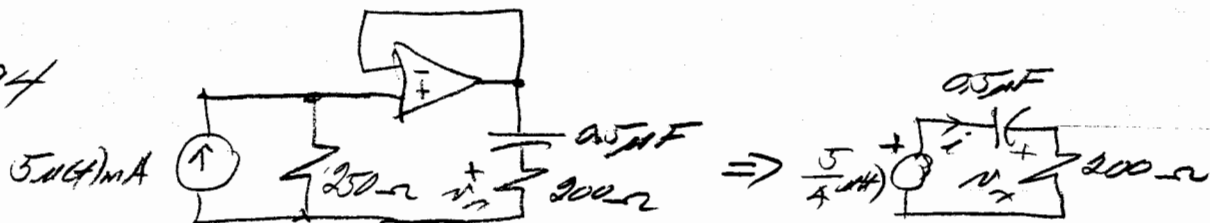


$$\frac{5}{4} = 200i + 2 \times 10^6 \int i dt \quad \text{or} \quad 0 = 200 \frac{di}{dt} + 2 \times 10^6 i$$

$$i = A e^{st} \quad ; \quad 200s + 2 \times 10^6 = 0 \quad \therefore s = -10^4$$

$$i(0) = \frac{5}{4 \times 200} \quad \therefore i(t) = \frac{5}{4 \times 200} e^{-10^4 t} \quad \text{and} \quad v_x = 200i = \frac{5}{4} e^{-10^4 t}$$

10.20

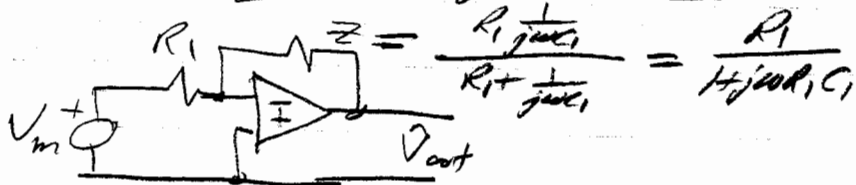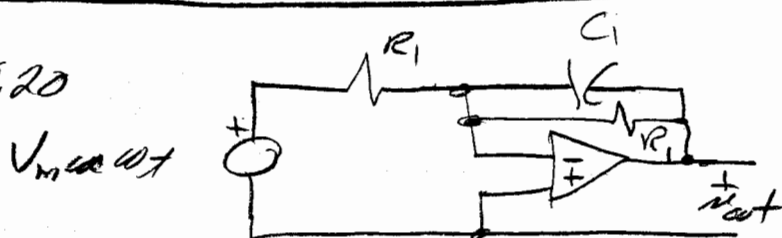


$$Z = \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$\hat{V}_{out} = -V_m \frac{1}{1 + j\omega R_1 C_1} \quad (\text{inverting amp}) \quad \text{Gain} = -\frac{Z_F}{Z_{in}}$$

$$\hat{V}_{out} = -V_m \frac{e^{-j \tan^{-1} \omega R_1 C_1}}{\sqrt{1 + (\omega R_1 C_1)^2}}$$

$$v_{out}(t) = -\frac{V_m}{\sqrt{1 + (\omega R_1 C_1)^2}} \cos(\omega t - \tan^{-1} \omega R_1 C_1)$$

Low Pass Filter!

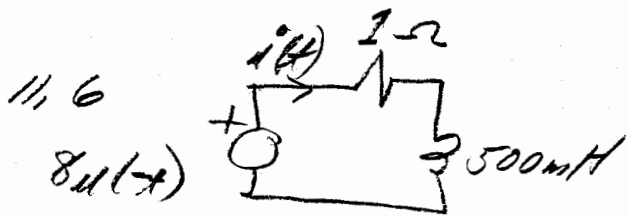

@ $t=0$ $i(t) = 8A$

for $t > 0$ $0 = i + \frac{1}{2} \frac{di}{dt}$


$i = Ae^{st}$; $0 = 1 + \frac{1}{2}s$ or $s = -2$

and $i(t) = 8e^{-2t}$

a) $P_R = i^2 R$ $\therefore P_R(t) = 8^2 \times 1 = 64 \text{ Watts}$ ←

b) $P_R(1) = [8e^{-2}]^2 = 1.17 \text{ Watts}$ ←

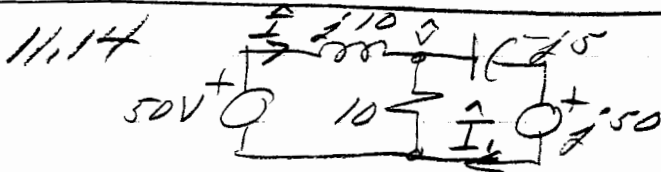c) $P_R(2) = [8e^{-4}]^2 = 2.647 \text{ mWatts}$ ←



$\frac{\hat{V}-50}{j10} + \frac{\hat{V}}{10} + \frac{\hat{V}-j50}{-j5} = 0$

$\hat{V}(-j\frac{1}{10} + \frac{1}{10} + j\frac{1}{5}) = -j5 - 10$ or $\hat{V}(1+j) = -50(2+j)$

$\hat{V} = \frac{-50(2+j)}{1+j} = \frac{50 \angle 100^\circ \sqrt{5} \angle j26.57^\circ}{\sqrt{2} \angle j45^\circ} = 79.06 \angle 161.57^\circ$ ←

$\hat{I} = \frac{50 - \hat{V}}{j10} = \frac{50 + 75 - j25}{j10} = \frac{127.48 \angle 11.31^\circ}{13.2 \angle 90^\circ} = 12.75 \angle -10.31^\circ$

$P_{AVR 50V} = \frac{1}{2} 12.75 \times 50 \cos(10.31^\circ) = 62.51 \text{ Watts}$ ←


$P_{AVR 10\Omega} = \frac{1}{2} \frac{|\hat{V}|^2}{10} = \frac{(79.06)^2}{20} = 312.52 \text{ Watts}$ ←

$\hat{I}_1 = \frac{\hat{V} - j50}{-j5} = \frac{-75 + j25 - j50}{-j5} = \frac{+75 + j25}{+j5} = 5 - j15 = 15.81 \angle -71.57^\circ$

$P_{AVR j50\Omega} = \frac{1}{2} 50 \times 15.81 \cos(90 + 71.57^\circ) = 395.25 \times (-0.949) = -375 \text{ Watts}$ ←

$Z = 0.05 \Omega$

10:54
10:27
27 min

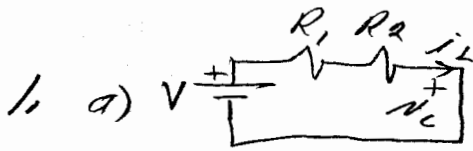


$i_L(0) = 0$

$i_L(0) = \frac{V}{R_1 + R_2} = \frac{4}{2} = 2A$

$v = L \frac{di}{dt}$

$i = C \frac{dv}{dt}$

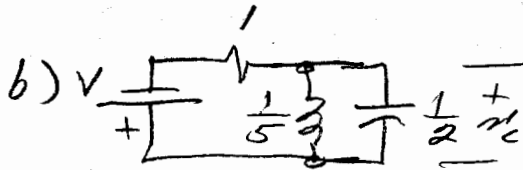

$i_C + 4 + 5 \int_0^t i_C dt + 2 + \frac{1}{2} \frac{dv_C}{dt} = 0$


or $\frac{d^2 v_C}{dt^2} + 2 \frac{dv_C}{dt} + 10 v_C = 0$; $v_C = A e^{s t}$

$5s^2 + 2s + 10 = 0 \implies s_{1,2} = \frac{-2 \pm \sqrt{4 - 200}}{10} = -1 \pm j3$

$v_C(t) = B_1 e^{-t} \cos 3t + B_2 e^{-t} \sin 3t$ but $v_C(0) = 0 \implies B_1 = 0$



$\left. \frac{dv_C}{dt} \right|_{t=0} = -12 = 3B_2 \implies v_C(t) = -4 e^{-t} \sin 3t$

c) Underdamped

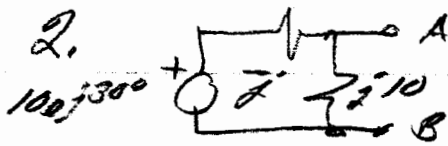

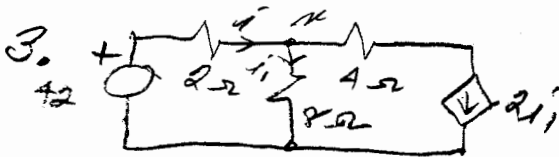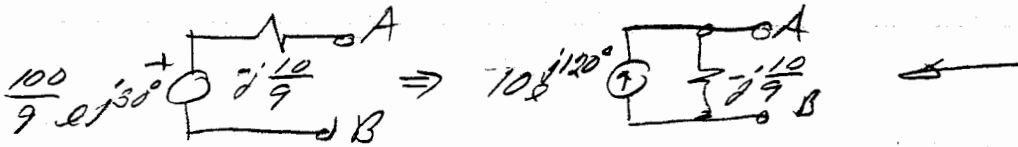a) $V_{Th} = V_{oc} = \frac{j10}{j9} \cdot 100 e^{j30^\circ} = \frac{100}{9} e^{j30^\circ}$

$Z_{Th} = Z_{eq} = \frac{j(4)10}{j9} = -j\frac{10}{9}$



$\frac{v-42}{2} + \frac{v}{8} + 2i_1 = 0$; $i_1 = \frac{v}{8}$

$\implies v \left(\frac{1}{2} + \frac{1}{8} + \frac{1}{4} \right) = 21$ so $v = 24V$

$i = 3i_1 = 9A$

4. $-V_1 + I(2R_1) + V_2 = 0$; $I = \frac{V_1 - V_2}{2R_1} \implies V_+ - V_- = IR_1 + V_2 = \frac{V_1 - V_2}{2} + V_2 = \frac{V_1 + V_2}{2}$

$V_- = \frac{V_{out} R}{2R}$ so $V_{out} = 2V_- = V_1 + V_2$

$$5. a) \left. \begin{aligned} -5 + 2i_1 + i_2 + 4 + 3i_2 &= 0 \\ i_2 - i_1 &= 2 \end{aligned} \right\} \begin{aligned} 2i_1 + 4i_2 &= 1 \\ -i_1 + i_2 &= 2 \end{aligned} \left| \begin{bmatrix} 2 & 4 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1 \\ 2 \end{bmatrix} \right.$$

$$b) \left. \begin{aligned} \frac{V_1 - 5}{2} - 2 + \frac{V_1 - V_2}{1} &= 0 \\ \frac{V_2 - V_1}{1} + \frac{V_3}{3} &= 0 \\ V_2 - V_3 &= 4 \end{aligned} \right\} \begin{aligned} \frac{3}{2}V_1 - V_2 &= \frac{9}{2} \\ -V_1 + V_2 + \frac{1}{3}V_3 &= 0 \\ V_2 - V_3 &= 4 \end{aligned} \left| \begin{bmatrix} 3 & -2 & 0 \\ -3 & 3 & 1 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 9 \\ 0 \\ 4 \end{bmatrix} \right.$$

$$c) \text{ from a) } i_1 = \frac{\begin{vmatrix} 1 & 4 \\ 2 & 1 \end{vmatrix}}{\begin{vmatrix} 2 & 4 \\ -1 & 1 \end{vmatrix}} = \frac{1-8}{2+4} = -\frac{7}{6} \leftarrow$$

$$i_2 = \frac{\begin{vmatrix} 2 & 1 \\ -1 & 2 \end{vmatrix}}{6} = \frac{4+1}{6} = \frac{5}{6} \leftarrow$$