
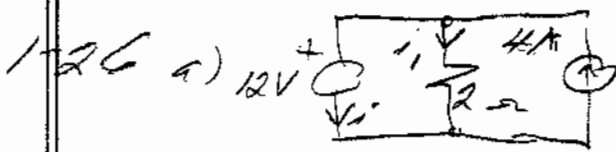


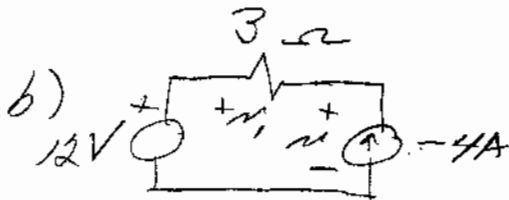
- a)  $v_s = 2V$ ;  $i_4 = i_2 + i_1 = 2 \quad \therefore v_4 = -4i_4 = -8V$   
 b)  $v_s = 4V$   $i_4$  does not change  $\therefore v_4 = -8$   
 c)  $v_s = 6V$   $i_4 = 2$   $v_4 = -8$



$i_1 = \frac{12}{2} = 6A$   
 $i = 4 - i_1 = -2A$



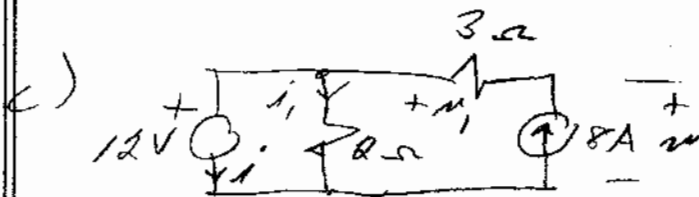$v_1 = -(-4) \times 3 = 12V$   
 $-12 + v_1 + v_1 = 0 \quad \therefore v_1 = 0$



$v_1 = -3 \times 8 = -24V$   
 $i_1 = 6A$  *did not ask in this*  
 $\therefore i = 8 - i_1 = 2A$

$-12 + v_1 + v_1 = 0 \quad \text{so} \quad v_1 = 12 + 24 = 36V$




$i_1 = 9A$   
 $v_2 = 6V$

$-v_1 + v_2 + 9 = 0 \quad \therefore v_1 = 9 + v_2 = 15V$

KCL  $-3 + i_1 + i - 2 = 0 \quad i = 5 - i_1 = 5 - 9 = -4A$

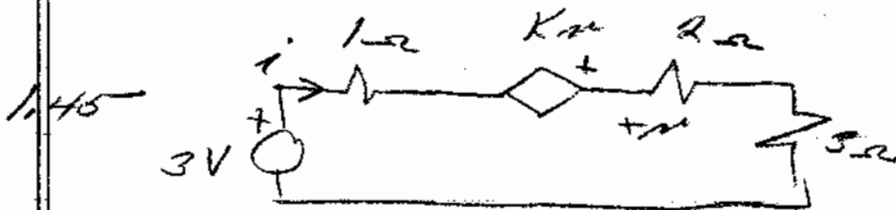
KCL  $-i_1 + v_2 - 4 + v_2 = 0 \Rightarrow v_2 = 4 + i_1 - v_2 = 4 + 15 - 6 = 13V$



1)  $K=2$        $-3 + i - 2i + 5i = 0$       but  $i = 2i$   
 $\therefore 2i = 3$       or       $i = \frac{3}{2} \text{ A}$  ←

2)  $K=4$        $-3 + i - 4(2i) + 5i = 0$       ;       $-2i = 3$   
 $i = -\frac{3}{2} \text{ A}$  ←

2.8

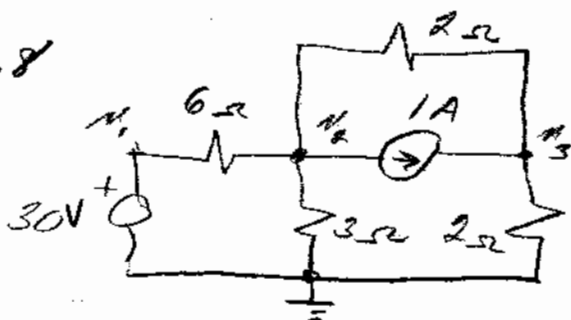

$n_1 = 30 \text{ V}$

$$\frac{n_2 - n_1}{6} + \frac{n_2}{3} + \frac{n_2 - n_3}{2} = -1$$


$$\frac{n_3 - n_2}{2} + \frac{n_3}{2} = 1 \Rightarrow n_3 = 1 + \frac{n_2}{2}$$

$$-\frac{n_1}{6} + n_2 \left( \frac{1}{6} + \frac{1}{3} + \frac{1}{2} \right) - \left( 1 + \frac{n_2}{2} \right) \frac{1}{2} = -1$$

$$-\frac{n_1}{6} + n_2 \left( \frac{9}{18} \right) = -\frac{1}{2} \Rightarrow n_2 \frac{9}{18} = -\frac{1}{2} + 5$$

$n_2 = \frac{4}{3} \left( \frac{9}{2} \right) = 6 \text{ V}$  ←

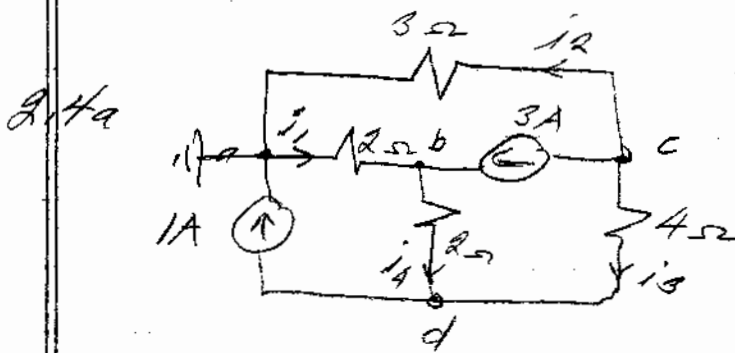and  $n_3 = 1 + \frac{n_2}{2} = 4 \text{ V}$  ←



Note voltage analysis

$$\frac{V_b}{2} + \frac{V_b - V_d}{2} = 3$$

$$\frac{V_c}{3} + \frac{V_c - V_d}{4} = -3$$

$$\frac{V_d - V_b}{2} + \frac{V_d - V_c}{4} = -1$$

$$\begin{cases} V_b - \frac{1}{2}V_d = 3 \\ \frac{7}{12}V_c - \frac{1}{4}V_d = -3 \\ -\frac{1}{2}V_b - \frac{1}{4}V_c + \frac{3}{4}V_d = -1 \end{cases}$$


$$\begin{cases} 2V_b - V_d = 6 \\ 7V_c - 3V_d = -36 \\ -2V_b - V_c + 3V_d = -4 \end{cases}$$

$$\therefore V_b = \frac{V_d + 6}{2}, \quad V_c = \frac{3V_d - 36}{7}$$

$$\text{so } -V_d - 6 - \frac{3V_d - 36}{7} + 3V_d = -4$$

$$V_d \left( -1 - \frac{3}{7} + 3 \right) = 6 - 4 - \frac{36}{7} = -\frac{22}{7}$$
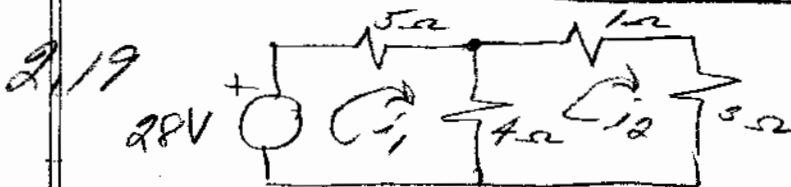
$$\begin{cases} V_d = -2V \\ V_b = -1 + 3 = 2V \\ V_c = -\frac{42}{7} = -6V \end{cases}$$



$$-28 + 5i_1 + 4(i_1 - i_2) = 0$$

$$4(i_2 - i_1) + 4i_2 = 0$$

$$\text{or } 9i_1 - 4i_2 = 28$$

$$-4i_1 + 8i_2 = 0$$


$$i_1 = \frac{\begin{vmatrix} 28 & -4 \\ 0 & 8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -4 & 8 \end{vmatrix}} = \frac{224}{72 - 16} = 4A$$

$$i_2 = \frac{\begin{vmatrix} 9 & 28 \\ -4 & 0 \end{vmatrix}}{56} = \frac{4 \times 28}{56} = \frac{112}{56} = 2A$$

ES 332

Homework 4

Q.25

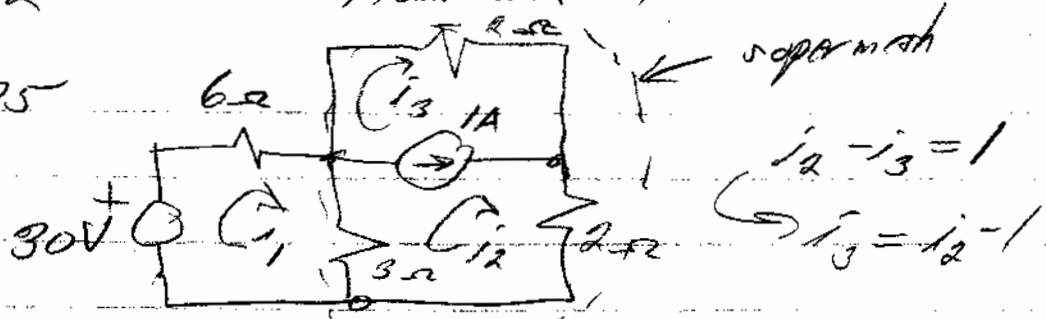


$$\begin{cases} -30 + 6i_1 + 3(i_1 - i_2) = 0 & 9i_1 - 3i_2 = 30 \\ 3(i_2 - i_1) + 2i_3 + 2i_2 = 0 & -3i_1 + 7i_2 = 2 \end{cases}$$

$$i_1 = \frac{\begin{vmatrix} 30 & -3 \\ 2 & 7 \end{vmatrix}}{\begin{vmatrix} 9 & -3 \\ -3 & 7 \end{vmatrix}} = \frac{210 + 6}{63 - 9} = \frac{216}{54} = 4 \text{ A}$$

$$i_2 = \frac{\begin{vmatrix} 9 & 30 \\ -3 & 2 \end{vmatrix}}{54} = \frac{18 + 90}{54} = \frac{108}{54} = 2 \text{ A}$$

Q.11

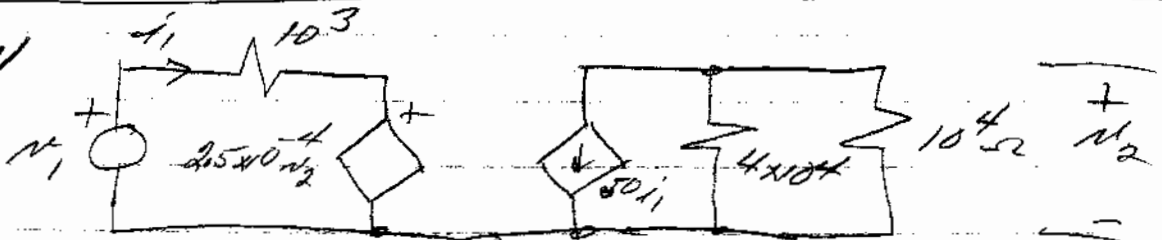

a)  $-N_1 + 10^3 i_1 + 2.5 \times 10^4 N_2 = 0$ ;  $N_2 = -50i_1$ ,  $\frac{4 \times 10^8}{5 \times 10^4} = -40 \times 10^4 i_1$

$\therefore -N_1 + 10^3 \left( \frac{N_2}{-40 \times 10^4} \right) + 2.5 \times 10^4 N_2 = 0$

$-N_1 = (2.5 \times 10^{-3} - 2.5 \times 10^{-4}) N_2 = 2.25 \times 10^{-3} N_2$

$$\frac{N_2}{N_1} = -\frac{1}{2.25 \times 10^{-3}} = -444.44$$


b)  $\frac{N_1}{11} = \frac{N_1 \times 10^3}{N_1 - 2.5 \times 10^{-4} (-444.44) N_1} = 0.900 \times 10^3 = 900 \Omega$

0.1111

3

Problem 2.8 using superposition

Voltage Source

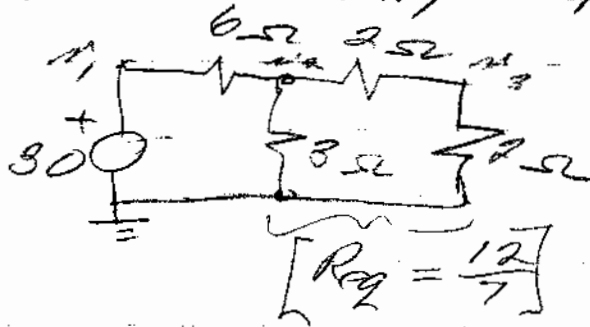


$$n_1 = 30$$

voltage division

$$v_{o,d_2} = 30 \frac{\frac{12}{7}}{\frac{12}{7} + 15} = 30 \frac{12}{54} = \frac{20}{3}$$

$$n_3 = n_2 \frac{2}{4} = \frac{90}{27} = \frac{10}{3}$$

Current Source

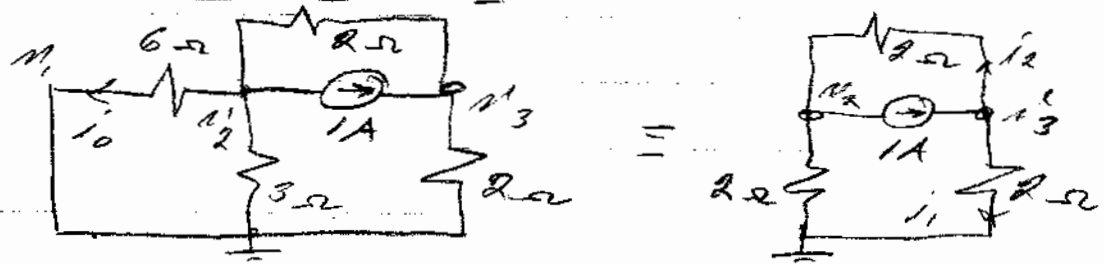


$$i_1 = 1 \times \frac{2}{6} = \frac{1}{3} A ; i_2 = 1 \times \frac{1}{6} = \frac{1}{6} A$$







$$\therefore n_3 = 2i_1 = \frac{2}{3} V ; n_2 = -\frac{2}{3} V ; n_1 = 0$$

So the results are
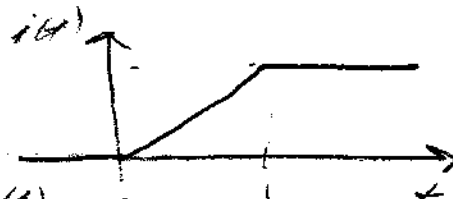
$$\left. \begin{aligned} n_1 &= 30 \\ n_2 &= \frac{20}{3} - \frac{2}{3} = \frac{18}{3} = 6V \\ n_3 &= \frac{10}{3} + \frac{2}{3} = 4V \end{aligned} \right\} \leftarrow$$



$$v = L \frac{di}{dt}$$

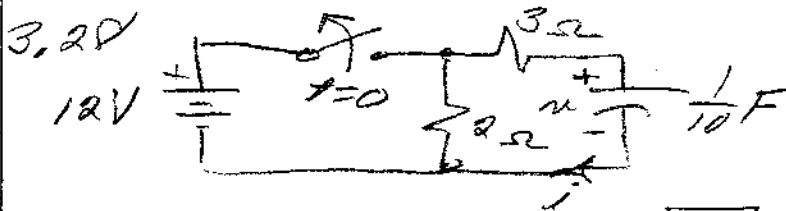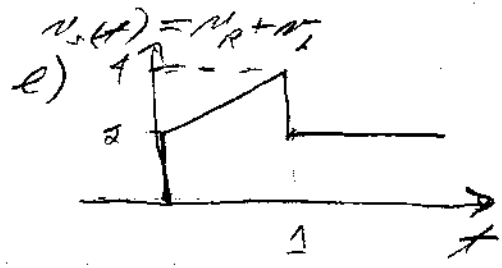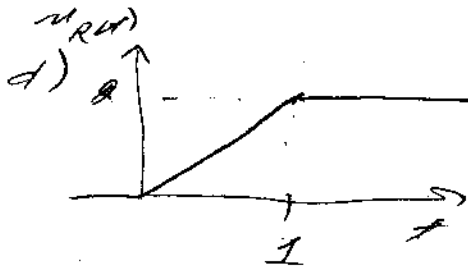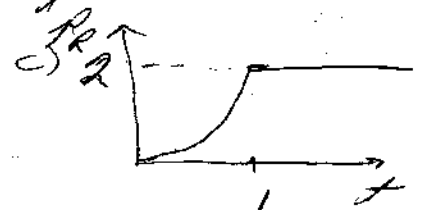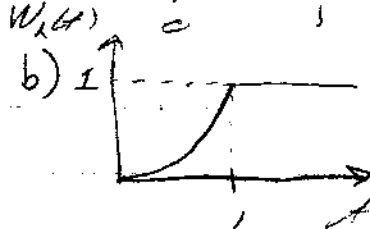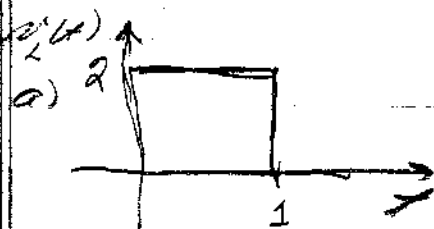

$$v(0) = 12V$$

for  $t > 0$  we have  $5\Omega$



$$(1) \quad 5i + 10 \int_0^t i dt + v(0) = 0 \Rightarrow 5 \frac{di}{dt} + 10i = 0$$

$$i = A e^{st} \Rightarrow 5s + 10 = 0; \quad s = -2 \quad (\tau = \frac{1}{2} \text{ sec})$$


from (1)  $5i(0) = -12; \quad i(0) = -\frac{12}{5}$

$$\therefore i(t) = -\frac{12}{5} e^{-2t}$$

$$v(t) = -5i = 12 e^{-2t}$$

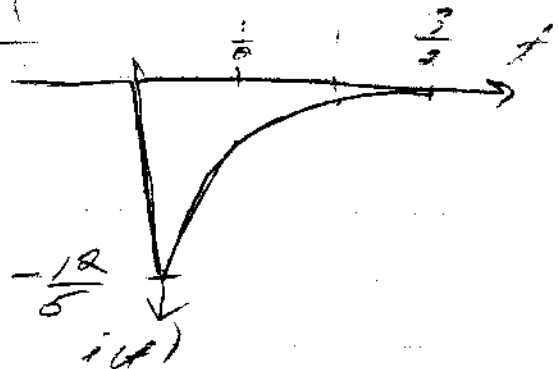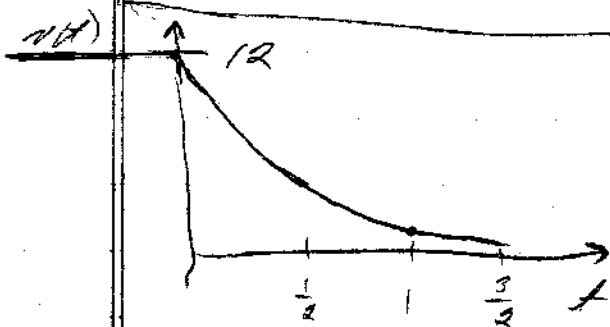


3.29

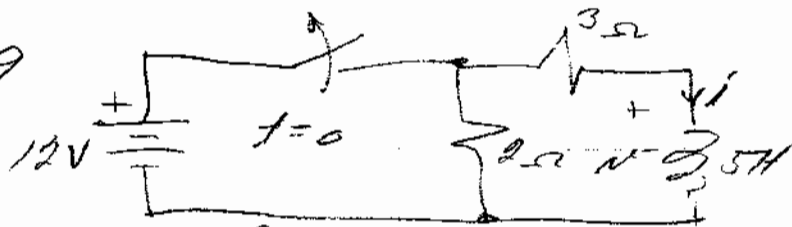

$i(0) = 4A$

for  $t > 0$


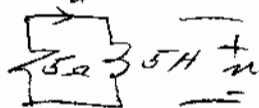


$5i + 3.5 \frac{di}{dt} = 0 ; i = Ae^{st}$


$5 + 3.5s = 0 ; s = -1$

$\therefore i(t) = 4e^{-t}$

$v(t) = -5i' = -20e^{-t}$

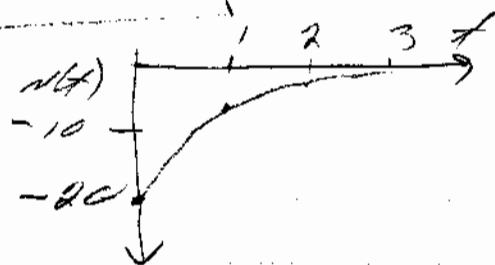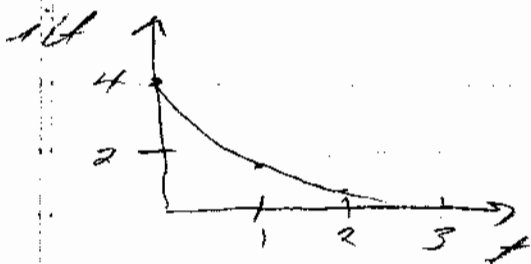

3.34

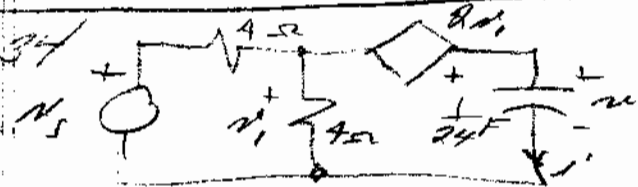


$v_s(t) = 18V$  for  $t < 0$

$v_s(t) = 0$  for  $t > 0$

for  $t < 0, i = 0$  so  $v_c = 6V$

and  $v = 3v_c = 18V$

for  $t > 0$  we have:

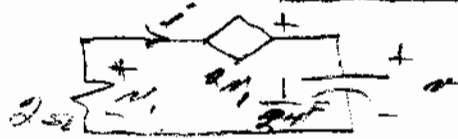

$v_c = -2i'$


(1)  $2i - 2i' + 24 \int_0^+ i dt + 18 = 0$

or  $\frac{di}{dt} + 4i = 0 ; i = Ae^{st} ; s = -4$

but from (1)  $6i(0) = 18 ; i(0) = -3$

$\therefore i = -3e^{-4t}$


$v = 3v_c = -6i = 18e^{-4t}$

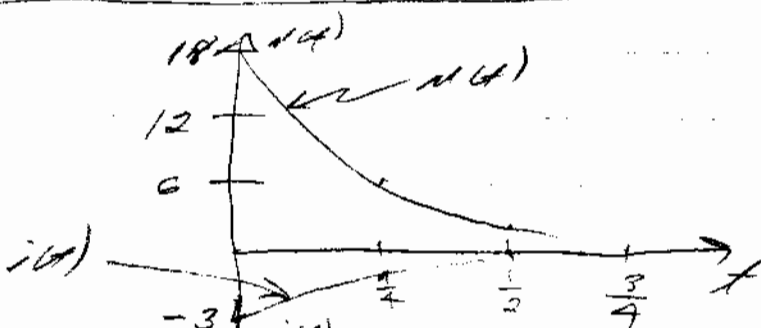

ES 332

Homework 8

3.57

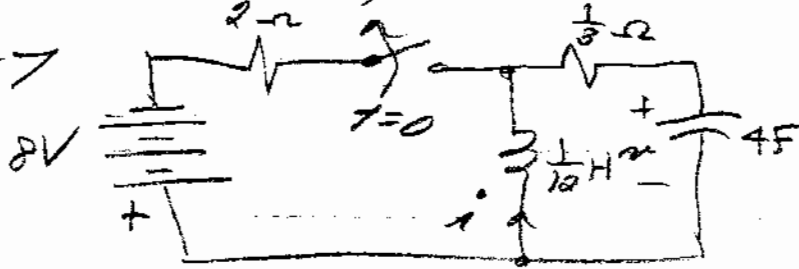

$$v(0) = 0$$

$$i(0) = \frac{2}{2} = 1A$$

for  $t > 0$   $\frac{1}{10} \frac{di}{dt} + \frac{1}{3}i + \frac{1}{4} \int_0^t i dt + 0 = 0$  (1)

or  $\frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 3i = 0$  ;  $i = A e^{st}$

$$s^2 + 4s + 3 = 0 \quad \therefore \boxed{s_{1,2} = -2 \pm \sqrt{4-3} = -1, -3}$$

$$i(t) = A_1 e^{-t} + A_2 e^{-3t} \quad \text{but } i(0) = 1$$

$$\therefore 1 = A_1 + A_2 \quad (2)$$

evaluating equation (1) @  $t=0$  gives

$$\left. \frac{di}{dt} \right|_{t=0} + 4i(0) = 0 ; \left. \frac{di}{dt} \right|_{t=0} = -16$$

$$\therefore -A_1 + 3A_2 = -16 \quad (3)$$

combining (2) + (3) gives  $4 - A_2 + 3A_2 = -16$

$$2A_2 = -20 \quad \therefore A_2 = -10$$


$$A_1 = -2$$

$$\therefore \boxed{i(t) = -2e^{-t} - 10e^{-3t}}$$

$$v(t) = -i \left( \frac{1}{3} + \frac{1}{10} \frac{di}{dt} \right) = -2e^{-3t} \left( \frac{1}{3} + \frac{1}{10} (-2e^{-t} - 10e^{-3t}) \right) + \frac{1}{3} (-2e^{-t} - 10e^{-3t})$$
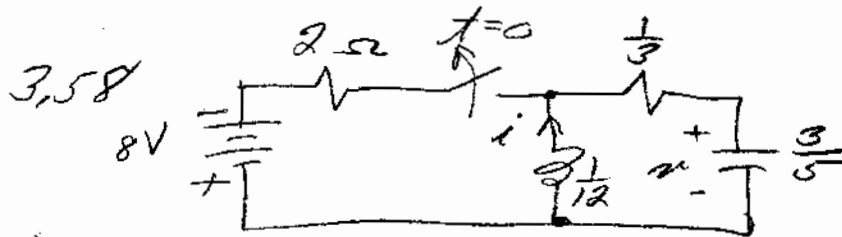
$$\boxed{v(t) = -\frac{1}{2} e^{-3t} + \frac{1}{2} e^{-t}}$$





$$i(0) = +4$$

$$v(0) = 0$$

for  $t > 0$   $\frac{1}{12} \frac{di}{dt} + \frac{1}{3} i + \frac{5}{3} \int_0^t i dt = 0$  (1)

or  $\frac{di}{dt} + 4i + 20 \int i dt = 0$  Let  $i = A e^{st}$

$$s^2 + 4s + 20 = 0, \quad s_{1,2} = \frac{-4 \pm \sqrt{16 - 80}}{2} = -2 \pm j4$$

$$\therefore i(t) = A_1 e^{-2t} \cos 4t + A_2 e^{-2t} \sin 4t$$

but  $i(0) = +4 \quad \therefore \boxed{+4 = A_1}$

from (1)  $\left. \frac{di}{dt} \right|_{t=0} = -4i(0) = -16$

$$\text{so } -16 = +4 \left[ -2 \times e^{-2t} \cos 4t - 4 \times e^{-2t} \sin 4t \right]_{t=0} + \left[ -2A_2 e^{-2t} \sin 4t + 4A_1 e^{-2t} \cos 4t \right]_{t=0}$$


$$-16 = -8 + 4A_2 \quad \text{or} \quad \boxed{A_2 = -2}$$

giving:  $\underline{i(t) = +4 e^{-2t} \cos 4t - 2 e^{-2t} \sin 4t}$  ←

$$v = -\frac{1}{3} i - \frac{1}{12} \frac{di}{dt} = -\frac{4}{3} e^{-2t} \cos 4t + \frac{2}{3} e^{-2t} \sin 4t$$



$$+ \frac{2}{3} e^{-2t} \cos 4t + \frac{4}{3} e^{-2t} \sin 4t - \frac{1}{3} e^{-2t} \sin 4t + \frac{2}{3} e^{-2t} \cos 4t$$
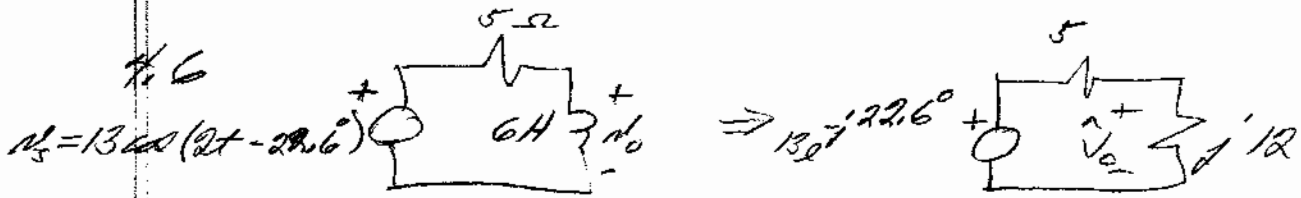
$$\boxed{v(t) = \frac{5}{3} e^{-2t} \sin 4t}$$
 ←



$$\hat{V}_o = \frac{j12}{5 + j12} \times 13 e^{j22.6^\circ} = \frac{12 \times 13 e^{j22.6^\circ} e^{j90^\circ}}{13 e^{j67.38^\circ}} = 12 e^{j0^\circ}$$

SO  $N_o(t) = 12 \cos(2t)$  ←

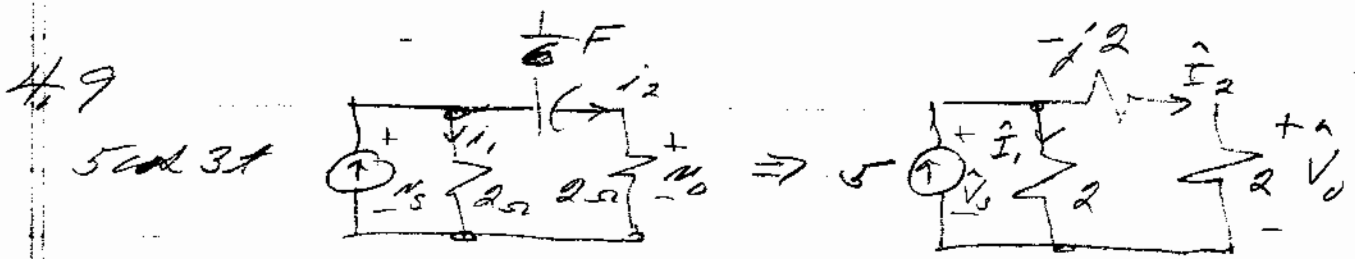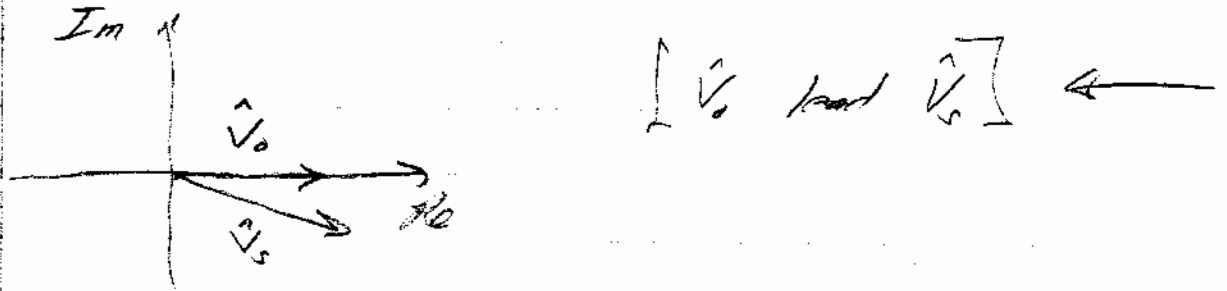


$$\hat{V}_s = \hat{I}_1 \times 2 = 2 \times 5 \frac{2 - j2}{4 - j2} = 10 \frac{2\sqrt{2} e^{j45^\circ}}{4.472 e^{j26.56^\circ}} = 6.33 e^{j18.4^\circ}$$

$$\hat{V}_o = \hat{I}_2 \times 2 = 2 \times 5 \frac{2}{4 - j2} = \frac{20}{4.472 e^{j26.56^\circ}} = 4.472 e^{j26.56^\circ}$$


SO  $N_s(t) = 6.33 \cos(3t - 18.4^\circ)$  ←

$N_o(t) = 4.472 \cos(3t + 26.56^\circ)$  ←

4.28

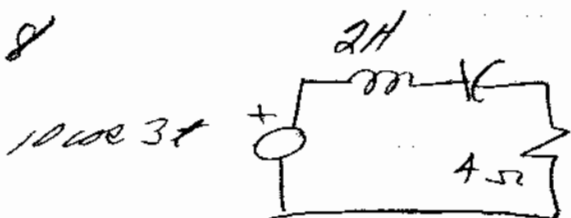


a)  $C = \frac{1}{6} F$

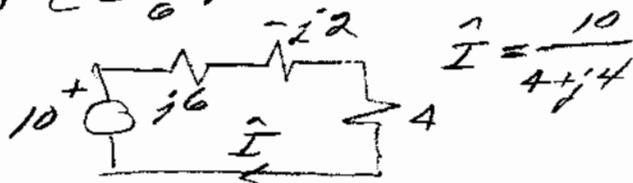

$$P_{avg_{4\Omega}} = \frac{1}{2} Re \left\{ \frac{40}{4+j4} \times \frac{10}{4-j4} \right\} = \frac{200}{32} = 6.25 \text{ Watts}$$


b)  $C = \frac{1}{18}$

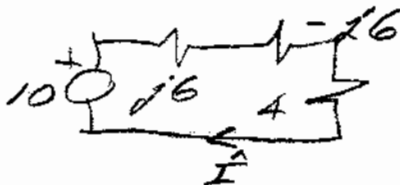

$$\hat{I} = \frac{10}{4} = \frac{5}{2}$$

$$P_{avg_{4\Omega}} = \frac{1}{2} \left(\frac{5}{2}\right)^2 \times 4 = \frac{25}{2} \text{ W}$$

c)  $C = \frac{1}{30} F$

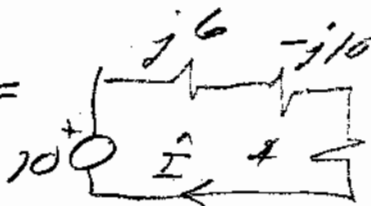


$$\hat{I} = \frac{10}{4-j4}$$

$$\therefore P_{avg_{4\Omega}} = 6.25 \text{ W}$$

4.44


60Hz, 220 rms

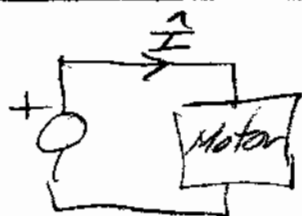

$$\left. \begin{aligned} |\hat{I}| &= 20_{rms} \\ pf &= 0.75 \text{ lagging} \end{aligned} \right\} \hat{I} = 20 e^{-j41.41^\circ}$$

$$P_{avg} = V_{rms} I_{rms} \times 0.75 = 3,300 \text{ Watts}$$

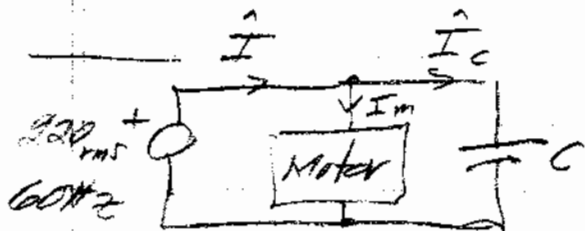from above  $\hat{I} = 20 e^{-j41.41^\circ} = 15 - j13.2288$



$\therefore$  for  $pf = 1$


$$\hat{I}_C = +j13.2288 = j220 \times 2\pi \times 60 C$$

$$\text{or } C = \frac{13.2288}{2\pi \times 60 \times 220} = 1.59 \times 10^{-4} F$$

ES 332

Homework 11

2.30

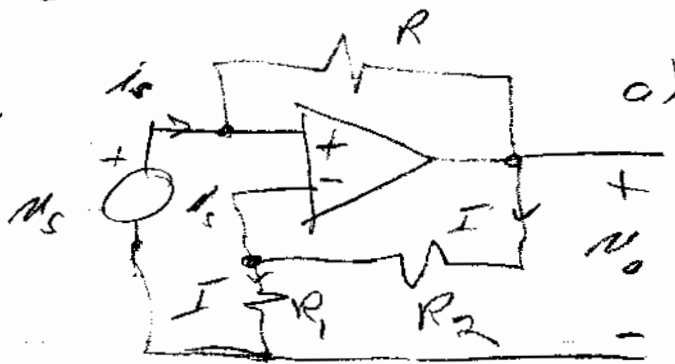

$$I = \frac{v_s}{R_1}$$

$$v_o = I(R_1 + R_2)$$


$$v_o = v_s \left( \frac{R_1 + R_2}{R_1} \right)$$

$$b) \quad i_s = \frac{v_s - v_o}{R} = \frac{v_s}{R} - \frac{v_s}{R} \left( 1 + \frac{R_2}{R_1} \right)$$

$$i_s = v_s \left( \frac{1}{R} - \frac{1}{R} - \frac{R_2}{RR_1} \right) = -\frac{R_2}{RR_1} v_s$$

$$\text{so } \boxed{\frac{v_s}{i_s} = -\frac{RR_1}{R_2}}$$

2.28

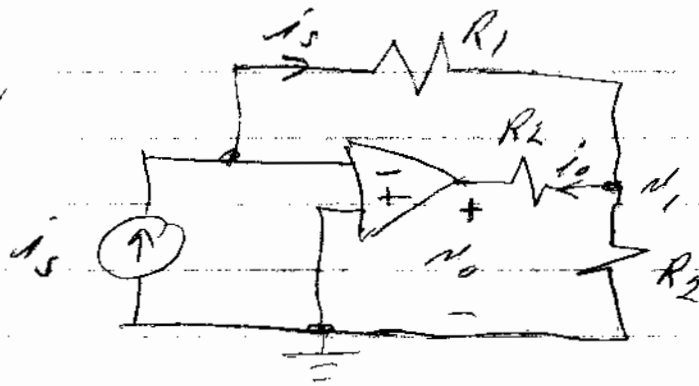

$$v_1 = -i_s R_1 \quad (1)$$

KCL @  $v_1$  gives  $-i_s + \frac{v_1 - v_o}{R_1} + \frac{v_1}{R_2} = 0 \quad (2)$

combining (1) + (2) gives  $-i_s + \frac{-i_s R_1 - v_o}{R_1} - i_s \frac{R_1}{R_2} = 0$


$$\text{or } i_s \left( -1 - \frac{R_1}{R_1} - \frac{R_1}{R_2} \right) = \frac{v_o}{R_1}$$

$$\text{so } v_o = -i_s \left( R_1 + R_1 + \frac{R_1 R_2}{R_1} \right) \leftarrow$$

$$i_o = \frac{v_1 - v_o}{R_1} = \frac{-i_s R_1 - (-i_s (R_1 + R_1 + \frac{R_1 R_2}{R_1}))}{R_1}$$

$$i_o = i_s \left( 1 + \frac{R_1}{R_2} \right) \leftarrow$$

2-35

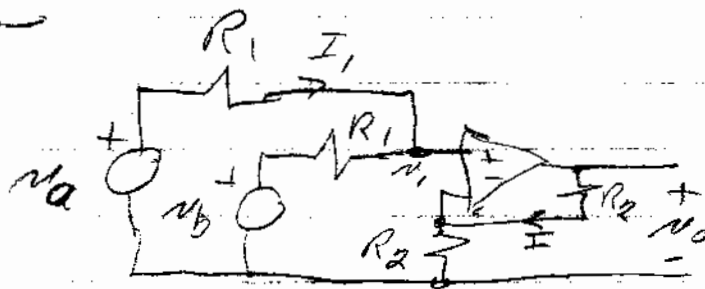

$$I = \frac{v_o}{2R_2}$$


$$v_1 = I R_2 = \frac{v_o}{2}$$

$$-v_a + I_1 R_1 + I_1 R_1 + v_b = 0 \quad \text{so } I_1 = \frac{v_a - v_b}{2R_1}$$

$$v_1 = I_1 R_1 + v_b = \frac{v_a - v_b}{2} + v_b = \frac{v_a + v_b}{2}$$


$$\text{but } v_o = 2v_1 = \boxed{v_a + v_b} \leftarrow$$

10.67

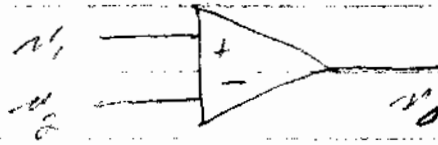


$v_1 = V_r > 0$

$v_2 = \text{input}$

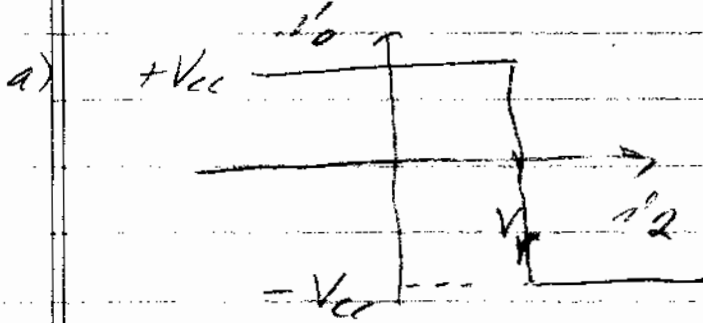

b)  $v_2 = V_r + V_r \sin \omega t$

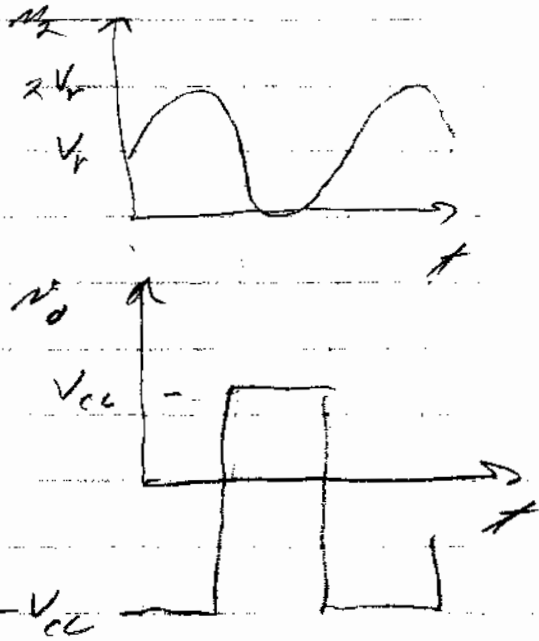

12.79 555 timer as astable multivibrator

$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

a)  $C = 0.1 \mu\text{F}$ ,  $R_1 = R_2 = 5 \text{ k}\Omega$

$$f = \frac{1.44}{(15) \times 10^3 \times 10^{-7}} = \boxed{960 \text{ Hz}} \leftarrow$$

b)  $R_1 = R_2 = 5 \text{ k}\Omega$ ,  $f = 1.6 \times 10^3$

$$C = \frac{1.44}{15 \times 10^3 \times 1.6 \times 10^3} = \boxed{0.06 \mu\text{F}} \leftarrow$$

c)  $R_2 = 10^4 \Omega$ ,  $C = 5 \times 10^{-9} \text{ F}$ ,  $f = 10^4$

$$(R_1 + 2R_2) = \frac{1.44}{fC}; \quad R_1 = \frac{1.44}{fC} - 2R_2$$

$$R_1 = \frac{1.44}{10^4 \times 5 \times 10^{-9}} - 2 \times 10^4 = 0.288 \times 10^5 - 2 \times 10^4$$

$$\therefore \boxed{R_1 = 0.88 \times 10^4 \Omega}$$


d)  $R_1 = 10 \text{ k}\Omega$ ,  $C = 5 \times 10^{-9} \text{ F}$ ,  $f = 10^4$

$$R_2 = \frac{1.44}{2fC} - \frac{R_1}{2} = \frac{1.44}{2 \times 10^4 \times 5 \times 10^{-9}} - \frac{10^4}{2} = (1.44 - 0.5) \times 10^4$$

$$\boxed{R_2 = 9.4 \times 10^3 \Omega} \leftarrow$$

11.26

| A | B | $A \odot B = \bar{A}\bar{B} + AB$ |
|---|---|-----------------------------------|
| 0 | 0 | 1                                 |
| 0 | 1 | 0                                 |
| 1 | 0 | 0                                 |
| 1 | 1 | 1                                 |

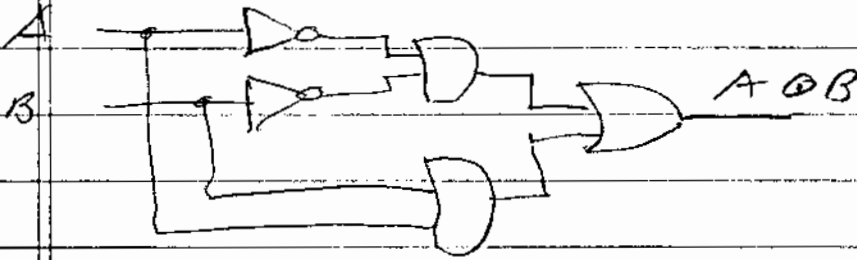


11.44


| A | B | C | F |       |
|---|---|---|---|-------|
| 0 | 0 | 0 | 0 | $m_0$ |
| 0 | 0 | 1 | 0 | $m_1$ |
| 0 | 1 | 0 | 0 | $m_2$ |
| 0 | 1 | 1 | 1 | $m_3$ |
| 1 | 0 | 0 | 0 | $m_4$ |
| 1 | 0 | 1 | 1 | $m_5$ |
| 1 | 1 | 0 | 1 | $m_6$ |
| 1 | 1 | 1 | 1 | $m_7$ |

$$F = m_3 + m_5 + m_6 + m_7 = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$
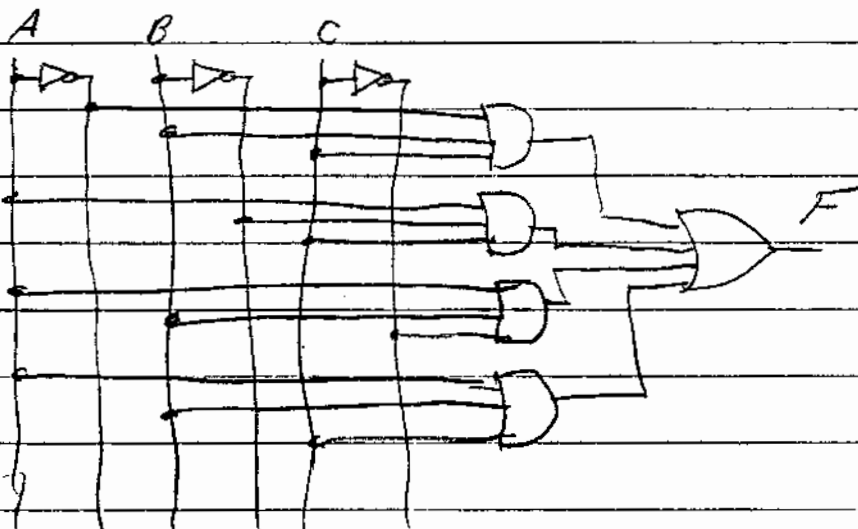
$$F = M_0 \cdot M_1 \cdot M_2 \cdot M_4 = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+B+C)$$





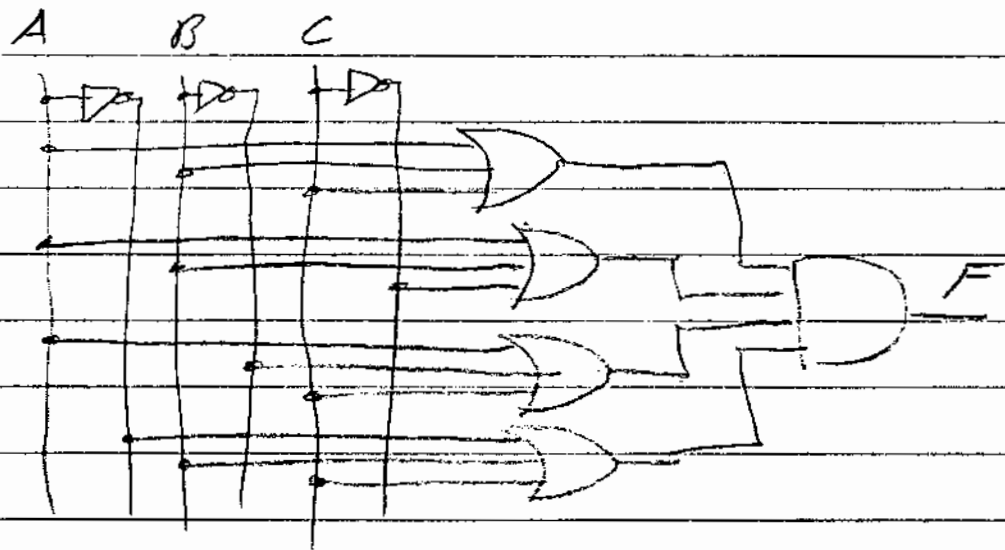

11.53 a)

|   |   |    |    |    |    |
|---|---|----|----|----|----|
|   |   | BC |    |    |    |
|   | A | 00 | 01 | 11 | 10 |
| 0 |   | 0  | 1  | 1  | 0  |
| 1 |   | 1  | 1  | 0  | 0  |

$F = A\bar{B} + \bar{B}C + \bar{A}B$

b)

|   |   |    |    |    |    |
|---|---|----|----|----|----|
|   |   | BC |    |    |    |
|   | A | 00 | 01 | 11 | 10 |
| 0 |   | 0  | 0  | 0  | 1  |
| 1 |   | 1  | 1  | 0  | 1  |

$F = B\bar{C} + AB + A\bar{C}$

c)

|   |   |    |    |    |    |
|---|---|----|----|----|----|
|   |   | BC |    |    |    |
|   | A | 00 | 01 | 11 | 10 |
| 0 |   | 1  | 1  | 1  | 1  |
| 1 |   |    | 1  |    | 1  |

$F = \bar{A} + \bar{B}C + B\bar{C}$

11.57 a)

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | CD |    |    |    |
|    | AB | 00 | 01 | 11 | 10 |
| 00 |    | 0  | 0  | 0  | 0  |
| 01 |    | 1  | 1  | 1  | 1  |
| 11 |    | 0  | 1  | 1  | 1  |
| 10 |    | 0  | 0  | 0  | 1  |

$F = \bar{A}B + BD + A\bar{C}D$

b)

|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | CD |    |    |    |
|    | AB | 00 | 01 | 11 | 10 |
| 00 |    | 0  | 1  | 1  | 1  |
| 01 |    | 0  | 0  | 0  | 1  |
| 11 |    | 0  | 1  | 0  | 1  |
| 10 |    | 0  | 1  | 1  | 1  |

$F = C\bar{D} + \bar{B}D + A\bar{C}D$


|    |    |    |    |    |    |
|----|----|----|----|----|----|
|    |    | CD |    |    |    |
|    | AB | 00 | 01 | 11 | 10 |
| 00 |    | 1  | 0  | 1  | 0  |
| 01 |    | 0  | 0  | 1  | 1  |
| 11 |    | 0  | 1  | 0  | 1  |
| 10 |    | 1  | 0  | 0  | 1  |

$F = \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + \bar{A}CD + B\bar{C}\bar{D} + A\bar{C}D$





or other combinations

| 13.14 | A | B | C | D | E | F | G | H | F <sub>1</sub> | F <sub>2</sub> | F <sub>3</sub> |
|-------|---|---|---|---|---|---|---|---|----------------|----------------|----------------|
|       | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0              | 0              | 0              |
|       | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0              | 0              | 1              |
|       | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0              | 1              | 0              |
|       | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0              | 1              | 1              |
|       | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1              | 0              | 0              |
|       | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1              | 0              | 1              |
|       | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1              | 1              | 0              |
|       | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1              | 1              | 1              |

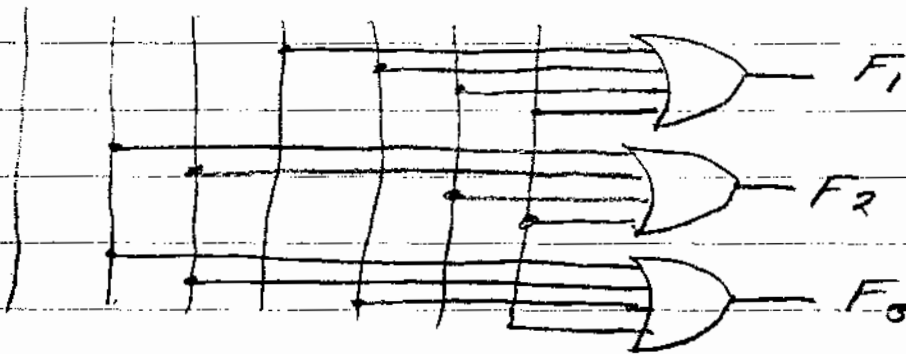$F_1 = E + F + G + H$  ;  $F_2 = C + D + G + H$  ;  $F_3 = B + D + F + H$   
 B C D E F G H



| 12-17 | A | B | C | D | E | F |
|-------|---|---|---|---|---|---|
|       | 0 | 0 | 0 | 0 | 0 | 0 |
|       | 0 | 0 | 1 | 0 | 0 | 1 |
|       | 0 | 1 | 0 | 0 | 1 | 1 |
|       | 0 | 1 | 1 | 0 | 1 | 0 |
|       | 1 | 0 | 0 | 1 | 1 | 0 |
|       | 1 | 0 | 1 | 1 | 1 | 1 |
|       | 1 | 1 | 0 | 1 | 0 | 1 |
|       | 1 | 1 | 1 | 1 | 0 | 0 |

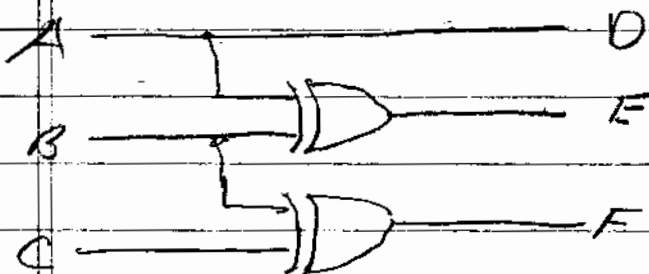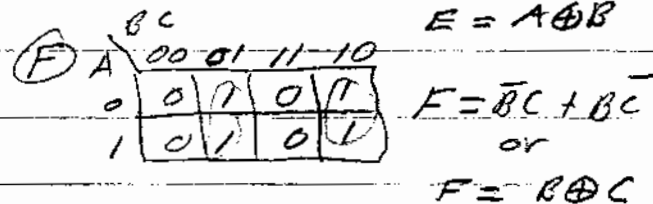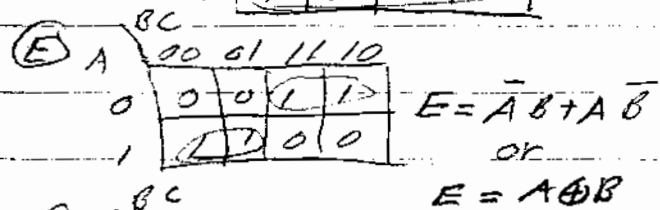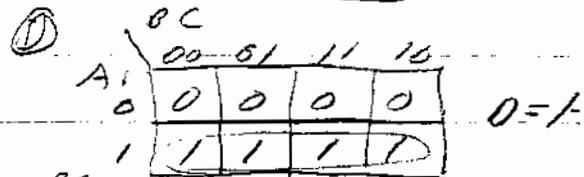

1A-42

| Input<br>X | Present state  |                | Next state                  |                             | Output<br>Y | D <sub>1</sub> | D <sub>2</sub> |
|------------|----------------|----------------|-----------------------------|-----------------------------|-------------|----------------|----------------|
|            | Q <sub>1</sub> | Q <sub>2</sub> | Q <sub>1</sub> <sup>+</sup> | Q <sub>2</sub> <sup>+</sup> |             |                |                |
| 0          | 0              | 0              | 1                           | 1                           | 1           | 1              | 1              |
| 0          | 0              | 1              | 0                           | 0                           | 0           | 0              | 0              |
| 0          | 1              | 0              | 0                           | 1                           | 1           | 0              | 1              |
| 0          | 1              | 1              | 1                           | 0                           | 0           | 1              | 0              |
| 1          | 0              | 0              | 0                           | 1                           | 1           | 0              | 1              |
| 1          | 0              | 1              | 1                           | 0                           | 0           | 1              | 0              |
| 1          | 1              | 0              | 1                           | 1                           | 1           | 1              | 0              |
| 1          | 1              | 1              | 0                           | 0                           | 0           | 0              | 0              |

| X | Q <sub>1</sub> , Q <sub>2</sub> |    |    |    | X | Q <sub>1</sub> , Q <sub>2</sub> |    |    |    | X | Q <sub>1</sub> , Q <sub>2</sub> |    |    |    |   |
|---|---------------------------------|----|----|----|---|---------------------------------|----|----|----|---|---------------------------------|----|----|----|---|
|   | 00                              | 01 | 11 | 10 |   | 00                              | 01 | 11 | 10 |   | 00                              | 01 | 11 | 10 |   |
| 0 | 1                               | 0  | 1  | 0  | 0 | 1                               | 0  | 0  | 1  | 0 | 1                               | 0  | 0  | 0  | 1 |
| 1 | 0                               | 1  | 0  | 1  | 1 | 1                               | 0  | 0  | 1  | 1 | 1                               | 0  | 0  | 1  | 1 |

$$D_1 = \bar{X}\bar{Q}_1\bar{Q}_2 + \bar{X}Q_1Q_2 + X\bar{Q}_1Q_2 + XQ_1\bar{Q}_2 = \bar{X} \cdot (Q_1 \oplus Q_2) + X \cdot (Q_1 \oplus Q_2)$$

or  $D_1 = X \oplus (Q_1 \oplus Q_2)$

$$D_2 = \bar{Q}_2 = Y$$

