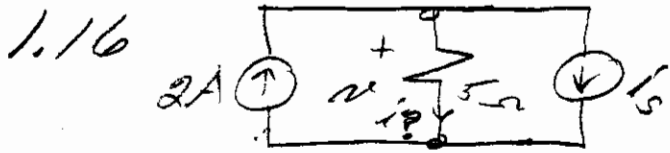


a) $i_1 = 4$; $v_1 = 20V$

b) $i_2 = -2$; $v_2 = 8V$

c) $i_3 = 2$; $v_3 = -6V$

d) $i_4 = -2$; $v_4 = -2V$



KCL


$i_? = 2 - i_s$

a) $i_s = 1, i_? = 1 \therefore v = 5V$

b) $i_s = 2, i_? = 0 \therefore v = 0V$

c) $i_s = 3, i_? = -1 \therefore v = 5V$

1.18

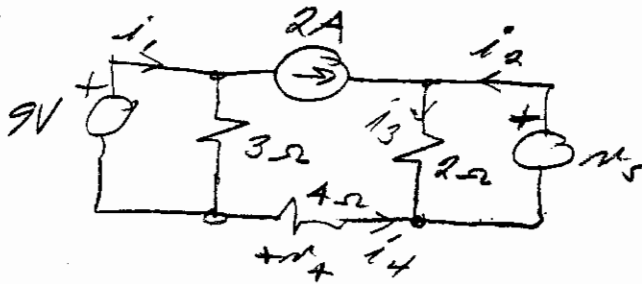


$2 = i_3 - i_2$


a) $v_4 = 2V$; $i_3 = \frac{v_4}{2} = 1A$; $i_4 = i_2 - i_3 = -2$; $\therefore v_4 = i_4 = -8V$

b) $v_4 = 4V$ but i_4 still is $i_2 - i_3 = -2$ $\therefore v_4 = -8V$ ←


c) $v_4 = 6V$ " $\therefore v_4 = -8V$ ←

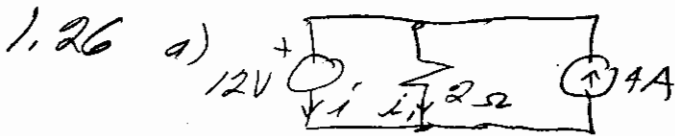

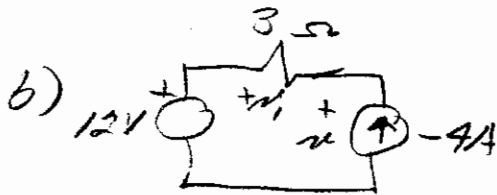$i_1 = \frac{12}{2} = 6A$
 $i = 4 - i_1 = -2A$ } ←




$v_1 = -(-4)3 = 12V$
 KVL $n = 0$ } ←

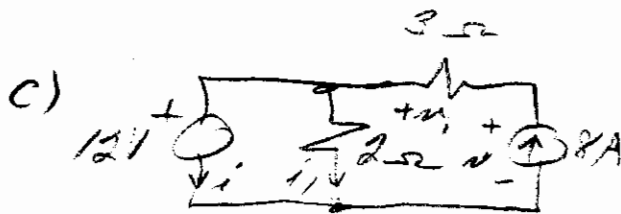

$i_1 = \frac{12}{2} = 6A$
 $i = -i_1 + 8 = 2A$ ←
 $v_1 = -3 \times 8 = -24V$ ←

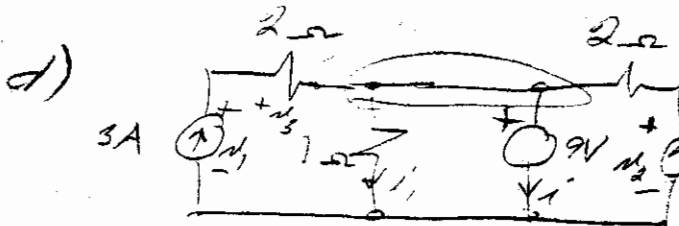$-12 + v_1 + n = 0$ or $n = 12 - v_1 = 36V$ ←




$-v_1 + v_3 + 9 = 0 \therefore v_1 = 15V$ ←
 KCL $i = 3 + 2 - i_1 = -4A$ ←

$i_1 = 9A$; $-9 - 2 \times 2 + v_2 = 0 \Rightarrow v_2 = +9 + 4 = +13V$ ←
 $v_3 = 6V$

ES 332


Homework 3

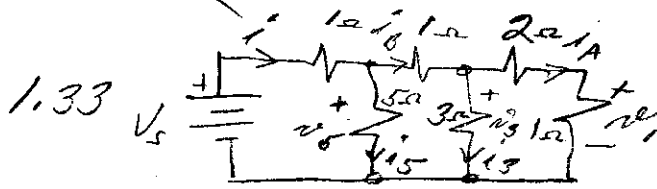

a) $v_1 = 2V \therefore i_A = \frac{v_1}{1} = 2A$
 $v_3 = 3i_A = 6V ; i_3 = \frac{v_3}{3} = 2A$
 so $i_B = i_3 + i_A = 4A ; v_5 = i_B \times 1 + v_3 = 10V$

$i_5 = \frac{v_5}{5} = 2A$ so $i = i_5 + i_B = 6A$ and $V_s = i \times 1 + v_5 = 16V$ ←

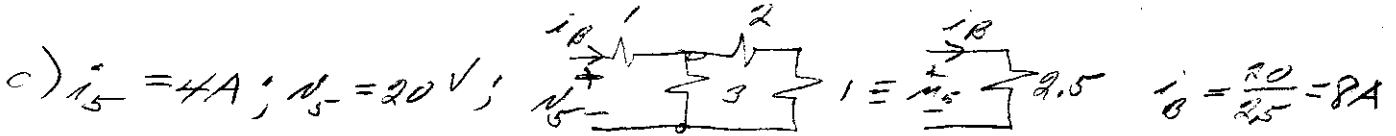
b) $i_3 = 3A ; v_3 = 9V ; i_A = 3A ; i_B = 6A ; v_5 = 6 + 9 = 15V ; i_5 = 3A$
 $i = i_B + i_5 = 9A$ so $V_s = 9 \times 1 + v_5 = 24V$ ←



c) $i_5 = 4A ; v_5 = 20V ; i_B = \frac{20}{2.5} = 8A$

$i = i_5 + i_B = 4 + 8 = 12A ; V_s = i \times 1 + v_5 = 32V$ ←

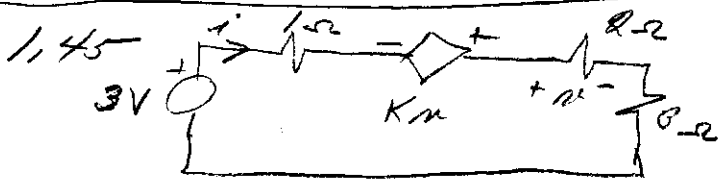
d) $\frac{V_s}{i} = \frac{24}{9} = \frac{8}{3} \Omega$ (same for all = Req seen by source)



a) $K = 2 ; v = 2i$
 KVL: $-3 + i - 2v + 2i + 3i = 0$

$\therefore i - 2(2i) + 2i + 3i = 3 \Rightarrow 2i = 3 ; i = \frac{3}{2}$ ←

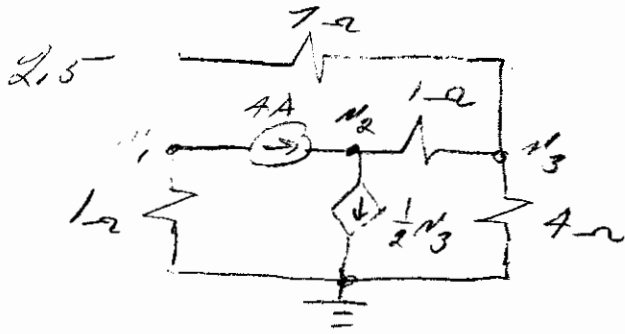b) $K = 4 ; -3 + i - 4(2i) + 2i + 3i = 0 \Rightarrow -2i = +3 ; i = -\frac{3}{2}$ ←



$$\frac{N_1}{1} + \frac{N_1 - N_3}{7} + 4 = 0$$

$$-4 + \frac{1}{2}N_3 + \frac{N_2 - N_3}{1} = 0$$

$$\frac{N_3 - N_1}{7} + \frac{N_3 - N_2}{1} + \frac{N_3}{4} = 0$$

$$\left. \begin{aligned} \frac{8}{7}N_1 - \frac{1}{7}N_3 &= -4 \\ N_2 - \frac{1}{2}N_3 &= 4 \\ -\frac{1}{7}N_1 - N_2 + N_3\left(\frac{1}{7} + 1 + \frac{1}{4}\right) &= 0 \end{aligned} \right\} \begin{aligned} 8N_1 - N_3 &= -28 \\ 2N_2 - N_3 &= 8 \\ -4N_1 - 28N_2 + 39N_3 &= 0 \end{aligned} \right\} \begin{aligned} N_1 &= \frac{N_3 - 28}{8} \\ N_2 &= \frac{N_3 + 8}{2} \end{aligned}$$

$$50 - 4\left(\frac{N_3 - 28}{8}\right) - 28\left(\frac{N_3 + 8}{2}\right) + 39N_3 = 0$$

$$N_3\left(-\frac{1}{2} - 14 + 39\right) = -14 + 4 \times 28$$

$$N_3 = \frac{98 + 14}{49} = 4V$$

$$N_1 = \frac{4 - 28}{8} = -3V$$


$$N_2 = \frac{4 + 8}{2} = 6V$$

probably a better way to solve

Σ

ES332

3a Homework 4

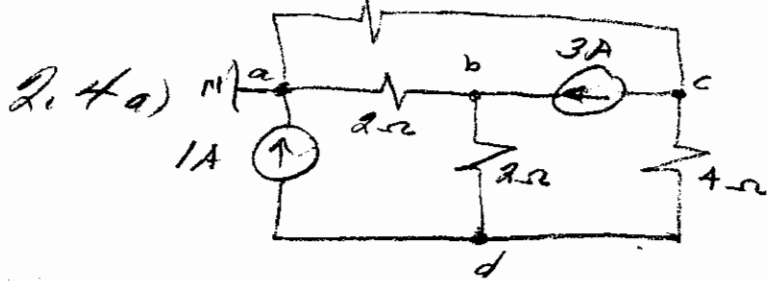

node b $\frac{V_b}{2} + \frac{V_b - V_d}{2} = 3$

node c $\frac{V_c}{3} + \frac{V_c - V_d}{4} = -3$

node d $\frac{V_d - V_b}{2} + \frac{V_d - V_c}{4} = -1$

$$V_b - \frac{1}{2}V_d = 3$$

$$\frac{3}{4}V_c - \frac{1}{4}V_d = -3$$

$$\frac{3}{4}V_d - \frac{1}{4}V_c - \frac{1}{2}V_b = -1$$

$$2V_b - V_d = 6 \quad (1)$$

$$7V_c - 3V_d = -36 \quad (2)$$

$$3V_d - V_c - 2V_b = -4 \quad (3)$$

from (1) $V_b = \frac{6 + V_d}{2} = 3 + \frac{1}{2}V_d$

from (2) $V_c = \frac{3V_d - 36}{7}$

$$\begin{cases} 2V_b - V_d = 6 \\ 7V_c - 3V_d = -36 \\ -2V_b - V_c + 3V_d = -4 \end{cases}$$

$\therefore V_b = \frac{V_d + 6}{2} ; V_c = \frac{3V_d - 36}{7}$

so $-V_d - 6 - \frac{3}{7}V_d + \frac{36}{7} + 3V_d = -4 \Rightarrow V_d(-1 - \frac{3}{7} + 3) = (-4 - \frac{36}{7} + 6)$

$$V_d = \frac{-22}{11} = -2V$$

$$V_b = 2V$$


$$V_c = -\frac{42}{7} = -6V$$

$$V_b = \frac{\begin{vmatrix} 6 & 0 & -1 \\ -36 & 7 & -3 \\ -4 & -1 & +3 \end{vmatrix}}{\begin{vmatrix} 2 & 0 & -1 \\ 0 & 7 & -3 \\ -2 & -1 & +3 \end{vmatrix}} = \frac{6(21-3) - 1(36+28)}{2(21-3) - 1(14)} = \frac{108-64}{36-14} = \frac{44}{22} = 2V$$

$$V_c = \frac{\begin{vmatrix} 2 & 6 & -1 \\ 0 & -36 & -3 \\ -2 & -4 & +3 \end{vmatrix}}{22} = \frac{2(-108-12) - 2(-18-36)}{22} = \frac{-240+108}{22} = -6V$$

$$V_d = \frac{\begin{vmatrix} 2 & 0 & 6 \\ 0 & 7 & -36 \\ -2 & -1 & -4 \end{vmatrix}}{22} = \frac{2(-28-36) + 6(4)}{22} = \frac{-108+24}{22} = -2V$$

2.8

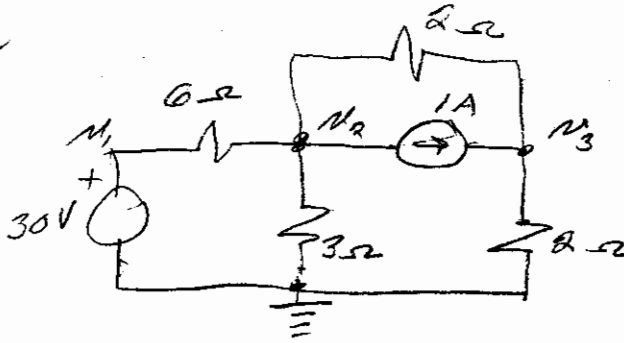

$N_1 = 30$

$$\frac{N_2 - 30}{6} + \frac{N_2}{3} + \frac{N_2 - N_3}{2} + 1 = 0$$

$$\frac{N_3 - N_2}{2} - 1 + \frac{N_3}{2} = 0$$

$$\text{or } N_2 \left(\frac{1}{6} + \frac{1}{3} + \frac{1}{2} \right) - \frac{1}{2} N_3 = 4$$

$$-\frac{1}{2} N_2 + N_3 \left(\frac{1}{2} + \frac{1}{2} \right) = 1$$

$$N_2 - \frac{1}{2} N_3 = 4$$


$$-\frac{1}{2} N_2 + N_3 = 1$$

$$\left. \begin{matrix} 2N_2 - N_3 = 8 \\ -N_2 + 2N_3 = 2 \end{matrix} \right\}$$

$$N_2 = \frac{\begin{vmatrix} 2 & -1 \\ 2 & 2 \end{vmatrix}}{\begin{vmatrix} 2 & -1 \\ -1 & 2 \end{vmatrix}} = \frac{16 + 2}{4 - 1} = \frac{18}{3} = \boxed{+6V}$$

$$N_3 = \frac{\begin{vmatrix} 2 & 4 \\ -1 & 2 \end{vmatrix}}{3} = \frac{4 + 4}{3} = \boxed{4V}$$

2.9

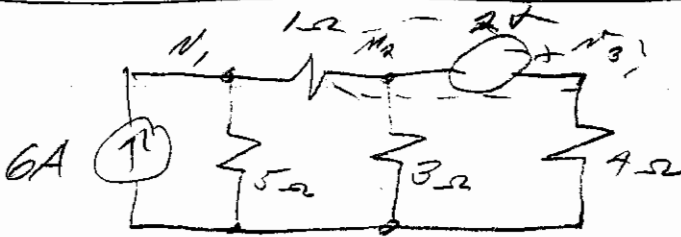

$$N_3 - N_2 = 2$$

$$-6 + \frac{N_1}{5} + \frac{N_1 - N_2}{1} = 0$$

$$\frac{N_2 - N_1}{1} + \frac{N_2}{3} + \frac{N_3}{4} = 0$$

$$\left. \begin{matrix} -N_2 + N_3 = 2 \\ \frac{6}{5} N_1 - N_2 = 6 \\ -N_1 + \frac{1}{3} N_2 + \frac{1}{4} N_3 = 0 \end{matrix} \right\} \begin{matrix} -N_2 + N_3 = 2 \\ 6N_1 - 5N_2 = 30 \\ -12N_1 + 16N_2 + 3N_3 = 0 \end{matrix}$$



$$N_1 = \frac{\begin{vmatrix} 2 & -1 & 1 \\ 30 & -5 & 0 \\ 0 & 16 & 3 \end{vmatrix}}{\begin{vmatrix} 0 & -1 & 1 \\ 6 & -5 & 0 \\ -12 & 16 & 3 \end{vmatrix}} = \frac{2(-15) - 30(-3-16)}{1(18) + 1(96-60)} = \frac{-30 + 570}{18 + 36} = \frac{540}{54} = \boxed{10V}$$

$$N_2 = \frac{\begin{vmatrix} 0 & 2 & 1 \\ 6 & 30 & 0 \\ -12 & 0 & 3 \end{vmatrix}}{54} = \frac{-2(18) + (12 \times 30)}{54} = \frac{-36 + 360}{54} = \boxed{6V}$$

$$N_3 = \frac{\begin{vmatrix} 0 & -1 & 2 \\ 6 & -5 & 30 \\ -12 & 16 & 0 \end{vmatrix}}{54} = \frac{1(30 \times 12) + 2(96 - 60)}{54} = \frac{360 + 72}{54} = \boxed{8V}$$

2.11

a)

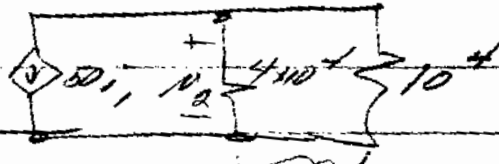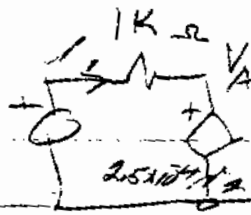

$$\frac{4}{5} \times 10^{-3} = 8 \times 10^{-3} = R_{eq}$$

$$V_A = 2.5 \times 10^{-4} N_2$$

$$i_1 = \frac{N_1 - V_A}{10^3} = \frac{N_1 - 2.5 \times 10^{-4} N_2}{10^3}$$

$$50i_1 + \frac{N_2}{8 \times 10^3} = 0 = 50 \left(10^{-3} N_1 - 2.5 \times 10^{-7} N_2 \right) + 0.125 \times 10^{-3} N_2$$

$$\therefore 50 \times 10^3 N_1 = 50 \times 2.5 \times 10^7 N_2 - 0.125 \times 10^{-3} N_2$$


$$N_1 = \left(2.5 \times 10^{-4} - 2.5 \times 10^{-3} \right) N_2 = -2.25 \times 10^{-3} N_2$$

$$\frac{N_2}{N_1} = -\frac{1}{2.25 \times 10^{-3}} = \boxed{-444.44} \leftarrow$$

$$b) i_1 = \frac{N_1 - V_A}{10^3} = \frac{N_1 - 2.5 \times 10^{-4} N_2}{10^3} = \frac{N_1 - 2.5 \times 10^{-4} (-444.44) N_1}{10^3}$$

$$\text{so } \frac{N_1}{N_2} = \frac{10^3}{1 + 0.1111} = \boxed{900 \Omega} \leftarrow$$

2.19

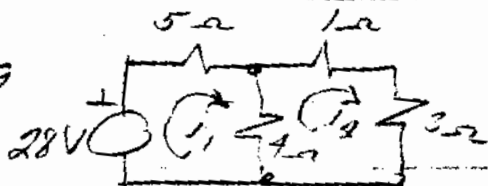

$$28 = 5i_1 + 4(i_1 - i_2)$$


$$0 = 4(i_2 - i_1) + 4i_2$$

$$\text{or } \begin{cases} 9i_1 - 4i_2 = 28 \\ -4i_1 + 8i_2 = 0 \end{cases}$$

$$i_1 = \frac{\begin{vmatrix} 28 & -4 \\ 0 & 8 \end{vmatrix}}{\begin{vmatrix} 9 & -4 \\ -4 & 8 \end{vmatrix}} = \frac{224}{72 - 16} = \frac{224}{56} = \boxed{4A} \leftarrow$$

$$\begin{vmatrix} 9 & 28 \\ -4 & 0 \end{vmatrix}$$
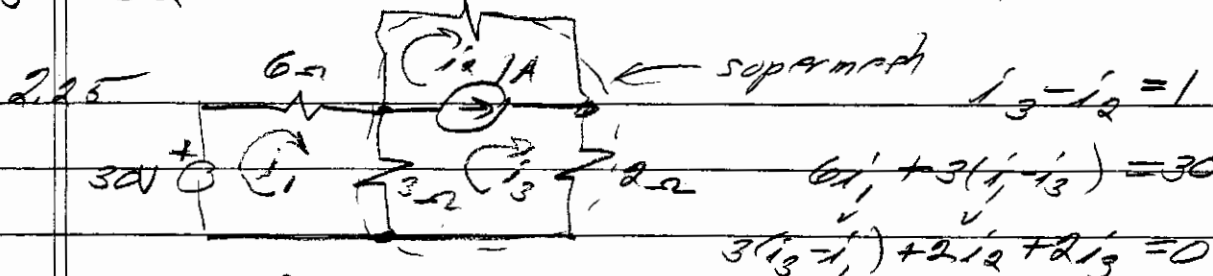
$$\frac{4 \times 28}{56} = \boxed{2A} \leftarrow$$



supermesh $i_3 - i_2 = 1$
 $6i_1 + 3(i_1 - i_3) = 30$
 $3(i_3 - i_1) + 2i_2 + 2i_3 = 0$



$$\begin{cases} -i_2 + i_3 = 1 \\ 9i_1 - 3i_3 = 30 \\ \text{or } -3i_1 + 2i_2 + 5i_3 = 0 \end{cases}$$

$$I_1 = \begin{vmatrix} 1 & -1 & 1 \\ 30 & 0 & -3 \\ 0 & 2 & 5 \end{vmatrix} = \frac{1 \times 6 - 30(-5-2)}{1(45-9) + 1 \times 18} = \frac{6 + 210}{36 + 18} = \frac{216}{54} = \boxed{4A}$$

$$I_2 = \begin{vmatrix} 0 & 1 & 1 \\ 9 & 30 & -3 \\ -3 & 0 & 5 \end{vmatrix} = \frac{-1(45-9) + 1 \times 90}{54} = \frac{34}{54} = \boxed{1A}$$


$$I_3 = I_2 + I_1 = \boxed{2A}$$

2.39

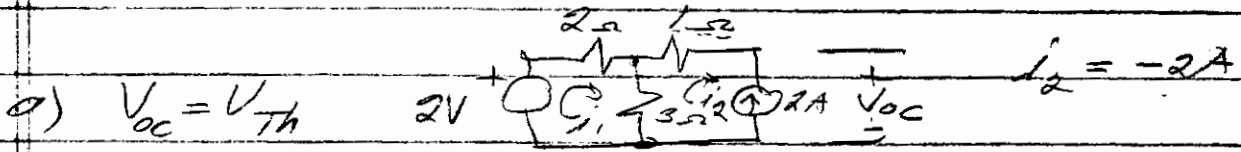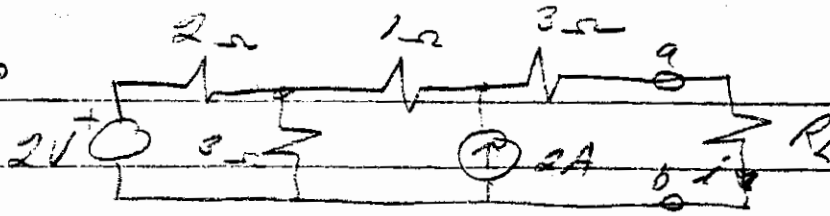

$$2 = 2i_1 + 3(i_1 - i_2) = 5i_1 - 3(-2) \text{ or } 5i_1 = -4; \quad i_1 = -\frac{4}{5}$$
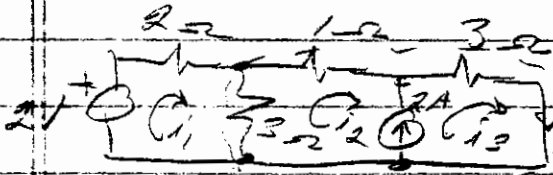
$$V_{oc} = V_{Th} = -i_2 \times 1 + (i_1 - i_2) \times 3 = 2 + \frac{6}{5} \times 3 = \frac{28}{5} \text{ V}$$



$$2 = 2i_1 + 3(i_1 - i_2) = 5i_1 - 3i_2$$

$$3(i_2 - i_1) + i_2 + 3i_3 = 0 = -3i_1 + 4i_2 + 3i_3$$


$$2 = -i_2 + i_3$$

$$I_{sc} = i_3 = \begin{vmatrix} 5 & -3 & 2 \\ -3 & 4 & 0 \\ 0 & -1 & 2 \end{vmatrix}$$

$$= \frac{2 \times 3 + 2(20 - 9)}{5(4 + 3) + 3(-3)} = \frac{28}{26} = \frac{14}{13}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{\frac{28}{5}}{\frac{14}{13}} = \frac{28 \times 13}{5 \times 14} = 5.2 \Omega$$

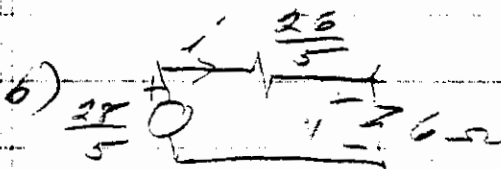check $R_{eq} = 3 + 1 + \frac{6}{5} = \frac{26}{5} \Omega$




$$i = \frac{\frac{28}{5}}{\frac{56}{5}} = \frac{28}{56} = \frac{1}{2} \text{ A}$$

$$P_{6\Omega} = i^2 \times 6 = \frac{1}{4} \times 6 = \frac{3}{2} \text{ Watt}$$

c) Max power for $R_L = \frac{26}{5} \Omega; i = \frac{28}{52} = \frac{28}{52} = 0.538$

$$P_{R_{MAX}} = 1.5077 \text{ Watts}$$

2.43

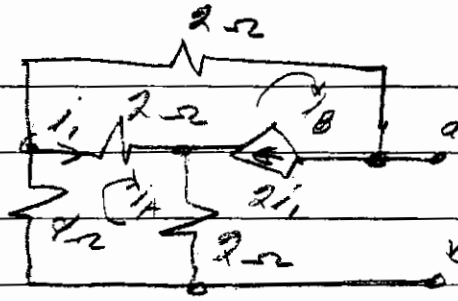


$$10i_A + 2(i_A - i_B) = 0$$

$$i_B = 2i_A = 2(i_A - i_B) = 2i_A - 2i_B$$

$$\rightarrow 3i_B = 2i_A \text{ or } i_B = \frac{2}{3}i_A$$
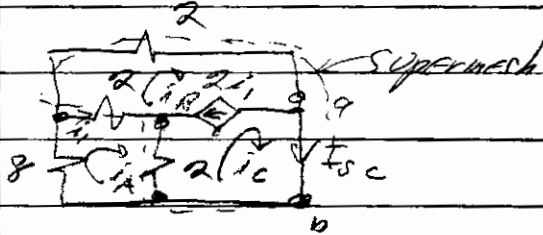
$$\therefore 10i_A + 2i_A - \frac{4}{3}i_A = 0 \quad \text{so } i_A = i_B = 0 \quad + \quad \boxed{V_{oc} = V_{TH} = 0}$$



$$8i_A + 2(i_A - i_B) + 2(i_A - i_C) = 0$$

$$2(i_C - i_A) + 2(i_B - i_A) + 2i_B = 0$$

$$i_B - i_C = 2i_A = 2(i_A - i_B)$$

$$\text{or } \begin{cases} 12i_A - 2i_B - 2i_C = 0 \\ -4i_A + 4i_B + 2i_C = 0 \\ 2i_A - 3i_B + i_C = 0 \end{cases}$$

$$i_A = i_B = i_C = 0 \text{ is a solution } \boxed{i_C = I_{sc}}$$

$$\boxed{R_{TH} = \frac{0}{0}} \text{ so we are not sure}$$

could put 1 amp source where I have labeled I_{sc} above and find resulting V_{ab} then $\frac{V_{ab}}{1} = R_{eq} = R_{th}$

$$\boxed{i_C = 1}$$

$$\therefore \begin{cases} 12i_A - 2i_B = 2 & \text{voltage across current source (not shown above)} \\ -4i_A + 4i_B + V_{ab} = -2 \\ 2i_A - 3i_B = -1 \end{cases}$$

$$V_{ab} = \begin{vmatrix} 12 & -2 & 2 \\ -4 & 4 & -2 \\ 2 & -3 & -1 \end{vmatrix} \begin{matrix} -120 & +16 & 8 \\ 12(-4-6) + 2(4+4) + 2(12-8) \\ -1(-36+4) \end{matrix} = \frac{-96}{32} = -3$$

$$\text{so } \boxed{R_{TH} = -3 \Omega}$$




voltage source only

$$2 = 5i_1 - 3i_2$$

$$0 = -3i_1 + 13i_2$$
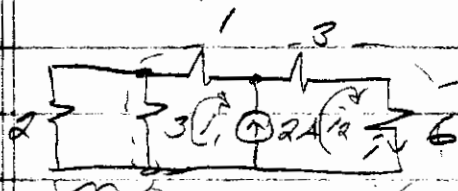
$$i_2 = i_{\text{voltage source}} = \frac{\begin{vmatrix} 2 & -3 \\ -3 & 13 \end{vmatrix}}{\begin{vmatrix} 5 & -3 \\ -3 & 13 \end{vmatrix}} = \frac{6}{65-9} = \frac{6}{56} = \frac{3}{28} \text{ A}$$



supermesh $\frac{6}{5}i_1 + i_1 + 3i_2 + 6i_2 = 0$

$$i_2 - i_1 = 2$$

$$R_{eq} = \frac{6}{5}$$

$$\begin{cases} \frac{11}{5}i_1 + 9i_2 = 0 \\ -i_1 + i_2 = 2 \end{cases} \quad \begin{cases} 11i_1 + 45i_2 = 0 \\ -i_1 + i_2 = 2 \end{cases}$$

$$i_2 = \frac{\begin{vmatrix} 11 & 0 \\ -1 & 2 \end{vmatrix}}{\begin{vmatrix} 11 & 45 \\ -1 & 1 \end{vmatrix}} = \frac{22}{11+45} = \frac{22}{56} = i_{\text{current source}}$$

$$i = i_{\text{voltage}} + i_{\text{current}} = \frac{6}{56} + \frac{22}{56} = \frac{28}{56} = \frac{1}{2} \text{ A}$$

$$P_{6\Omega} = i^2 \times 6 = \frac{6}{4} = \frac{3}{2} \text{ Watt}$$

Could solve for Thevenin equivalent using superposition and then use result to solve problem with 6Ω load.

from source $V_{oc \text{ voltage}} = 2 \frac{3}{5} = \frac{6}{5} \text{ V}$; $V_{oc \text{ current}} = 2(1 + \frac{6}{5}) = \frac{22}{5} \text{ V}$

$$V_{TH} = V_{oc} = V_{oc \text{ voltage}} + V_{oc \text{ current}} = \frac{28}{5} \text{ V}$$

for $I_{sc \text{ voltage}}$ set 6Ω across = 0 then

$$2 = 5i_1 - 3I_{sc} ; 0 = -3i_1 + 7I_{sc}$$

$$I_{sc} = \frac{\begin{vmatrix} 2 & -3 \\ -3 & 7 \end{vmatrix}}{\begin{vmatrix} 5 & -3 \\ -3 & 7 \end{vmatrix}} = \frac{6}{35-9} = \frac{6}{26} = \frac{3}{13}$$

$$I_{sc \text{ current}} = 2 \frac{1 + \frac{6}{5}}{4 + \frac{6}{5}} = 2 \frac{11}{26} = \frac{22}{26}$$









$$I_{sc \text{ total}} = \frac{6}{26} + \frac{22}{26} = \frac{28}{26} = \frac{14}{13}$$

$$R_{TH} = \frac{V_{TH}}{I_{sc}} = \frac{28}{\frac{14}{13}} = \frac{26}{5}$$

ES 332

Homework 8
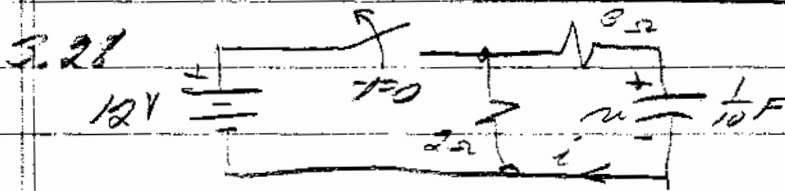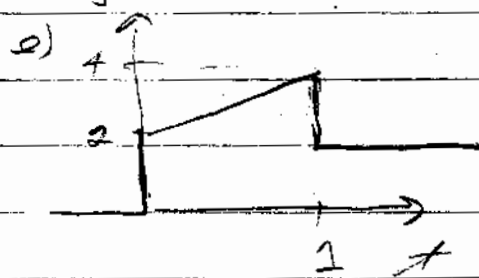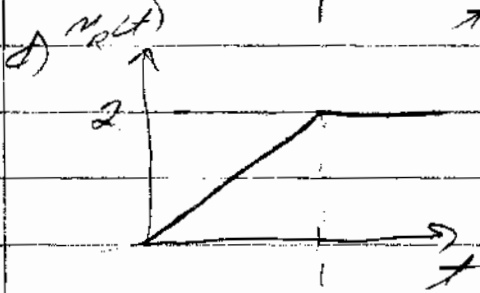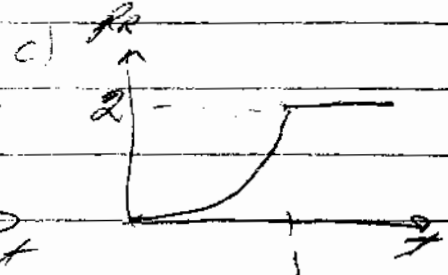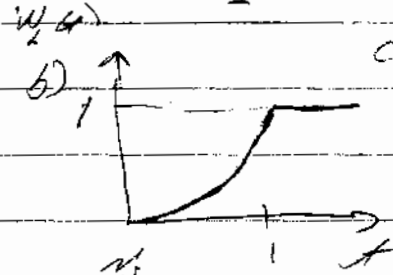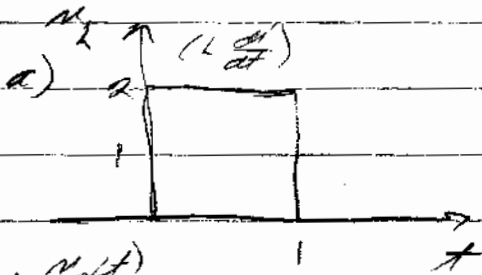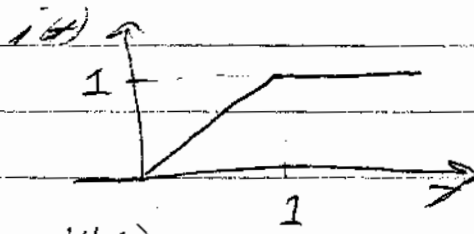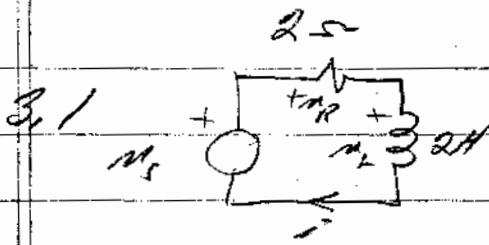
$$\begin{aligned}
 w &= w_R + w_L \\
 w_L &= L \frac{di}{dt} \\
 w_L &= \frac{1}{2} L i^2 \\
 P_R &= i^2 R \\
 w_R &= iR
 \end{aligned}$$



$$w_C(t) = 12$$



for $t > 0$ $5i' + 10 \int_0^t i dt + 12 = 0$

or $5 \frac{di}{dt} + 10i = 0$; $i = A e^{st}$ $s = -2$ ($\tau = \frac{1}{2}$)

from initial equation $5i(0) = -12$ or $i(0) = -\frac{12}{5}$


$$i(t) = -\frac{12}{5} e^{-2t}$$

$$w(t) = -5i = 12 e^{-2t}$$

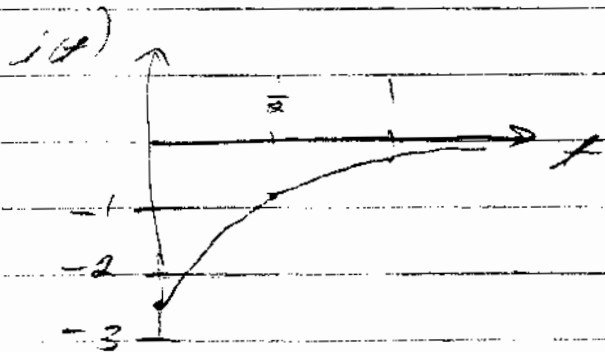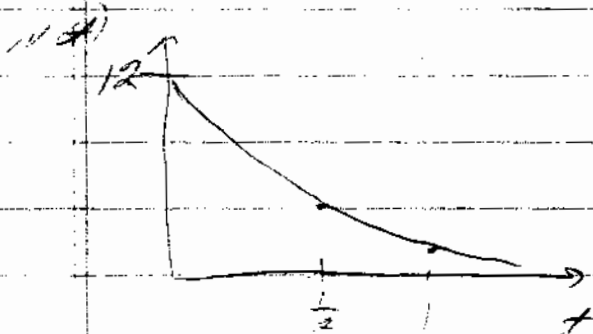

ES332

Homework 9

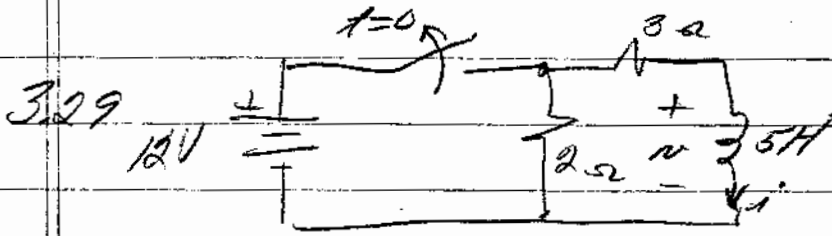

$i(0) = 4A$



$5i + 5 \frac{di}{dt} = 0$; $i = A e^{st}$ $s = -1$

but $i(0) = 4$ so


$i(t) = 4e^{-t}$

and $v(t) = 5 \frac{di}{dt} = -20e^{-t}$

v(t)

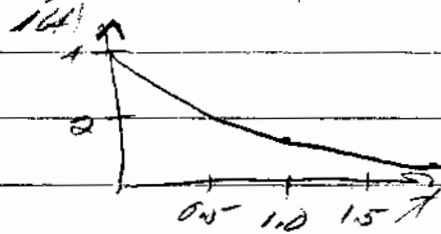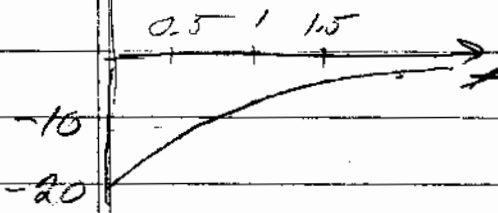

330

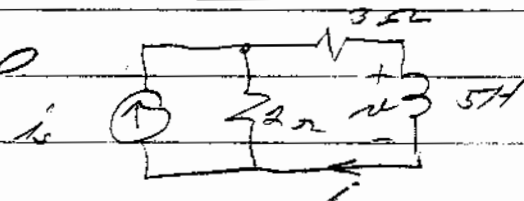

$i_s = 10$ for $t < 0$

$i_s = 0$ for $t > 0$

this gives $i(0) = 10 \frac{2}{5} = 4A$

for $t > 0$ $5i + 5 \frac{di}{dt} = 0$

$i = A e^{-t}$ but $i(0) = 4$


so $i = 4e^{-t}$

and $v(t) = 5 \frac{di}{dt} = -20e^{-t}$

[see curves above]

ES332

Homework 10

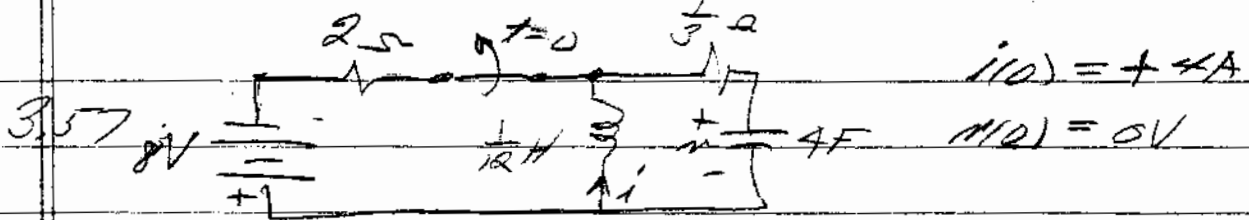

(1) $\frac{1}{3}i + \frac{1}{4} \int_0^t i dt + \frac{1}{12} \frac{di}{dt} = 0 \Rightarrow \frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 3i = 0$

$s^2 + 4s + 3 = 0 = (s+3)(s+1) \quad s_{1,2} = -3, -1$

$i(t) = A_1 e^{-3t} + A_2 e^{-t}$ but $i(0) = +4$ so $4 = A_1 + A_2$

from (1) $+\frac{4}{3} = -\frac{1}{12} \frac{di}{dt} \Big|_{t=0}$ or $\frac{di}{dt} \Big|_{t=0} = -16 = -3A_1 - A_2$

adding two equations for A_1, A_2 gives: $-12 = -2A_1$ or $A_1 = 6$

and $A_2 = -2$

$i(t) = 6e^{-3t} - 2e^{-t}$

$v(t) = -\frac{1}{3}i - \frac{1}{12} \frac{di}{dt} = -2e^{-3t} + \frac{2}{3}e^{-t} - \frac{1}{2}(-3)e^{-3t} + \frac{1}{6}(-1)e^{-t}$

$v(t) = -\frac{1}{2}e^{-3t} + \frac{1}{2}e^{-t}$

3.58 same problem with $C = \frac{3}{5} F$ {initial condition the same?}

(1) $\frac{1}{3}i + \frac{5}{3} \int_0^t i dt + \frac{1}{12} \frac{di}{dt} = 0 \Rightarrow \frac{d^2i}{dt^2} + 4 \frac{di}{dt} + 20i = 0$

$s^2 + 4s + 20 = 0 \quad s_{1,2} = \frac{-4 \pm \sqrt{16 - 80}}{2} = -2 \pm j4$


$i(t) = A_1 e^{-2t} \cos 4t + A_2 e^{-2t} \sin 4t$; $i(0) = +4$; $4 = A_1$

from (1) $\frac{di}{dt} \Big|_{t=0} = -16 = \left[+4(-2)e^{-2t} \cos 4t + A_2 e^{-2t} 4 \cos 4t \right]_{t=0}$

or $16 = -8 + A_2 4 \Rightarrow A_2 = 8 \Rightarrow A_2 = -2$

$i(t) = +4e^{-2t} \cos 4t - 2e^{-2t} \sin 4t$

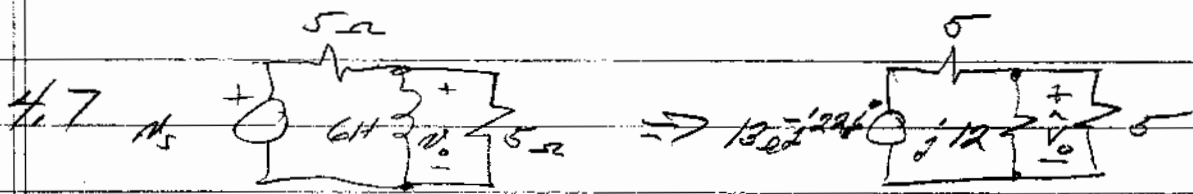$v(t) = -\frac{1}{3}i - \frac{1}{12} \frac{di}{dt} = \frac{5}{3} e^{-2t} \sin 4t$




$$i_s = 13 \cos(3t - 22.6^\circ)$$


$$Z_{eq} = \frac{j60}{5 + j12}$$

$$\hat{V}_o = \frac{13 \angle -22.6^\circ \cdot Z_{eq}}{5 + Z_{eq}} = 13 \angle -22.6^\circ \times \frac{j60}{20 + j60 + j60} = \frac{13 \times 60 \angle j67.4^\circ}{132.5 \angle j78.23^\circ}$$

$$\hat{V}_o = 6.37 \angle -10.83^\circ$$

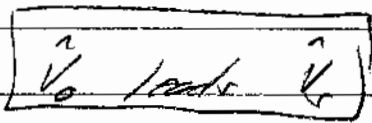

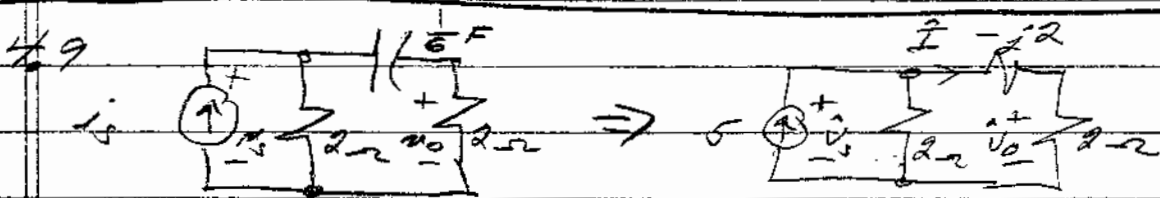so $i_o(t) = 6.37 \cos(3t - 10.83^\circ)$




$$i_s(t) = 5 \cos 3t \quad ; \quad \hat{I} = 5 \frac{2}{4 - j2} \quad \text{so} \quad \hat{V}_o = 2\hat{I} = \frac{20}{4 - j2}$$

$$\hat{V}_o = \frac{20}{\sqrt{20}} \angle j26.56^\circ = \sqrt{20} \angle j26.56^\circ = 4.47 \angle j26.56^\circ$$

so $v_o(t) = \sqrt{20} \cos(3t + 26.56^\circ)$


$$\hat{V}_o = \hat{I} (2 - j2) = \frac{10(2 - j2)}{4 - j2} = \frac{20 \sqrt{2} \angle j45^\circ}{\sqrt{20} \angle j26.56^\circ} = \sqrt{40} \angle j18.44^\circ$$

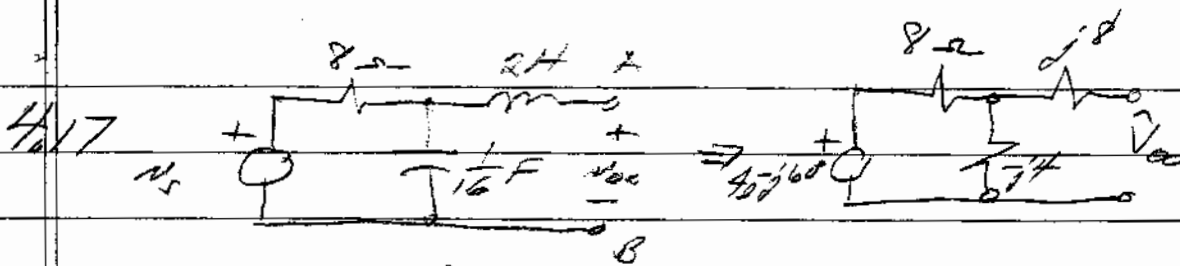$i_s(t) = \sqrt{40} \cos(3t - 18.44^\circ) = 6.32 \cos(3t - 18.44^\circ)$



$$v_s = 40 \cos(4t - 60^\circ)$$
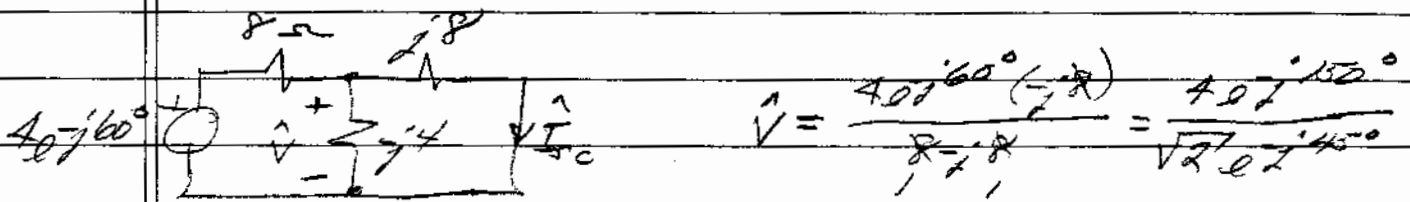
$$\hat{V}_{OC} = \hat{V}_{TH} = \frac{40 \angle 160^\circ (-j4)}{8 - j4} = \frac{40 \angle 150^\circ}{\sqrt{5} \angle 26.56^\circ} = 1.79 \angle 123.43^\circ$$




$$\hat{I}_{SC} = \frac{40 \angle 160^\circ (-j4)}{8 - j4} = \frac{40 \angle 150^\circ}{\sqrt{2} \angle 45^\circ}$$

$$Z_{eq} = \frac{j8(-j4)}{j4} = -j8$$

$$\hat{I}_{SC} = \frac{\hat{V}}{Z} = \frac{40 \angle 150^\circ}{8 \angle 90^\circ \sqrt{2} \angle 45^\circ} = \frac{1}{2\sqrt{2}} \angle 15^\circ$$

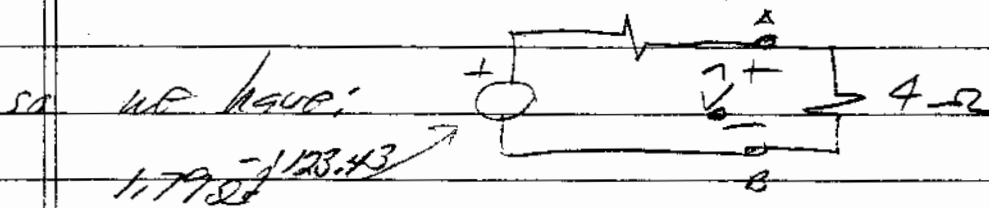
$$Z_{TH} = \frac{\hat{V}_{OC}}{\hat{I}_{SC}} = \frac{1.79 \angle 123.43^\circ}{\frac{1}{2\sqrt{2}} \angle 15^\circ} = 5.06 \angle 71.57^\circ$$



$$\hat{V}_o = 1.79 \angle 123.43^\circ \frac{4}{4 + 5.06 \angle 71.57^\circ} = \frac{7.16 \angle 123.43^\circ}{5.6 \angle 4.8^\circ}$$

$$\hat{V}_o = \frac{7.16 \angle 123.43^\circ}{7.37 \angle 40.16^\circ} = 0.972 \angle -16.7^\circ$$


$i_o(t) = 0.972 \cos(4t - 16.7^\circ)$

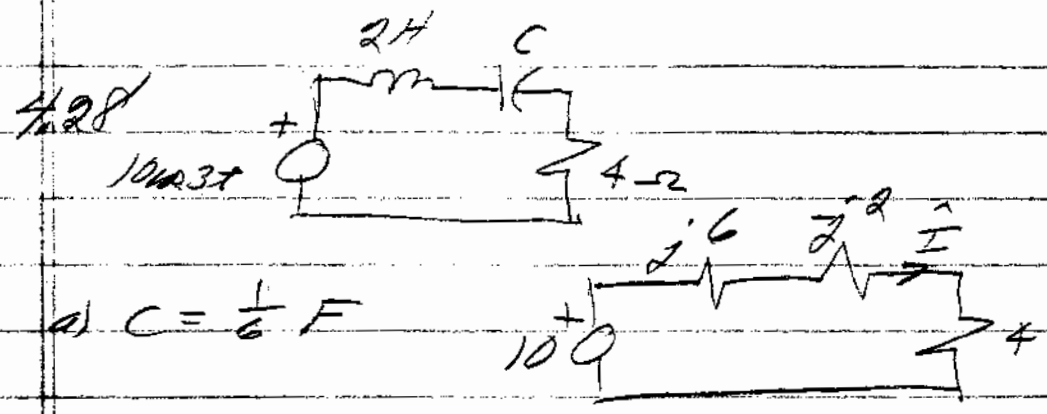

a) $C = \frac{1}{6} F$


$$\underline{I} = \frac{10}{4 + j4} = \frac{10 \angle -45^\circ}{4\sqrt{2}} = 1.768 \angle -45^\circ$$

$$P_{avg_{4\Omega}} = \frac{1}{2} |\underline{I}|^2 \cdot 4 = 2 \cdot 1.768^2 = 6.25 \text{ Watts}$$

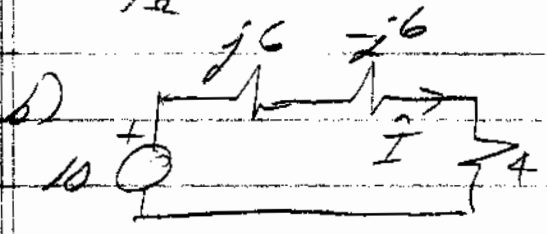

$$\underline{I} = \frac{10}{4} = \frac{5}{2}$$

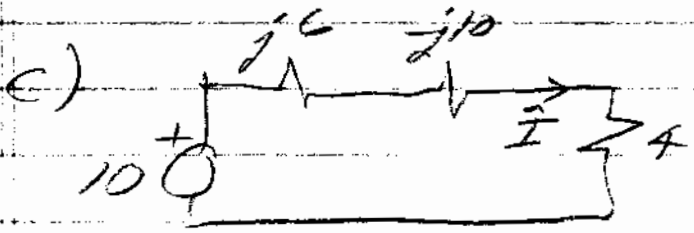
$$P_{avg_{4\Omega}} = \frac{1}{2} \cdot \frac{25}{4} = \frac{25}{8} = 3.125 \text{ W}$$



$$\underline{I} = \frac{10}{4 - j4}$$

$$\underline{I} = \frac{10}{4\sqrt{2}} \angle +45^\circ$$

$$P_{avg_{4\Omega}} = \frac{1}{2} |\underline{I}|^2 \cdot 4 = 6.25 \text{ Watts}$$

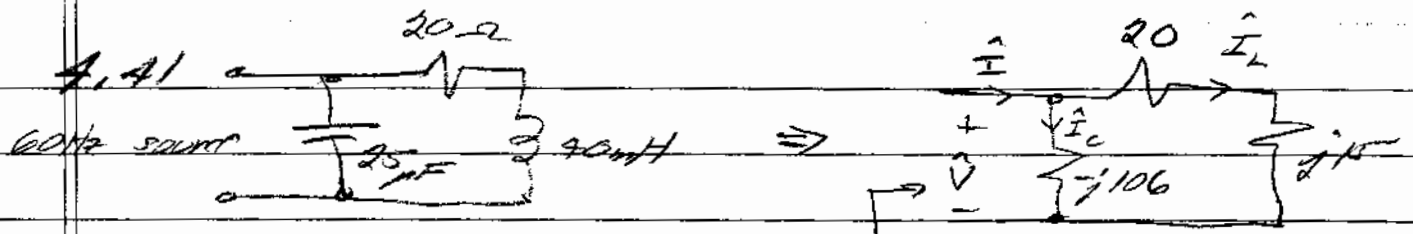


$$j\omega C = \frac{1}{Z} = \frac{1}{20 + j15} = -j106.1$$

$$j\omega L = j2\pi \times 60 \times 4 \times 10^{-2} = j15$$


$$e) Z_{in} = \frac{V}{I} = \frac{-j106(20 + j15)}{20 - j91} = \frac{106 \angle -90^\circ \cdot 25 \angle 36.86^\circ}{93.17 \angle -77.6^\circ} = 28.44 \angle 24.46^\circ$$

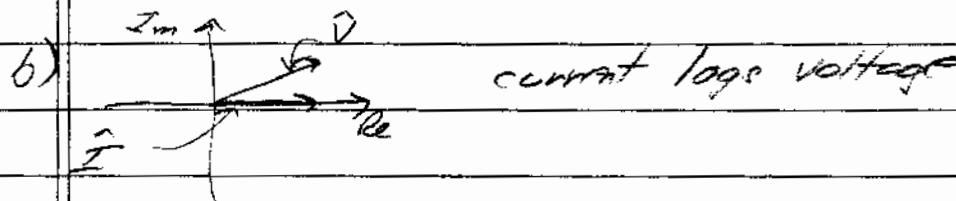so $\theta_v - \theta_i = 24.46^\circ$ (power factor angle) }
 pf = $\cos(24.46^\circ) = 0.91$



$$c) \hat{I}_L = \frac{V}{20 + j15} = \frac{V}{6.25} \quad \therefore \text{want } -\hat{I}_C = +\frac{V}{6.25}$$
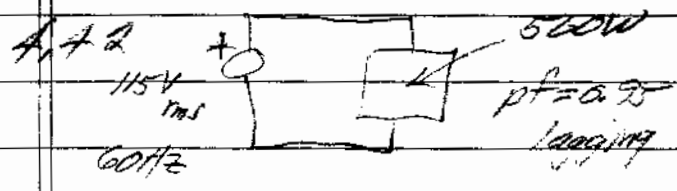
$$\hat{I}_C = V j\omega C \quad \therefore j\omega C = \frac{3}{125} \quad \text{or } C = \frac{3}{125 \times 2\pi \times 60} = 63.7 \mu\text{F}$$



$$P_{out} = V_{rms} I_{rms} (\text{pf})$$


$$\therefore I_{rms} = \frac{P_{out}}{V_{rms} \text{pf}} = \frac{500}{115 \times 0.95} = 4.58 \text{ A}$$

ES 332

Homework 1A

2.28
2.30

2.28

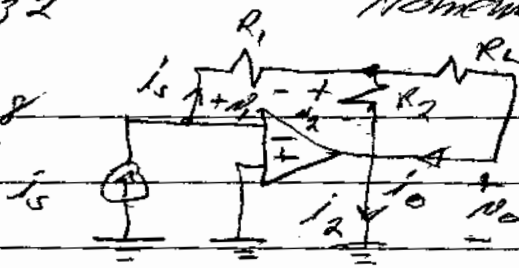


$$N_1 = i_1 R_1 \quad ; \quad N_2 = i_2 R_2$$

$$\therefore i_2 = \frac{N_2}{R_2} = -\frac{N_1}{R_2} = -\frac{i_1 R_1}{R_2}$$

$$i_0 = i_1 - i_2 = i_1 + i_2 \frac{R_1}{R_2} = i_1 \left(1 + \frac{R_1}{R_2}\right) \leftarrow$$

$$N_0 = -i_0 R_L + i_2 R_2 = -i_1 \left(1 + \frac{R_1}{R_2}\right) R_L - i_1 R_1 = -i_1 \left(R_L + R_1 + \frac{R_1 R_L}{R_2}\right) \leftarrow$$

2.30

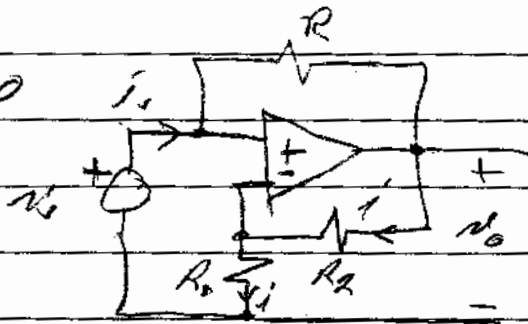

$$i = \frac{N_2}{R_1} \quad ; \quad N_0 = i(R_1 + R_2)$$

$$\text{or } N_0 = N_2 \left(1 + \frac{R_2}{R_1}\right) \leftarrow$$

$$i_1 = \frac{N_1 - N_0}{R} = \frac{N_2 \left(1 - \frac{R_2}{R_1}\right)}{R} = -N_2 \frac{R_2}{R_1 R} \leftarrow$$

$$\therefore \boxed{\frac{N_1}{N_2} = -\frac{R_1 R}{R_2}} \leftarrow$$

Assignment 15

ES 332 Spring 2008


A temperature sensor has an output of 0.01 volts per degree Fahrenheit from $T = 0$ to $T = 100^\circ\text{F}$ (at $T = 0$ $V_{\text{out}} = 0$). Design an Op-Amp circuit using this sensor that will provide an output voltage of 0 to 10 Volts for a temperature variation of 0 to 100°F .

for sensor @ $T = 0$ $V_{\text{out}} = 0$

@ $T = 100^\circ\text{F}$ $V_{\text{out}} = 0.01 \times 100 = 1\text{V}$

We want output to vary from 0 to 10 Volts

so we need a circuit with a gain of +10

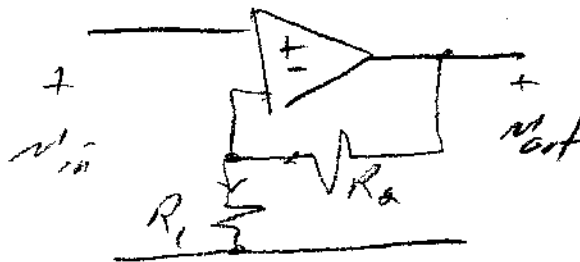

$$i = \frac{v_{in}}{R_1}$$

$$v_{out} = i (R_1 + R_2)$$

$$\therefore v_{out} = v_{in} \left(1 + \frac{R_2}{R_1} \right)$$

for a gain of 10, $\boxed{\frac{R_2}{R_1} = 9}$


ES 332

Homework 16

1426

A	B	$A \odot B$ ← "exclusive" NOR
0	0	1
0	1	0
1	0	0
1	1	1

$$A \odot B = \bar{A}\bar{B} + AB$$

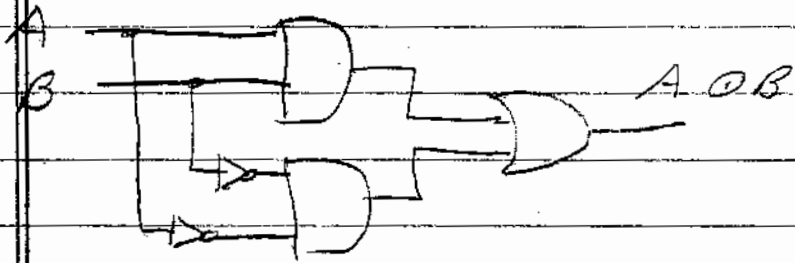


N.44

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

a) $F = m_3 + m_5 + m_6 + m_7$

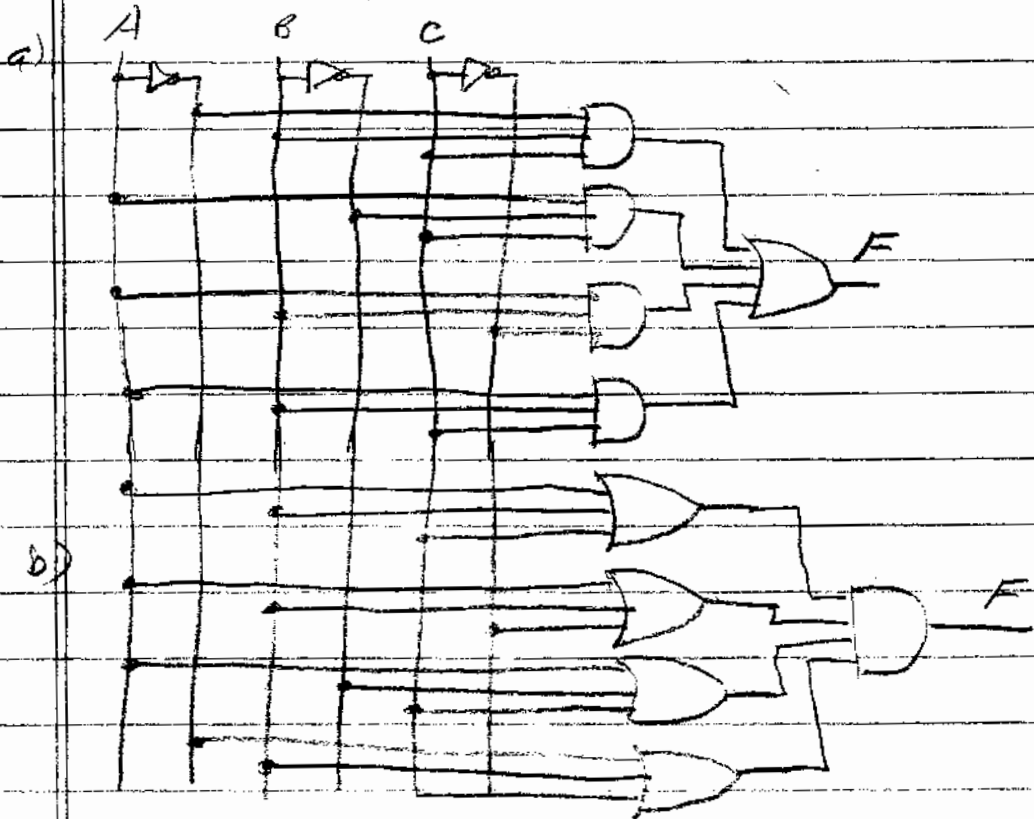b) $F = M_0 \cdot M_1 \cdot M_2 \cdot M_4$



N.53

A	BC			
	00	01	11	10
0	0	1	1	1
1	1	1	0	0

A	BC			
	00	01	11	10
0	0	0	0	1
1	1	1	1	1

A	BC			
	00	01	11	10
0	1	1	1	1
1	0	1	0	1

$F = \bar{A}C + \bar{A}B + A\bar{B}$; $F = A\bar{C} + AB + B\bar{C}$; $F = \bar{A} + \bar{B}C + B\bar{C}$