 


**EE 231**  
**Homework 8**  
**Due October 20, 2010**

1. Consider the circuit below. It has three inputs ( $x$  and clock), and one output ( $z$ ). At reset, the circuit starts with the outputs of all flip-flops at 0.



(a) Is this a Mealy machine or a Moore machine?

The output depends on one of the present inputs ( $x$ ) as well as the present state, so it is a Mealy machine.

(b) Derive the state transition table for the circuit

Call the output of the J-K flip-flop  $A$  and the output of the D flip-flop  $B$ . We need to find the  $J$  and  $K$  inputs to the J-K flip flop ( $J_A, K_A$ ). From these, we can find the next state of  $A$ . The next state of  $B$  will be the input to the D flip-flop.

$$J_A = Bx$$


$$K_A = x + B'$$

$$D_B = B'x' + A'B$$

$$z = AB'x$$

$A$	$B$	$x$	$J_A$	$K_A$	$A$	$B$	$z$
0	0	0	0	1	0	1	0
0	0	1	0	1	0	0	0
0	1	0	0	0	0	1	0
0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	0
1	0	1	0	1	0	0	1
1	1	0	0	0	1	0	0
1	1	1	1	1	0	0	0

 (c) Draw a state diagram for the circuit.



- (d) Write a Verilog program to implement the functionality of the circuit. Be sure to reset the machine with all flip-flops at 0.

We could implement a J-K flip-flop in a Verilog module, then use that flip-flop and the equations for  $J_A$  and  $K_A$ . Instead, I will tell the Verilog compiler implement the state transition table.

```
module hw8_p1(input x, clk, output z);
```

```
  reg A,B;
```

```
  always @(posedge clk)
    if (~A & ~B & ~x) begin
      A <= 0; B <= 1;
    end
    if (~A & ~B & x) begin
      A <= 0; B <= 0;
    end
    if (~A & B & ~x) begin
      A <= 0; B <= 1;
    end
    if (~A & B & x) begin
      A <= 1; B <= 1;
    end
    if (A & ~B & ~x) begin
      A <= 0; B <= 1;
    end
    if (A & ~B & x) begin
      A <= 0; B <= 0;
    end
    if (A & B & ~x) begin
      A <= 1; B <= 0;
    end
    if (A & B & x) begin
      A <= 0; B <= 0;
    end
  end
```


```
  assign z = A & ~B & x;
```

```
endmodule
```

2. Consider the following state transition table. It implements a twisted ring counter:

Present State			Next State		
A	B	C	A	B	C
0	0	0	1	0	0
1	0	0	1	1	0
1	1	0	1	1	1
1	1	1	0	1	1
0	1	1	0	0	1
0	0	1	0	0	0

(a) Draw a state diagram for the system.

 

(b) Write a Verilog program to implement the system.

```

module hw8_p2(input clock, output reg A, B, C);

always @(posedge clock)
  case ( {A,B,C} )
    3'b000: {A,B,C} <= 3'b100;
    3'b100: {A,B,C} <= 3'b110;
    3'b110: {A,B,C} <= 3'b111;
    3'b111: {A,B,C} <= 3'b011;
    3'b011: {A,B,C} <= 3'b001;
    3'b001: {A,B,C} <= 3'b000;
    default: {A,B,C} <= 3'b000;
  endcase

endmodule
  
```

3. Design a synchronous sequential circuit to control the operation of an automatic coffee machine. A cup of coffee costs 15¢ and the machine has two input slots. In one slot, only 10¢ coins can be inserted; in the other, only 5¢ coins. The machine will give change in 5¢ coins only, and only one such coin per transaction.


(a) Draw a state diagram for the circuit.

There are two inputs: a nickel deposited ( $n$ ) or a dime deposited ( $d$ ). I will assume you cannot put in a nickel and a dime at the same time.

There are two outputs: dispense of cup of coffee ( $k$ ) and give a nickel change ( $c$ ).

You could design this as a Mealy machine or a Moore machine. Here I design it as a Moore machine.

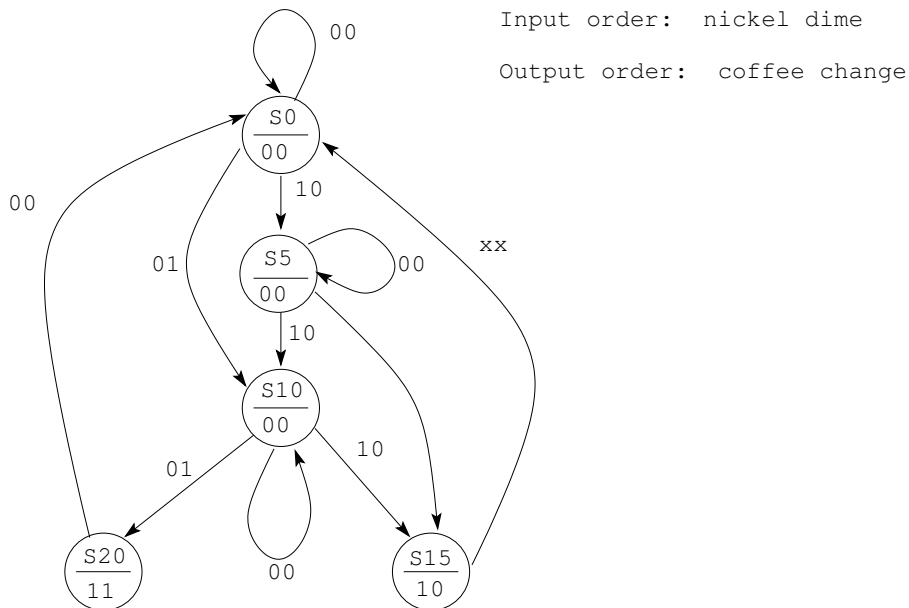There are 5 states: No money deposited, 5¢ deposited, 10¢ deposited, 15¢ and 20¢. When 15¢ is deposited, the dispenser should dispense a cup of coffee. When 20¢ is deposited, the dispenser should dispense a cup of coffee and return 5¢ change.



I assume that another coin cannot be inserted between states  $S15$  and  $S0$ , or between states  $S20$  and  $S0$ . This is a reasonable assumption – it will take at least several milliseconds before a person can deposit another coin and the coin can fall into the coin box, while the time between state  $S15$  and  $S0$  is one clock cycle, probably less than a microsecond.

(b) Assign states, and draw a state transition table.

There are five states, so you need at least three flip-flops. To simplify the output logic, I make the following state assignments:

State	<i>A</i>	<i>B</i>	<i>C</i>	<i>n</i>	<i>d</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>k</i>	<i>c</i>
S0	0	0	0	0	0	0	0	0	0	0
	0	0	0	0	1	0	0	1	0	0
	0	0	0	1	0	0	1	0	0	0
	0	0	0	1	1	x	x	x	x	x
S5	0	0	1	0	0	0	0	1	0	0
	0	0	1	0	1	0	1	0	0	0
	0	0	1	1	0	1	0	0	0	0
	0	0	1	1	1	x	x	x	x	x
S10	0	1	0	0	0	0	1	0	0	0
	0	1	0	0	1	1	0	0	0	0
	0	1	0	1	0	1	0	1	0	0
	0	1	0	1	1	0	x	x	x	x
S15	1	0	0	0	0	0	0	0	1	0
	1	0	0	0	1	x	x	x	x	x
	1	0	0	1	0	x	x	x	x	x
	1	0	0	1	1	x	x	x	x	x
S20	1	0	1	0	0	0	0	0	0	0
	1	0	1	0	1	x	x	x	x	x
	1	0	1	1	0	x	x	x	x	x
	1	0	1	1	1	x	x	x	x	x

(c) Write a Verilog program to implement the circuit.

```
module hw8_p3(input clock, n, d, output k, c);

    reg [2:0] state;

    parameter S0 = 3'b000,
              S5 = 3'b001,
              S10 = 3'b010,
              S15 = 3'b100,
              S20 = 3'b101;


    always @(posedge clock)
        case (state)
            S0: if (n) state <= S5;
                else if (d) state <= S10;
                else state <= S0;
            S5: if (n) state <= S10;
                else if (d) state <= S15;
                else state <= S5;
            S10: if (n) state <= S15;
                else if (d) state <= S20;
                else state <= S10;
            S15: state <= S0;
            S20: state <= S0;
            default: state <= S0;
        endcase

    assign k = ((state == S15) || (state == S20)) ? 1'b1 : 1'b0;
    assign c = (state == S20) ? 1'b1 : 1'b0;

endmodule
```

4. Here I will repeat Problem 3, but design the system as a Mealy machine. For a Mealy machine, you don't need the states S15 or S20. If you are in state S10 and someone deposits a nickel, the machine can dispense a cup of coffee and go back to state S0.

Here is the state machine:

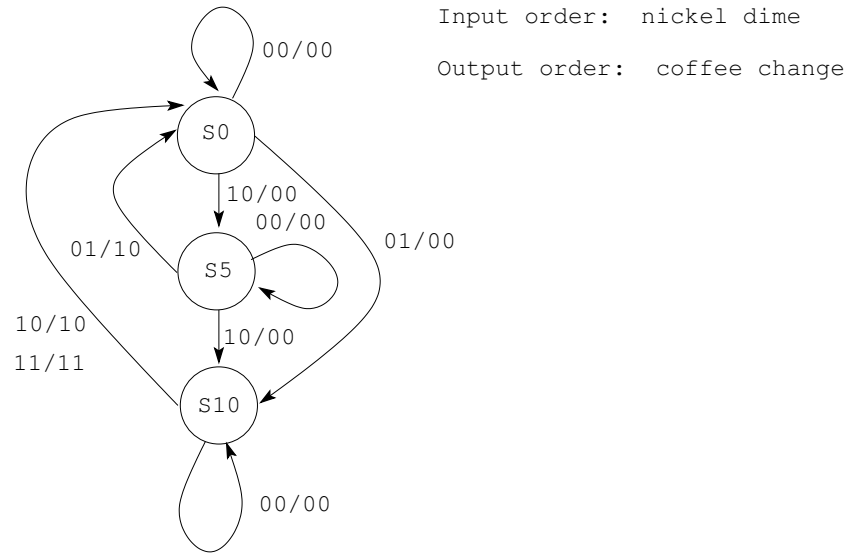

Here is a Verilog program:

```
module hw8_p3(input clock, n, d, output reg k, c);

reg [1:0] state;

parameter S0 = 3'b000,
          S5 = 3'b001,
          S10 = 3'b010;

always @( posedge clock )
  case (state)
    S0: if (n) state <= S5;
        else if (d) state <= S10;
        else state <= S0;
    S5: if (n) state <= S10;
        else if (d) state <= S0;
        else state <= S5;
    S10: if (n) state <= S0;
         else if (d) state <= S0;
         else state <= S10;
    default: state <= S0;
  endcase

always @( state, n, d) begin
  if ((state == S5) && (d)) k = 1;
  else if ((state == S10) && (n)) k = 1;
  else if ((state == S10) && (d)) k = 1;
  else k = 0;

  if ((state == S10) && (d)) c = 1;
  else c = 0;
end

endmodule
```