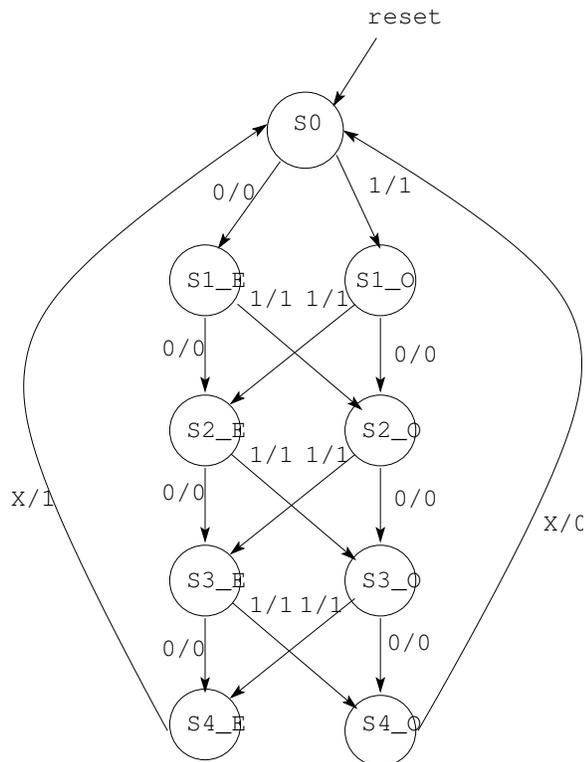


EE 231
Homework 9
Due October 29, 2010

1. A serial parity-bit generator is a sequential circuit that does the following: it receives an n -bit message followed by a 0 (so there are $n + 1$ clock bits to send the message). At the output, the circuit sends the original n -bit message, but replaces the 0 with a parity bit. Design a 4-bit serial parity-bit generator which replaces the zero bit with an odd parity bit.

(a) Draw a state diagram for the circuit.

As you receive the four data bits, you want to send out the same bits, and keep track of whether you received an even or odd number of bits. You need a state which tells you that you have received one bit, and that you have seen an even number of ones (state $S1_E$); and you need a state which tells you that you have received one bit, and that you have seen an odd number of ones (state $S1_O$). You need similar states for receiving two, three, and four bits. After you receive the fourth bit, you will go back to the reset state (no bits received), and send out a 0 if you have seen an odd number of ones, and put out a 1 if you have seen an even number of ones.



(b) Draw a state transition table for the circuit.

You have 9 states, so you need at least 4 flip-flops. There are 7 unused states. I assign the states so the bits Q_2, Q_1, Q_0 tell me how many bits of data we have received, and bit Q_3 indicates whether we have received an even or odd number of 1's. In State S_0 , we haven't received any bits, so we have seen an even number of 1's.

State	Present Flip-Flops				Input D_{in}	State	Next Flip-Flops				Output D_{out}
	Q_3	Q_2	Q_1	Q_0			Q_3	Q_2	Q_1	Q_0	
S_0	0	0	0	0	0	S_{1E}	0	0	0	1	0
S_0	0	0	0	0	1	S_{1O}	1	0	0	1	1
S_{1E}	0	0	0	1	0	S_{2E}	0	0	1	0	0
S_{1E}	0	0	0	1	1	S_{2O}	1	0	1	0	1
S_{1O}	1	0	0	1	0	S_{2O}	1	0	1	0	0
S_{1O}	1	0	0	1	1	S_{2E}	0	0	1	0	1
S_{2E}	0	0	1	0	0	S_{3E}	0	0	1	1	0
S_{2E}	0	0	1	0	1	S_{3O}	1	0	1	1	1
S_{2O}	1	0	1	0	0	S_{3O}	1	0	1	1	0
S_{2O}	1	0	1	0	1	S_{3E}	0	0	1	1	1
S_{3E}	0	0	1	1	0	S_{4E}	0	1	0	0	0
S_{3E}	0	0	1	1	1	S_{4O}	1	1	0	0	1
S_{3O}	1	0	1	1	0	S_{4O}	1	1	0	0	0
S_{3O}	1	0	1	1	1	S_{4E}	0	1	0	0	1
S_{4E}	0	1	0	0	0	S_0	0	0	0	0	1
S_{4E}	0	1	0	0	1	S_0	0	0	0	0	1
S_{4O}	1	1	0	0	0	S_0	0	0	0	0	0
S_{4O}	1	1	0	0	1	S_0	0	0	0	0	0

(c) Show how to implement the circuit using D flip-flops.


You have 4 flip-flops and 1 input bit, so you would have to draw five 5-input Karnaugh maps to find the inputs to the flip-flops and the output bit. Rather than doing that, I note that the three least significant bits $Q_2Q_1Q_0$ count 0, 1, 2, 3, 4, 0, 1, 2, 3, 4 ... I can get this behavior by using a modulus five counter.

To get bit Q_3 , I note that if bit Q_3 was a 0 and the input is 0, Q_3 stays a 0; if bit Q_3 was a 0 and the input is 1, Q_3 goes to a 1; if bit Q_3 was a 1 and the input is 0, Q_3 goes to a 1; if bit Q_3 was a 1 and the input is 1, Q_3 stays a 1 (except that in state S_4 , Q_3 always goes to 0). If you are in states S_0 through S_3 , bit Q_3 will become $Q_3 \oplus D_{in}$; if you are in state S_4 , bit Q_3 will become 0. If you are in states S_0 through S_3 , Q_2 will be 0, and if you are in state S_4 , Q_2 will be 1. This gives the equation:

$$Q_3(t+1) = Q_2'(Q_3 \oplus D_{in})$$

The output is always equal to the input in states S_0 through S_3 ; the output in S_{4E} is 1 and the output in S_{4O} is 0. This gives the equation:

$$D_{out} = Q_2'D_{in} + Q_2Q_3'$$

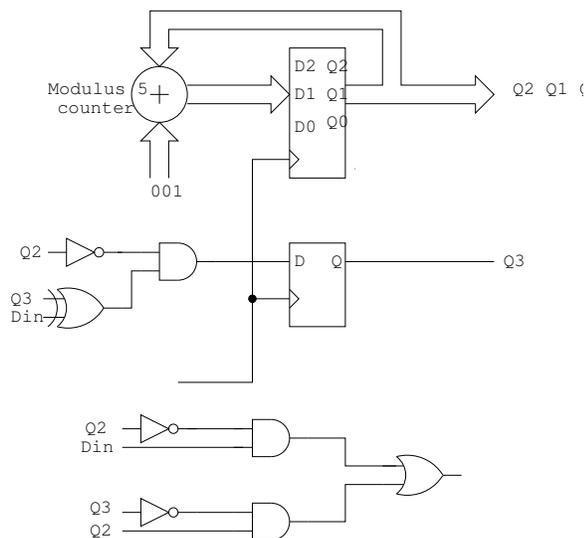

(d) Write a Verilog program to implement the circuit.

```

module serial_parity_generator(input clk, reset, Din, output reg Dout);
parameter S0    = 4'b0000, /* List the names of the states */
          S1_E  = 4'b0001,
          S1_O  = 4'b1001,
          S2_E  = 4'b0010,
          S2_O  = 4'b1010,
          S3_E  = 4'b0011,
          S3_O  = 4'b1011,
          S4_E  = 4'b0100,
          S4_O  = 4'b1100;

```

```
/* Need 4 ff's for 9 states */
reg [3:0] state;

always @(posedge clk, negedge reset)
if (~reset) state <= S0;
else case (state)
S0:   if (Dout) state <= S1_0;
      else state <= S1_E;
S1_E: if (Dout) state <= S2_0;
      else state <= S2_E;
S1_0: if (Dout) state <= S2_E;
      else state <= S2_0;
S2_E: if (Dout) state <= S3_0;
      else state <= S3_E;
S2_0: if (Dout) state <= S3_E;
      else state <= S3_0;
S3_E: if (Dout) state <= S4_0;
      else state <= S4_E;
S3_0: if (Dout) state <= S4_E;
      else state <= S4_0;
S4_E: state <= S0;
S4_0: state <= S0;
default: state <= S0;
endcase

always @(state, Din)
case (state)
S0   : Dout = Din;
S1_E: Dout = Din;
S1_0: Dout = Din;
S2_E: Dout = Din;
S2_0: Dout = Din;
S3_E: Dout = Din;
S3_0: Dout = Din;
S4_E: Dout = 1'b1;
S4_0: Dout = 1'b0;
endcase


endmodule
```

(e) Is this a Mealy machine or a Moore machine? Why?

The output depends on the present state and the current input, so it is a Mealy machine.

2. Design a synchronous sequential circuit that will count through the sequence 0, 2, 4, 6 when its control input x is 0, and through the sequence 6, 4, 2, 0 when $x = 1$. The circuit should return to the 0 state if it finds itself in an invalid state.

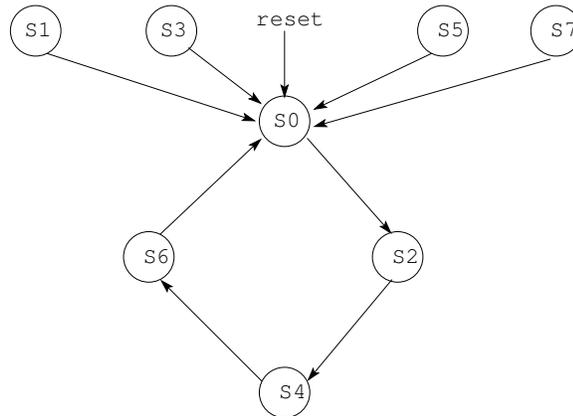(a) Draw a state diagram for the circuit.



(b) Draw a state transition table for the circuit.

You have eight states, so you need three flip-flops:

State	Present Flip-Flops			State	Next Flip-Flops		
	Q_2	Q_1	Q_0		Q_2	Q_1	Q_0
S_0	0	0	0	S_2	0	1	0
S_1	0	0	1	S_0	0	0	0
S_2	0	1	0	S_4	1	0	0
S_3	0	1	1	S_0	0	0	0
S_4	1	0	0	S_6	1	1	0
S_5	1	0	1	S_0	0	0	0
S_6	1	1	0	S_0	0	0	0
S_7	1	1	1	S_0	0	0	0

(c) Write a Verilog module to implement the system.

```
module hw9_p2(input reset, clk, output reg [3:0] Q);

parameter S0 = 3'b000,
          S1 = 3'b001,
          S2 = 3'b010,
          S3 = 3'b011,
          S4 = 3'b100,
          S5 = 3'b101,
          S6 = 3'b110,
          S7 = 3'b111;

always @(posedge clk, negedge reset)
if (~reset) Q <= S0;
else case (Q)
S0: Q <= S2;
S2: Q <= S4;
S4  Q <= S6;
S6: Q <= S0;
default: Q <= S0;
endcase

endmodule
```

3. The serial adder of Fig. 6.6 uses two four-bit shift registers. Register A holds the binary number 1101 and register B holds 0110. The carry flip-flop is initially reset to 0. List the binary values in register A and the carry flip-flop after each shift.

The system will behave according to the state table of Figure 6.2:

Present State	Inputs		Next State	Output
Q	x	y	Q	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

x and y are the LSB of A and B . After each clock cycle, we will have:

Before Clock					After Clock			
A	B	x	y	Q	S	Q	A	B
1101	0110	1	0	0	1	0	1110	x011
1110	x011	0	1	0	1	0	1111	xx01
1111	xx01	1	1	0	0	1	0111	xxx0
0111	xxx0	1	0	1	0	1	0011	xxxx

Before the first clock cycle, x will be 1 and y will be 0 (the LSB of A and B), and Q will be 0 (reset condition). This will make S equal to 1, and the $J - K$ inputs will be 00, so the $J - K$ flip-flop will hold Q at 0. After the clock, A will shift one to the right, and S will shift in from the right, so A becomes $1 \rightarrow 1101 \Rightarrow 1110$, and Q will become 0. We don't know what is on the Serial Input to B , so B becomes $x \rightarrow 0110 \Rightarrow x011$. The second clock cycle will start with $A = 1110$, $B = x011$, and $Q = 0$. After four clock cycles, A will become 0011, and Q will be 1. This is correct: $1101 + 0110 = 1_0011$.

4. Consider the following Verilog statements

(a) `RegA <= 32;`
`RegB <= RegA;`

Assume that `RegA` contains the value of 45 and `RegB` contains the value of 32 initially. What are the values of `RegA` and `RegB` after execution?

The two statements are executed at the same time, on the rising edge of the clock. Before the clock edge, `RegA` has a 45, so after the clock edge, `RegA` will have a 32 and `RegB` will have a 45.

(b) `RegA = 32;`
`RegB = RegA;`

Assume that `RegA` contains the value of 45 and `RegB` contains the value of 32 initially. What are the values of `RegA` and `RegB` after execution?

The two statements are executed sequentially. A 32 goes into `RegA`, then that 32 goes into `RegB`. After the clock edge, `RegA` and `RegB` will both be 32.

,

5. Consider the following Verilog code fragment:

```
reg [3:0] A, B;

always @( posedge clock )
begin
A = 5;
B = A + 2;
end
```

Before the clock edge, A has the value of 3, and B has the value of 6. What will be the values of A and B after the clock edge?

The statements are executed sequentially. A will go to 5, then B will go to 7 ($A + 2$).

6. Consider the following Verilog code fragment:

```
reg [3:0] A, B;

always @( posedge clock )
begin
A <= 5;
B <= A + 2;
end
```

Before the clock edge, A has the value of 3, and B has the value of 6. What will be the values of A and B after the clock edge?

The statements are executed simultaneously. A will go to 5, then B will go to 7 ($3 + 2$).