

## EE 231


## Homework 11

Due November 11, 2009

1. Design a synchronous Moore machine that monitors two inputs  $x$  and  $y$ , and asserts an output  $z$  if the number of 1's observed on the inputs is a multiple of 4. The inputs and outputs will look like this:


$x$	0	1	1	0	1	0	1	1	0	1	0	1	0
$y$	1	0	1	0	0	0	1	1	0	0	0	1	1
Number of 1's	1	2	4	4	5	5	7	9	9	10	10	12	13
$z$	0	0	1	1	0	0	0	0	0	0	0	1	0

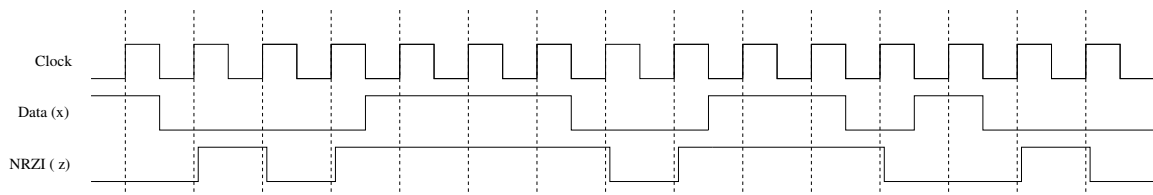- (a) Draw a state diagram for the system.
- (b) Find the state transition table for the system.
- (c) Find the excitation equations for the flip-flops.
- (d) Write a Verilog program to implement the system.
2. The USB bus transmits data using a protocol called Non Return to Zero Inverted (NRZI). An NRZI encoder has one input  $x$  (as well as the clock and reset lines) and one output  $z$ . If  $x$  is 0, the output  $z$  will change value (if  $z$  was a 0, it will change to a 1; if  $z$  was a 1 it will change to a 0). If the input  $x$  is 1, the output  $z$  will stay the same (remain 0 if it was a 0, and 1 if it was a 1). An example is shown below:



- (a) Draw a Moore state diagram for the system.
- (b) Find the state transition table and make state assignments.
- (c) Find the excitation equations for the flip-flops.
- (d) Write a Verilog program to implement the system.

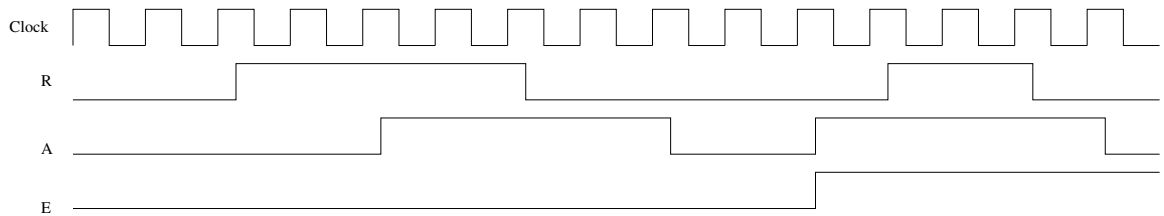3. A pair of signals Request ( $R$ ) and Acknowledge ( $A$ ) is used to coordinate the transactions between a CPU and a peripheral. The interaction of these signals is often called a “handshake”. For a transaction to be valid, the sequence of signals is that shown on the left below: both signals low,  $R$  goes high,  $A$  goes high,  $R$  goes low,  $A$  goes low. You are to design a circuit which looks for errors in the handshake. The circuit has two inputs  $R$  and  $A$  (as well as the clock and reset), and one output  $E$ . If the input sequence is in the correct order,  $E$  will be 0. If the circuit observes a different sequence (as shown on the right side of the figure below), the error signal  $E$  will go high and stay high until the system is reset.



- Draw a Mealy state diagram for the system.
- Find the state transition table for the system.
- Find the excitation equations for the flip-flops.
- Write a Verilog program to implement the system.