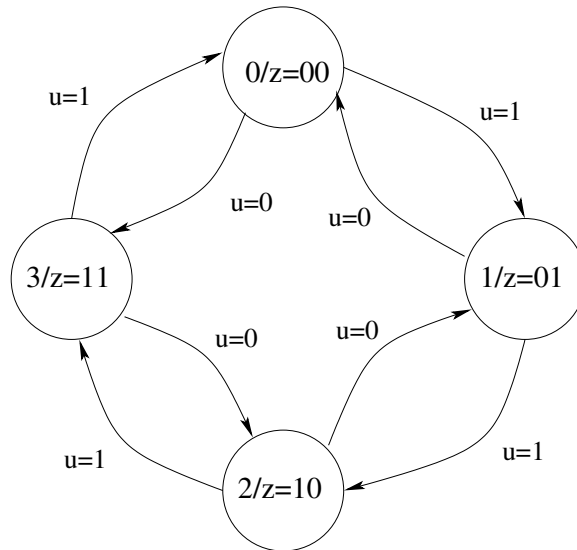


EE 231L

Using AHDL to Design State Machines

Finite state machine is another name for sequential circuits. A two-bit up-down counter can be described as a state machine with one input and two outputs:



There are many ways to design state machines using AHDL. Here are one design for the two-bit up-down counter:

```

SUBDESIGN two_bit
(  count[1..0]  : OUTPUT;
  clock         : INPUT;
  up           : INPUT;
)

VARIABLE
  ss : MACHINE WITH STATES(s0, s1, s2, s3);

BEGIN
  ss.clk = clock;          % Specify the clock for the state machine %

  CASE ss IS
    WHEN s0 =>
      count[] = B"00";
      IF (up == 1) THEN ss = s1; ELSE ss= s3; END IF;
    WHEN s1 =>
      count[] = B"01";
      IF (up == 1) THEN ss = s2; ELSE ss= s0; END IF;
    WHEN s2 =>

```

```

        count[] = B"10";
        IF (up == 1) THEN ss = s3; ELSE ss= s1; END IF;
    WHEN s3 =>
        count[] = B"11";
        IF (up == 1) THEN ss = s0; ELSE ss= s2; END IF;
    END CASE;

```

```
END;
```

The two-bit up-down counter is a Moore machine — i.e., the outputs of the machine depend only on the current state, and not on the current input. You can design a Moore machine by specifying a bit pattern associated with each state. In this example, we use a state transition table rather than a CASE statement. The count[1..0] outputs are directly associated with bits of the state machine. This means that the count[1..0] outputs will be the outputs of flip-flops, and will not change value until the machine changes states.

```
SUBDESIGN two_bit
```

```
(
    count[1..0] : OUTPUT;
    clock       : INPUT;
    up          : INPUT;
)

```

```
VARIABLE
```

```

    ss : MACHINE OF BITS (count[1..0])
        WITH STATES(s0 = B"00",
                    s1 = B"01",
                    s2 = B"10",
                    s3 = B"11");

```

```
BEGIN
```

```

    ss.clk = clock;          % Specify the clock for the state machine %

```


```
TABLE
```

% current % state	current input	next % state %
ss,	up =>	ss;
s0,	1 =>	s1;
s1,	1 =>	s2;
s2,	1 =>	s3;
s3,	1 =>	s0;
s0,	0 =>	s3;
s1,	0 =>	s0;
s2,	0 =>	s1;
s3,	0 =>	s2;

```
END TABLE;
```

```
END;
```

 You can use AHDL to design state machines with asynchronous outputs, also called Mealy machines. Here is an example from your textbook:



Here is an AHDL file to implement the design. This example shows how to reset a state machine. When `reset` goes high, the machine will be reset to the first state in the state machine list; in this case, that will be state A. The reset is done using the `clr` and `prn` inputs to D flip-flops, so the reset is done as soon as `reset` goes high; it is not necessary to wait for a clock edge.

When in state B, the output will be 0 when the input is 0, and the output will be 1 when the input is 1. The output will change multiple times while in state B if the input changes multiple times. For a Moore machine, the output changes only when the machine switches from one state to another.

```

SUBDESIGN mealy
(
  clock      : INPUT;
  reset      : INPUT;
  w          : INPUT;
  z          : OUTPUT;
)

VARIABLE
  ss : MACHINE WITH STATES(A, B);

BEGIN
  ss.clk = clock;      % Specify the clock for the state machine %
  ss.reset = reset;    % Specify the reset for the state machine %

  CASE ss IS
    WHEN A =>
      if (w == GND) THEN
        z = GND;
        ss = A;
      else
        z = GND;
        ss = B;
      END IF;
    WHEN B =>
      if (w == 1) THEN
        z = 1;
        ss = B;
  
```

```

        else
            z = 0;
            ss = A;
        END IF;
    END CASE;

END;

```

Here is the same system designed using a state transition table:

```

SUBDESIGN mealy
(
    clock      : INPUT;
    reset      : INPUT;
    w          : INPUT;
    z          : OUTPUT;
)

VARIABLE
    ss : MACHINE WITH STATES(A, B);

BEGIN
    ss.clk = clock;      % Specify the clock for the state machine %
    ss.reset = reset;   % Specify the reset for the state machine %

    TABLE
        % current      current      current  next  %
        % state        input        output   state %
        ss,           w           =>      z,     ss;
        A,            0           =>      0,     A;
        A,            1           =>      0,     B;
        B,            0           =>      0,     A;
        B,            1           =>      1,     B;
    END TABLE;

END;

```

Note that this just describes in a table what the state diagram described in a figure.