

EE 231L Lab 4**Prelab Part 1**

1. Read Section 3.8.8 of the Text, which discusses tri-state buffers. What does a tri-state buffer do?
2. The final circuit for the computer (Figure 3 of the lab overview) uses two tri-state buffers. The right-hand buffer is enabled when `OUTPUT_ENA` is active. Under what conditions will this tri-state buffer be enabled? (What is the state of the signals `ADDR = 0xFF`, `RESET`, `EXT_R`, `EXT_W`, `STORE`, and `READ`?)
3. Under what conditions will the left-hand buffer be enabled? (What is the state of the signals `ADDR = 0xFF`, `RESET`, `EXT_R`, `EXT_W`, `STORE`, and `READ`?)
4. Write the AHDL program to implement the multiplexer.
5. Write the AHDL program to implement the decoder.