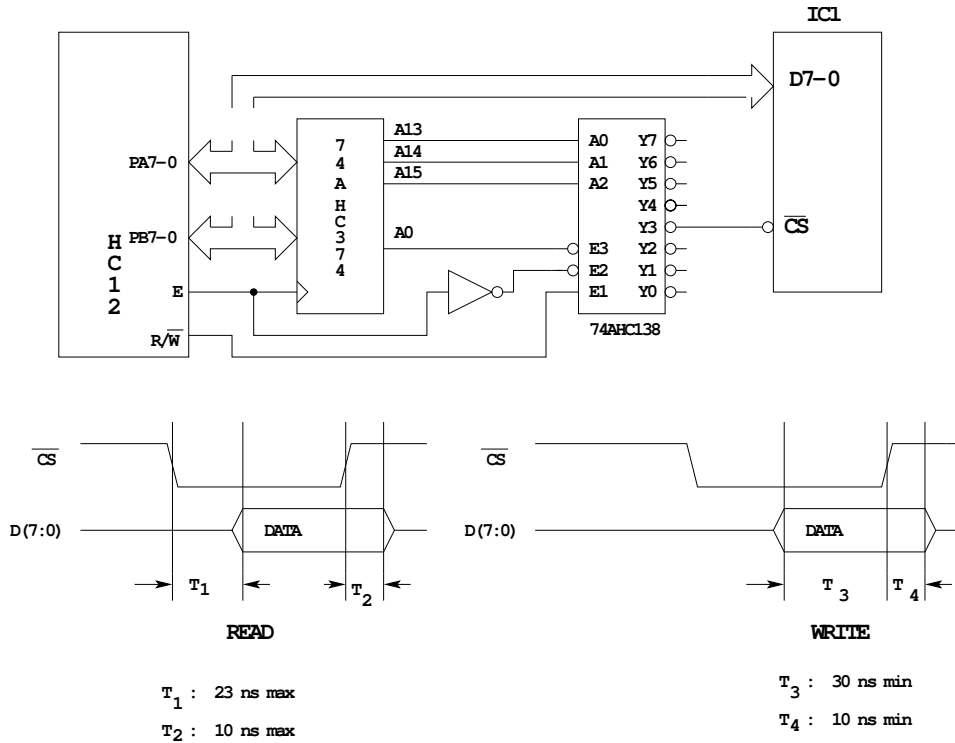




2. An engineer drew a quick sketch of an IC interfaced to the HC12. She accidentally spilled some coffee on the sketch, and some details were lost. On the same piece of paper she drew the timing diagram for an input IC and an output IC, but forgot to label which diagram corresponds to IC1 interfaced to the HC12. The figure below shows her sketch:



- (a) Is IC1 an input or an output port? Explain.
- (b) Should the data lines of IC1 be connected to the Port A or the Port B pins? Explain.
- (c) For what range of addresses will IC1 be selected? Explain.
- (d) If IC1 is an input port, write some C code to read a byte of data from IC1 and save it in a variable called `data`. If IC1 is an output port, write some C code to write a 0x55 to IC1.
- (e) Is the timing of IC1 compatible with an HC12 with an 8 MHz E-clock, and no E-clock stretches? Explain. (Assume the propagation delays through each glue logic chip is 10 ns.)
- (f) Is the timing of IC1 compatible with an HC12 with an 8 MHz E-clock, and one E-clock stretch? Explain.