
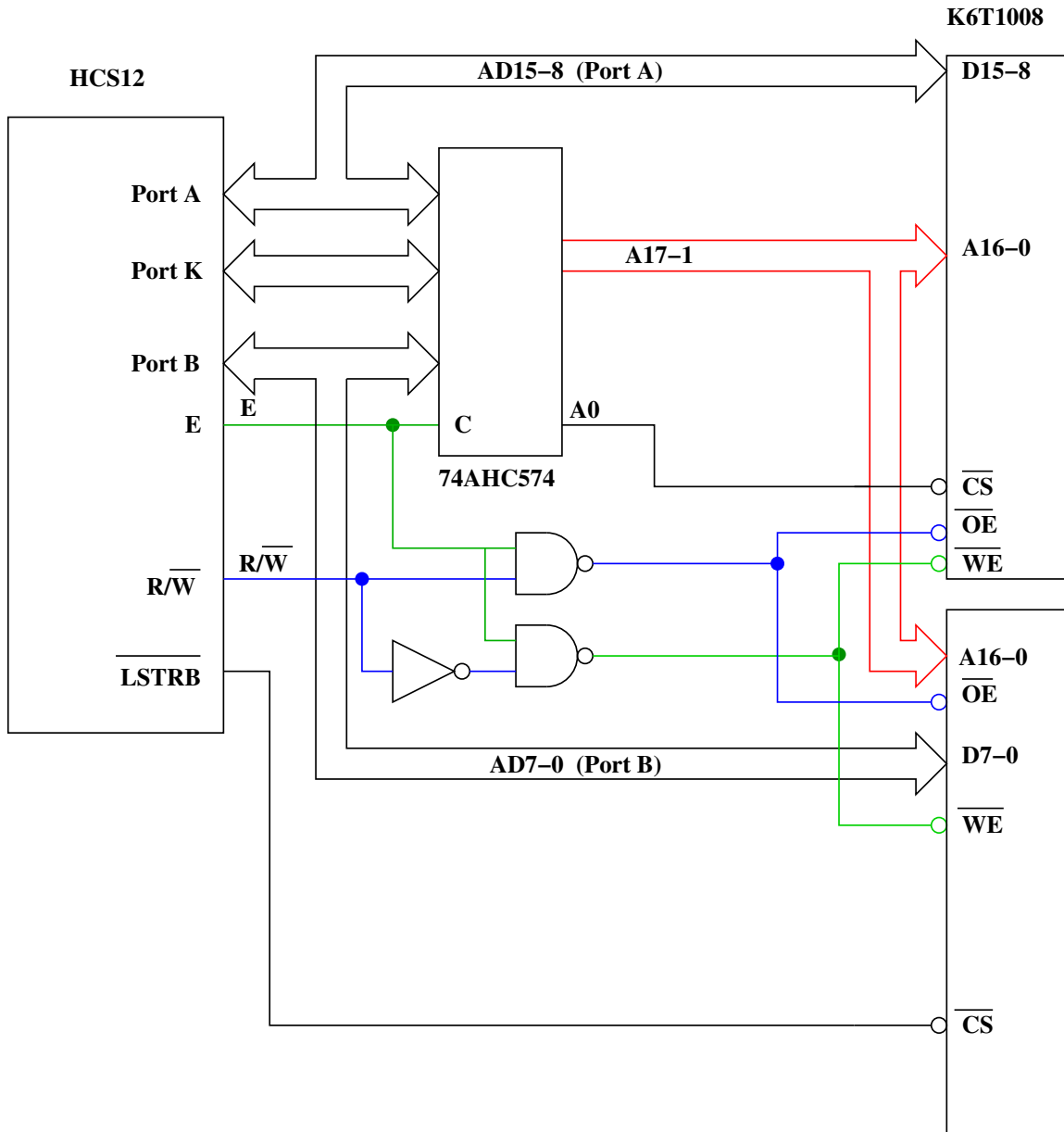


Using the HCS12 Expanded Bus — Timing Issues


- In expanded mode, memory and peripherals can be added to the HCS12.
- In order for the expansion to work, the interface timing must be correct.
- Here we will discuss adding more RAM memory to the HCS12.
- It is necessary to look at the timing of the HCS12, the “glue logic” (the chips between the HCS12 and the memory) and the memory to see if all the specs are met.
- Below we will analyze the timing issues for the external memory, and find out what frequency of HCS12 bus clock is needed to be able to use the external RAM.
- The RAM we will evaluate is a 55 ns [Samsung K6T1008C2E](#)
- Note that the interface uses 18 address lines (A17-0). The MC9S12 allows you to use more than 16 address lines by paging the memory. You select a memory page with Port K, and use a CALL and RTC (Return from CALL) instructions to switch pages.
 - The PPAGE register keeps the page value, which is written to Port K.
 - The CALL instruction pushes the 16-bit return address and the current 8-bit page register onto the stack, then loads the address register and page register with new values.
 - The RTC instruction pulls the return address and page register from the stack.

Schematic of Memory Expansion

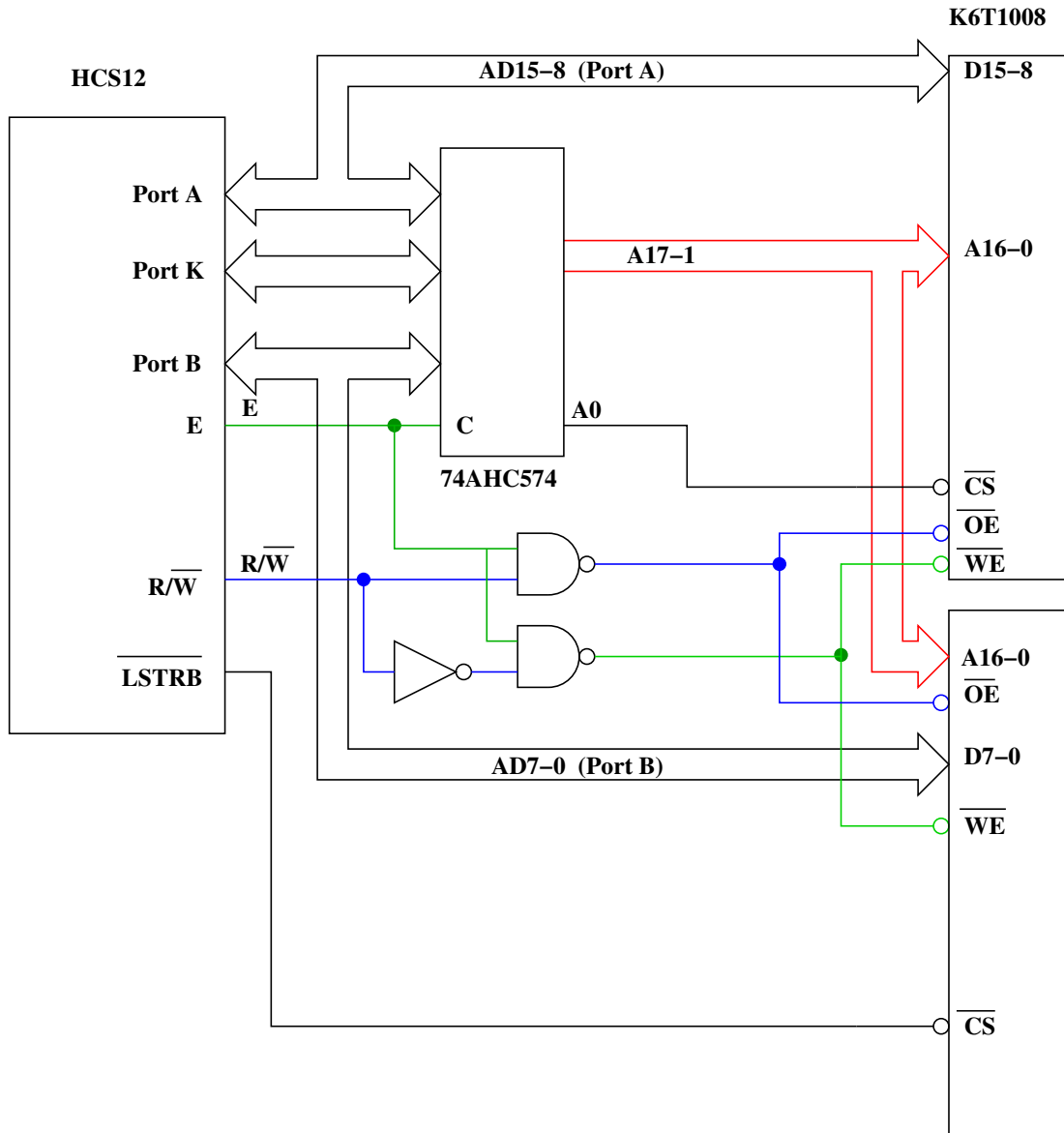



READ CYCLE

 

Bus clock frequency needed for memory expansion

- The control signals for the memory are generated by the HCS12 and the glue logic.
- With a 24 MHz bus clock, the time E-clock is high is about 21 ns.
- The memory chip needs the address stable for 55 ns before it can get the data out of its memory.
- The memory cannot work with an HCS12 using a 24 MHz clock.
- With a 4 MHz oscillator, the HCS12 can use a bus clock of 4 MHz, 8 MHz, 12 MHz, 16 MHz, 20 MHz or 24 MHz.
- To have the address stable for 55 ns, the clock period must be greater than 110 ns, which corresponds to a 9 MHz frequency.
- To have the address stable for 55 ns, the bus clock frequency must be less than 9 MHz. The expansion board uses an 8 MHz bus clock.
- Assume 3 ns for signals to propagate through the glue logic chips.

MC9S12DP256B Device User Guide — V02.13

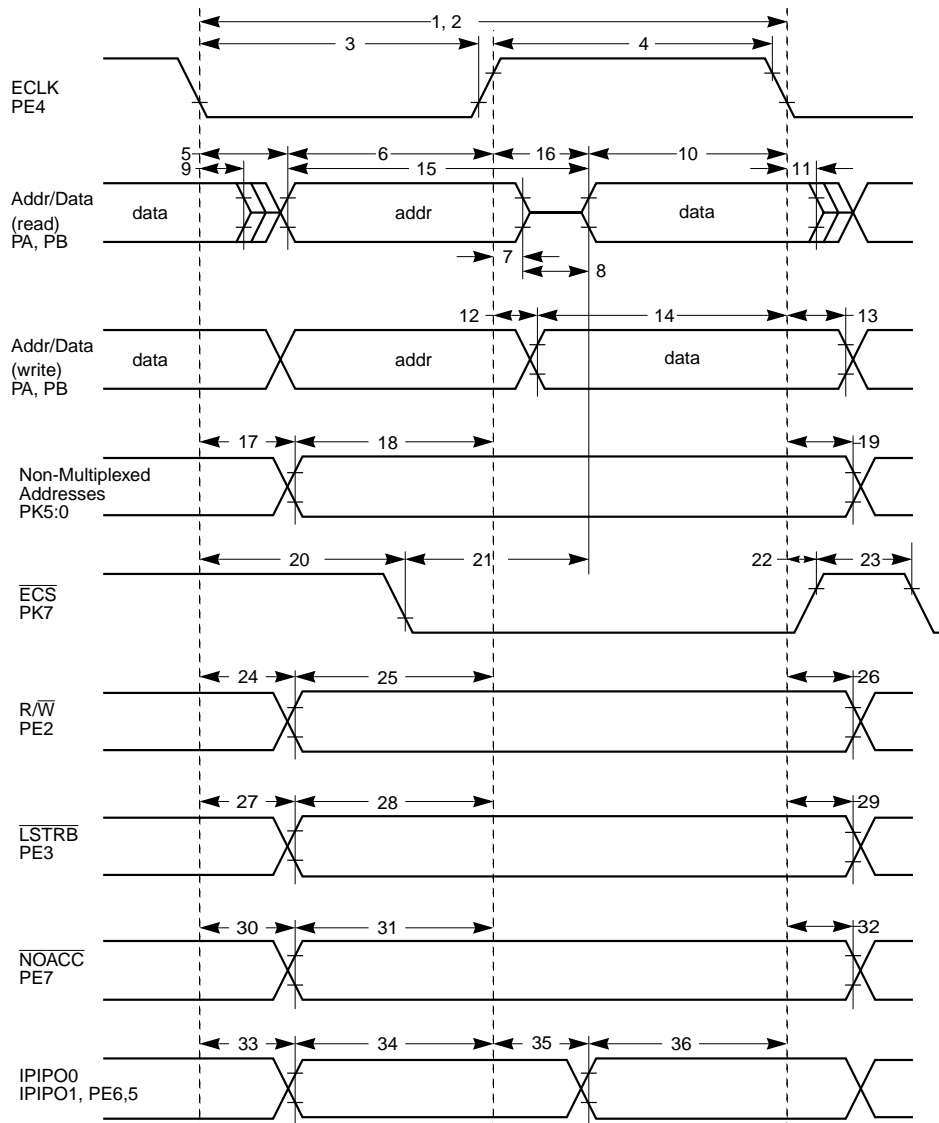


Figure A-9 General External Bus Timing

MC9S12DP256B Device User Guide — V02.13

Table A-20 Expanded Bus Timing Characteristics


Conditions are shown in Table A-4 unless otherwise noted, $C_{LOAD} = 50pF$


Num	C	Rating	Symbol	Min	Typ	Max	Unit
1	P	Frequency of operation (E-clock)	f_o	0		25.0	MHz
2	P	Cycle time	t_{cyc}	40			ns
3	D	Pulse width, E low	PW_{EL}	19			ns
4	D	Pulse width, E high ¹	PW_{EH}	19			ns
5	D	Address delay time	t_{AD}			8	ns
6	D	Address valid time to E rise ($PW_{EL}-t_{AD}$)	t_{AV}	11			ns
7	D	Muxed address hold time	t_{MAH}	2			ns
8	D	Address hold to data valid	t_{AHDS}	7			ns
9	D	Data hold to address	t_{DHA}	2			ns
10	D	Read data setup time	t_{DSR}	13			ns
11	D	Read data hold time	t_{DHR}	0			ns
12	D	Write data delay time	t_{DDW}			7	ns
13	D	Write data hold time	t_{DHW}	2			ns
14	D	Write data setup time ¹ ($PW_{EH}-t_{DDW}$)	t_{DSW}	12			ns
15	D	Address access time ¹ ($t_{cyc}-t_{AD}-t_{DSR}$)	t_{ACCA}	19			ns
16	D	E high access time ¹ ($PW_{EH}-t_{DSR}$)	t_{ACCE}	6			ns
17	D	Non-multiplexed address delay time	t_{NAD}			6	ns
18	D	Non-muxed address valid to E rise ($PW_{EL}-t_{NAD}$)	t_{NAV}	15			ns
19	D	Non-multiplexed address hold time	t_{NAH}	2			ns
20	D	Chip select delay time	t_{CSD}			16	ns
21	D	Chip select access time ¹ ($t_{cyc}-t_{CSD}-t_{DSR}$)	t_{ACCS}	11			ns
22	D	Chip select hold time	t_{CSH}	2			ns
23	D	Chip select negated time	t_{CSN}	8			ns
24	D	Read/write delay time	t_{RWD}			7	ns
25	D	Read/write valid time to E rise ($PW_{EL}-t_{RWD}$)	t_{RWV}	14			ns
26	D	Read/write hold time	t_{RWH}	2			ns
27	D	Low strobe delay time	t_{LSD}			7	ns
28	D	Low strobe valid time to E rise ($PW_{EL}-t_{LSD}$)	t_{LSV}	14			ns
29	D	Low strobe hold time	t_{LSH}	2			ns
30	D	NOACC strobe delay time	t_{NOD}			7	ns
31	D	NOACC valid time to E rise ($PW_{EL}-t_{NOD}$)	t_{NOV}	14			ns

Memory Read


- CS for even memory chip
 1. E goes low
 2. 8 ns later, AD15-0 change into address (HCS12 spec)
 3. 3 ns later, A15-0 comes out of 74AHC573 (glue logic)
 4. 6 ns later, CS goes low for even memory chip. (glue logic)
 5. CS goes low 17 ns after E goes low. (Total)
- CS for odd chip about same; CS for odd chip goes low 14 ns after E goes low
- Output Enable (OE)
 1. E goes high
 2. 3 ns later, OE goes low (glue logic)
 3. OE goes low 3 ns after E goes high (Total)
- Valid Data from Memory
 1. E goes low
 2. 8 ns later, AD15-0 change into address (HCS12)
 3. 3 ns later, A15-0 comes out of 74AHC573 (glue logic)
 4. 55 ns later, valid data is available from memory chip (memory)
 5. 66 ns after E goes low, valid data is available (but not on bus) (Total)
- Data from Memory put onto bus
 1. E goes high
 2. 3 ns later, OE goes low (glue logic)
 3. 25 ns later, memory chip puts data onto bus (memory)
 4. 28 ns after E goes low, data from memory is put onto bus (total)

- HCS12 reads data
 1. HCS12 needs data on bus 13 ns before E goes low (HCS12)
 2. E goes low 62 ns - 28 ns = 34 ns before E goes low (Total)
 3. **This meets the HCS12 data setup time**
- Data removed from bus
 1. HCS12 needs data on bus 0 ns after E goes low (HCS12)
 2. OE goes high 3 ns after E goes low (glue logic)
 3. Data removed from bus 0 to 20 ns after OE goes high (memory)
 4. Data on bus 3 ns to 23 ns after E goes low (Total)
 5. **This meets the HCS12 data hold time**
- **The memory chip will work with the RAM for read cycles**

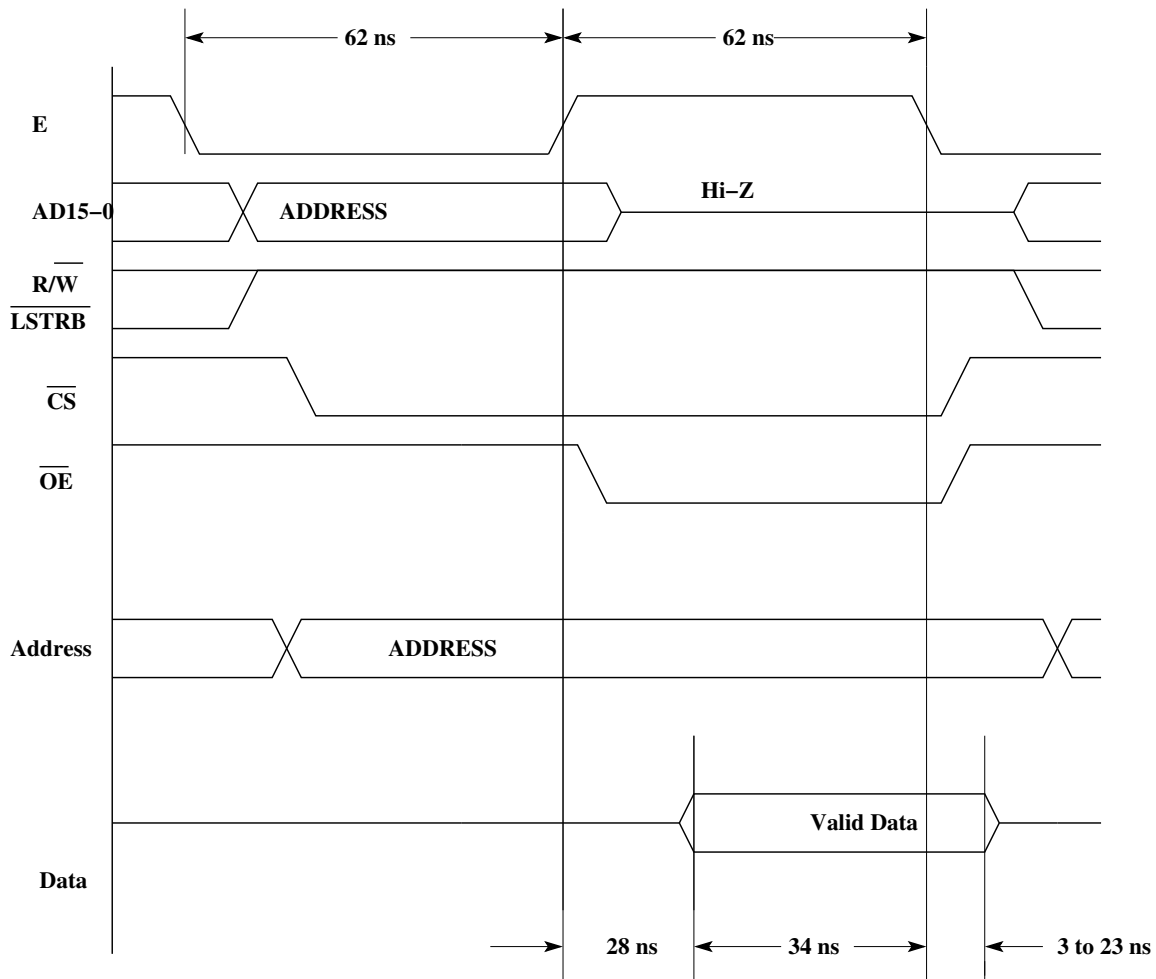

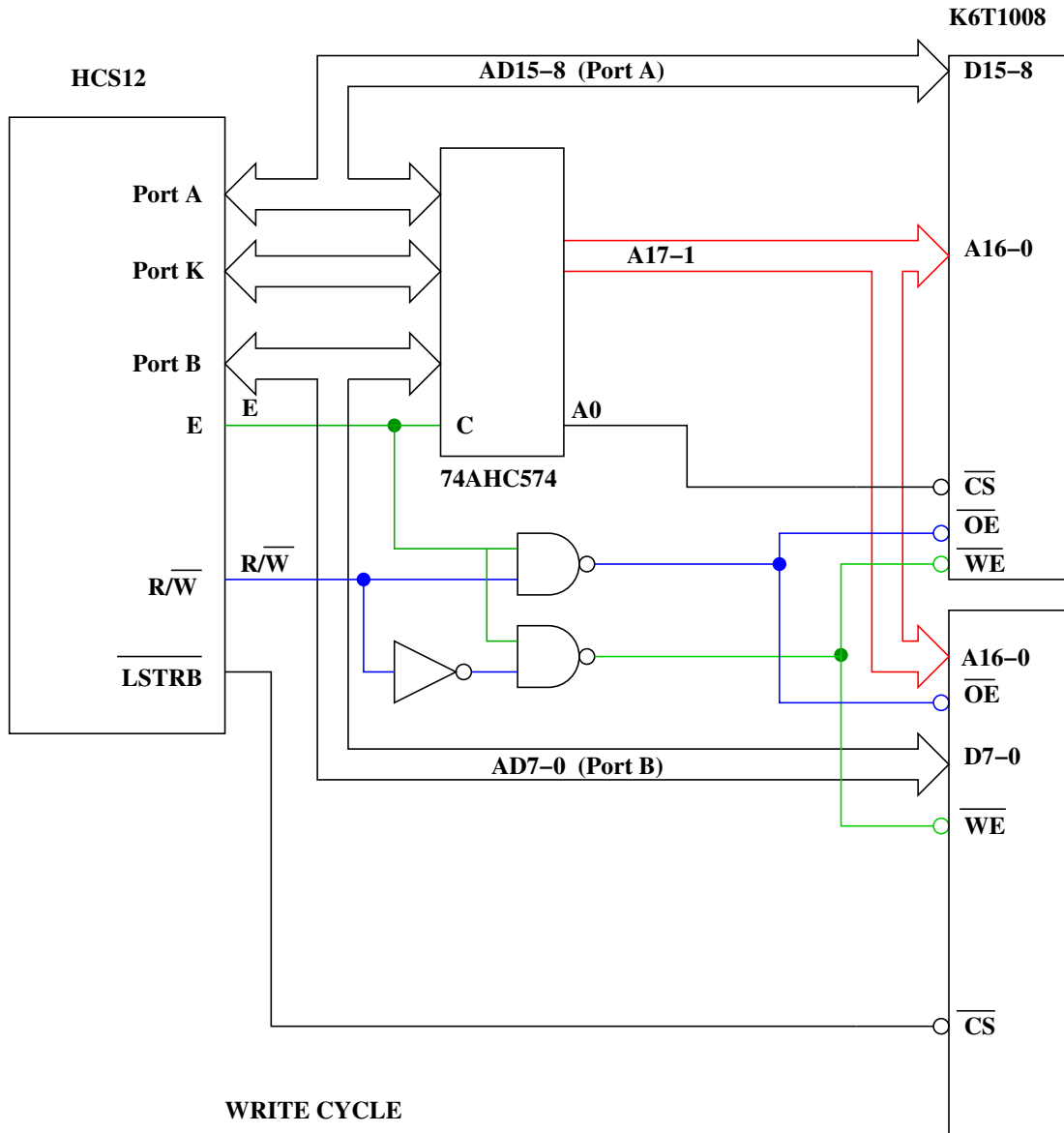


WRITE CYCLE

 

Memory Write

- CS for even memory chip
 1. E goes low
 2. 8 ns later, AD15-0 change into address (HCS12)
 3. 3 ns later, A15-0 comes out of 74AHC573 (glue logic)
 4. 6 ns later, CS goes low for even memory chip. (glue logic)
 5. CS goes low 17 ns after E goes low (Total)
- CS for odd chip about same; CS for odd chip goes low 14 ns after E goes low
- Write Enable (WE)
 1. E goes high
 2. 3 ns later, WE goes low (glue logic)
 3. WE goes low 3 ns after E goes low (Total)
- HCS12 puts data on bus
 1. E goes high
 2. 7 ns later, AD15-0 change into data (HCS12)
 3. 7 ns after E goes high, HCS12 puts data on bus (HCS12)
- Memory latches data
 1. E goes low
 2. 3 ns later, WE goes high (glue logic)
 3. Memory needs data on bus 20 ns before WE goes high (memory)
 4. Data is on bus 58 ns before WE goes high (Total)
 5. **This meets the memory write setup time**

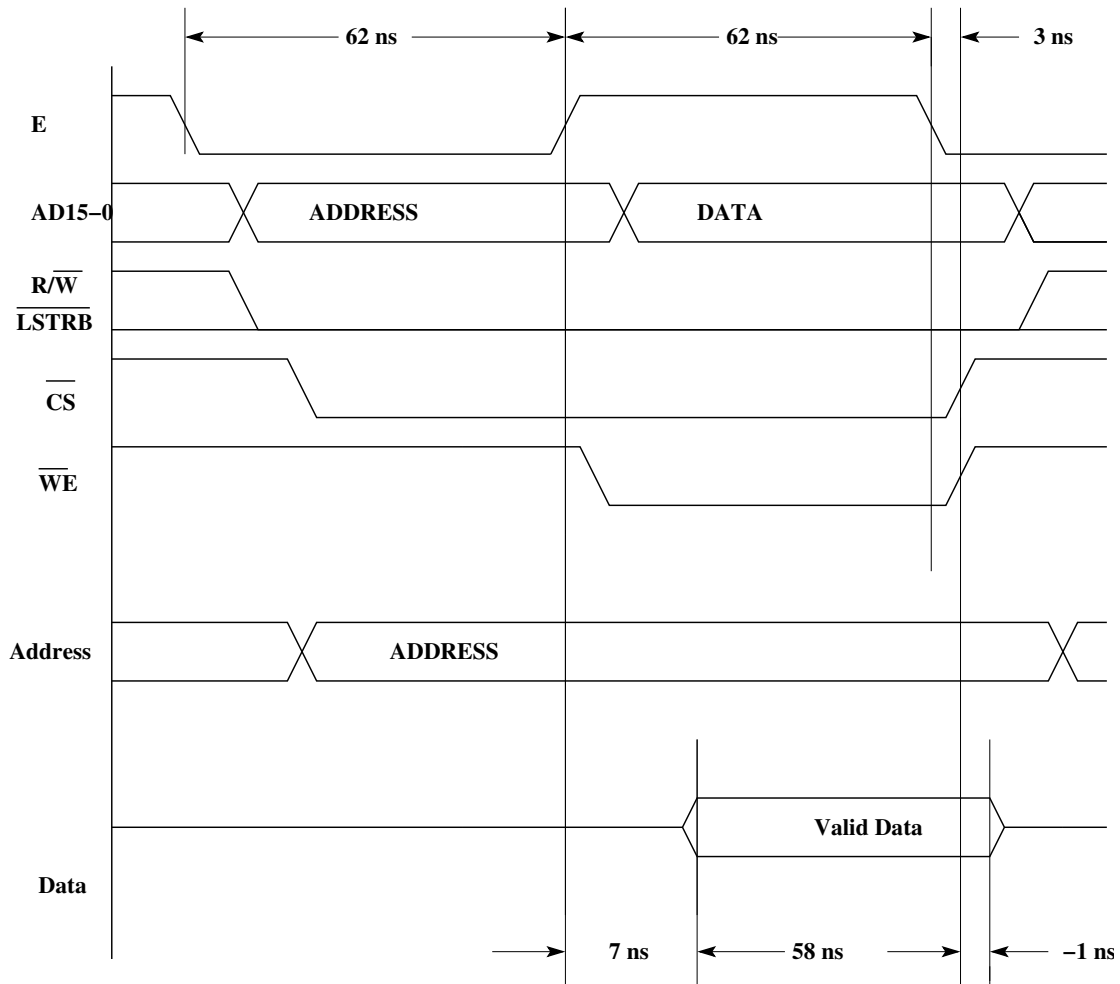- Data removed from bus
 1. Memory needs data on bus 0 ns after WE goes high (memory)
 2. WE goes high 3 ns after E goes low (glue logic)
 3. Data removed from bus 2 ns after E goes low (HCS12)
 4. Data on bus -1 ns WE goes high (Total)
 5. **Close; will probably meet specs**
- **The memory chip will work with the RAM for write cycles**



A Faster Memory Chip

- Access time of a memory chip is usually the amount of time from when the chip is selected to the data being available
- For a MC9S12 with a 24 MHz clock, time from address available to time MC9S12 needs data to be ready is

6

+

4

, or $11 \text{ ns} + 19 \text{ ns} = 30 \text{ ns}$. It will take a few nanoseconds for the glue logic to latch the address, and determine if the chip should be selected. For the circuit shown, there are two propagation delays between a new address available and the chip being selected, so if this is 6 ns, the access time of the memory chip must be less than 24 ns.

- A 12 ns memory chip would probably work for interfacing to the MC9S12 with a 24 MHz bus clock.